

Fast inverse square root

## 7 components of a computer (And more)

- Case
- Power Supply } Simple
- Mother Board
- CPU
- RAM } Complex
- (Diskdrive) • Hard drive
- Graphics processing unit (GPU) • Graphics card

Case - Hold everything

Power Supply - plugs into outlet, regulates power

Mother Board - Circuit board, communicates between components  
- connects everything

CPU - Central Processing unit, or Processor

- Doesn't store data
- everything goes through it
- Reads & arranges calculations
- Programs run from pt.
- ↳ Run more/fancier programs

RAM - Random access memory, or memory

- Data files stored
- ↳ currently using, get in and out quickly
- Small storage space
- Fast access → long thin sticks

Hard drive - Data / files stored

- ↑ Have more installed
- ↳ own but Not currently using
- Large storage space
- Slow access → small wire

\* CPU takes info out of hard drive, stores them in RAM for quick access

Graphics/video card - GPU

Difference between a hard drive and a solid state drive

- Standalone computer
- What does it look like, or supposed to look like
- ↳ own dedicated RAM

Alternative to a graphics/video card is integrated graphics, where it borrows from RAM and is attached to the CPU

- Huge process power
- ATI

\* Dumbdumb  
tips

PC - personal computer

Desktop - Keyboard + mouse separate

Laptop - all together

Voltage - Force of electrons  
Amp - Amount of electrons

## Optical drive - reads CDs + DVDs (outdated)

### Input/Output devices - Sends info in + out

- Mice, keyboards, camera

- Monitors, printer, speaker

### Heat sinks - increases airflow away from hot device

### Expansion slot - Insert more

### Networking card - Connects computer to other machines (Printer, Ethernet, Wi-Fi)

### Sound card - converts digital to analog (Inconsistent waves → sound) - Sometimes in the motherboard


### External connectors ("Ports") - Connects to the outside world (Peripherals)

I wanna do this!  
(stack of program)

Let's do it!

To wake up!

I'll hold you.

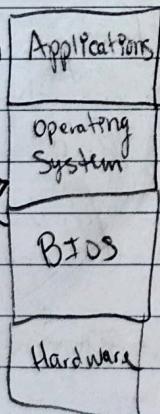

Input, memory/storage, processing, output

Programs → Software

Physical parts → hardware

### WHAT IS BIOS!?

Bios is a program that tells your operating system what to do. First thing to turn on when press power. (Firmware)

All components plug into - motherboard

CPU - central processing unit

RAM - random access memory (main memory) (Dynamic RAM DRAM) 4 GB

byte =  $10^3$

K =  $1,000 = 10^3$

M = mega =  $10^6$

G = giga =  $10^9$

T = tera =  $10^{12}$

Peta =  $10^{15}$

Exa =  $10^{18}$

zetta =  $10^{21}$

otta =  $10^{24}$

GPU - graphics processing unit

CPU - one piece of info at a time

GPU - many pixels in parallel

Hard drive - large storage, slow speed

4 TB

Secondary Mass Drive

Brain = CPU

? SSD = solid state drive → electronic transistors - no moving

not I/O - power supply

GPU Specialized for pixel display - true

A common cause of slow comp - too little memory

Disk? (Task manager)

Mega Hz? Hertz = measure of frequency, 1 cycle per second

# Voltage

Static electricity = unbalanced of electrons

Unit for electric charge = Coulomb (C) =  $6.242 \times 10^8$  electrons

Ampere =  $1\text{C}/\text{Sec}$

electron =  $-1.602 \times 10^{-19}\text{C}$

proton =  $+1.602 \times 10^{-19}\text{C}$

Energy: J → What makes change happen

$1\text{J} = 1\text{N} \times 1\text{m}$  N, measure of force =  $1\text{kg} \cdot \text{m/s}^2$

Voltage = measure of electric potential between 2 points

The amount of work  $\text{J}$  a C can do?

$$1 = V = \frac{1\text{J}}{1\text{C}}$$
 (energy per charge)

(holding, wants to go back)

$$10\text{V} = \frac{10\text{J}}{1\text{C}}$$

$$9\text{V} = \frac{9\text{J}}{1\text{C}}$$

$10\text{J}$  of electric potential energy

$$\frac{30\text{J}}{3\text{C}} = 10\text{V}$$

Voltage → pressure of electrons

Even if there are no positive particles, the potential between the two points is still 10V.


Electrostatic discharge (ESD) - sudden flow of electricity neutralizing two statically charged objects

## Current electricity



Closed circuit

open → not closed

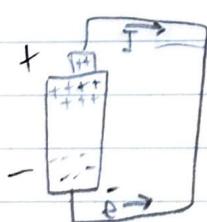

Conventional current = I  
behaves as if there is positive charge carriers causing current flow


Question: If  $1\text{V} = \frac{1\text{kg} \cdot \text{m/s}^2 \cdot \text{m}}{1\text{C}}$ , does that mean that  $1\text{V} = 1\text{C}$  of charge can accelerate  $1\text{kg}$  at a rate of  $1\text{m/s}^2$  for  $1\text{m}$ ?

$$V = I \cdot R$$

$$I = 4$$
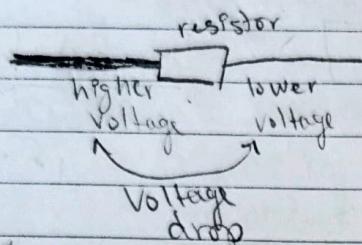
## Ohm's Law

resistor - restricts the flow of electrons



George Ohm ↗

Voltage and current are proportional

Resistor → electrical energy converted to heat

- toasters
- stoves
- heaters

$$S = I \cdot 500$$
$$\frac{S}{500} = \frac{1}{100}$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

$$V = IR$$

The voltage between 2 points = current flowing × resistance

$$I = \frac{V}{R}$$


$$V = IR$$

$$IS = 5S \cdot 10$$

Resistance,  $\Omega$  (ohm, omega)

$$10 = 10$$

$$I = 0.6$$

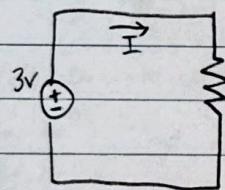

Red = positive  
Black = negative

If 3.03 volts,  $I = 0.03A$

$$\text{then } R = 101 \Omega$$

There is also resistance in the wire and the power supply itself.  
As resistance increases, current decreases.

Electric power → rate which energy is used

$$1W = J/S$$

$$\frac{900J}{3S} = 300W$$

$$\frac{900J}{1S} = 900W$$

$$1V = 1J/C$$

$$1A = 1C/S$$

$$1V \times 1A = 1J/C \times 1S = 1J/S = 1W$$

$$P(\text{power}) = V \times I /$$

$$10 \cdot 10$$


Ion - charged atom or particle

Grounding - allows safe route of electricity
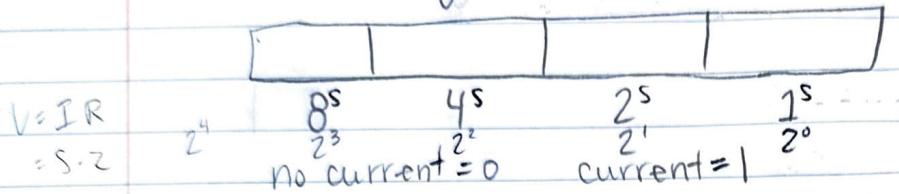
# Binary number system

Bit → Binary Digit

8 bits - byte → represent 256 values, from 0 to 255




Dec.

Hexadecimal

Represented by 16 characters

- easier to read

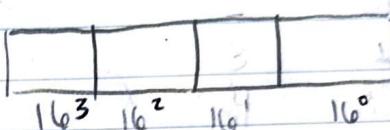- separate binary into bytes of 4 then translate



Decimal    Hexadecimal    Binary

0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
10	A	1010
11	B	1011
12	C	1100
13	D	1101
14	E	1110
15	F	1111

bit  $\boxed{4}$

nibble 4 bits

byte 8 bits

## Binary to hexadecimal

- Split into groups of 4
- find matching hex. sets (use table)

## Decimal to hexadecimal

- divide by 16
- remainder in hex. form
- divide by 16 until result is 0

ex;  $1128_{10}$  to  $x_{16}$

1. take  $1128 /$  greatest power of 16 possible

$$1128_{10} = 4 \times 16^2 + 104_{10}$$

3 place in hex

2. take remainder, convert back to dec., then do again in the next smallest power

$$104_{10} \cdot 16^1 = 104 \quad 104/16 = 6 \cdot 5$$

3. do until can't.  $5 \cdot 16 = 8$   $\rightarrow 468_{16}$

$16^1 \cdot 16^0$

E 7

160 ones

E sixteens + 7 ones

$$\underbrace{14}_{16} \cdot \underbrace{1}_{16} + \underbrace{7}_{1} \cdot 1$$

$$224 + 7 = 231$$

A F

7 C 3 F 9

$16^4 \cdot 16^3 \cdot 16^2 \cdot 16^1 \cdot 16^0$

$$7 \cdot 16^4 + 12 \cdot 16^3 + 3 \cdot 16^2 + 16$$

$$508688$$

$$\begin{array}{r} 1 0 0 0 1 1 \\ 128 \cdot 64 \quad 32 \cdot 16 \quad 8 \cdot 4 \cdot 2 \cdot 1 \end{array}$$

$$32 + 8 + 2 + 1 \\ 43$$

000111001110

I C E

3 C I

64 - 4, 2+1  
71

0011, 1100, 0001



# A.S.C.I.I.

"ask ee"

American Standard Code for Information Interchange

numbers = text

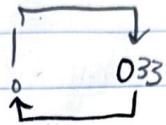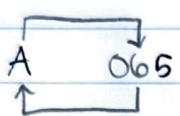letters, characters, symbols - characters



ASCII is a subset of unicode

Micro transistors → on or off (binary)

single transistor = bit

transistor on = 1

off = 0

Spelling in binary → ASCII

How hard drives work

how - magnets

ferromagnetic material (can be magnetically charged)

- full of tiny magnetic regions

↳ positive charge → 1

negative → 0

- arm sends tiny charges to the disk and reads the ones already there (reading & writing info)

How does it know where to find it? (cache + file Allocation Table)

- file Allocation table

regions

↳ tracks

↳ Sectors

↳ clusters (multiple sectors)

Actuarmy arm → checks file allocation table, then goes there

track 13,  
cluster 52

Cache - <sup>way</sup> more precise map  
- faster loading time  
- Hard drive, RAM, or CPU  
- info very quickly & very often

Why store data?

What lack in speed, make up in Space

(Solid State - made up of transistors)  
Disk drive → 500 GB → operating system → programs  
→ 3000 GB → Data

How does Blu-ray work

→ to read → lasers  
pits + flat areas  
- pits → 0  
- flats → 1 (a pit no)

when laser hits flat area, bounces off + hits  
a photodiode cell which detects the light  
- uses blue lasers → Blu-ray!  
↳ smaller wavelength → more can be read

# Questions for the J.A.

What IS a Volt?!

- "water" pressure - electric potential
- $J/C$
- $= IR$


- What is it used for? If it's not a measurement of power, why do we care?
  - What does it mean to measure Volts across a resistor? Not at a point?  $\rightarrow$  water pressure?
  - What is a volt vs. a Watt?

Can you calculate resistance + Amperes across a whole circuit or only at a point? (Demo)

$$\text{If } V = \frac{1J}{1C},$$

$$\text{then } V = \frac{N \cdot 1m}{1C} = \frac{1\text{kg} \cdot \text{m/s}^2 \cdot 1\text{m}}{1C}$$

Regular transistor:

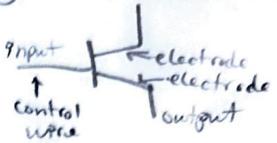


# Boolean logic & logic gates

Boolean algebra → values of variables are true & false.  
NOT, AND, OR

Not : True → False  
False → True

$$A = A' = \text{"Not } A\text{"}$$

Not gate:

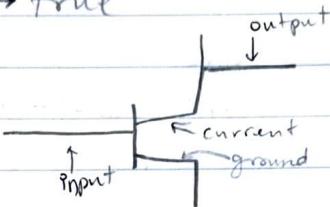

If input is on, output  
doesn't receive current

If input is off, output on

$$x = AB \rightarrow \text{"}x = A \text{ and } B\text{"}$$


multiply  
 $\times$

AND : True + true = true

True + False = false

False + true = false

False + False = false

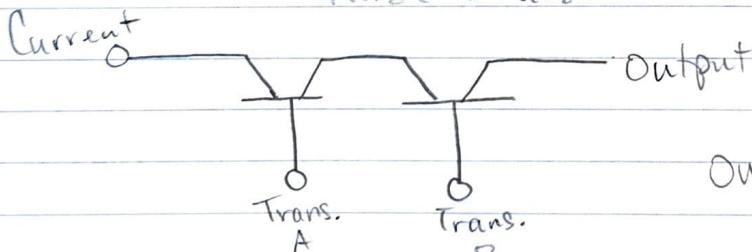

Output only if both are on

+ add

$$x = A + B + C \rightarrow \text{"}x = A \text{ or } B \text{ or } C\text{"}$$



→ OR :

$$T + T = T$$

$$T + F = T$$

$$F + T = T$$

$$F + F = F$$

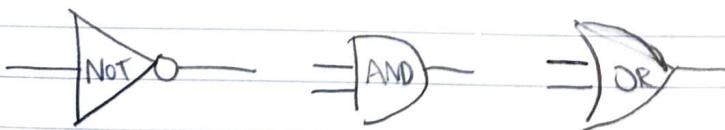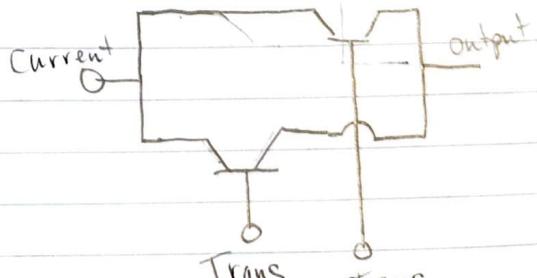

If one or the other is on, the output is on.

(exclusive or)

$x = A \oplus B$  = "A exclusive or B"

XOR


Only true if one is true + one is false

$$T + T = F$$

$$T + F = T$$

$$F + T = T$$

$$F + F = F$$

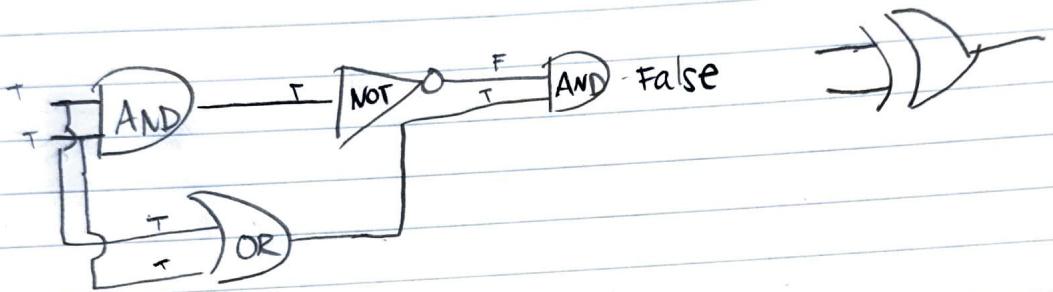

1 → true  
0 → false

AND

$X$	$Y$	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

$X$	$Y$	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1



NOT

$X$	$Z = \bar{X}$
0	1
1	0




	And	OR	Not
000	0	0	1
001	0	1	0
010	0	1	0
011	0	1	0
100	0	1	0
101	0	1	0
110	0	1	0
111	1	1	0

"A not"

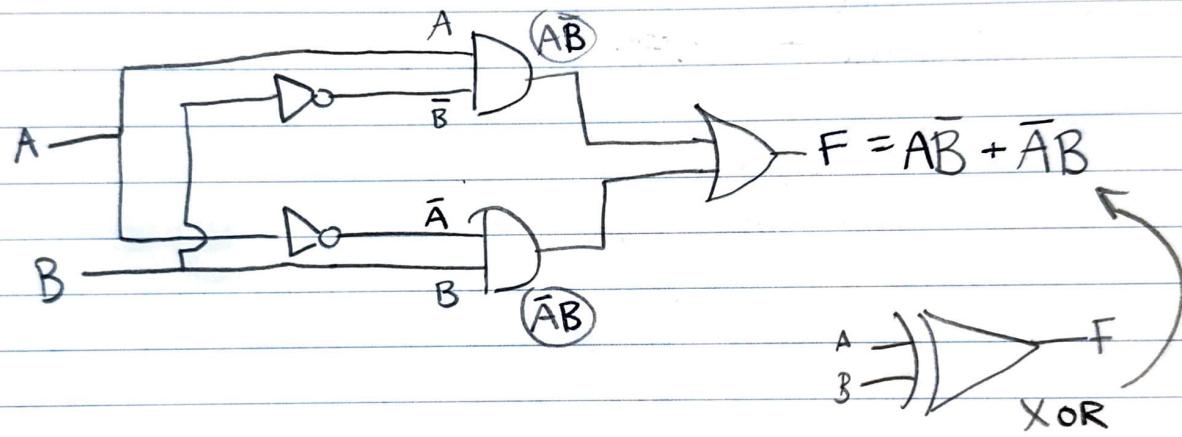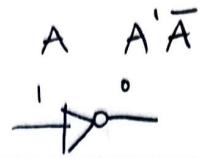


$$F = AB + \bar{A}\bar{B}$$

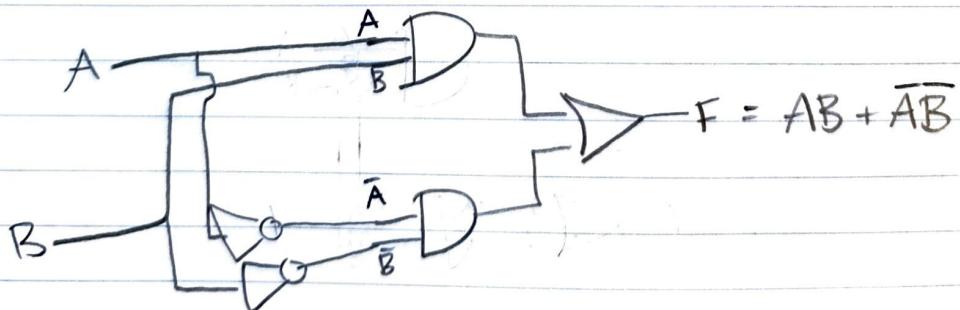

Resistors → check table for  $\text{r}$  value +  
accuracy

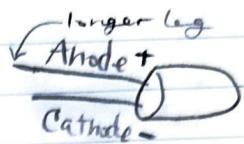LED → Light-Emitting Diode  
→ NEED a resistor!




How much resistance?

- Component LED
- Voltage 9V
- Forward voltage → manufacturer ex; 3.2V
  - how many volts the LED will use up
- Amps → manufacturer ex; 0.024A

$$R = (\text{Power source} - \text{fwd voltage}) / \text{Amps}$$


ex;  $R = (9 - 3.2) / .024 = 240 \Omega$

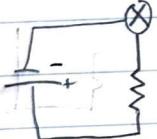Question: does it matter which side  
the resistor is on?



load




## Breadboards!

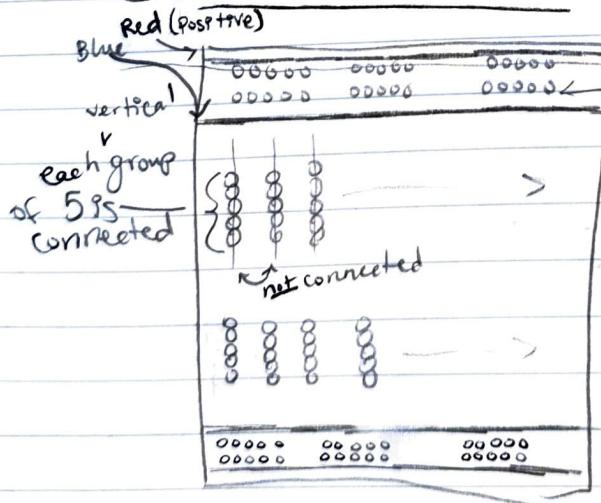


metal connecting them all

This whole line IS connected  
Same w/this. But NOT to each  
other

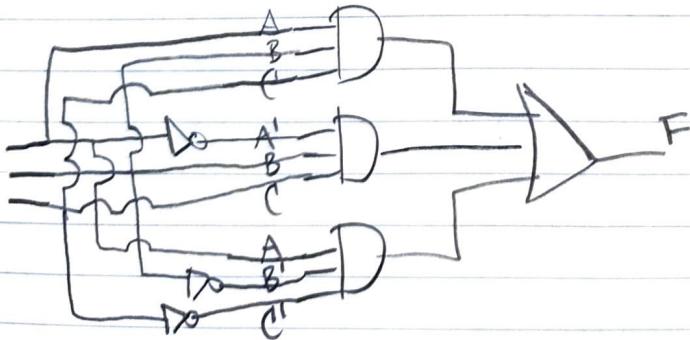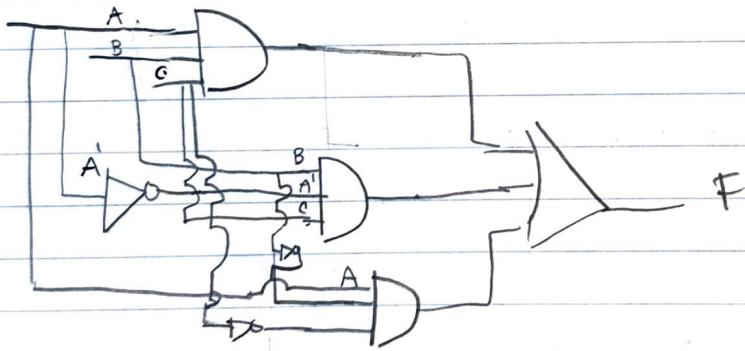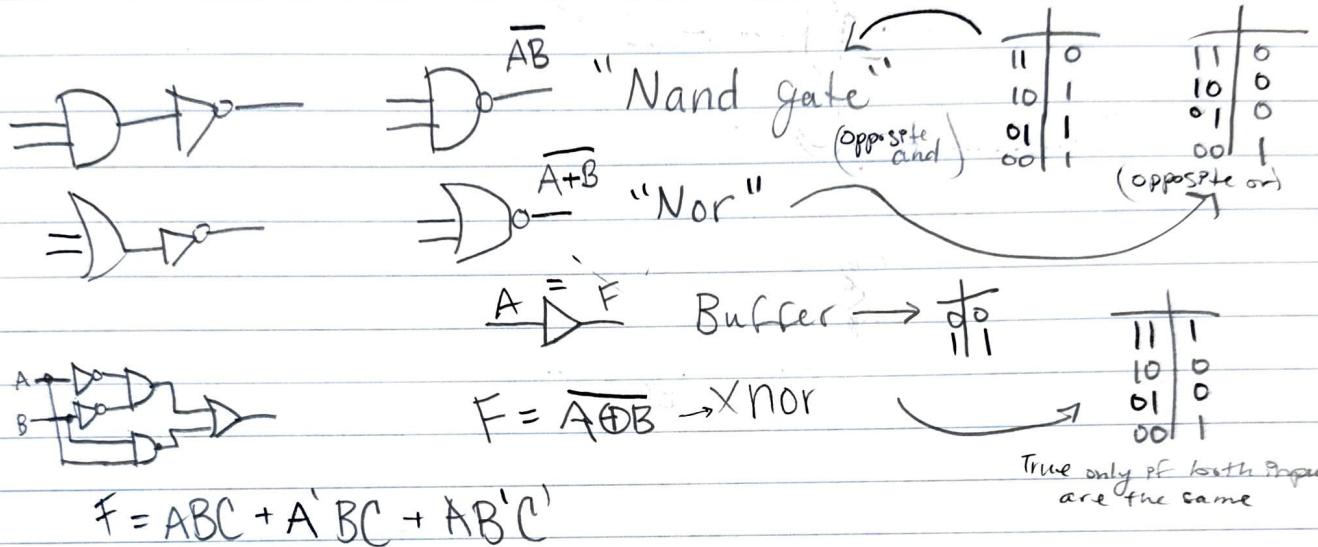Multimeter - measures volt., resistance, and amps.  
 - auto-ranging - don't have to put in a range  
 $OL \rightarrow$  open leads (not connected)


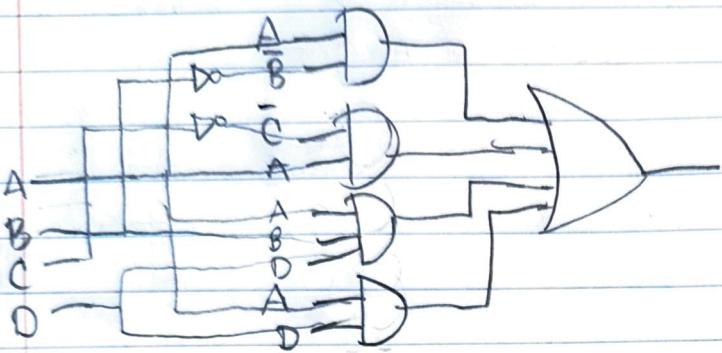
$$F = A\bar{B} + \bar{C}\bar{A} + ABD + A\bar{D}$$



Truth table to logic equation

ABC	F
000	0
001	0
010	0
011	0
100	0
101	1
110	0
111	0

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$$

$$000 + 011 + 101$$


Logic equation to truth table

$$F = A + B\bar{C}$$

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$


ABC	F
000	0
→ 001	1
010	0
→ 011	1
100	0
101	0
→ 110	1
→ 111	1

ABC	F
000	0
001	0
→ 010	1
011	0
A&B → 100	1
→ 101	1
→ 110	1
→ 111	1

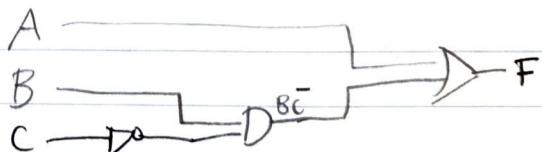

Story Problems: Three board members vote on corporate policies. Their names are Adam (A) Baker (B) and Cheney (C). If two or more of them vote yes, the policy (P) is implemented. Create the Boolean equation.

A	B	C	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
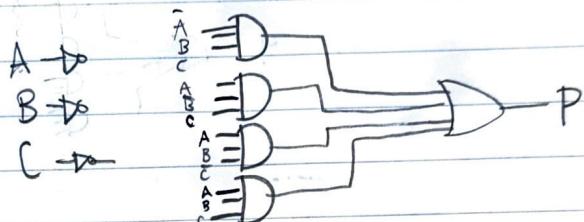
$$P = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + ABC$$


Fluid level, Temperature, pressure. Alarm sounds if T and P are both too high, or L is wrong.



L	T	P	A
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$A = \bar{L}\bar{T}P + L\bar{\bar{T}}\bar{P} + L\bar{T}\bar{P} + LT\bar{P} + LTP$$

Simplify  $A = TP + L$

What is open source?

## Schematics

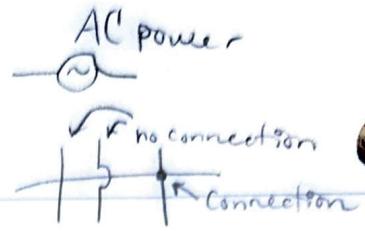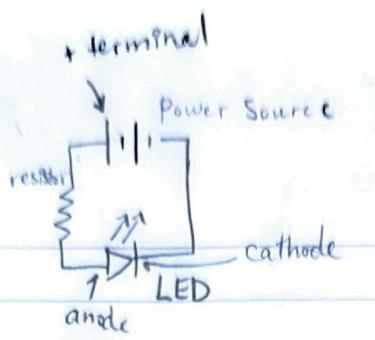

## Switches

toggle switches, slide switch, dopswitches



SPST Switch (single pole, single throw)




SPDT (single pole, double throw)



DPST (Double pole, single throw)



DPDT (Double pole, double throw)

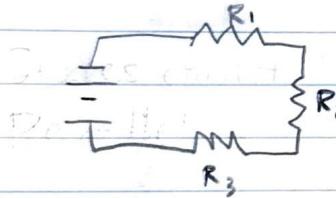


Series

I same

V differ

$$R_T = R_1 + R_2 + R_3 \dots$$

add R,  $R_T \uparrow$  I  $\uparrow$

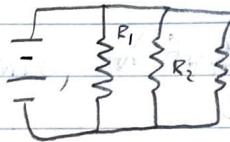


Parallel

I differ

V same

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

add R,  $R_T \downarrow$  I  $\uparrow$

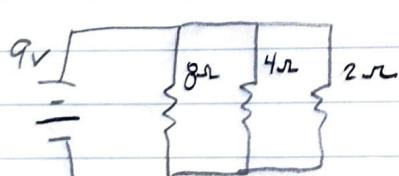


$$\frac{1}{R_T} = \frac{1}{8} + \frac{1}{4} + \frac{1}{2} = \frac{7}{8} \quad R_T = \frac{8}{7} \Omega$$

$$I = \frac{V}{R_T} = 9 \cdot \frac{7}{8} = 7.875 \text{ A}$$

$$I_1 = \frac{V}{R_1} = \frac{9}{8} \text{ A}$$

$$I_2 = \frac{9}{4} \text{ A}$$

$$I_3 = \frac{9}{2} \text{ A}$$

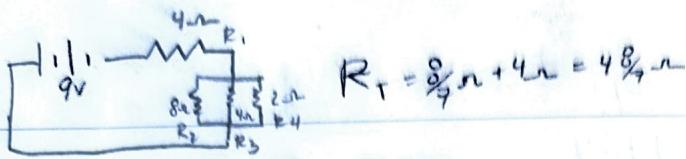

$$R_T = \frac{8}{7} \Omega + 4\Omega = 4\frac{8}{7} \Omega$$

$$I_S = \frac{V}{R} = \frac{9}{4\frac{8}{7}\Omega} = 1.75A$$

$$V_{R_1} = (1.75)(4) = 7V$$

So only 2V going through parallel part

$$V=IR$$

$$I=\frac{V}{R}$$

$$I_2 = \frac{2}{8} = \frac{1}{4}A$$

$$I_p = \frac{2}{\frac{8}{7}} = \frac{14}{8} = 1.75A$$

$$I_3 = \frac{3}{4} = \frac{1}{2}A$$


$$I_4 = \frac{3}{2} = 1A$$

$$I_p = \frac{2}{\frac{8}{7}} = \frac{14}{8} = 1.75A$$

$$V=IR$$

$$V=5 \text{ } R=666\Omega$$

Proof:

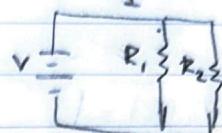

$$R_1 = \frac{V}{I_1}, \quad R_2 = \frac{V}{I_2}$$

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$

$$I = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Analog measures voltage from Ground to analog pin.

$$S = I \cdot (330 + R)$$

$$3.03 = I \cdot 330$$

$$V=IR$$

$$S = I 220$$

# Adding Base-2

Magic table
$0+0=0$
$0+1=1$
$1+0=1$
$1+1=10$

$$1+1+1=11$$

$$\begin{array}{r} 10101 \\ + 1101 \\ \hline 110010 \end{array}$$

$$\begin{array}{r} 110 \\ + 101 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 10101 \\ 11101 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 101101 \\ - 101100 \\ \hline \end{array}$$

# Subtract Binary

Magic table

$$1-1=0$$

$$0-0=0$$

$$1-0=1$$

$$0-1=1 \text{ * Carry required}$$

$$10-1=1$$

$$\begin{array}{r} 10111 \\ - 10101 \\ \hline 00010 \end{array}$$

$$\begin{array}{r} 10011 \\ - 01101 \\ \hline 00110 \end{array}$$

$$\begin{array}{r} 110 \\ - 101 \\ \hline 001 \end{array}$$

$$\begin{array}{r} 11010 \\ - 10101 \\ \hline 10010 \end{array}$$


"Two's complement" → represent negative numbers

throw remainder away

$$\begin{array}{r} 10011 \\ - 01101 \\ \hline \end{array} \rightarrow \text{Invert bottom} \rightarrow \text{add } 1 \rightarrow \begin{array}{r} 10011 \\ 10011 \\ \hline 10011 \end{array}$$

$$\begin{array}{r} 10011 \\ + 10011 \\ \hline 00110 \end{array}$$

↑  
if 0, positive  
if 1, negative

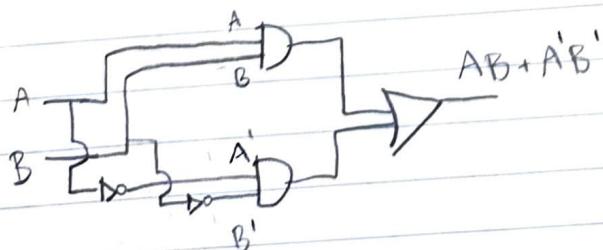

$$F = \bar{A} + \bar{B}C'D$$

$$\begin{array}{ccc} 1011 & 1101 & 1110 \\ AB' + AC' + AD' = G \end{array}$$

ABCD	F	G
0000	1	0
0001	1	0
0010	1	0
0011	1	0
0100	1	0
0101	1	0
0110	1	0
0111	1	0
1000	0	1
1001	1	1
1010	0	1
1011	0	1
1100	0	1
1101	0	1
1110	0	1
1111	0	0

$A \rightarrow \text{pink}$   
 $B \rightarrow \text{paper}$   
 $C \rightarrow \text{jammed}$

$$\text{Alarm} = 2 \text{ or more are true}$$

$$AB + AC + BC = F$$

ABC	F
000	0
001	0
010	0
011	1
100	0
101	1
110	1
111	1



Half-adder and full adder?

ALU - Arithmetic logic unit

What it started with  
before adding

110 ← carry in (c<sub>in</sub>)

$$\begin{array}{r} 01 \\ 11 \\ \hline 100 \end{array}$$

011 ← carry out (c<sub>out</sub>)



What was left after  
adding

$$\begin{aligned}
 0+0+0 &= 1 \\
 0+0+1 &= 1 \\
 0+1+0 &= 1 \\
 0+1+1 &= 0 \text{ carry } 1 \\
 1+0+0 &= 1 \\
 1+0+1 &= 0 \text{ carry } 1 \\
 1+1+0 &= 0 \text{ carry } 1 \\
 1+1+1 &= 1 \text{ carry } 1
 \end{aligned}$$


Ones complement

$$1001 \rightarrow 0110$$

Half-adder - no carry-in number

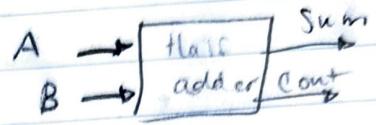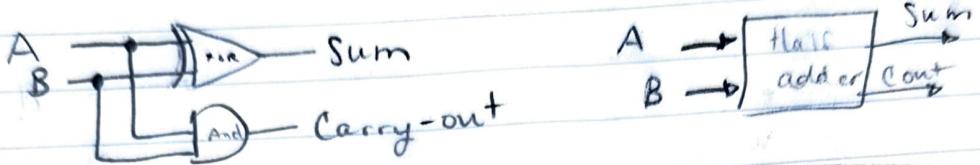


Full-adder - includes carry-in number

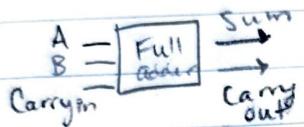

A	B	$C_i$	$C_o$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A'B'C_i + A'BC'_i + AB'C'_i + ABC_i$$
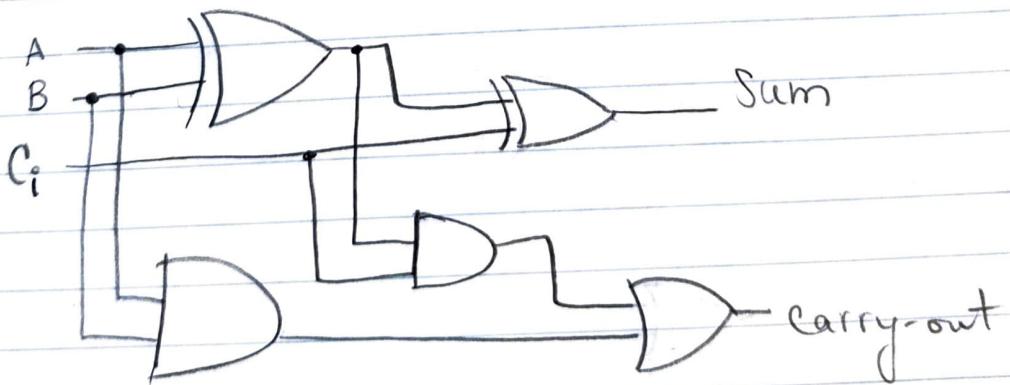
$$C_o = A'BC_i + AB'C_i + ABC'_i + ABC_i$$



## Better explanation: Representing negative numbers

One's complement:

0 → positive  
1 → negative

$$\begin{array}{r} 3 \\ -3 \\ \hline 0 \end{array} \quad \begin{array}{r} 0011 \\ +1100 \\ \hline 1111 \end{array}$$

Sign  
Indicator  
flip

flip all bits  
for storing value

\* Has problem of 0 being + and - \*

$$\begin{array}{r} 2 = 17 \\ 1 = 16 \\ 0 = 15 \\ -1 = 14 \\ -2 = 13 \\ -3 = 12 \\ -4 = 11 \\ -5 = 10 \end{array}$$

$$\frac{3}{-3} \frac{3}{+12} \frac{3}{0 = 15}$$

→ discard (minus, 16, again)

Two's complement:

$$\begin{array}{r} 3 \\ -3 \\ \hline 0 \end{array} \quad \begin{array}{r} 0011 \\ +1101 \\ \hline 0000 \end{array}$$

Sign  
Indicator

flip flip and add 1

$$\begin{array}{r} 0100 \\ -0011 \\ \hline 1101 \end{array} \quad \begin{array}{r} 4 \\ -3 \\ \hline 1 \end{array} \quad \begin{array}{r} 0100 \\ +1101 \\ \hline 10001 \end{array}$$

positive

$$\begin{array}{r} 7 = 23 \\ 6 = 22 \\ 5 = 21 \\ 4 = 20 \\ 3 = 19 \\ 2 = 18 \\ 1 = 17 \\ 0 = 16 \\ -1 = 15 \\ -2 = 14 \\ -3 = 13 \\ -4 = 12 \\ -5 = 11 \\ -6 = 10 \\ -7 = 9 \end{array}$$

$$\frac{3}{-3} \frac{3}{+13} \frac{3}{16}$$

4a

Take the number, add 16 (flip the bits and add 1)  
add them together, minus 16 (by discarding  
the remainder) (or by flipping +1 again) → only if answer is -  
4th bit in original answer → sign indicator

$$0010 \quad \begin{array}{r} 5 \\ -2 \\ \hline 0001 \end{array} \quad \begin{array}{r} 0011 \\ +1100 \\ \hline 00011 \end{array}$$

Trevor's  
answer

$$\begin{array}{r} 10.1 \\ 10011010 \\ -100 \\ \hline 100 \end{array}$$

$$\begin{array}{r} 10 \\ -11 \\ \hline 11 \\ -11 \\ \hline 00 \end{array}$$

$$0001 \quad \begin{array}{r} 2 \\ -5 \\ \hline 0001 \end{array} \quad \begin{array}{r} 0010 \\ +1011 \\ \hline 00101 \end{array}$$

4a

$$\begin{array}{r} 0 \\ -1 \\ -2 \\ -3 \end{array} \quad \begin{array}{r} 4 \\ 3 \\ 2 \\ 1 \end{array}$$

# Binary Multiplication

(Same as base-ten)

$$\begin{array}{r} 10 \\ \times 2 \\ \hline 20 \end{array}$$

$$\begin{array}{r} 1010 \\ \times 10 \\ \hline 0000 \\ 10100 \\ \hline 10100 \end{array}$$

$$\begin{array}{r} Q \\ \times S \\ \hline 1001 \\ \times 101 \\ \hline 1001 \\ 0000 \\ \hline 101101 \end{array}$$

# Binary division (You can start crying now)

$$\begin{array}{r} 10 \\ \times 2 \\ \hline 210 \\ -10 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 101 \\ 1010 \\ \hline 01 \\ 10 \end{array}$$

$$\begin{array}{r} 45 \\ 5 \overline{)45} \\ \hline 0 \end{array}$$

$$\begin{array}{r} 1001 \\ 101 \overline{)10101} \\ \hline 0101 \end{array}$$

"A hard one"

$$\begin{array}{r} 1.75 \\ 4 \overline{)7.00} \\ \hline 4 \\ 3.0 \\ 2.8 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 1.11 \\ 100 \overline{)111.000} \\ \hline 100 \\ 110 \\ 100 \\ \hline 000 \end{array}$$


$$\dots 8 \ 4 \ 2 \ 1. \ \frac{1}{2} \ \frac{1}{4} \ \frac{1}{8}$$

$$1.11 \rightarrow 1 + \frac{1}{2} + \frac{1}{4} = 1\frac{3}{4} = 1.75$$


7408 - AND  
7432 - OR  
7486 - XOR

# FULL ADDER


C8 32 86

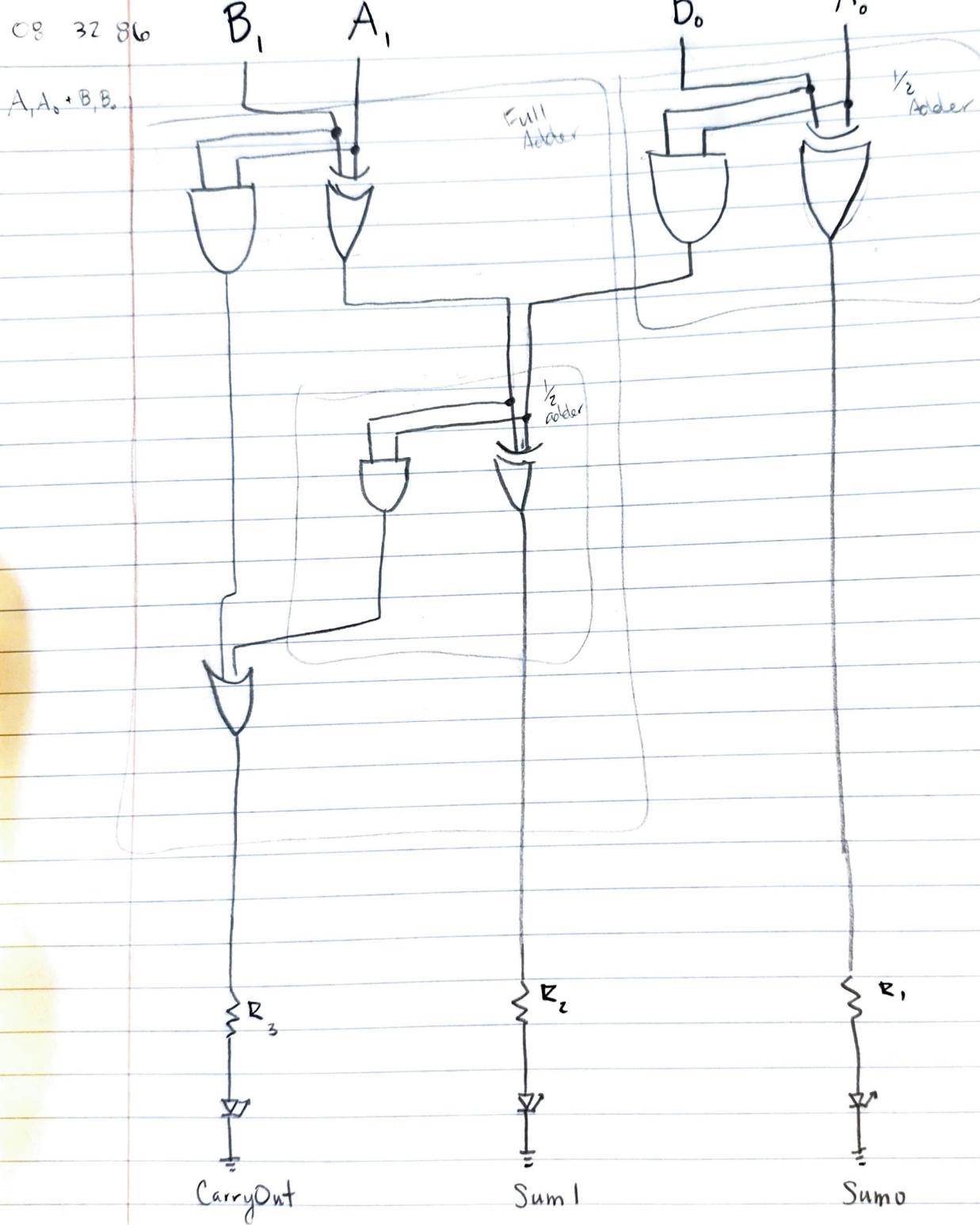
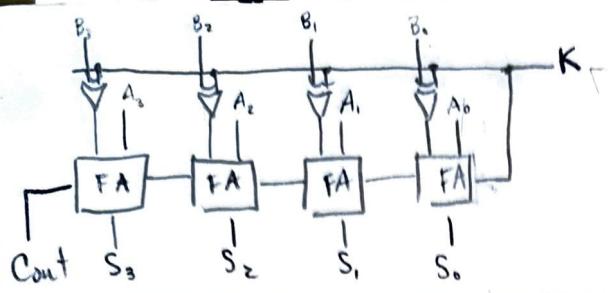
$$A_1 A_0 + B_1 B_0 = \text{CarryOut} \text{ Sum}_1 \text{ Sum}_0$$



# FULL ADDER / SUBTRACTOR

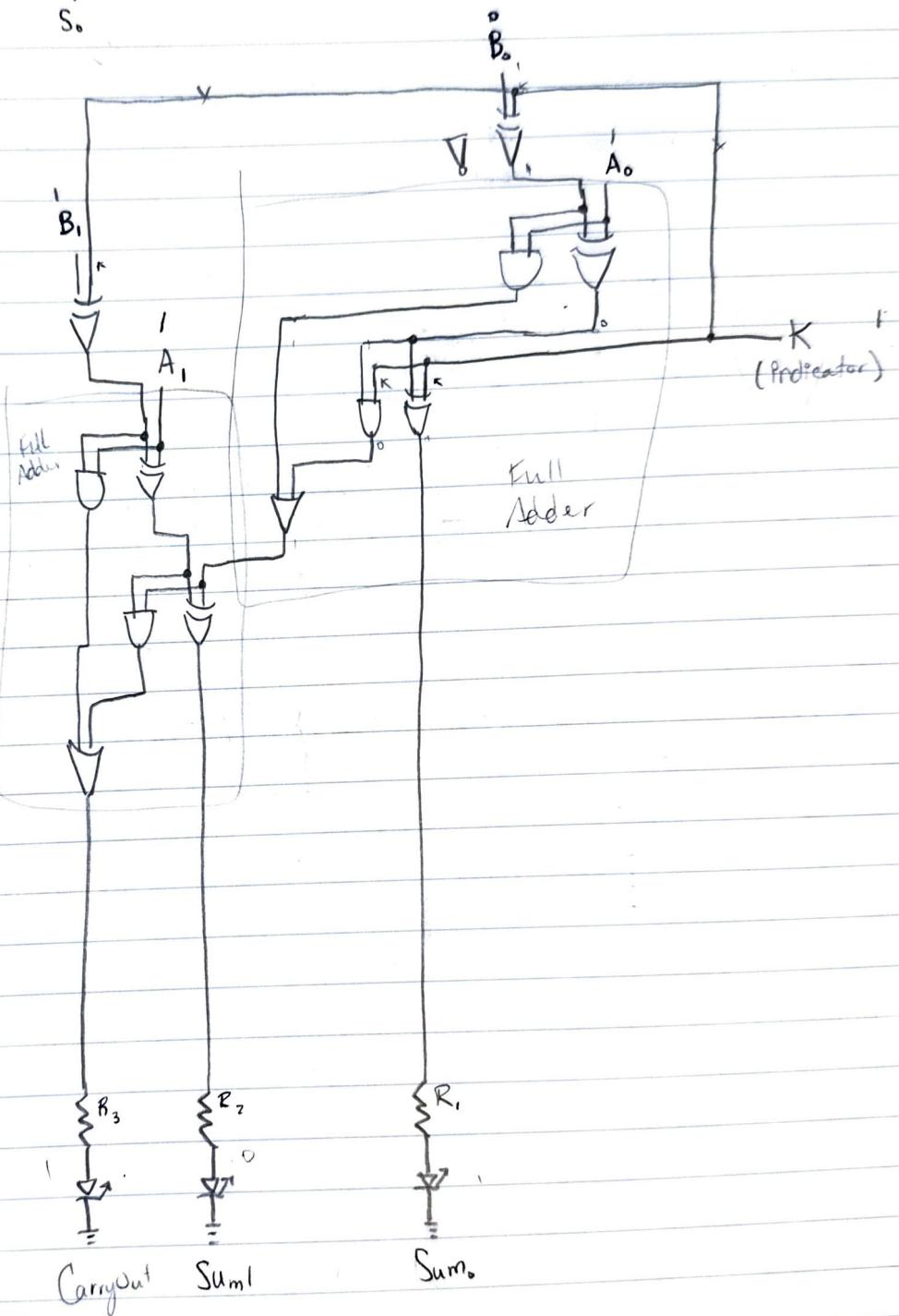




$$A_3 \cdot -B_3 = \text{Carryout Sum}_1 \text{ Sum}_0$$

(For only subtractor, change initial XOR gates to invertent and only 1 input K into second XOR in first full-adder)
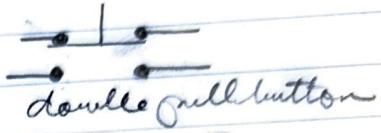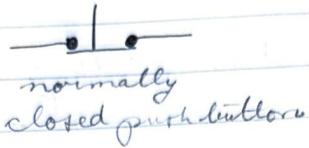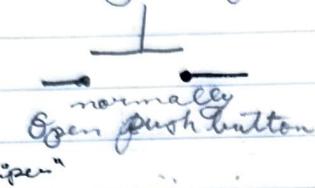
## Buttons



Tactile buttons

- May have more than one lead
- May stay on until pushed again


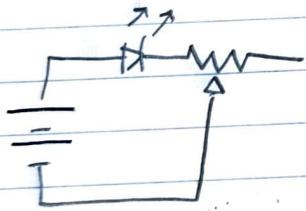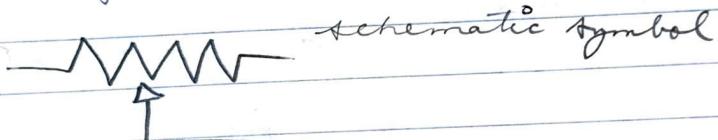
## Potentiometers

- three metal leads + pole comes out to turn
- variable resistor  $200 - 1000 \Omega$
- wiper moves along track as turn pole
- can hook up to one end and middle to control resistance



## Capacitors

- stores electric energy
- not the same as a battery

## Electrolytic capacitor


- longer lead  $\rightarrow$  anode (like CED)

## Ceramic Disc capacitor

- not polarized
- smaller values & than


## Poly film capacitors

- not polarized

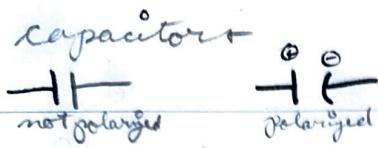


Farads (F)
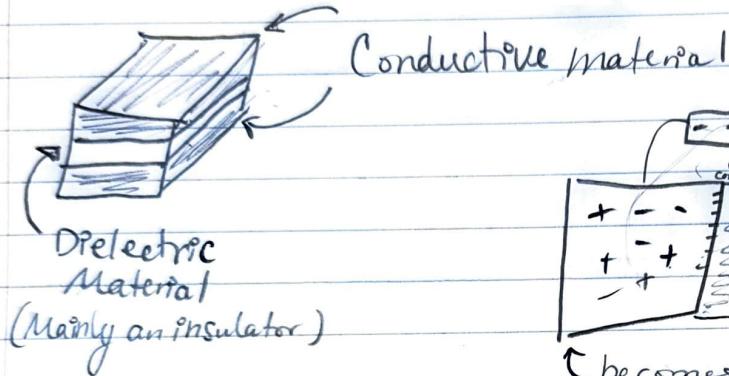
$$\mu\text{F} \rightarrow \text{micro farads} = 0.000\ 001\ \text{F}$$



No current flows "through" the capacitor

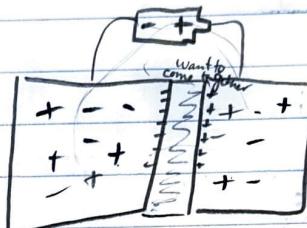

negative flows out, and leads this + charged

When connected to something, it wants to equalize and acts like a battery


$$T = \text{Resistance} \cdot \text{Capacitance (F)} \quad (\text{s})$$

T (towe) time to charge 63%

98% after 4T


$$\text{ex: } T = 10\text{s}, T \cdot 4 = 40\text{s} \rightarrow 100\% \text{ charge}$$

Capacitors in series

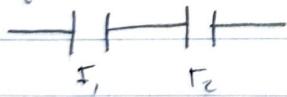

$$\frac{1}{T_F} = \frac{1}{C_1} + \frac{1}{C_2}$$

Parallel

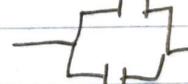


$$T_F = C_1 + C_2 \dots$$

NOR

Latch set, reset


$\Rightarrow D \rightarrow D$  SR latch - a one bit memory

$\Rightarrow D \rightarrow D$   
NAND

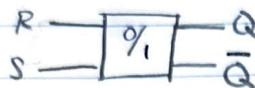

\* Reset w/ latch w/ NOR gate: controlled by pulses

high logic\*

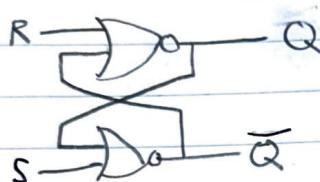

To reset, R put to 1 and  $\bar{Q}$  is 1


To Set, S = 1 and Q is 1

S	R	Q	$\bar{Q}$
0	0	0	1
0	1	0	1
1	0	1	0
1	1	0	0

← INVALID. Leads to "race" problem

\* Reset w/ latch w/ NAND gate: "active-low SR latch"

low logic\*

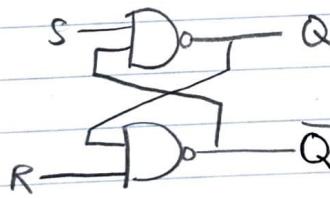


S	R	Q	$\bar{Q}$
0	0	1	1
0	1	0	0
1	0	0	1
1	1	0	1



\* Debouncing effect? \*



## And-OR Latch

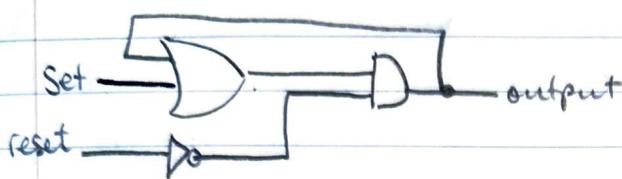

## Gated latch

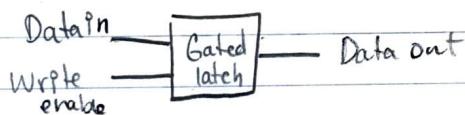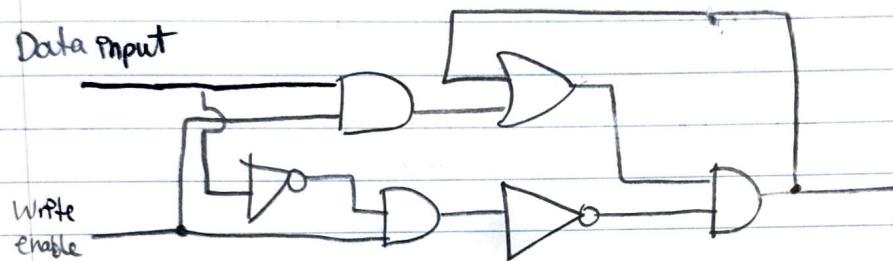


In order to change memory,  
the write enable needs to be on

Group of latches → register  
the # of latches → width


## 8-BIT REGISTER

D Data in  
E Write enable  
Q Data out

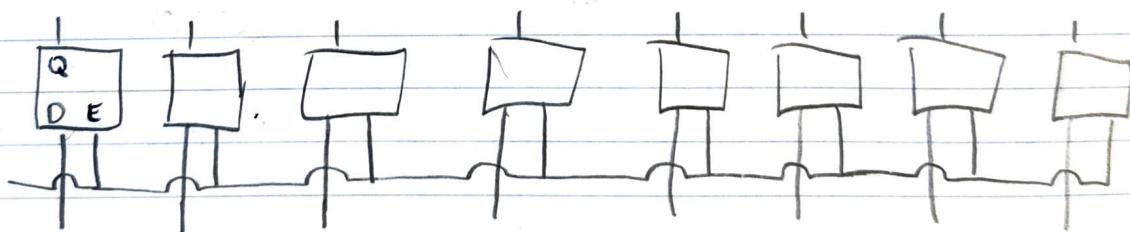

Tots of wires? solution → matrix

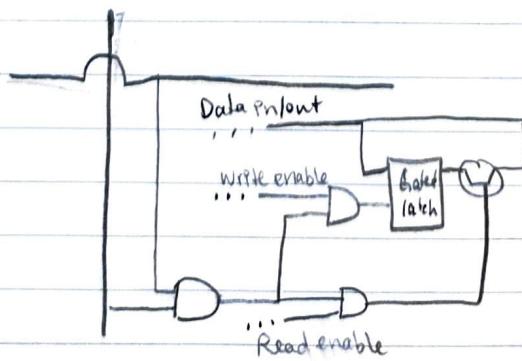
to turn on latch, turn on row and column  
AND write enable




Memory address → binary

12,8  
11001000

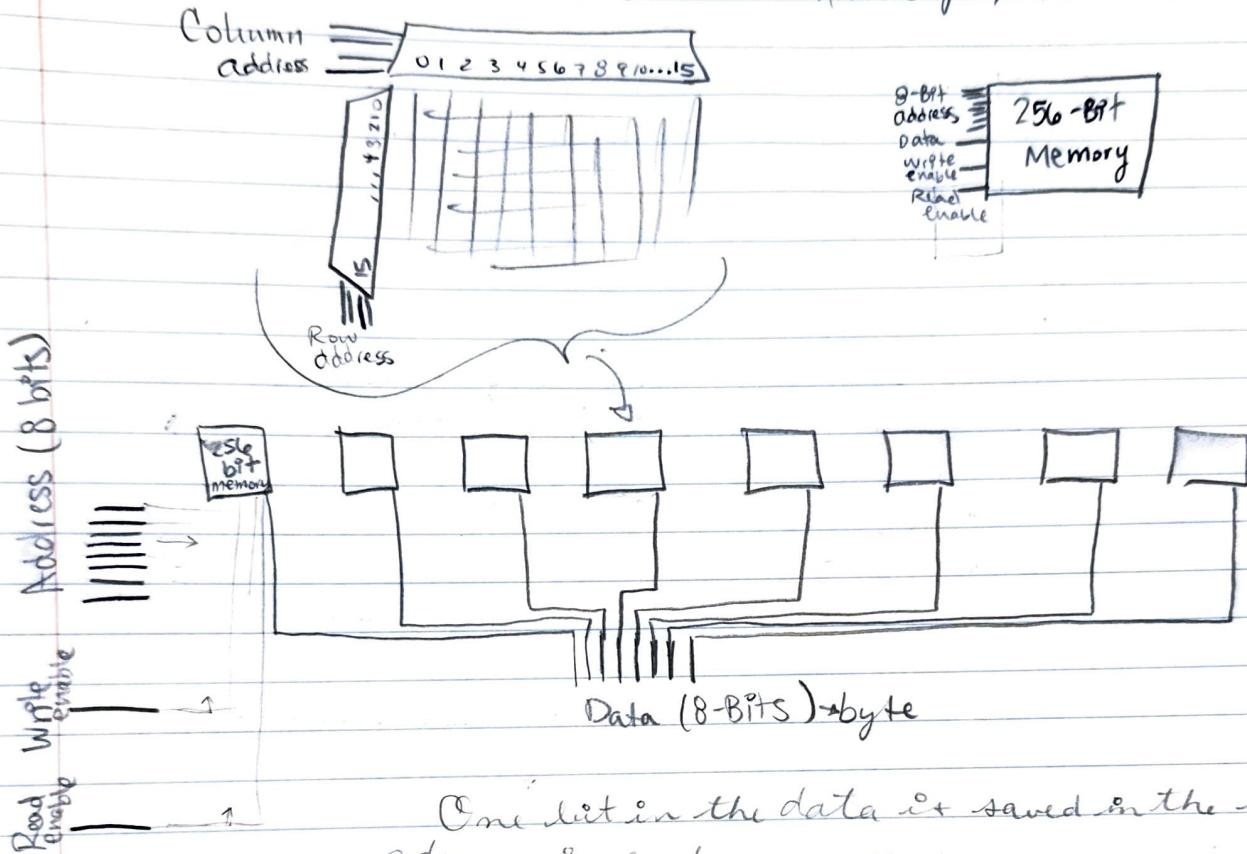To choose row and column  $\rightarrow$  multiplexer



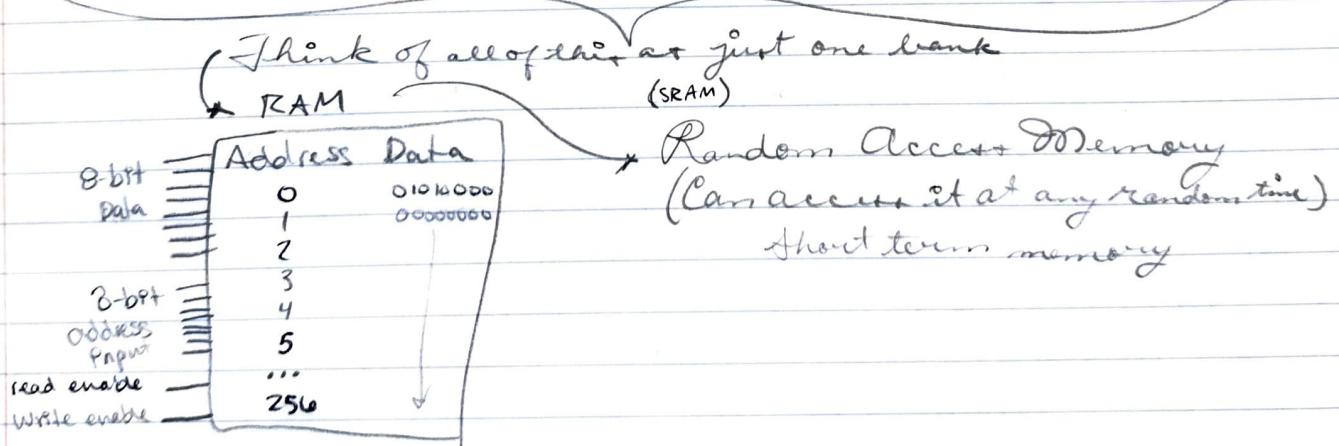One bit in the data is saved in the same address in each memory




Cache

### Static RAM

- Stores less
- + Faster access
- + Use less power

6  
istors

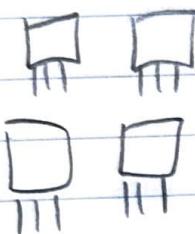

(only transistors)

= 1 Bit

Less storage because  
the transistors take up space

- Uses boolean logic
- constant state
- faster access


- Low Capacity
- Hard change
- Fast access

★ Small but important  
info ★

Main memory
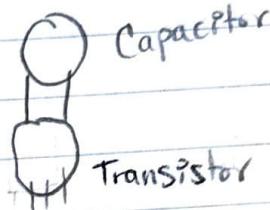
### Dynamic RAM

- + Stores more
- + Faster rewrite
- + cheaper



> 1 BIT

Capacitor loses charge super fast, but  
that's okay because RAM changes so fast  
anyway

- High Capacity
  - Easy change
  - Slow access
- \* Everything else \*

- SRAM is to RAM as RAM is to computer
- DRAM is to RAM as HardDrive is to computer


# flip-flop

'edge-triggered' → has a clock that changes periodically

## CPU (Central Processing Unit)

- executes programs

Micro-architecture

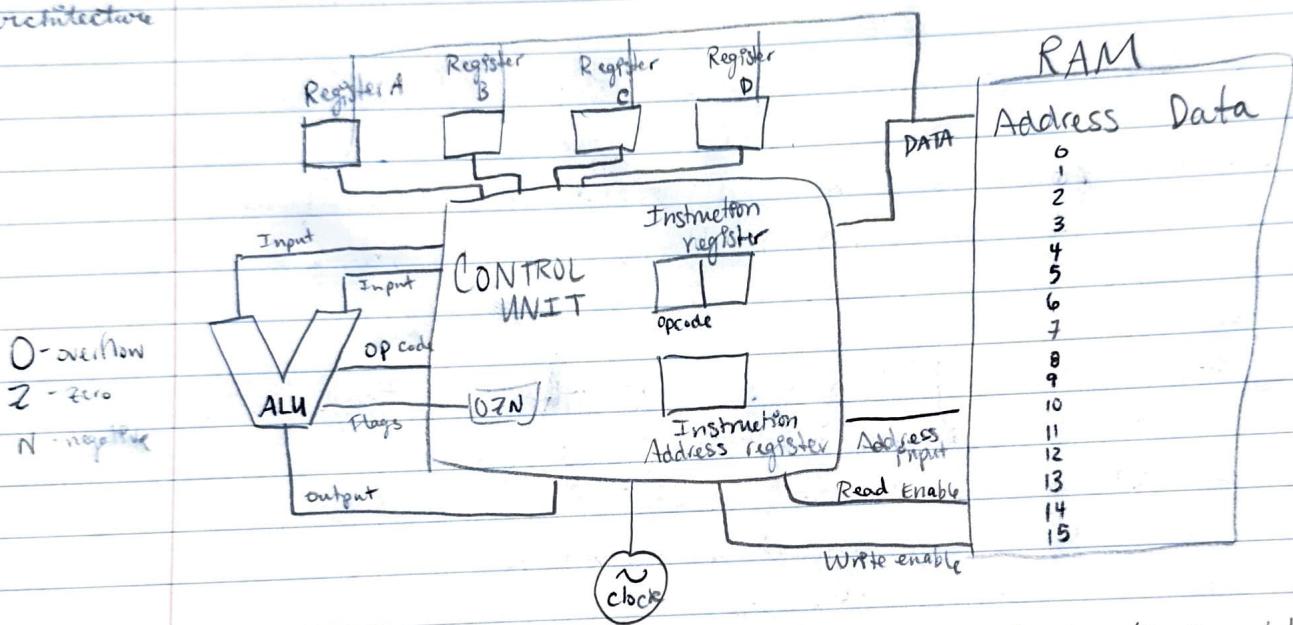

Fetch phase: retrieve instructions, Instructions address register connects to RAM, and it copied into instruction register

Decode Phase: First 4 bits → "opcode", which corresponds with instructions in instruction table  
 RAM address → last 4 bits  
 - Put into control unit

Execute phase: Performs instruction, and add 1 to the instruction address register

### Instruction table

LOAD-A	Read RAM location into rA
LOAD-B	Read " " " " rB
STORE-A	Write from rA into RAM location
ADD	Add two registers, store result into second register
...	...

4-bit opcode

0010  
0001  
0100  
1000  
...

Address or register

4-bit RAM address  
" "

" "  
2-bit register ID,  
2-bit register ID  
..."

Speed at which a CPU can carry out - Clock speed  
- Measured in Hertz = 1 cycle/second

Variable length instructions? - instructions can be any length??

Pseudo-code → informal code instructions

Von Neumann → instructions and data put in memory


Decode - type of code to be executed is determined directly to machine language

Optical Mouse - takes 2,000 pictures/second, and compares it to the previous one to compare where it has gone,  $1600 \text{ pixels}^2/\text{in}^2$   
- images not stored  
- sends info to CPU, occurs in the "Kernel" operating system

Computer monitors


RGB color scheme → can make any color

LCD monitors -

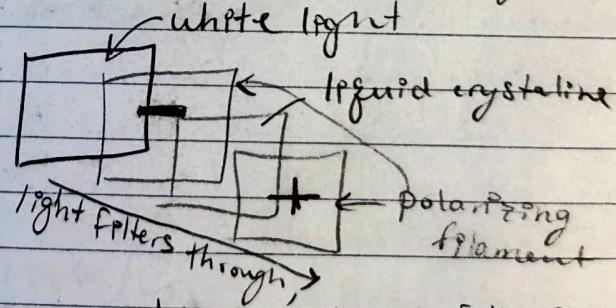

and each pixel on the filter screen is charged by an electrical signal, allowing it to change the color

LED monitor, has a layer of LED pixels

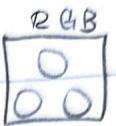

RGB each has 255 different shades it can be  
- Computer uses hexadecimal

3F | AB3  
R G B

## Touchscreen

Resistive - like a keyboard but it's pushing down a conducting polyester onto a conducting glass

Capacitive - multiple layers of conductive glass that change when a conductive finger touches it


Infrared - interrupt beams of light

Surface Acoustic Wave - uses Ultrasonic sound waves

Near field imaging - electric field changes and registers touch

# Computer Networks


Ethernet

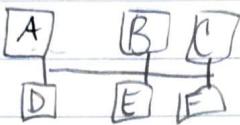

Mac address → to which computer

Bandwidth - rate a carrier can transmit data

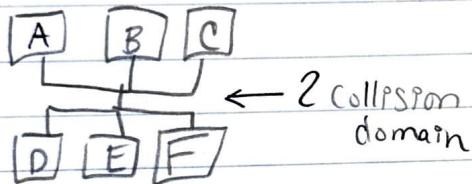Exponential backoff - if the line is in use, computer waits 1 second, ... 2... 4... 8...



Message switching - messages passed through several steps

Messages split into "packets", each has an address, or IP address (Internet Protocol)

- "Packet switching"


## Internet!!

Local area network → LAN

Wide area network → WAN

Traceroute

### Internet Protocol

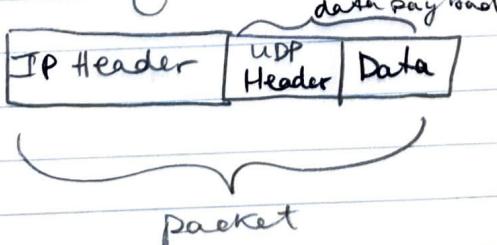

### User datagram Protocol

= Port checksum ...

port # → which application


checksum → adds all the data, and checks to see if it was the same b4 & after. If not, something went wrong

## Transmission Control Protocol - TCP/IP

- address
- checksum
- given sequential numbers (can be un-scrambled)
- sent a an "ACK" (acknowledgment) that it was sent alright

Domain Name System → "phonebook" google.com → 172.27.7.28:80

## Domain Structure

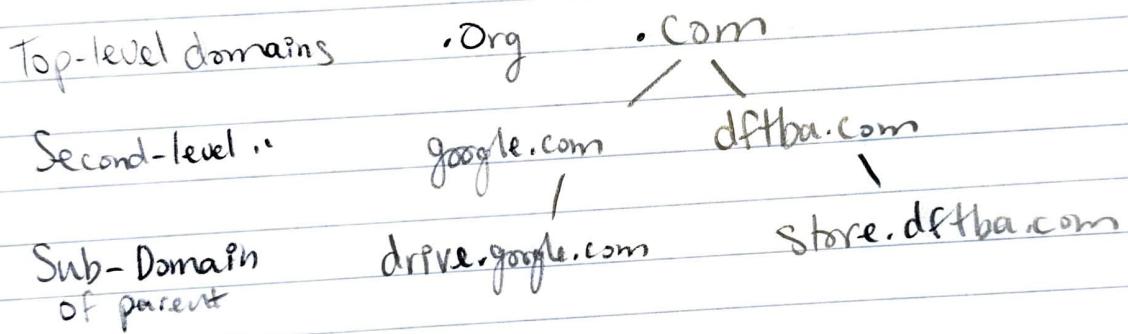

## Layers of OSI Model (Open system interconnection)

Application

Presentation

Session layer - Open + close connection

Transport layer - UDP + TCP

Network layer - routing

Data link layer - mediate access to ↓


Physical layer - wires + air

server - computer that holds the data for a website  
Coaxial - connects to great network ↗  
Modem + Router = Gateway ↙  
- Provides ethernet & wifi  
Mac address → device  
IP address → gateway

The cloud → data saved in a server backed up

The World Wide Web ≠ internet  
↳ connected by hyperlinks (hypertext)  
↳ specified by URL

Hypertext transfer Protocol → HTTP

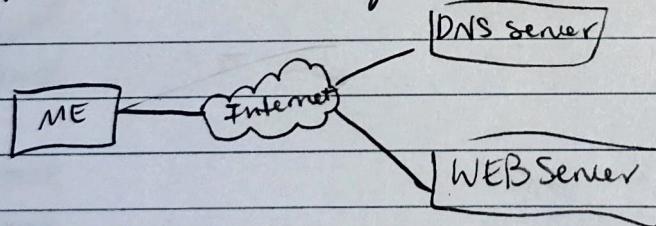

Hypertext Markup Language - HTML

Search Engine → searches websites for words

Net neutrality - debate of whether all packets should be treated equally