

# Electric Circuit Analysis

Memorize scientific notation  
Prefixes

$$1.3E3 = 1.3 \cdot 10^3$$

"mantissa"

$$5\mu\text{m} = 5E-6$$

$$10\text{KV} = 10E3$$

$$2E2\text{g} = 0.2E3 = 0.2\text{kg}$$

$$e = -1.602 \times 10^{-19}\text{C}$$

$$1\text{C} = 1/1.602E19 = 6.24E18 \text{ electrons}$$

$$I = \frac{dq}{dt} \quad \text{or} \quad \text{C/S} \quad 1\text{A} = \text{1 C/S}$$

$$10\mu\text{A} \cdot 2\text{k}\Omega = 10E-6 \cdot 2E3 = 20$$

~  
400  
2.16  
2.5  
s  
20


## SI prefixes

$10^{18}$	exa	E	my exa gf said I'm shaped like a snowman
$10^{15}$	peta	P	my pet goldfish?
$10^{12}$	tera	T	Twelve → Tera
$10^9$	giga	G	me singing at my first gig!
$10^6$	mega	M	mega baymax! Big hero 6!
$10^3$	kilo	K	3E KISS mary Kilo
$10^2$	hecto	h	only 2 places. heaven or hell
10	deka	da	$\approx 50$ cards deka cards
$10^{-1}$	deci	d	first decimal
$10^{-2}$	Centi	c	centimeter = 100
$10^{-3}$	milli	m	$m \rightarrow 10^{-3}$ milli
$10^{-6}$	micro	μ	new (μu) is pretty small, it would be too if 3000 m <sup>2</sup> / 1000
$10^{-9}$	nano	n	nano → nine
$10^{-12}$	pico	p	1...2... pico few... PP 100!
$10^{-15}$	femto	f	femto → fifteen
$10^{-18}$	atto	a	1@ don't ato me right now!
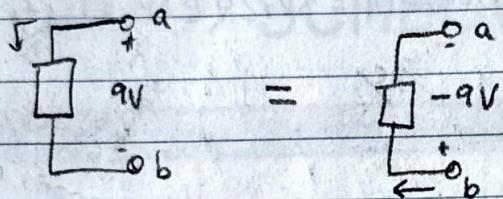
## Section 1.4 Voltage

emf - external electromotive force (battery)  
 ↳ voltage / potential difference

$$1 \text{ Volt} = 1 \text{ J/C} = 1 \text{ N-Meter/C} = \frac{\text{Aw}}{\text{A}} \quad \text{or } q$$



electric current → through an element  
 " voltage → across " or between points

## 1.5 Power & Energy


Power is the time rate of expending or absorbing energy, watts (W)

$$P = \frac{dw}{dt} = \dot{E}_S = \dot{E}_C \cdot I_S = VI$$

↳ instantaneous power + power, element is absorbing  
 - power, element is supplying

<sup>PS used here</sup> Passive sign convention: when current enters through + terminal and  $P = +VI$

Active is opposite)

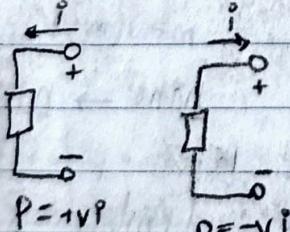

Passive sign

Active sign

$$+ \text{Power absorbed} = - \text{Power supplied}$$

$$\Sigma P = 0$$

Energy is the capacity to do work, measured in Joules (J)

Watt-hours (Wh)

$$1 \text{ Wh} = 3,600 \text{ J}$$

$$Q(t) \text{ (charge)} = \int_{t_0}^t i(t) dt$$

## 1.1.6 Circuit Elements


Active element: able to generate energy

Passive: not


→ Generator, batteries, operational amplifier  
resistor, capacitor, inductor

ideal independent source: active element that provides a specified voltage/current that is independent from other elements

batteries/  
generators


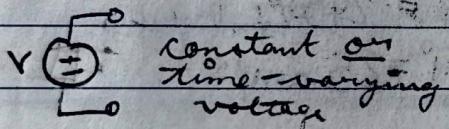


only constant  
voltage (DC)

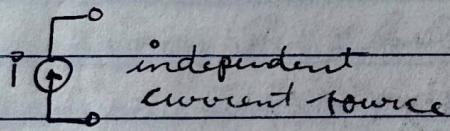


transistors,  
operational  
amp, integrated  
circuits

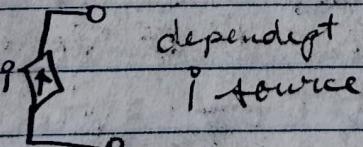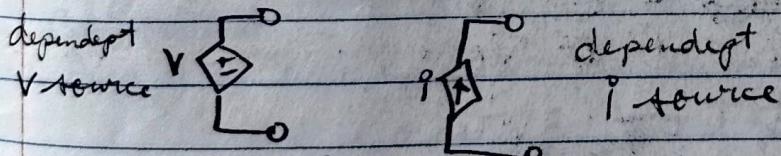ideal dependent (or controlled) source: source quantity is controlled by another voltage/current



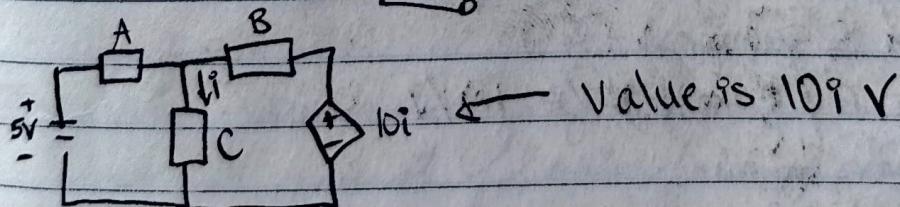4 types:  
V-controlled V source (VCSV)  
current-controlled V source (CCSV)  
(VCCS)  
(CCCS)



\* Ask about p4 on example 1.7!

- why is it -0.288

- where are the terminals??

- Why is voltage positive ??

Voltage: "how much energy was expected to move a unit of charge from a to b  
• sep pos + neg creates voltage

Energy = P · t kWh-hours (kW per hour)

1.) 6KW charger, 240V

$$P = VI$$

$$6\text{KW} = 6,000 \text{W} = 240\text{V} \cdot I$$

$$I = 25 \text{amps}$$

2.)  $6\text{KW} \cdot 4\text{h} = 24\text{kWh}$

3.) \$0.112 per kWh  $\rightarrow 2.68$

4.)  $\$2.68 / 70 = 4¢ / \text{mile}$

5.)  $\$4.00 / 25 = 16¢ / \text{mile}$

Current going into positive  $\rightarrow$  power consumed

# Basic Electr. Hw.

$$P_1 = 10V \cdot 1.0A = 10W$$

$$P_2 = 3V \cdot 0.5A = 1.5W$$

$$P_3 = 2V \cdot 1.0A = 2W$$

$$P_4 = 2.5W$$


$$P_5 = 8V \cdot 0.5A = 4W$$

$$1.2\text{ kW} \cdot 2\text{ h} = 2.4 \text{ kWh} \therefore 1S =$$

$$1\text{ kW} \cdot \frac{1}{6}\text{ h} = 0.167$$

## Chapter 2

Section 2.1 (intro): Remember to Analyze stuff.  
Section 2.2 Ohm's Law:

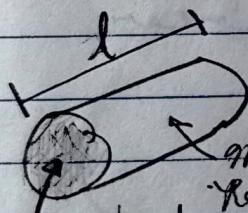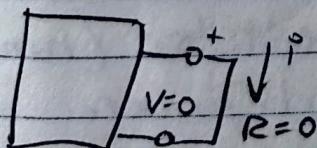

$$R = \rho \frac{l}{A}$$

Material w/  
Resistivity "ρ"  
Cross-sectional  
Area A


$$\text{Ohm's law} : V = IR \quad R = \frac{V}{I} \quad I = \frac{V}{R} = \frac{A}{l} \cdot \rho$$

Must be passive sign convention.

Current must flow from high to low for  $V = IR$ . If low to high,  $V = -IR$ .



"Short circuit"

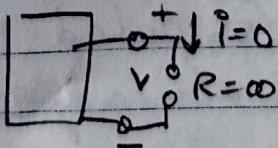

Open circuit ( $R = \infty$ )

Fixed resistor: no main + constant



- wirewound

- composition = large resistance

Variable resistor: changes

- potentiometer

- also wirewound or composition

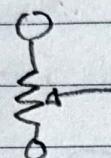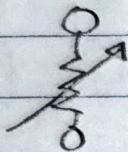

Variable  
resistor in  
General

potentiometer

Resistors that obey Ohm's law: linear

" " don't: Nonlinear

↳ lightbulb, diode

Conductance:  $G = \frac{1}{R} = \frac{i}{V}$

— how well conducts current

unit → mho or  $\Omega^{-1}$

↳ Siemens (S)

$$1S = 1\Omega^{-1} = 1A/V$$

$$10\Omega = 0.1S$$

$$P = VI = i^2 R = \frac{V^2}{R}$$

↳ power dissipated in a resistor (non- $P_{max}$ )

Resistors always absorb power.

Reg = "equivalent resistance"

$$V = iR \rightarrow i = V/R \quad P = \frac{V^2}{R}$$

$$P = iV$$

$$V = iR$$

$$P = i^2 R$$

1.)  $V = 10V, R_{eq} = 100\Omega$

$$i = 10/100 = 0.1A$$

2.)  $i = 250E-6 A \quad R = 1E3 \quad V = 25V$


3.)  $R = 2\Omega \quad i = 100E-3 A \quad P = .2W$

4.)  $R = R \quad V = 3V \quad i = ?$

$$V = iR \quad 3V = iR$$

$$\begin{aligned} & 5\Omega \\ & P = \quad i = \frac{1}{5}A \\ & 1V \quad i = \frac{1}{5}A \\ & P = \frac{1}{5}A \end{aligned}$$

Increased by 300%

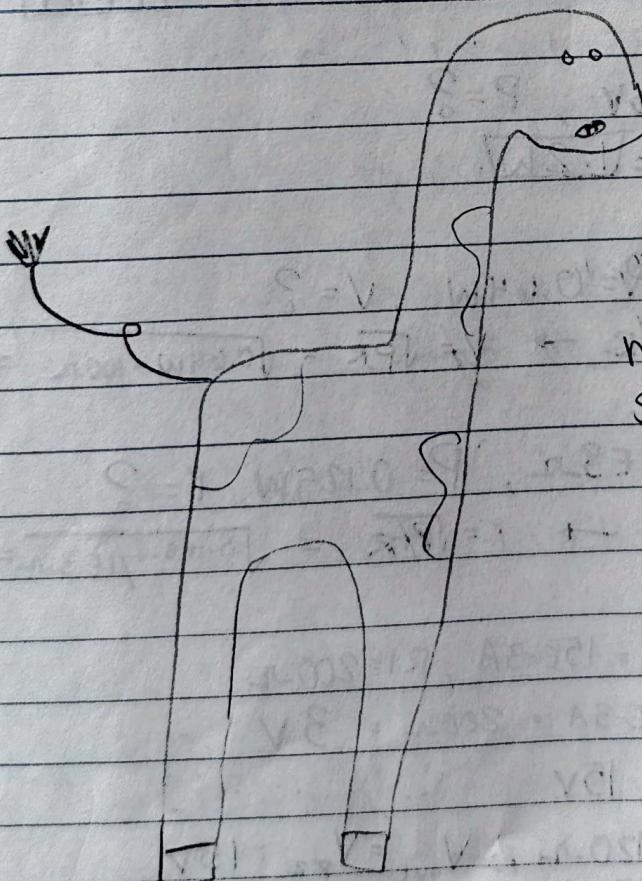

"I'm so grateful I'm  
not a giraffe. I'm tall and  
skinny, but at least I'm not  
tall, skinny and stupid."

# Ohm's Law HW

Seth Ricks  
Bro. Jack

1.)  $V = 6V, R = 3.3 \text{ k}\Omega = 3300 \Omega, i = ?$   
 $i = \frac{6V}{3300 \Omega} = .0018 A = 1.8 \text{ mA}$

2.)  $V = 8V, i = 3.3 \text{ mA} = 3.3 \times 10^{-3} A, R = ?$   
 $R = \frac{8V}{3.3 \times 10^{-3} A} = 2424 \Omega = 2.4 \text{ k}\Omega$

3.)  $i = 320 \mu A = 320 \times 10^{-6} A, R_{eq} = 10 \text{ k}\Omega = 10 \times 10^3 \Omega, V = ?$   
 $V = 320 \times 10^{-6} A \cdot 10 \times 10^3 \Omega = 3.2 \text{ V}$

4.)  $V = 9V, G_{eq} = 1.0 \text{ mS} = 1.0 \times 10^{-3} S, P = ?$   
 $\frac{1}{R} = S = \frac{i}{V} \rightarrow i = 1.0 \times 10^{-3} S \cdot 9V = 9 \text{ mA}$

5.)  $i = 0.2A, V = 6V, P = ?$   
 $P = 0.2 \cdot 6 = 1.2 \text{ W}$

6.)  $R_{eq} = 100 \Omega, P = 0.64 \text{ W}, V = ?$   
 $P = \frac{V^2}{R} \rightarrow V = \sqrt{PR} = \sqrt{0.64 \text{ W} \cdot 100 \Omega} = 8V$

7.)  $R_{eq} = 1 \text{ k}\Omega = 1000 \Omega, P = 0.125 \text{ W}, i = ?$   
 $P = i^2 R \rightarrow i = \sqrt{P/R} = \sqrt{0.125 \text{ W} / 1000 \Omega} = 0.011 A = 11 \text{ mA}$

8.)  $V_{R1} = ?, P = 15 \text{ mA} = 15 \times 10^{-3} A, R1 = 200 \Omega$   
 $V_{R1} = 15 \times 10^{-3} A \cdot 200 \Omega = 3V$

$V_{out} = 5(3V) = 15V$

$i_{R2} = ?, R2 = 120 \Omega, V_{out} = V_{R2} = 15V$   
 $i_{R2} = \frac{15V}{120 \Omega} = 0.125 A = 12.5 \text{ mA}$

$$i_{R1} = ?, V = 6V, R1 = 300\Omega$$


$$i_{R1} = \frac{6V}{300\Omega} = 0.02A$$

$$I_{out} = (2.5)(0.02A) = 0.05A$$

$$V_{R2} = ?, P_{R2} = P_{out} = 0.05A, R2 = 150\Omega$$

$$V_{R2} = 0.05A \cdot 150\Omega = \boxed{7.5V}$$

Question:

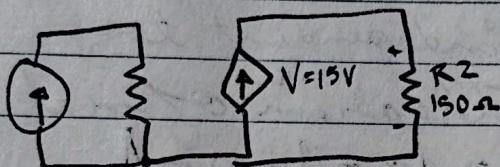

How can we assume that the voltage across R2 is 15V?

## 2.3 Nodes, Branches, and Loops

- \* Branch - a single element such as a voltage source or a resistor
- \* Node - point of connection between two or more branches
- \* loop - any closed path in a circuit
  - \* mesh - independent loop

fundamental theorem of network topology:  $b = l + n - 1$

$$b = \text{branches} = \text{meshes} + \text{nodes} + 1$$


Difference between circuit & network?

## 2.4 Kirchhoff's Laws

Kirchhoff's current law: (KCL)


$$\sum_{n=1}^N i_n = 0$$

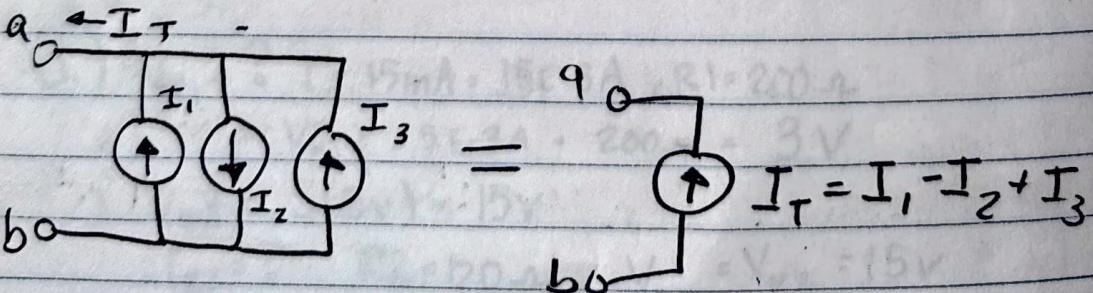The sum of the currents entering a node is equal to the sum of the currents leaving the node.  
- can be applied to a closed boundary



# Kirchoff's voltage law (KVL):

$$\sum_{m=1}^M V_m = 0$$

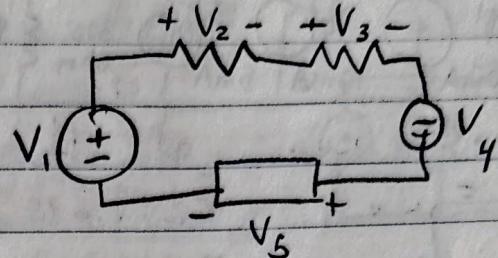


$$-V_1 + V_2 + V_3 - V_4 + V_5 = 0$$

$$V_2 + V_3 + V_5 = V_1 + V_4$$

Sum of Voltage drops = Sum of Voltage rise

\* Why is this a negative voltage drop?

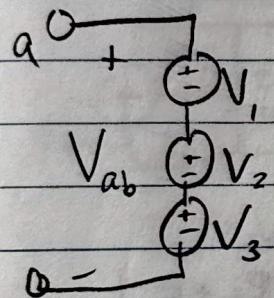

$$V_{ab} = V_1 + V_2 - V_3$$


$$V_{ab} = V_1 + V_2 - V_3$$

$$V_S = V_1 + V_2 - V_3$$

$$V_{ab} = V_1 + V_2 - V_3$$


→ All points on a single node have the same voltage (not current)

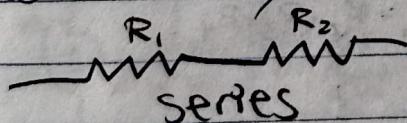Series: exclusively share a node → same  $i$  not  $V$





Not Series

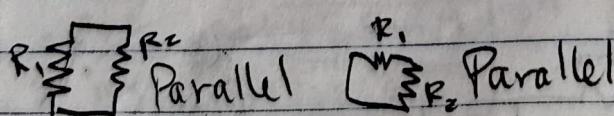Parallel: 2 nodes in common → same  $V$  not  $i$



- Okay to have something putting  $q_H$

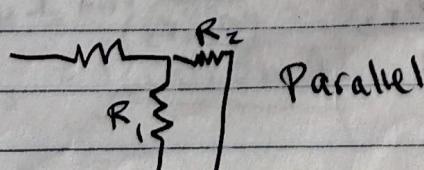

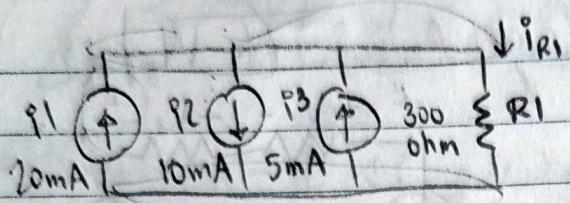

1.) K nodes


$$2.) I_1 + I_3 = I_2 + I_{R1}$$

$$3.) 20\text{mA} + 5\text{mA} = 10\text{mA} + I_{R1}$$

$$I_{R1} = 15\text{mA}$$


$$4.) V_{R1} = 4.5V$$

$$5.) V_{I2} = 4.5V$$

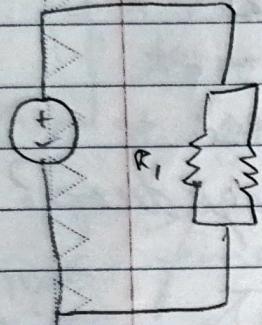

$$R_{eq} = R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


Tab 1:

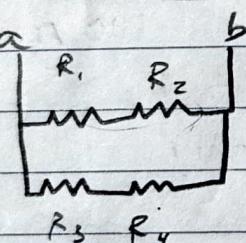3.) 

$$R_{eq} = \frac{(R_1 + R_2) \cdot (R_3 + R_4)}{(R_1 + R_2) + (R_3 + R_4)}$$


$$= (0.82 + 4.3) \cdot (22 + 6.2)$$

$$0.82 + 4.3 + 22 + 6.2$$

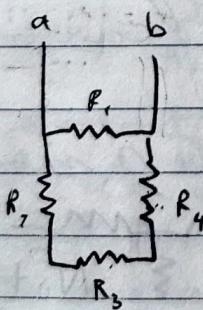4.) 

$$R_{eq} = \frac{R_1 (R_2 + R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$\underline{\underline{R_1}} \quad \underline{\underline{R_2+R_3+R_4}}$$

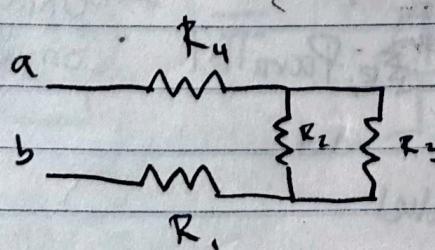5.) 

$$\frac{R_2 \cdot R_3}{(R_2 + R_3)} + R_4 + R_1$$


# KCL HW

① Number of branches: 7

Number of nodes: 5

Number of loops: 6


Number of master: 3

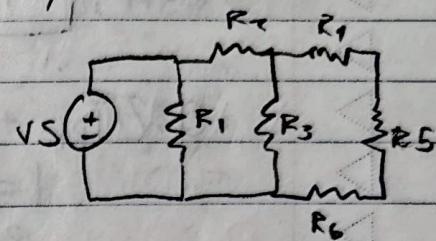

Components in parallel: VS & R1

Components in series: R4 + R5 + R6

②

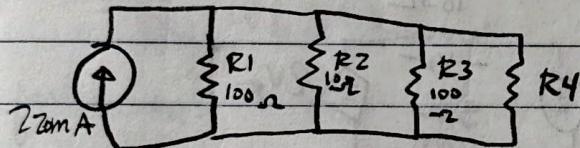

$$I_{R1} = 60.0 \text{ mA} \quad V_{R1} = 0.06 \text{ A} \cdot 100 \Omega = 6 \text{ V}$$

$$I_T = 220 \text{ mA}$$


$$V_{R4} = 6 \text{ V}$$

$$I_T = 220 \text{ mA} = 60.0 + 60.0 + 60.0 + I_{R4}$$

$$I_{R4} = 40.0 \text{ mA}$$

$$P_{R4} = VI = 6 \text{ V} \cdot 0.04 \text{ A} = 0.24 \text{ W}$$

③

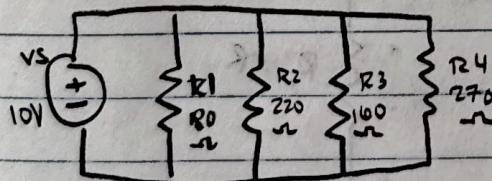


$$I_{R1} = \frac{10 \text{ V}}{180 \Omega} = 0.0556 \text{ A} = 55.6 \text{ mA}$$

$$I_{R2} = \frac{10 \text{ V}}{220 \Omega} = 45.5 \text{ mA}$$

$$I_{R3} = \frac{10 \text{ V}}{160 \Omega} = 62.5 \text{ mA}$$

$$I_{R4} = \frac{10 \text{ V}}{270 \Omega} = 37.0 \text{ mA}$$

$$I_S = 200.5 \text{ mA}$$

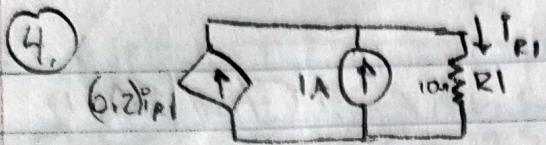

$$0.2i_{R1} + 1 = i_{P1}$$


$$1 = 0.8i_{R1}$$

$$i_{R1} = 1.25 \text{ A}$$

$$V_{P1} = i_{R1} \cdot R1 = 12.5 \text{ V}$$

$$P_{R1} = 1.25 \text{ A} \cdot 12.5 \text{ V} = 15.6 \text{ W}$$

KVL practice;  
find  $V_x$  and  $V_o$

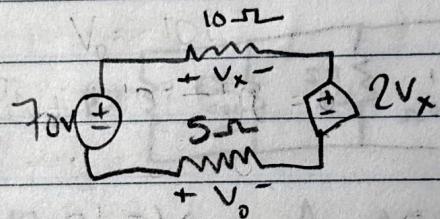


why - twice?

$$-70 + V_x + 2V_x - V_o = 0 \quad V_x = 10^\circ \quad V_o = -5^\circ$$


$$-70 + 10^\circ + 20^\circ + 5^\circ = 0$$

$$i = 2$$
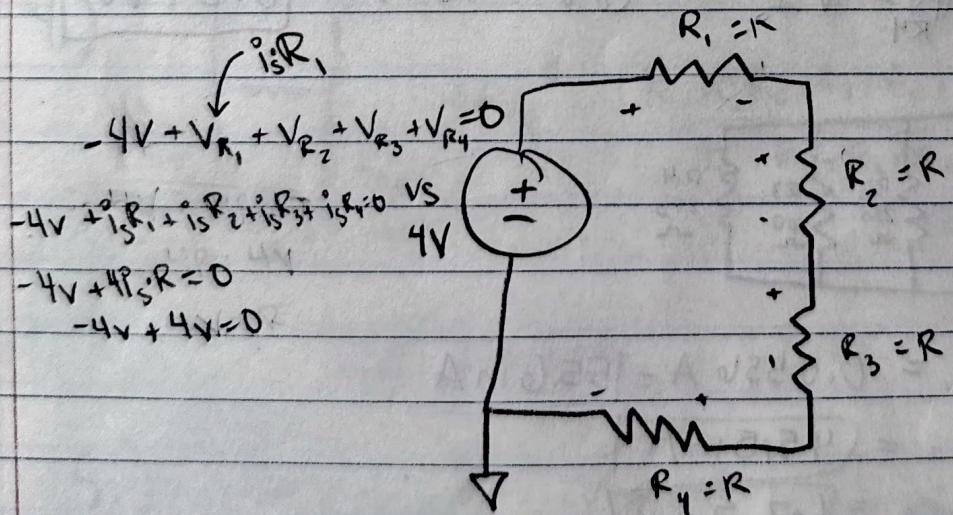
$$V_x = 20 \text{ V}, V_o = -10 \text{ V}$$


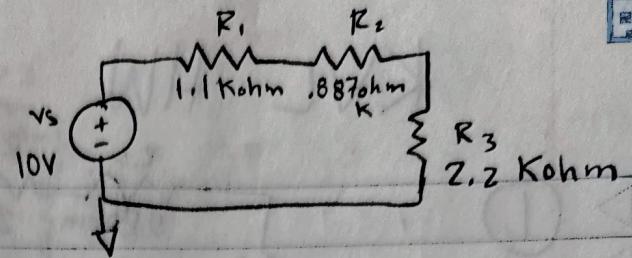
$$I_S = \frac{10V}{(1.1 + .887 + 2.2) \text{ kohm}} = 2.39 \text{ mA}$$



$$V_{R1} = .00239 \cdot 1100 \Omega = 2.6 \text{ mV}$$

$$V_{R2} = .00239 \cdot 887 \Omega = 2.12 \text{ V}$$

$$V_{R3} = .00239 \text{ A} \cdot 2200 \Omega = 5.26 \text{ V}$$

$$-10V + V_{R1} + V_{oc} + V_{R4} = 0$$

$$V_{oc} = V_{R1} + V_{R4}$$


$$\begin{aligned} V_1 + V_2 &= 15 \\ -2 + V_2 + V_2 &= 15 \end{aligned}$$

$$2V_2 - 2 = 15$$

$$2V_2 = 17$$

$$V_2 = \frac{17}{2}$$
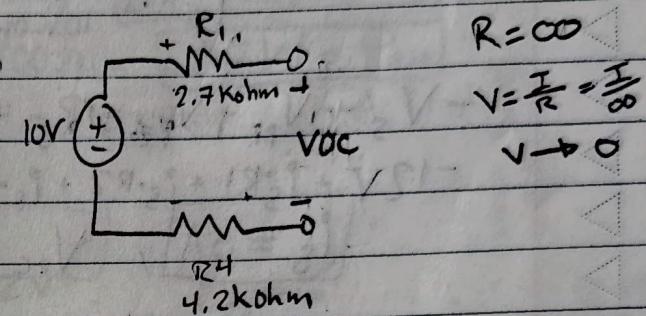
$$\begin{matrix} V_2 \\ V_1 \\ 8.5, 6.5 \end{matrix}$$




# KVL HW

Seth Ricks  
ECEN 180

1/20/2023

(1)

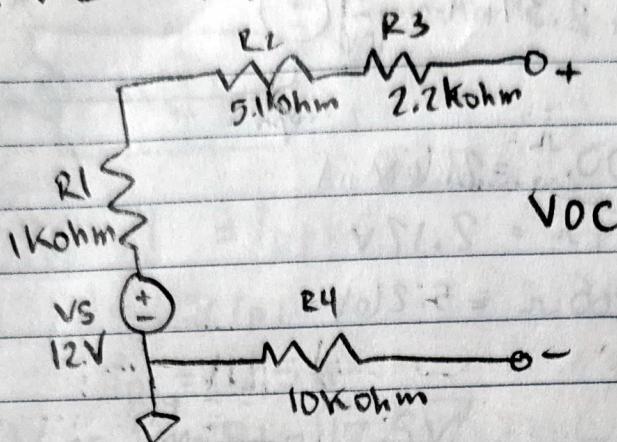


$$-V_s + V_{R1} + V_{R2} + V_{R3} + V_{oc} + V_{R4} = 0$$

$$-12V + i_s \cdot R1 + i_s \cdot R2 + i_s \cdot R3 + V_{oc} + i_s \cdot R4 = 0$$

$$i_s = 0A, V_{oc} = 12V$$

(2)

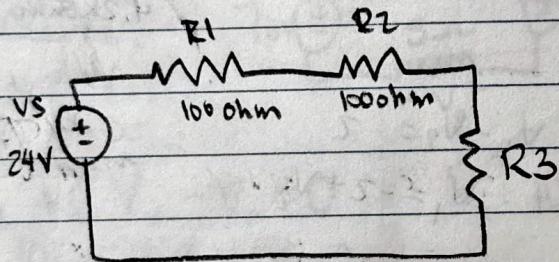

$$V_{R1} = 4.80V \quad i_{R3} = ? \quad P_{R3} = ?$$

$$i_{R1} = 4.80V / 100\Omega = 0.048 A \quad i_{R3} = 48 mA$$

$$-VS + i_s R1 + i_s R2 + i_s R3 = 0$$


$$-24 + 0.048(100 + 100 + R3) = 0$$

$$R3 = 24 / 0.048 - 100 - 100$$

$$R3 = 300 \Omega$$

$$P_{R3} = i^2 \cdot R3 = 69 mW$$

(3.)

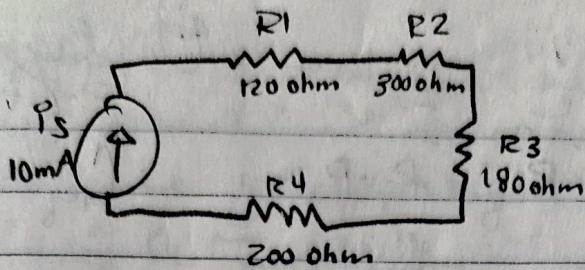


$$V_a = I_s (R_1 + R_2 + R_3 + R_4)$$

$$= 0,01 \text{ A} (120 + 300 + 180 + 200) = 8 \text{ V} = V_a$$

$$P_{R4} = I_s^2 \cdot R_4 = (0,01 \text{ A})^2 \cdot 200 \Omega = 20 \text{ mW} = P_{R4}$$

(4.)

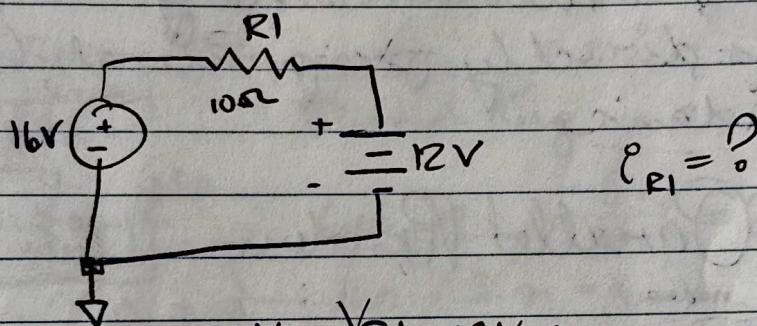


$$= V_s + V_{R1} + 12 \text{ V} = 0$$

$$-16 \text{ V} + V_{R1} \cdot 10 \Omega + 12 \text{ V} = 0$$

$$V_{R1} = 0,40 \text{ A}$$

(5.)

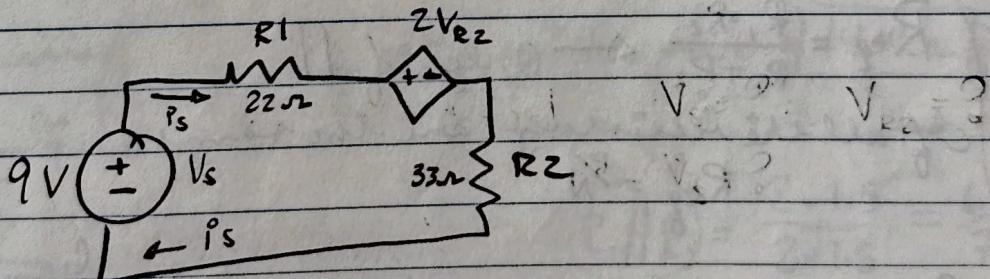

$$-V_s + V_{R1} + 2V_{R2} + V_{R2} = 0$$

$$-9 + i_s \cdot 22 \Omega + 3(i_s \cdot 33 \Omega) = 0$$

$$i_s (22 \Omega + 99 \Omega) = 9$$

$$i_s = \frac{9}{22+99} \approx 0,074$$

$$-V_s + i_s R_1 + 3V_{R2} = 0$$


$$V_{R2} = \frac{V_s - i_s R_1}{3}$$

$$V_{R2} = 2,45 \text{ V}$$

Same  
dif i
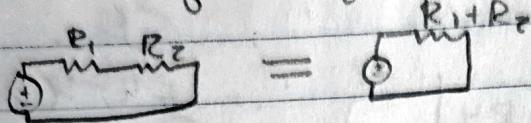
## 2.5 Series resistors & Voltage Division

$$V = i R_{eq}, R_{eq} = R_1 + R_2 \dots$$




$$G_{eq} = \frac{G_1 G_2}{G_1 + G_2}$$

$$V_1 = \frac{R_1}{R_1 + R_2} V, \quad V_2 = \frac{R_2}{R_1 + R_2} V, \quad V_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} V$$

Voltage  $v$  is divided among the resistors and is directly proportional to their resistance.

Same v  
dif i
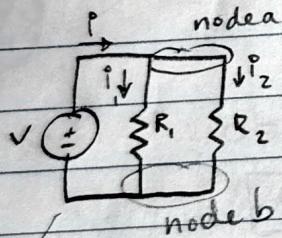
## 2.6 Parallel Resistors and Current Division



$$V = i_1 R_1 = i_2 R_2$$

$$i = i_1 + i_2$$

$$i = \frac{V}{R_1} + \frac{V}{R_2} = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_{eq}}$$

$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \text{Only if } R_1 = R_2$$

If all the resistors are the same,

$$R_{eq} = \frac{R}{N}$$


$$i_1 = \frac{G_1}{G_1 + G_2} i$$

Conductance:

$$G_{eq} = G_1 + G_2 + G_3 + \dots + G_N$$

$$\text{where } G_1 = \frac{1}{R_1}, G_2 = \frac{1}{R_2}, \dots, G_N = \frac{1}{R_N}$$
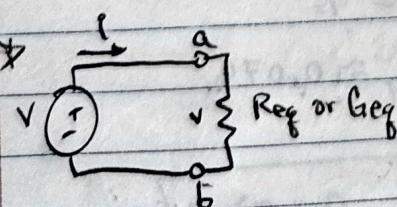
$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$



$$V = i R_{eq} = \frac{i R_1 R_2}{R_1 + R_2}$$


$$i_1 = \frac{R_2 i}{R_1 + R_2}$$

$$i_2 = \frac{R_1 i}{R_1 + R_2}$$

Total current  $i$  is shared by the resistors in inverse proportion to their resistance.

- Principle of current division
- current travels through the path of least resistance.
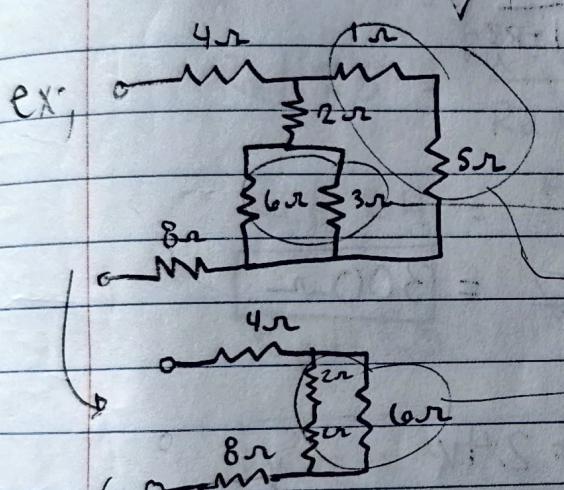
$$i_1 = \frac{G_1}{G_1 + G_2} i; i_2 = \frac{G_2}{G_1 + G_2} i; i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$





Find  $R_{eq}$

$$(6\Omega || 3\Omega) = \frac{6 \cdot 3}{6+3} = 2\Omega$$

$$1\Omega + 5\Omega = 6\Omega$$

$$4\Omega || 6\Omega = \frac{4 \cdot 6}{4+6} = 2.4\Omega$$

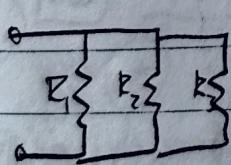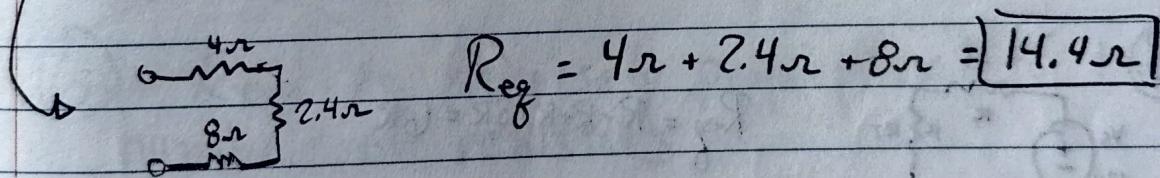


$$R_1 = 2 \text{ kohm}$$

$$R_2 = 1.5 \text{ kohm}$$

$$R_3 = 1.2 \text{ kohm}$$

$$R_1 || R_2 = \frac{2 \cdot 1.5}{2+1.5} = \frac{6}{7}$$

$$R_{eq} = R_1 || R_2 || R_3 = \frac{\frac{6}{7} \cdot 1.2}{\frac{6}{7} + 1.2} = 0.5 \text{ kohm} = 500\Omega$$

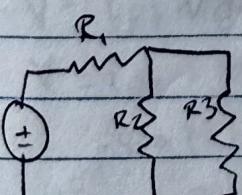

$$R_1 = 3.3 \text{ k}\Omega$$

$$R_2 = 4.7 \text{ k}\Omega$$

$$R_3 = 2.7 \text{ k}\Omega$$


$$R_2 || R_3 = \frac{4.7 \cdot 2.7}{4.7 + 2.7} =$$

$$R_1 + R_2 || R_3 = \frac{3.3 \cdot 11}{740} \text{ k}\Omega \approx 5.01 \text{ k}\Omega$$

# Voltage and Current Division HW

① Once equivalent resistance is calculated, it has similar properties to a single resistor with the same value.

②

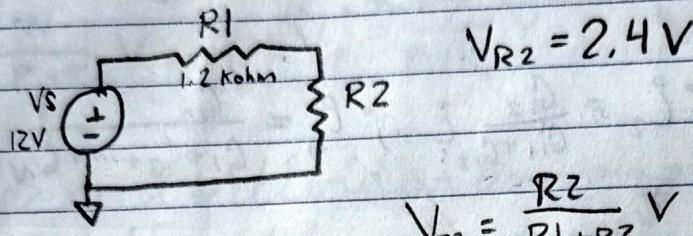

$$V_{R2} = \frac{R2}{R1+R2} V$$

$$\frac{V_{R2}}{V} = \frac{R2}{R1+R2}$$


$$\frac{V_{R2}}{V} \cdot R1 = R2 - \frac{V_{R2}}{V} \cdot R2$$

$$R2 \left(1 - \frac{V_{R2}}{V}\right) = \frac{V_{R2}}{V} \cdot R1$$

$$R2 = \frac{\left(\frac{V_{R2}}{V} \cdot R1\right)}{\left(1 - \frac{V_{R2}}{V}\right)} = \frac{2.4V}{12V} \cdot 1200\Omega = 300\Omega$$

$$\text{Check: } 2.4V = \frac{300\Omega}{1200\Omega + 300\Omega} \cdot 12V = 2.4V$$


③

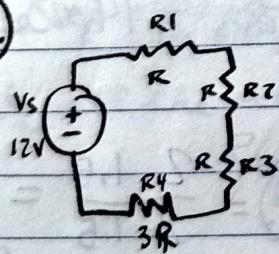

$$R_{eq} = R + R + R_1 + 3R = 6R$$

$$V_{BR} = \frac{R4}{R1+R2+R3+R4} V = \frac{3R}{6R} = \frac{1}{2} V = 6V$$

④

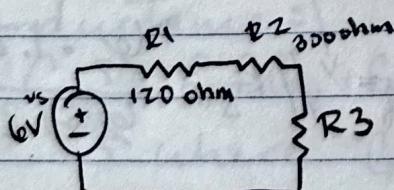

30% VS dropped across R3

$$V_{R3} = \frac{3}{10} \cdot 6V = 1.8V$$

$$V_{R3} = \frac{R3}{R1+R2+R3} V$$

$$\frac{V_{R3}}{V} (R1+R2) = R3 - \frac{V_{R3}}{V} R3$$


$$R3 \cdot \frac{\frac{V_{R3}}{V} (R1+R2)}{\left(1 - \frac{V_{R3}}{V}\right)} = R3$$

$$R3 = 180\Omega$$

# Control Systems

Check

5.

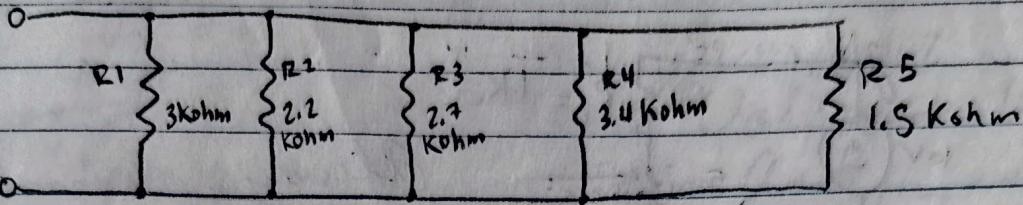

$$R_a = \frac{3\text{k}\Omega \cdot 2.2\text{k}\Omega}{3\text{k}\Omega + 2.2\text{k}\Omega} = R_a$$

$$R_b = \frac{R_a \cdot 2.7\text{k}\Omega}{R_a + 2.7\text{k}\Omega} = R_b$$


$$R_c = \frac{R_b \cdot 3.4\text{k}\Omega}{R_b + 3.4\text{k}\Omega} = R_c$$

$$R_d = \frac{R_c \cdot 1.5\text{k}\Omega}{R_c + 1.5\text{k}\Omega} = 0.472\text{k}\Omega = 472\text{\Omega}$$

$$R_{eq} = 472\text{\Omega}$$

6.  $R_{eq}$  is inversely proportional to the number of resistors

7.

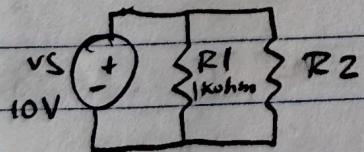

$$i_{R2} = 60\% \text{ of } i_T$$

$$R2 = ?$$

$$i_{R1} = 40\% \text{ of } i_T$$

$$i_T = \frac{3}{500}$$

$$V = i_{R1} \cdot R1 = 0.4 \cdot i_T \cdot R1 = 0.4 \cdot i_T \cdot 1000\text{\Omega}$$

$$V = i_{R2} \cdot R2 = 0.6 \cdot i_T \cdot R2$$

$$400\text{\Omega} = 0.6 i_T \cdot R2$$

$$R2 = \frac{400\text{\Omega}}{0.6 i_T} = 666.7\text{\Omega}$$

$$R_{eq} = \frac{1000 \cdot 666.7}{1000 + 666.7} \approx 400\text{\Omega}$$

$$i_T = \frac{10\text{V}}{400\text{\Omega}} = 25\text{mA}$$



$$i_{R1} = 10\text{mA}$$

$$i_{R2} = 15\text{mA}$$

$$V = 0.4 \cdot 15 \cdot 1000 = 10\text{V}$$

$$i_T = 0.6 \cdot 10 \cdot 1000 = 600\text{mA}$$

## Potentiometer

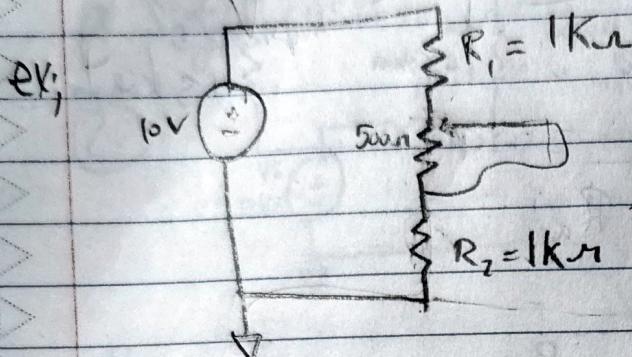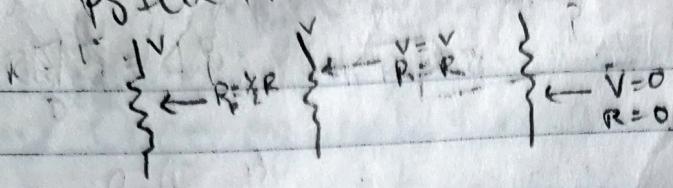

Always assume ground  
to ground if not explicitly  
said otherwise

## 3.2 Nodal Analysis

(non-voltage source)

Choose node voltage instead of element voltages → node-voltage method

Steps to determine Node Voltages: (n nodes)


"datum node" or ground → 1. Select a reference node. Assign voltages  $V_1, V_2, \dots, V_{n-1}$  to remaining nodes. Voltages referenced with respect to reference node

2. Apply KCL to each n-1 nonreference nodes.

Use Ohm's law to express the branch currents in terms of node voltages.

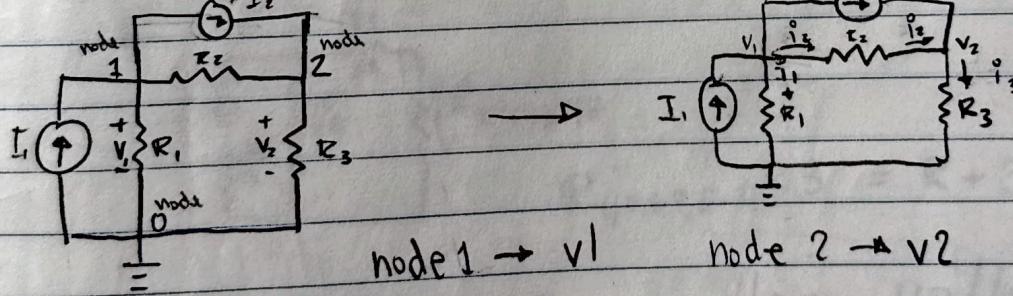3. Solve the resulting simultaneous to obtain the unknown node voltages.

Chassis ground → case or enclosure is used as ground earth ground → using the earth



$$(KCL) \quad \text{Node 1: } I_1 = I_2 + i_1 + i_2 \quad \text{Node 2: } I_2 + i_2 = i_3$$

\* Current flows from a higher potential to a lower potential in a resistor.

$$i = \frac{V_{\text{higher}} - V_{\text{lower}}}{R} = \frac{\text{Previous voltage} - \text{next voltage}}{\text{Resistor between}}$$

$$i_1 = \frac{V_1 - 0}{R_1} \quad \text{or} \quad i_1 = G_1 V_1 \quad i_2 = \frac{V_1 - V_2}{R_2} \quad \text{or} \quad i_2 = G_2 (V_1 - V_2)$$

$$i_3 = \frac{V_2 - 0}{R_3} \quad \text{or} \quad i_3 = G_3 V_2$$

Voltages are measured with respect to the node 0 (ground).  
Voltage drop across resistor  $R$  is  $V_{\text{higher}} - V_{\text{lower}}$ .

$$I_1 = I_2 + \frac{V_1}{R} + \frac{V_1 - V_2}{R_2}$$

$$I_2 + \frac{V_1 - V_2}{R_2} = \frac{V_2}{R_3}$$

$$I_1 = I_2 + G_1 V_1 + G_2 (V_1 - V_2)$$


or

$$I_2 + G_2 (V_1 - V_2) = G_3 V_2$$

→ Solve system of equations for  $V_1$  &  $V_2$


# Series-Parallel Circuits HW

(1)

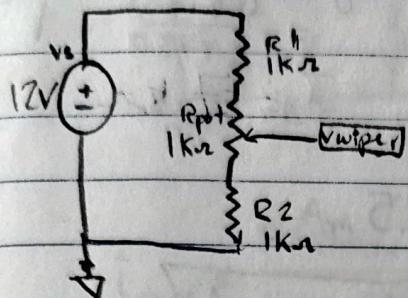

$$V_{wiper} = \frac{R_2}{R_1 + R_2 + R_{pot}} \cdot 12V = \frac{1k\Omega}{3k\Omega} = 4V$$


(2)

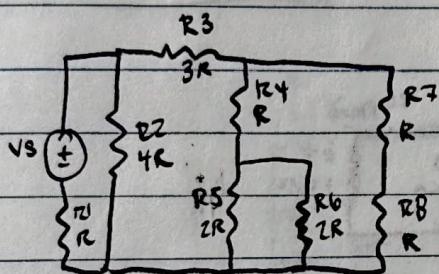


$$R_5 \parallel R_6 = 2R \parallel 2R = R$$

$$R_4 + R_{5,6} = R + R = 2R$$


$$R_7 + R_8 = R + R = 2R$$

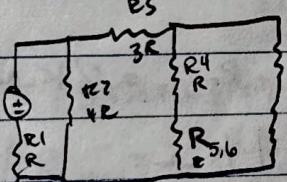

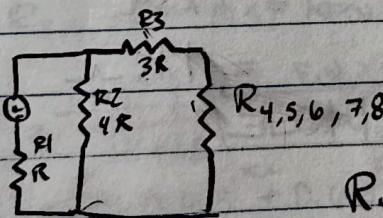
$$R_{4,5,6} \parallel R_{7,8} = 2R \parallel 2R = R$$



$$R_{4,5,6,7,8} + R_3 = R + 3R = 4R$$

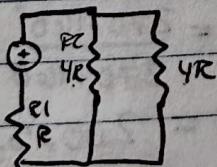

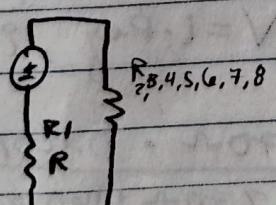
$$R_{3,4,5,6,7,8} \parallel R_2 = 4R \parallel 4R = 2R$$



$$R_1 \parallel R_{2,3,4,5,6,7,8} = R + 2R = 3R$$

(3.)

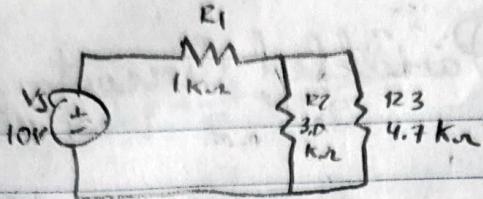

$$R_{eq} = (R_2 \parallel R_3) + R_1$$

$$= \frac{4.7 \cdot 3.0}{4.7 + 3.0} + 1$$


$$= 7 \text{ k}\Omega$$

$$-10V + V = i \cdot R_{eq}$$

$$i = \frac{10V}{7 \text{ k}\Omega} = 3.5 \text{ mA}$$

$$i_2 = \frac{R_1 \cdot i}{R_1 + R_2} = \frac{4.7 \cdot 3.5}{3.0 + 4.7} = 2.14 \text{ mA}$$

(4.)

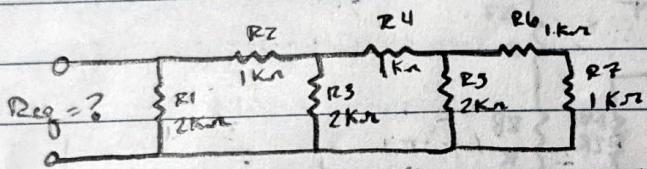

$$R_6 \parallel R_7 = 0.5 \text{ k}\Omega \quad R_5 \parallel R_{6,7} = 1 \text{ k}\Omega$$

$$R_4 + R_{5,6,7} = 2 \text{ k}\Omega$$


$$R_3 \parallel R_{4,5,6,7} = 1 \text{ k}\Omega$$

$$R_2 + R_{3,4,5,6,7} = ? \text{ k}\Omega$$

$$R_1 \parallel R_{2,3,4,5,6,7} = 1 \text{ k}\Omega$$

$$\boxed{R_{eq} = 1 \text{ k}\Omega}$$

(5.)

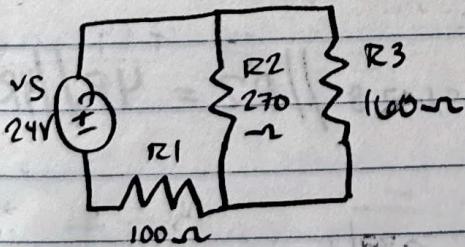

$$R_{eq} = R_2 \parallel R_3 + R_1$$


$$= \frac{270 \cdot 160}{270 + 160} + 100$$

$$= 200.5 \Omega$$


$$V = i \cdot R_{eq}, i = \frac{24V}{200.5 \Omega} = 0.120A$$

$$i_{R3} = \frac{R_2 \cdot i}{R_2 + R_3} = \frac{270 \Omega \cdot 0.120A}{270 \Omega + 160 \Omega} = 0.072A$$

$$= 75mA$$

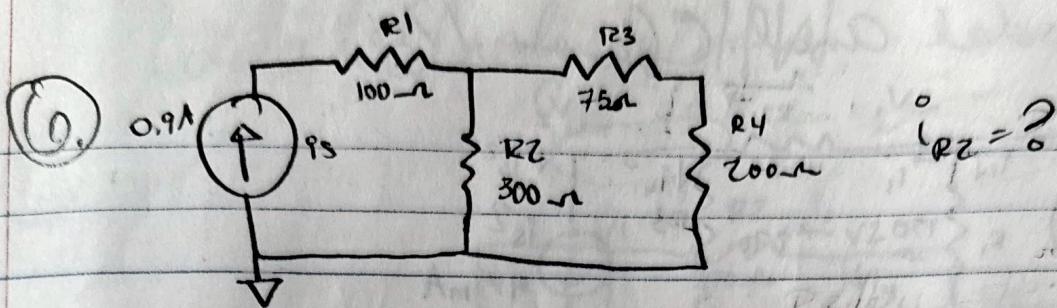
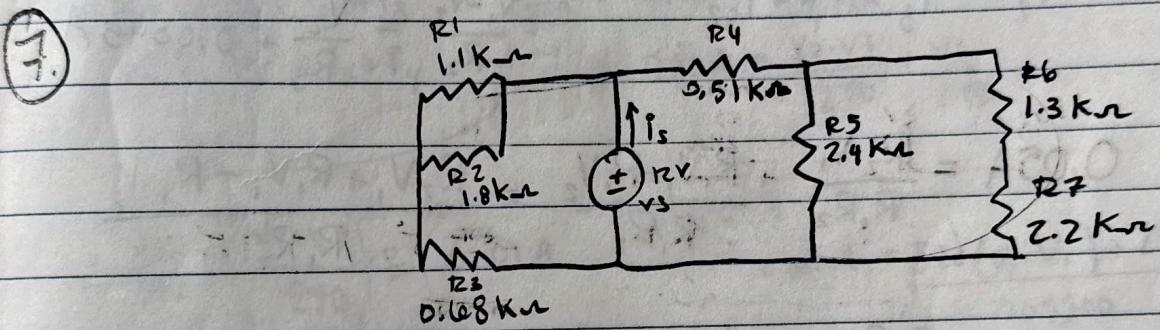
$$i_{R2} = \frac{(R3 + R4) \cdot I_S}{R2 + R3 + R4} = 430 \text{ mA}$$



$$R6 + R7 = 1.3 \text{ k}\Omega + 2.2 \text{ k}\Omega = 3.5 \text{ k}\Omega$$

$$R5 // R_{6,7} = \frac{2.4 \text{ k}\Omega \cdot 3.5 \text{ k}\Omega}{2.4 + 3.5 \text{ k}\Omega} = 1.4 \text{ k}\Omega$$

$$R4 + R_{5,6,7} = 0.51 \text{ k}\Omega + 1.4 \text{ k}\Omega = 1.93 \text{ k}\Omega$$


$$R1 // R2 = \frac{1.1 \cdot 1.8}{1.1 + 1.8} = 0.68 \text{ k}\Omega$$

$$R_{1,2} + R_3 = 0.68 + 0.68 = 1.36 \text{ k}\Omega$$

$$R_{1,2,3} // R_{5,6,7} = \frac{1.36 \cdot 1.91}{1.36 + 1.91} = 799 \text{ m}\Omega = R_{\text{eq}}$$

$$V = I \cdot R_{\text{eq}} \quad I_S = \frac{12V}{799 \text{ m}\Omega} = 15 \text{ mA} = I_S$$

# Nodal Anal. Class 1/20

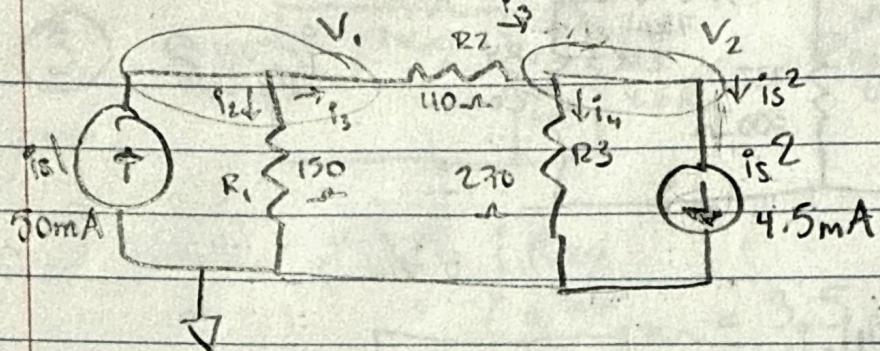

$$V_1: i_{s1} = i_2 + i_3$$

$$0.05A = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$


$$V_2: i_3 = i_4 + i_{s2}$$

$$\frac{V_1 - V_2}{R_2} = \frac{V_2}{R_3} + 0.0045A$$

$$0.05A = \frac{R_2 V_1}{R_1 R_2} + \frac{R_1 V_1 - R_2 V_2}{R_1 R_2} = \frac{R_2 V_1 + R_1 V_1 - R_1 V_2}{R_1 R_2}$$

$$0.05 R_1 R_2 = V_1 (R_1 + R_2) - V_2 R_1$$

\*Do for other one \*

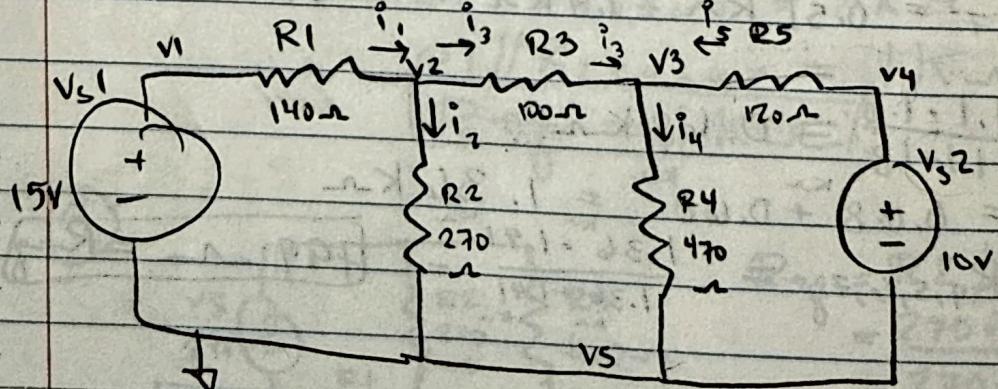


$$V_2: -\frac{V_1}{R_1} = i_2 + i_3 \quad \frac{15V - V_2}{R_2} = \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4}$$

$$V_3: i_3 + i_6 + i_5 = i_4$$

$$\frac{V_2 - V_3}{R_4} + \frac{10V - V_3}{R_5} = \frac{V_3}{R_6}$$

# Nodal Analysis HW

1)

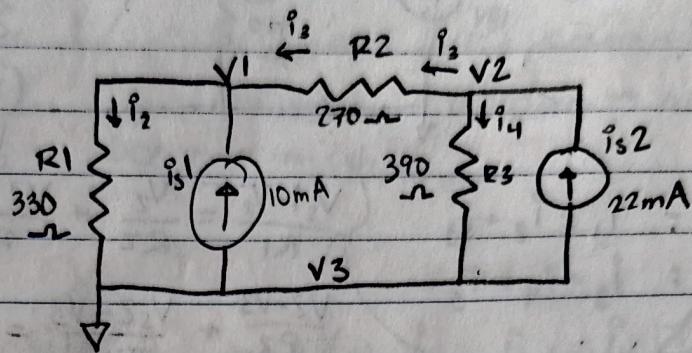

$$A.) \quad V_1: \quad i_2 = i_{s1} + i_3 \quad \frac{V_1}{330} = 0.01 A + \frac{V_2 - V_1}{270}$$

$$V_2: \quad i_{s2} = i_3 + i_4 \quad 0.022 A = \frac{V_2 - V_1}{270} + \frac{V_2}{390}$$

$$\frac{V_1}{330} - \left( \frac{V_2 - V_1}{270} \right) = 0.01 A$$

$$0.022 A = \frac{390(V_2 - V_1)}{105300} + 270 V_2$$

$$\frac{270V_1 - 330V_2 + 330V_1}{89100} = 0.01$$


$$(600V_1 - 330V_2 = 891)$$

$$2316.6 = 390V_2 - 390V_1 + 270V_2$$

$$2316.6 = 660V_2 - 390V_1$$

\* MATLAB \*
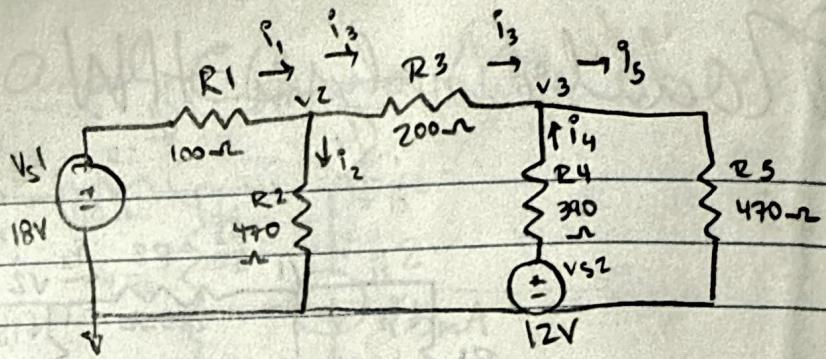
$$B.) \quad V_1 = 5.06 V \quad V_2 = 6.5 V$$



$$V_2: i_1 = i_2 + i_3$$

$$V_3: i_3 + i_4 = i_5$$

$$\frac{V_s 1 - V_2}{R1} = \frac{V_2}{R2} + \frac{V_2 - V_3}{R3}$$

$$\frac{V_2 - V_3}{R3} + \frac{V_s 2 - V_3}{R4} = \frac{V_3}{R5}$$

$$\frac{18 - V_2}{100} = \frac{V_2}{470} + \frac{V_2 - V_3}{200}$$

$$\frac{18}{100} = \frac{V_2}{470} + \frac{V_2}{100} + \frac{V_2 - V_3}{200}$$

$$\frac{18}{10} = \frac{V_2}{47} + \frac{V_2}{10} + \frac{V_2 - V_3}{20}$$

$$= \frac{20V_2}{940} + \frac{94V_2}{940} + \frac{47(V_2 - V_3)}{940}$$

$$= \frac{20V_2}{940} + \frac{94V_2}{940} + \frac{47V_2 - 47V_3}{940}$$

$$\frac{18}{10} = \frac{161V_2 - 47V_3}{940}$$

$$1692 = 161V_2 - 47V_3$$

$$\frac{V_2 - V_3}{200} + \frac{12 - V_3}{390} = \frac{V_3}{470}$$

$$\frac{V_2 - V_3}{200} = -\frac{V_3}{390} - \frac{V_3}{470} = -\frac{12}{390}$$

$$1833(V_2 - V_3) - 940V_3 - 780V_3 = -\frac{12}{390}$$

$$1833V_2 - 1833V_3 - 940V_3 - 780V_3 = -11280$$

$$1833V_2 - 3553V_3 = -11280$$

★ MATLAB ★


$$V_2 = 13.5V$$

$$V_3 = 10.1V$$

### 3.4 Mesh Analysis

Meth-loop/mo other loops (loop or mesh-current method)

apply KVL to find unknown currents

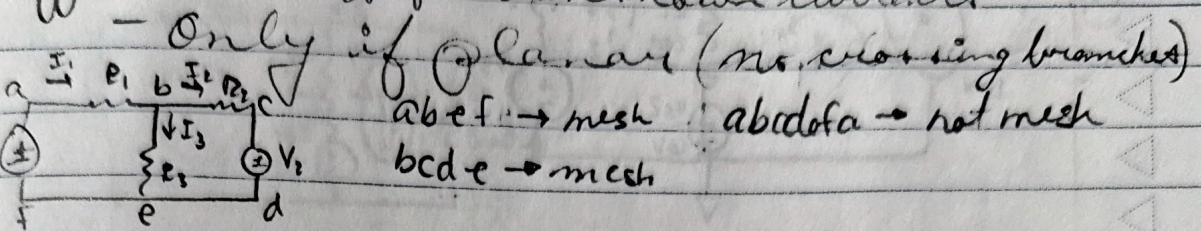


Steps:

- 1.) Assign mesh currents  $i_1, \dots, i_2, \dots, i_n$  to meshes
- 2.) Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of mesh currents
- 3.) Solve resulting  $n$  equations to get mesh currents

Mesh 1:  $-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0 \text{ or } V_1 = (R_1 + R_3) i_1 - R_3 i_2$

Mesh 2:  $R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0 \text{ or } -V_2 = -R_3 i_1 + (R_2 + R_3) i_2$

\* Solve for  $i_1$  and  $i_2$

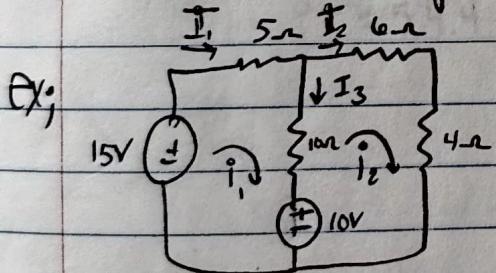

mesh 1:  
 $-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$   
 $3i_1 - 2i_2 = 1$

mesh 2:  
 $(6i_2 + 4i_2 + 10(i_2 - i_1)) - 10 = 0$   
 $i_1 = 2i_2 - 1$

$6i_2 - 3A2i_2 = 1$


$i_2 = 1A$

$i_1 = i_2 = 1A$

$i_2 = i_2 = 1A$

$\rightarrow i_3 = i_1 - i_2 = 0$

Nodal Analysis	Mesh Series
parallel	
nodes < meshes	meshes < nodes
op amp circuit	transistors
non-planar	planar

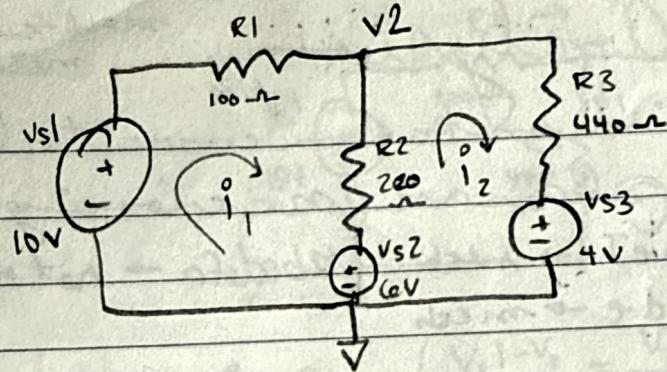

$$-10V + \dot{P}_1 R_1 + (\dot{P}_1 - \dot{P}_2) R_2 + 6V = 0$$

$$4V - 6V + (\dot{P}_2 - \dot{P}_1) R_2 + \dot{P}_2 R_3 = 0$$


$$4V = \dot{P}_1(R_1 + R_2) - \dot{P}_2(R_2)$$

$$2V = \dot{P}_2(R_2 + R_3) - \dot{P}_1(R_2)$$

$$4V = 320\dot{P}_1 - 220\dot{P}_2$$

$$2V = 160\dot{P}_2 - 220\dot{P}_1$$

# Mesh Analysis HW

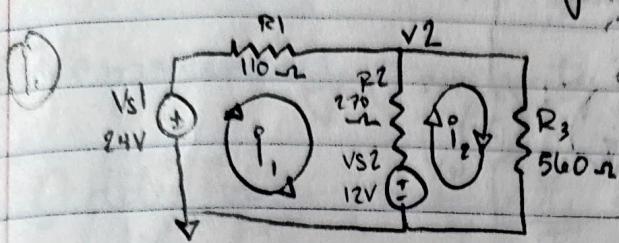

$$\text{mesh 1: } -24V + i_1 R_1 + (i_1 - i_2) R_2 + 12V = 0$$

$$(R_1 + R_2) i_1 - R_2 i_2 = -2V$$

$$380i_1 - 270i_2 = -12V$$

$$\text{mesh 2: } -12V + (i_2 - i_1) R_2 + i_2 R_3 = 0$$

$$-12V + (R_2 + R_3) i_2 - R_2 i_1 = 0$$


$$-12V + 830i_2 - 270i_1 = 0$$

$$830i_2 - 270i_1 = 12V$$

\*W/ MATLAB\*

$$i_1 = 54.4 \text{ mA} \quad i_2 = 32.2 \text{ mA}$$

2.

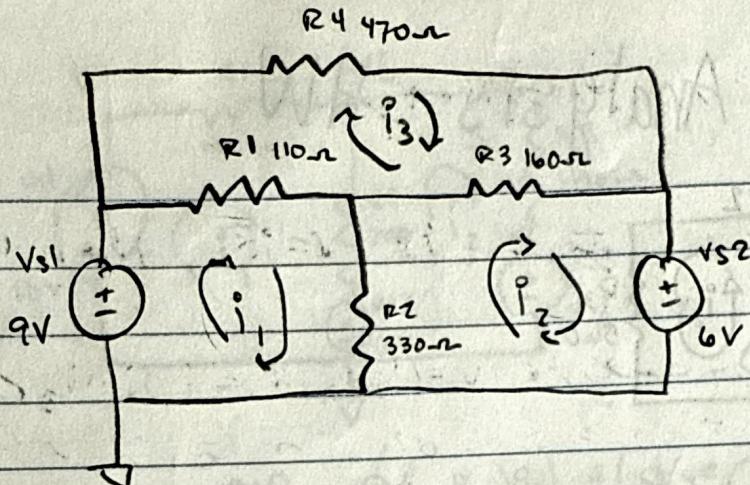

$$\text{mesh 1 : } -9V + (i_1 - i_3)R_1 + (i_1 - i_2)R_2 = 0$$

$$-9V + R_1 i_1 - R_1 i_3 + R_1 i_2 - R_2 i_2 = 0$$

$$-9V + (R_1 + R_2)i_1 - R_2 i_2 - R_1 i_3 = 0$$

$$-9V + 440i_1 - 330i_2 - 110i_3 = 0$$

$$440i_1 - 330i_2 - 110i_3 = 9V$$

$$\text{mesh 2 : } 6V + (i_2 - i_1)R_2 + (i_2 - i_3)R_3 = 0$$

$$6V + R_2 i_2 - R_2 i_1 + R_3 i_2 - R_3 i_3 = 0$$

$$6V + -R_2 i_1 + (R_2 + R_3)i_2 - R_3 i_3 = 0$$

$$6V - 330i_1 + 490i_2 - 160i_3 = 0$$

$$-330i_1 + 490i_2 - 160i_3 = -6V$$

$$\text{mesh 3 : } (i_3 - i_2)R_3 + (i_3 - i_1)R_1 + i_3 R_4 = 0$$

$$R_3 i_3 - R_3 i_2 - R_1 i_3 - R_1 i_1 + R_4 i_3 = 0$$

$$-R_1 i_1 - R_3 i_2 + (R_1 + R_3 + R_4)i_3 = 0$$

$$-110i_1 - 160i_2 + 740i_3 = 0$$

\*MATLAB\*

$$i_1 = 29.2 \text{ mA}$$

$$i_2 = 9.5 \text{ mA}$$

$$i_3 = 6.4 \text{ mA}$$

## 4.2 Linearity Property

Homogeneity Property: If  $V = iR$ , then  $KiR = KV$


Additivity Property:  $V = (i_1 + i_2)R = i_1 R + i_2 R = V_1 + V_2$

- Response to a sum of inputs is the sum of the response to each input separately.

Circuit is linear if both are satisfied.

- Output is linearly related to its input (power relation not linear)
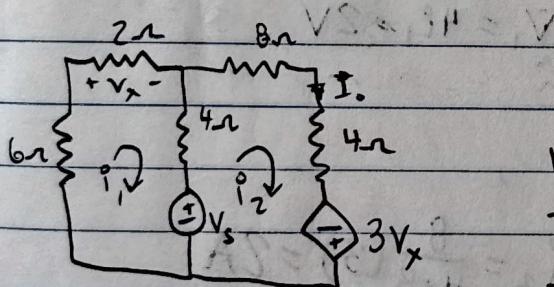
$$\hookrightarrow \text{if } P_1 = R\vec{i}_1^2, \quad P_2 = R\vec{i}_2^2 \\ P_3 = R(\vec{i}_1 + \vec{i}_2)^2 \neq P_1 + P_2$$



Find  $I_0$  when  $V_s = 12V$  and  $V_x = 24V$

$$12i_1 - 4i_2 + V_s = 0 \quad (\text{KVL}) \\ -4i_1 + 16i_2 - 3V_x - V_s = 0 \quad | \quad V_x = 2i_1 \\ -10i_1 + 16i_2 - V_s = 0$$

$$2i_1 + 12i_2 = 0 \Rightarrow i_1 = -6i_2$$

$$-76i_2 + V_s = 0 \Rightarrow i_2 = \frac{V_s}{76}$$


$$\text{When } V_s = 12V, \quad I_0 = i_2 = \frac{12}{76} A$$

$$= \frac{27}{76} A$$

## 4.3 Superposition


Superposition : Voltage (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or current through) that element due to each independent source acting alone.

Ex:

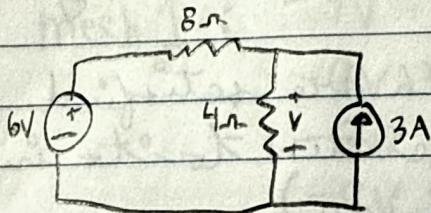


$$\text{let } V = V_1 + V_2$$

\*SPLIT\*

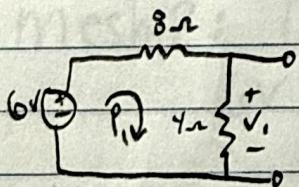

$$12\Omega \parallel 4\Omega = 0 \Rightarrow I_1 = 0.5A$$

$$V_1 = 4I_1 = 2V$$

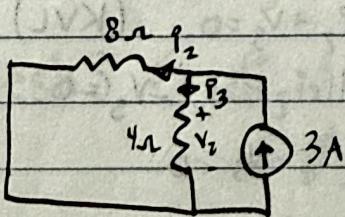



$$I_3 = \frac{8}{4+8}(3) = 2A$$

$$V_2 = 4I_3 = 8V$$

$$V = V_1 + V_2 = 2 + 8 = 10V$$

To turn off voltage  $\rightarrow$  short circuit (0V)

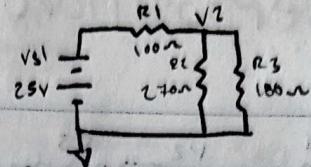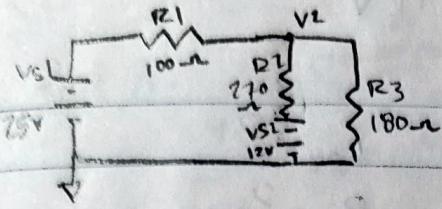
To turn off current  $\rightarrow$  open circuit (0A)



$$R_{eq} = \frac{R_2 || R_3 + R_1}{R_1} = \frac{180 \cdot 270}{180 + 270} + 100 = 208 \Omega$$

$$I_T = \frac{25V}{208 \Omega} = 0.12A$$
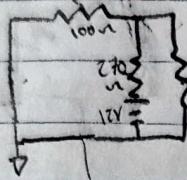
$$I_B = \frac{R_L \cdot I_T}{R_2 + R_3} = 7.2mA$$




$$R_{eq} = \frac{R_1 || R_3 + R_2}{R_1} = \frac{100 \cdot 180}{100 + 180} + 270 = 334 \Omega$$

$$I_T = \frac{12V}{334 \Omega} = 35.9mA$$

# Superposition HW

1.

Part A:

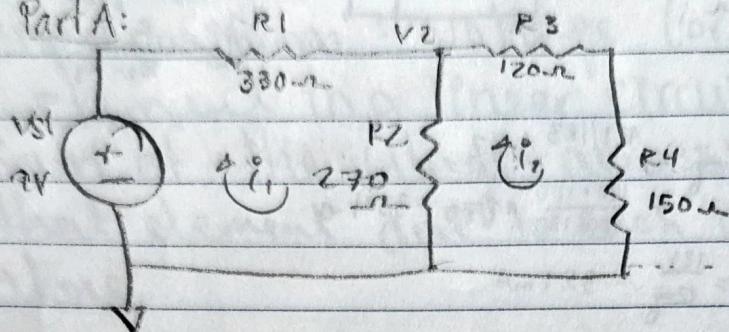

$$\varrho_{R2} = ?$$

$$P_{R2} = ?$$

$$R_{eq} = R_1 + R_2 // (R_3 + R_4)$$

$$R_3 + R_4 = 270 \Omega$$

$$R_2 // R_{3,4} = 135$$

$$R_1 + R_{2,3,4} = 465 \Omega = R_{eq}$$

$$i_{TA} = \frac{9V}{465 \Omega} = 19.4 \text{ mA}$$

$$-9V + i_1 R_1 + (i_1 - i_2) R_2 = 0$$

$$i_2 (R_4 + R_3) + (i_2 - i_1) R_2 = 0$$

$$V_{R2A} = i_{TA} \cdot$$

$$R_2 // (R_3 // R_4)$$

$$= 2.619 \text{ V}$$

$$-9V + i_1 R_1 + i_2 R_2 - i_2 R_2 = 0$$

$$-9V + (R_1 + R_2) i_1 - i_2 R_2 = 0$$

$$-9 + 600 i_1 - 270 i_2 = 0$$


$$(R_4 + R_3 + R_2) i_2 - R_2 i_1 = 0$$

$$540 i_2 - 270 i_1 = 0$$

$$i_1 = 19.4 \text{ mA} \quad i_2 = 9.7 \text{ mA}$$

$$i_{R2A} = i_1 - i_2 = 9.7 \text{ mA}$$

Part B:

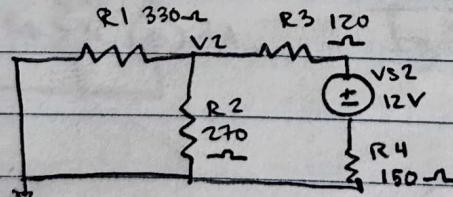

$$R_{eq} = R_4 + R_1 // R_2 + R_3$$

$$R_1 // R_2 = 148.5 \Omega$$

$$R_{eq} = 418.5 \Omega$$

$$i_{TB} = \frac{12V}{418.5 \Omega} = 28.7 \text{ mA}$$

$$V_{R2} = i_{TB} \cdot (R_1 // R_2)$$

$$= \frac{12V}{418.5 \Omega} \cdot \frac{330 \Omega}{330 \Omega + 270 \Omega} = 44.0 \text{ mV}$$

$$i_{R2B} = \frac{V_{R2}}{R_2} = 15.8 \text{ mA}$$


$$i_{R2T} = i_{R2A} + i_{R2B} = 25.5 \text{ mA}$$

$$V_{R2} = V_{R2A} + V_{R2B} = 6.879$$

$$P_{R2} = i_{R2T} \cdot V_{R2} = 175 \text{ mW}$$

(2)

Part A:

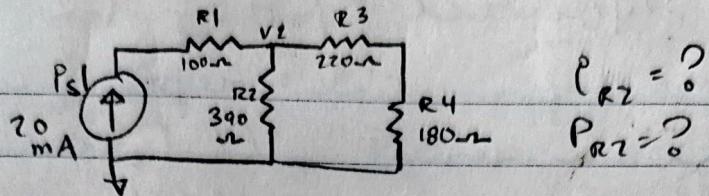

$$P_{R2} = ?$$

$$P_{eR2} = ?$$


$$R_{eq} = R1 + (R2 \parallel (R3 + R4)) \quad R2 \parallel R_{3,4} = 197.5 \Omega$$

$$= 297.5 \Omega$$

$$V_{R2A} = 0.02 \cdot 197.5 = 3.95V$$

$$i_{R2A} = \frac{3.95V}{390 \Omega} = 10mA$$

Part B:

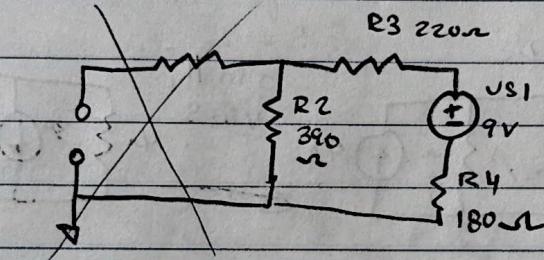

$$R_{eq} = R3 + R2 + R4 = 790 \Omega$$

$$i_{TB} = \frac{9V}{790 \Omega} = 11.4mA = i_{R2B}$$

$$V_{R2B} = i_{R2B} \cdot R2$$

$$= 4.44V$$


$$i_{R2T} = i_{R2A} + i_{R2B} = 21.4mA$$

$$V_{R2} = V_{R2A} + V_{R2B} = 8.39V$$


$$P_{eR2} = i_{eR2T} \cdot V_{R2} = 180mW$$
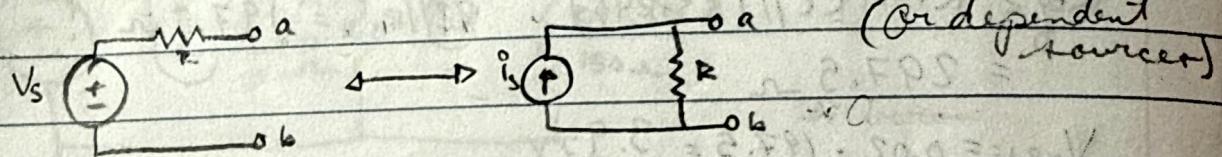
## 4.4 Source Transformation

Source transformation: replacing a voltage source in series with a resistor  $R$  by a current source in parallel with  $R$ , or vice versa



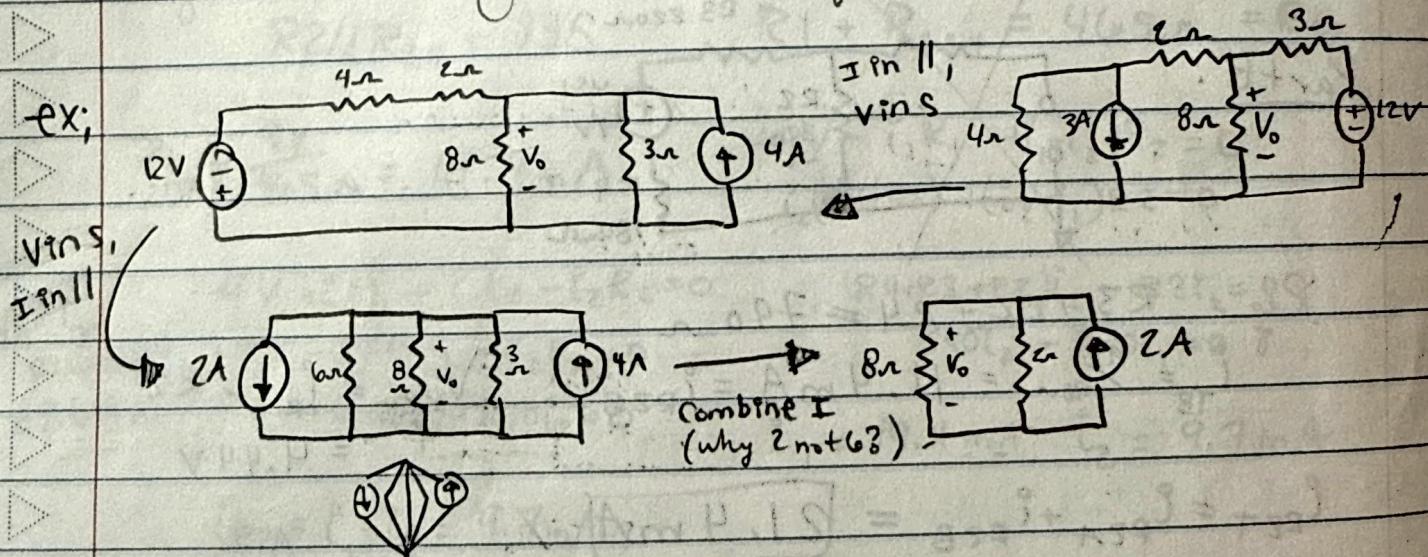
Note: arrows of current  $\Rightarrow +$  of voltage  
: Not possible if  $R=0$



$R_S \rightarrow$  Source resistance
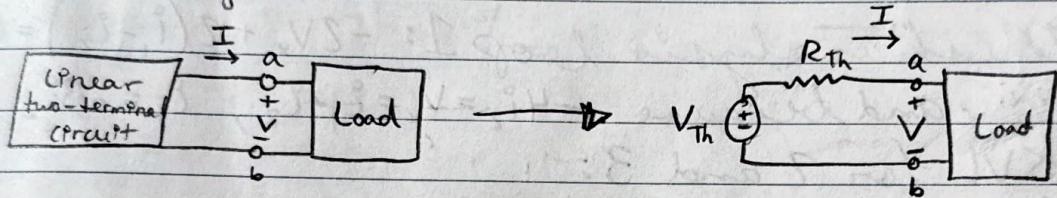
## 4.5 Thevenin's Theorem

A linear, two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series w/  $R_{Th}$ .  $V_{Th} \rightarrow$  open circuit voltage  
 $R_{Th} \rightarrow R_{eq}$




Sum of all independent sources. Not dependent.


Apply  $V_o$  to determine  $i_o$ , or apply  $i_o$  to find  $V_o$ . Then  $R_{Th} = V_o/i_o$

$$R_{Th} = \frac{V_o}{i_o}$$

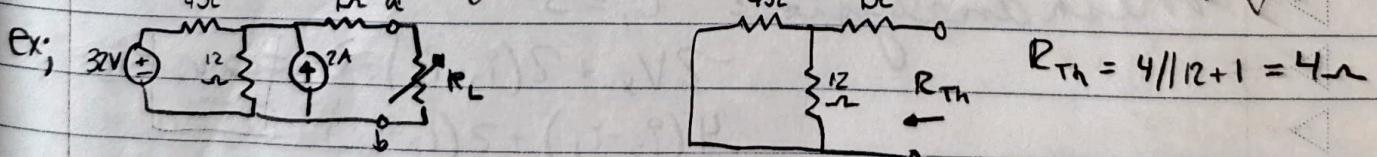\* If  $R_{Th}$  is negative, the circuit is supplying power.


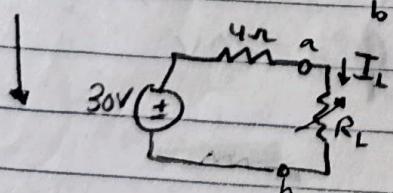
$$\frac{32 - V_{Th}}{4} + 2 = \frac{V_{Th}}{12} \quad V_{Th} = 30V$$




$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

$$\text{If } R_L = 6, \quad I_L = \frac{30}{10} = 3A$$


$$= 16, \quad I_L = \frac{30}{20} = 1.5A$$

$$= 36, \quad I_L = \frac{30}{40} = 0.75A$$

★ w/ Dependent Source!! ★

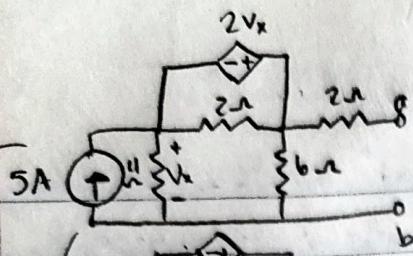

Find Thevenin equivalent

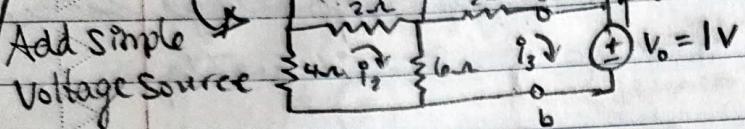

Mesh analysis loop 1:  $-2V_x + 2(i_1 - i_2) = 0$  or  $V_x = i_1 - i_2$   
and because  $-4i_2 = V_x = i_1 - i_2$ ,  $i_1 = -3i_2$

KVL for 2 and 3:

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$


$$10(i_3 - i_2) + 2i_3 + 1 = 0$$

$$\text{Solve: } i_3 = \frac{1}{6} A$$

$$\text{And } i_1 = -i_3 = \frac{1}{6} A$$

$$\text{So } R_{TH} = 1/i_1 = \frac{1}{\frac{1}{6}} = 6 \Omega$$

Use open circuit to find  $V_{TH}$

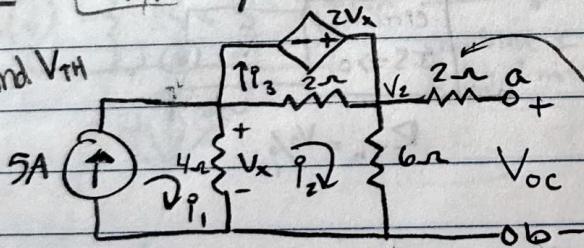

$V_{oc} = V_{TH}$  because current through  $\text{RS}$  is 0

Mesh analysis:  $i_1 = 5$

$$-2V_x + 2(i_3 - i_2) = 0 \Rightarrow V_x = i_3 - i_2$$


$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$$


$$12i_2 - 4i_1 - 2i_3 = 0 \text{ and } 4(i_1 - i_2) = V_x$$

Solving leads to  $i_2 = 10/3$ ,

$$\text{At } V_{TH} = V_{oc} = 6i_2 = 20V$$


Thevenin Equivalent:

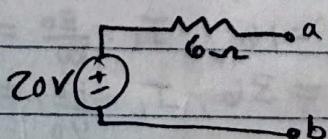

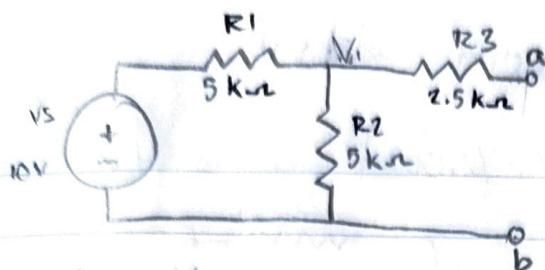

$$\frac{10V - V_{TH}}{5k\Omega} + \frac{V_{TH}}{5k\Omega} = 0$$

$$V_{TH} = 5V$$

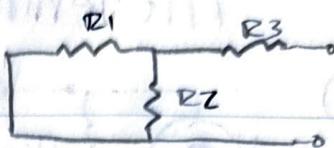


$$R_{TH} = R_1 // R_2 + R_3$$


$$= 5k\Omega$$

# Thevenin's Theorem HW


1.

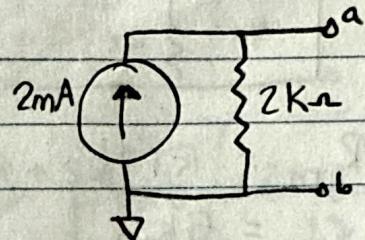

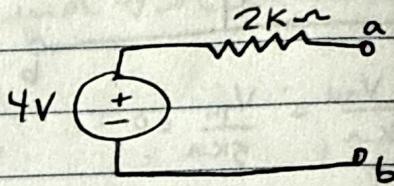
$$V = 0.002 \cdot 2000 \text{ k}\Omega = 4 \text{ V}$$





2.

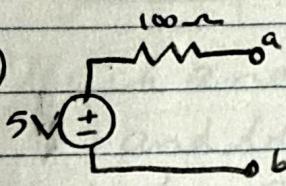
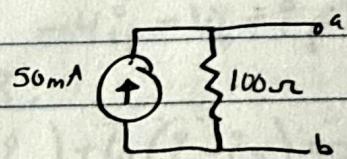
$$I = \frac{V}{R} = \frac{5 \text{ V}}{100 \Omega} = 50 \text{ mA}$$



3.

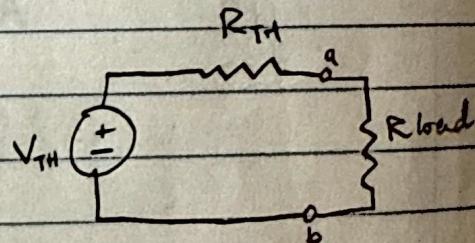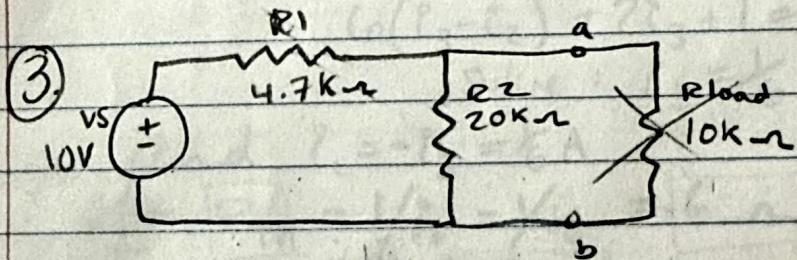



$$R_{TH} = R_1 // R_2 = 3.8 \text{ k}\Omega$$

$$V_{TH} = V_{R2} = V_s \left( \frac{R_2}{R_1 + R_2} \right)$$


$$= 10 \cdot \left( \frac{20}{24.7} \right) = 8.10 \text{ V}$$

$$V_{TH} = (R_{TH} + R_{load}) I_T \quad 46.9 \text{ mA}$$
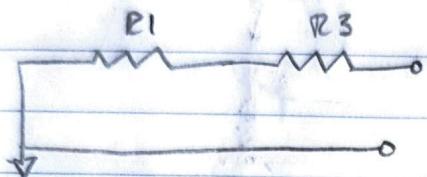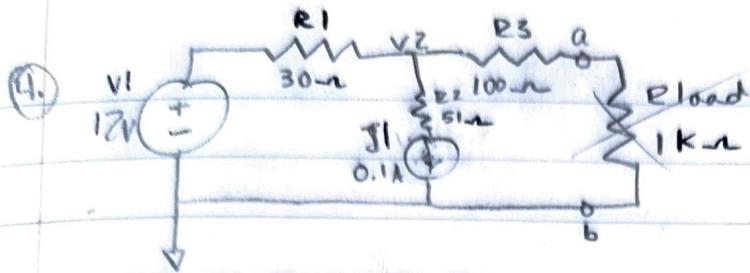
$$I_T = V_{TH} / (R_{TH} + R_{load}) = 586 \mu\text{A}$$



$$R_{TH} = 130 \Omega$$

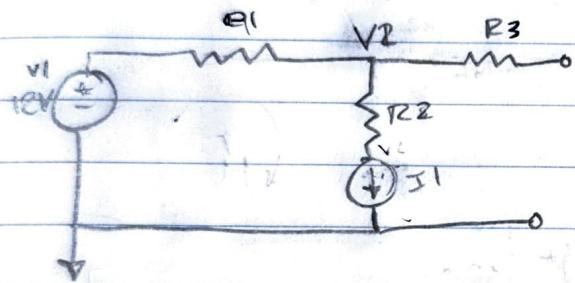



$$\begin{aligned} V2 &= V1 - V_{R1} \\ &= 12 - (0.1)(30) = 9V \end{aligned}$$

$$V_{TH} = 9V$$

$$I_{Rload} = \frac{9V}{(130 \Omega + 1k\Omega)} = 7.9mA$$

$$P_{Rload} = (7.9mA)^2 \cdot 1k\Omega = 63.4W$$


(5)

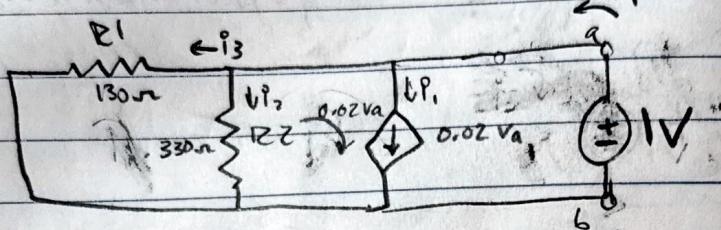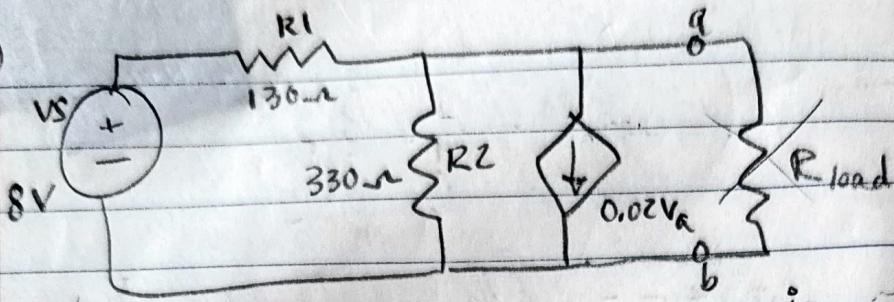

$$R_{TH} / V_a = 1V \quad (330\Omega) \rightarrow 0$$

$$330 \cdot I_T = I_1 + I_2 + I_3 \\ -1V = 0.02(1) + \frac{1V}{330\Omega} + \frac{1V}{130\Omega} \\ = 0.031A$$
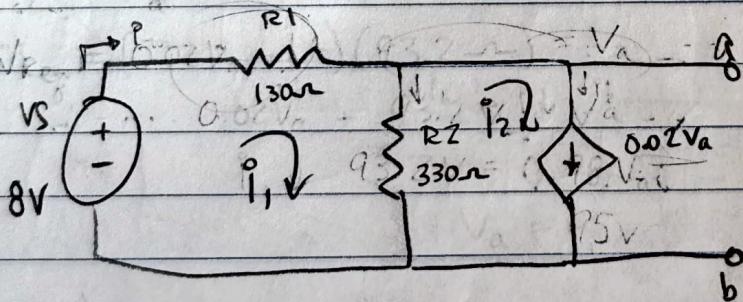
$$R_{TH} = \frac{1V}{0.031A} = 32.5\Omega$$



$$\text{Mesh 1: } -8V + 130i_1 + 330(i_1 - 0.02V_a) = 0$$

$$\text{Mesh 2: } I_2 = 0.02V_a$$

$$I_1 = \frac{8V - V_a}{130}$$


$$-8V + 130\left(\frac{8V - V_a}{130}\right) + 330\left(\frac{8V - V_a}{130} - 0.02V_a\right) = 0$$

→ Mathematica

$$V_a = 2.0V$$

FANFARE MUSIC




## 4.6 Norton's Theorem

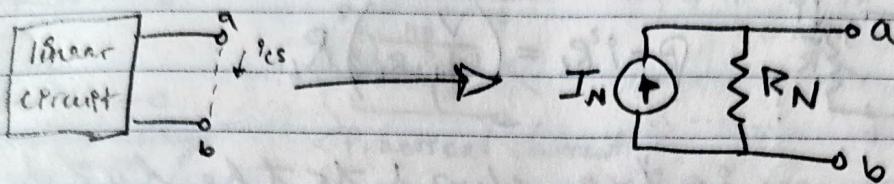


$$R_N = R_{TH} \quad I_N = \frac{V_{TH}}{R_{TH}}$$

If you short a+b,  $I_{sc} = I_N$

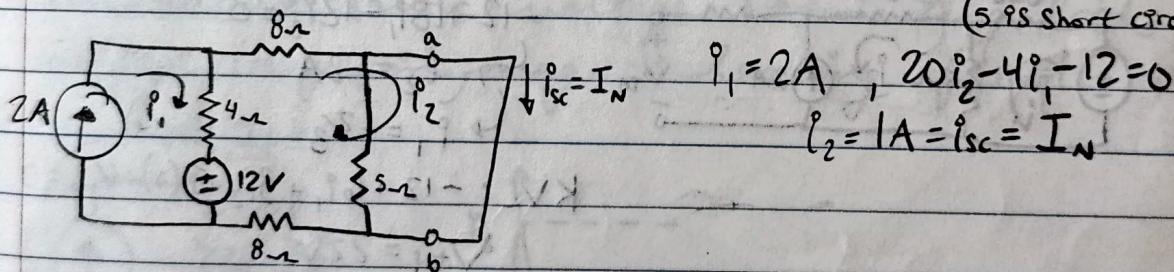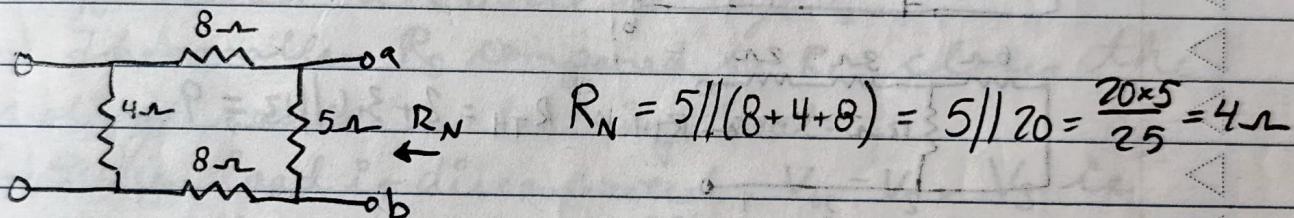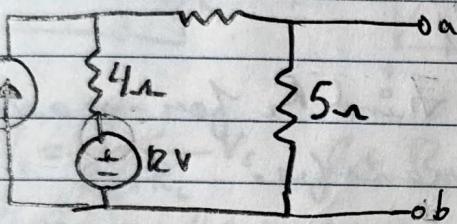
$$V_{oc} = V_{TH} \quad R_{TH} = \frac{V_{oc}}{I_{sc}} = R_N$$



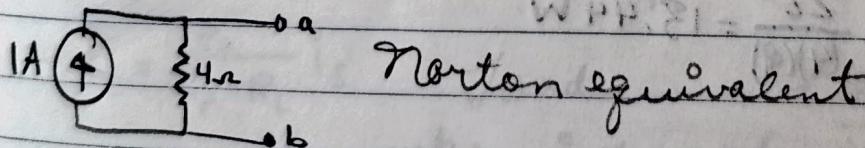(Or, you could find  $V_{TH}$  and divide by  $R_{TH}$ )




## 4.8 Maximum power transfer

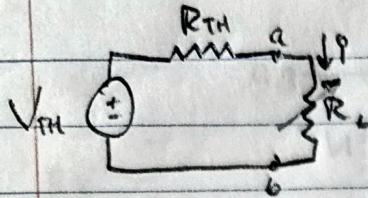


$$P = I^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

Max power is transferred to the load when the load resistance = thvenin resistance.


$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

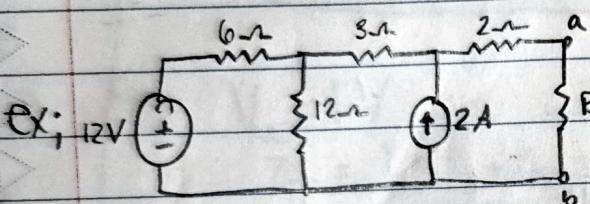

Find  $R_L$  for max power transfer.

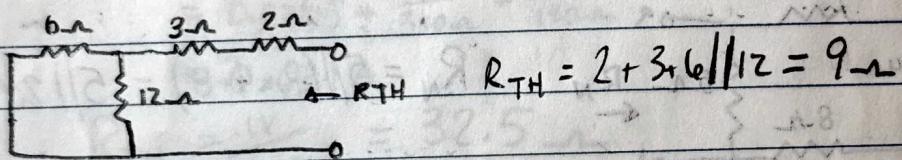

$$R_{TH} = 2 + 3 + 6 / 12 = 9 \Omega$$

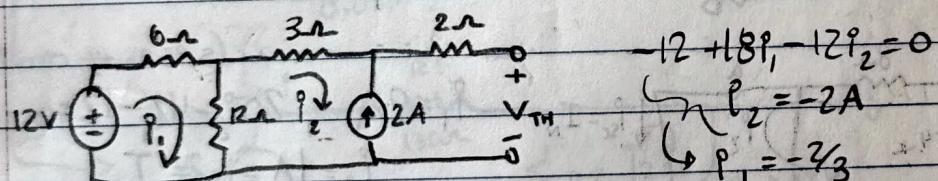


$$\text{KVL: } -12 + (6i_1 + 3i_2 + 2(0) + V_{TH}) = 0$$

$$V_{TH} = 22V$$

$$R_L = R_{TH} = 9 \Omega$$

$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{22^2}{4 \cdot 9} = 13.44W$$

## 4.10.1 Source Modeling

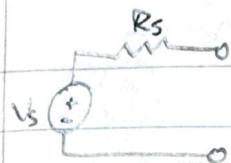



Practical voltage source

Ideal:  $R_s \rightarrow 0$





Practical current source

Ideal:  $R_p \rightarrow \infty$

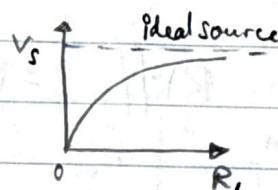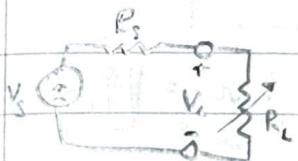

$V_L = \frac{R_L}{R_s + R_L} V_s$  At  $R_L$  increases, the load voltage approaches a source voltage  $V_s$ .

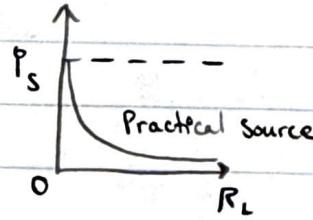
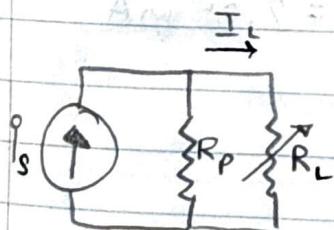
- 1.) The smaller  $R_s$  compared to  $R_L$ , closer the voltage source is to being ideal.
- 2.) When load is disconnected,  $V_{oc} = V_s$ .  $V_s$  is unloaded source voltage. Connecting load, terminal voltage drops in mag.  $\rightarrow$  loading effect



$$I_L = \frac{R_p}{R_p + R_L} I_s$$

Load current is constant when internal resistance is very large.

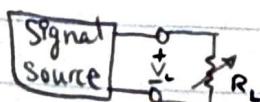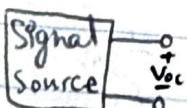To find unloaded source voltage  $V_s$ , and internal resistance  $R_s$ .





Measure  $V_{oc}$ , then adjust  $R_L$  until  $V_L = V_{oc}/2$ .


$$R_L = R_{TH} = R_s$$

# Norton's Theorem HW

①.

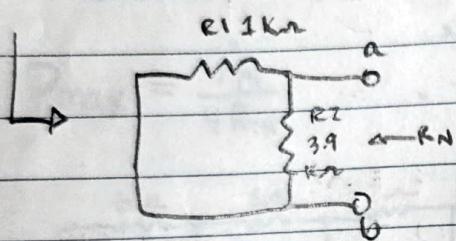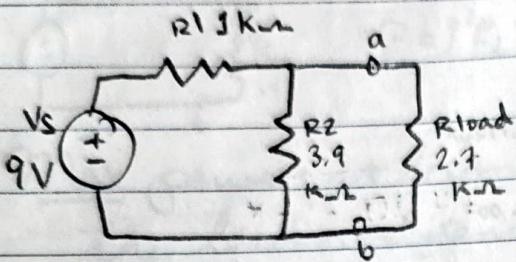

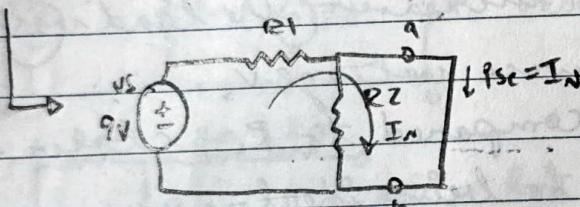
$$R_1 / R_2 = 0.796 \text{ k}\Omega = 796\text{-m} = R_N$$



$$-9V + (R_1)(I_N) = 0$$




$$I_N = 9 \text{ mA}$$

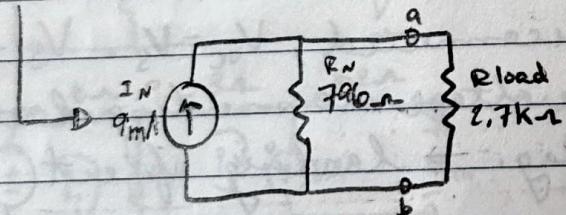

$$R_{load} = I_N \left( \frac{R_N}{R_N + R_{load}} \right)$$

$$= 0.009 \left( \frac{796}{796 + 2700} \right)$$

$$I_{load} = 2.05 \text{ mA}$$

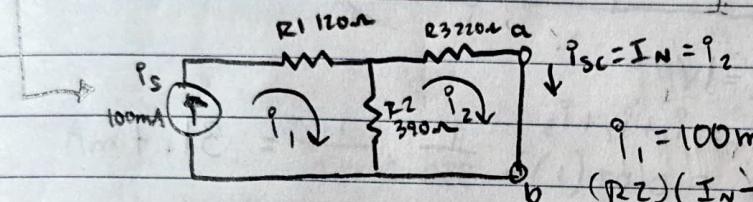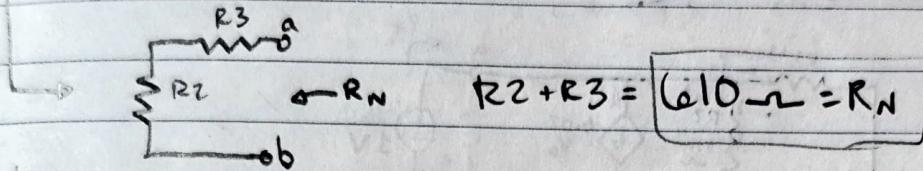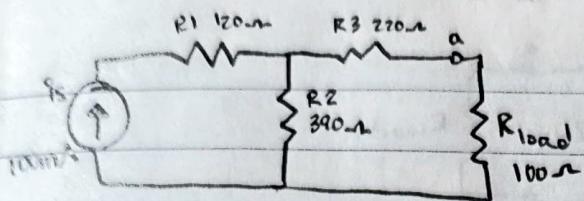


$$(R_2)(I_N - I_1) + R_3(I_N) = 0$$


$$(R_2 + R_3)(I_N) - (R_2)(I_1) = 0$$

$$I_N = \frac{(R_2)(I_1)}{(R_2 + R_3)} = \frac{(390)(0.1)}{(390 + 220)}$$

$$I_N = 63.9 \text{ mA}$$

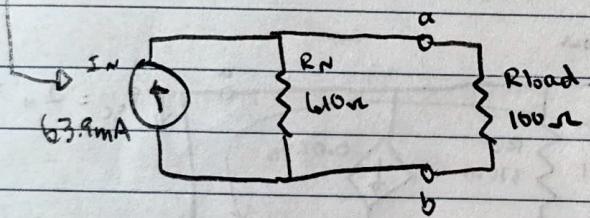

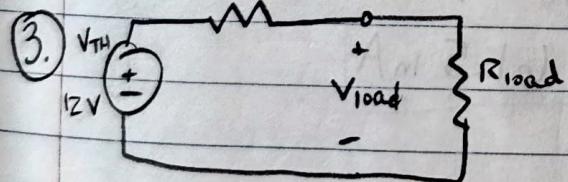
$$P_{R_{load}} = I_N \left( \frac{R_N}{R_N + R_{load}} \right) = 154.9 \text{ mA}$$



$$R_L = R_{TH} = 100\Omega$$

$$P_{max} = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L = \left( \frac{12}{100 + 100} \right)^2 (100)$$


$$P_{max} = 0.36 \text{ W}$$

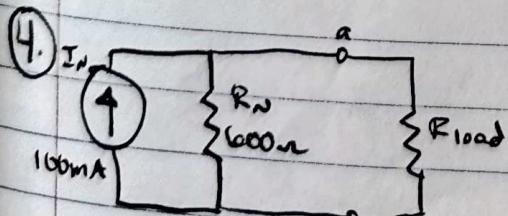



$$R_L = R_N = 600\Omega$$

$$P_{max} = \left( \frac{V_N}{R_N + R_L} \right)^2 R_L = \left( \frac{60}{1200} \right)^2 (600)$$

$$P_{max} = 1.5 \text{ W}$$

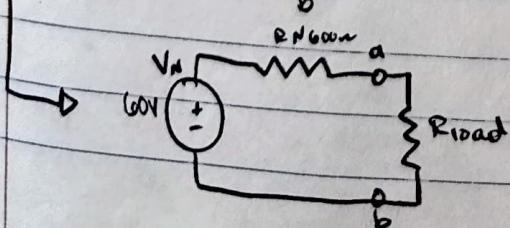


5.

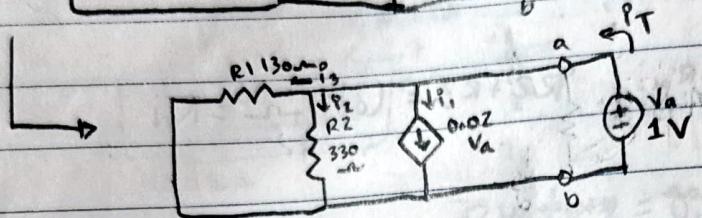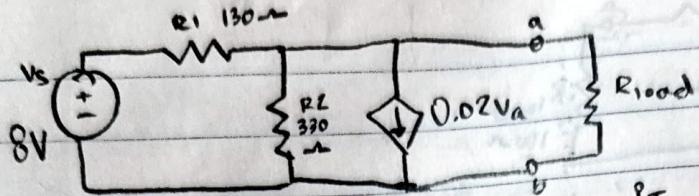

$$V_a = 1V$$

$$I_T = i_1 + i_2 + i_3 \\ = 0.02(1) + \frac{1}{330} + \frac{1}{130} = 31.7 \text{ mA}$$
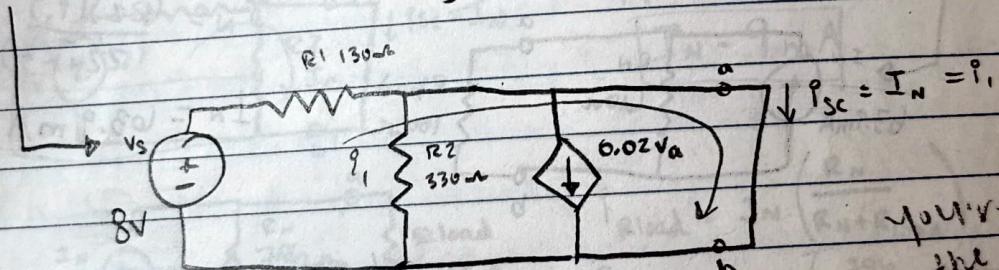
$$R_{ph} = \frac{1V}{31.7 \text{ mA}} = \boxed{32.5 \Omega}$$






$$-8V + (R1)(I_N) = 0$$

$$I_N = (61.5 \text{ mA})$$

you're  
the  
best!  
-12/21

Class 2/14/2023

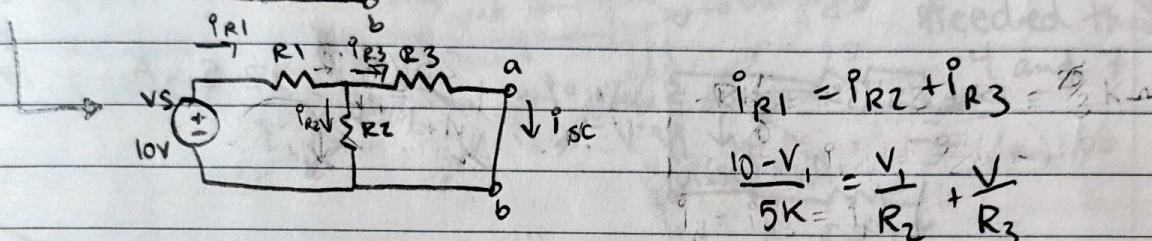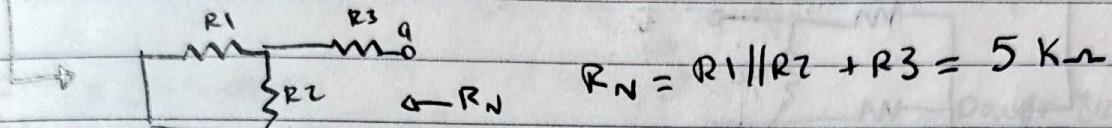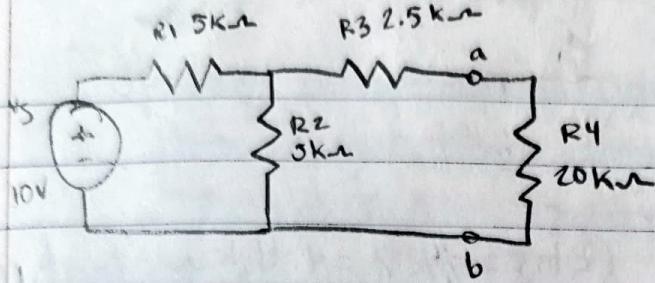

$$R_N = R_1 \parallel R_2 + R_3 = 5 \text{ k}\Omega$$

$$I_{R1} = I_{R2} + I_{R3}$$


$$\frac{10 - V_a}{5\text{k}} = \frac{V_a}{R_2} + \frac{V_a}{R_3}$$

$$\frac{10}{5\text{k}} = V_a \left( \frac{1}{5\text{k}} + \frac{1}{5\text{k}} + \frac{1}{2.5\text{k}} \right)$$



$$V_a = 2.5\text{V}$$

$$I_{SC} = \frac{2.5}{R_3} = 1\text{mA}$$

Lab 2/17/2023

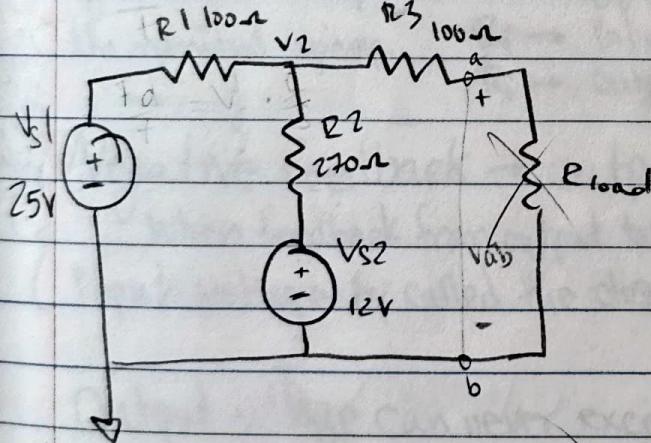

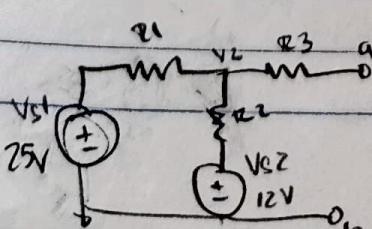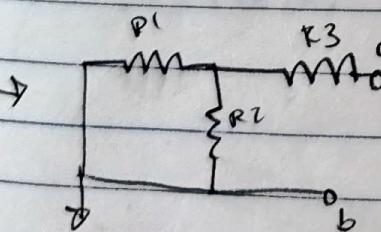
$$R_{TH} = R_1 \parallel R_2 + R_3 = 173\text{\Omega}$$





$$-25\text{V} + I_{R1} + I_{R2} + 12\text{V} = 0$$

$$I = \frac{13\text{V}}{(R_1 + R_2)} = 0.035\text{A}$$

$$V_{ab} = 21.49\text{V}$$

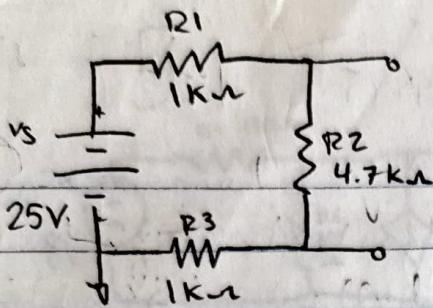
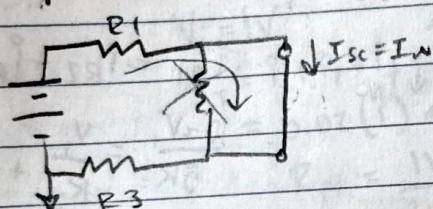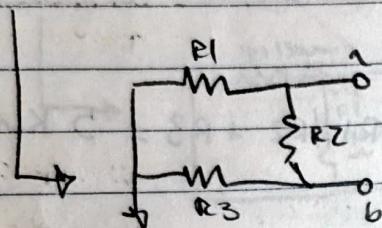
$$(R_1 + R_3) // R_2 = 1.4 \text{ k}\Omega$$



$$\frac{25V}{1+1\text{k}\Omega} = 12.5\text{mA}$$

# 5.1 Introduction / 5.2 Op amp


op amp → operational amplifier

↳ behaves like a voltage-controlled voltage source


↳ able to sum, amplify, integrate, and differentiate signals

Silicon dual in-line package (DIP) → type of op amp

Balance	31	8	No connection
Inverting input	32	7	$V^+$
Noninverting input	33	6	Output
Input	34	5	Balance

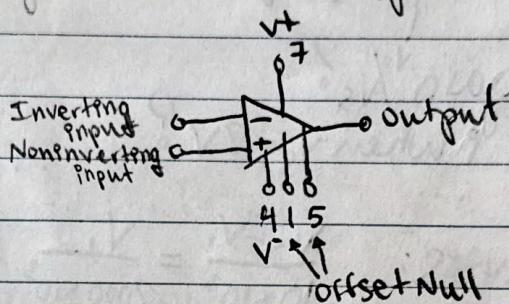

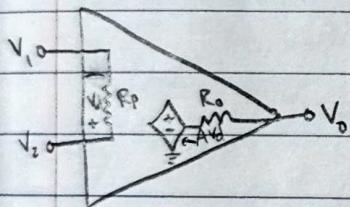power supply is  
needed through  
4 and 7



$$V_d = V_2 - V_1$$

$$V_o = A V_d = A (V_2 - V_1)$$

equivalent circuit of  
the nonideal opamp.

$A \rightarrow$  open loop voltage gain

$R_i \rightarrow$  input resistance

$R_o \rightarrow$  output resistance

{ Negative feedback → output is fed back to the inverting terminal  
When feedback from output to input, ratio of output voltage to  
input voltage is called the closed-loop gain.


Output voltage can never exceed power supply voltage.

Example on back.

given the circuit: And  $A = 2 \times 10^5$

$$R_F = 2 M\Omega$$

$$R_o = 50 \Omega$$

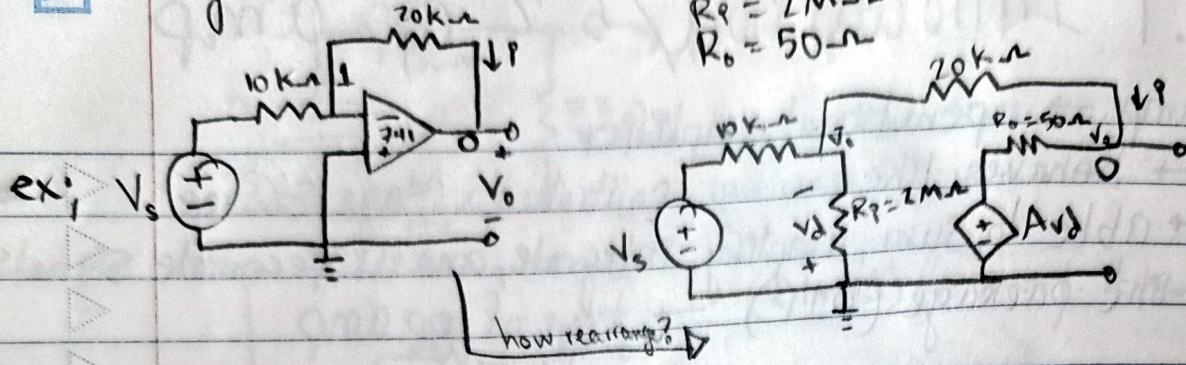

Closed-loop gain  $\frac{V_o}{V_s}$ ?  
current  $i$  when  $V_s = 2V$ ?

Nodal Analysis:  $\frac{V_s - V_1}{10 \times 10^3} = \frac{V_1}{2000 \times 10^3} + \frac{V_1 - V_o}{20 \times 10^3}$

$$V_1 = \frac{2V_s + V_o}{3}$$

At node 0,  $\frac{V_1 - V_o}{20 \times 10^3} = \frac{V_o - AV_d}{50}$

$$V_d = -V_1, A = 200,000$$

$$V_1 - V_o = 400(V_o + 200,000V_1)$$

$$\therefore \frac{V_o}{V_s} = -1.999$$

$$\text{When } V_s = 2V, V_o = -3.999V, V_1 = 20.066 \text{ mV}$$


$$i = \frac{V_1 - V_o}{20 \times 10^3} = 0.1999 \text{ mA}$$

What does Neg Voltage mean??

## 5.3 Ideal Op Amp

Ideal opamp:

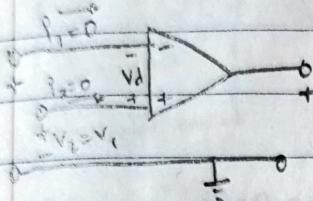- 1.) Infinite loop gain,  $A \approx \infty$
- 2.) Infinite input resistance,  $R_i \approx \infty$
- 3.) Zero output resistance,  $R_o \approx 0$




Properties of Ideal opamp:

$$I_1 = 0, I_2 = 0 \text{ (because of } \infty \text{ resistance)}$$

$$V_d = V_2 - V_1 = 0$$

$$V_1 = V_2$$

## 5.4 Inverting Amplifier

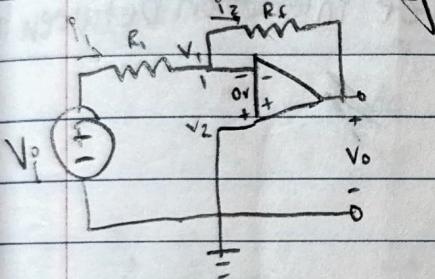


$$I_1 = I_2 \Rightarrow \frac{V_p - V_1}{R_1} = \frac{V_1 - V_o}{R_f}$$

$$\frac{V_p}{R_1} = \frac{V_o}{R_f} \quad V_o = -\frac{R_f}{R_1} V_p$$


$$\text{Voltage gain: } A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

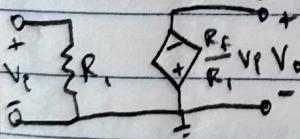An inverting amplifier reverses polarity of input signal whilst amplifying it.



Equivalent circuit for  
Inverting Amplifier

## 5.5 Noninverting Amplifier

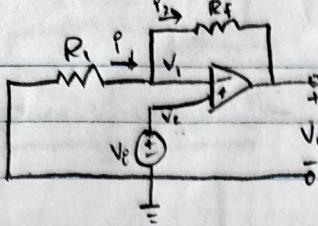


$$R_1 = R_2 \Rightarrow \frac{O-V_i}{R_1} = \frac{V_i - V_o}{R_F}$$

$$-\frac{V_i}{R_1} = \frac{V_p - V_o}{R_F}$$

$$V_o = \left(1 + \frac{R_F}{R_1}\right)V_i$$


Voltage gain:  $A_v = \frac{V_o}{V_p} = 1 + \frac{R_F}{R_1}$

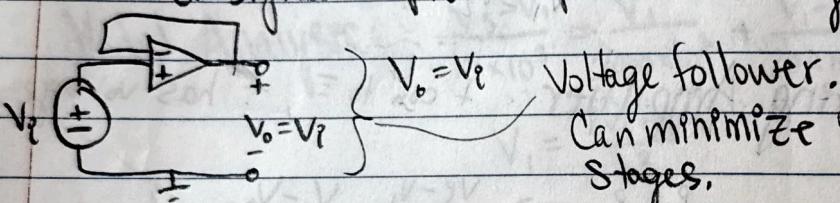designed to provide positive voltage gain



$V_o = V_i$  Voltage follower.


Can minimize interaction between stages.

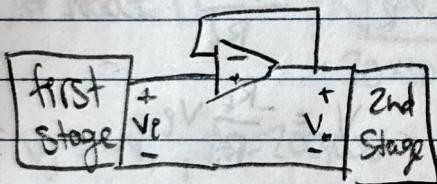
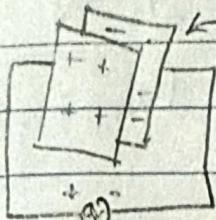
## 6.1 Intro / 6.2 Capacitors

Capacitor  $\rightarrow$  stores energy

$\hookrightarrow$  two conducting plates separated by an insulator (dielectric)



capacitor.

$$\text{charge stored} \rightarrow q = CV$$

$C$   $\rightarrow$  constant of proportionality (capacitance)

$\hookrightarrow$  unit Farad (F)  $1 \text{ Farad} = \frac{1 \text{ C}}{1 \text{ V}}$


Capacitance  $\rightarrow$  ratio of the charge on one plate to the voltage between the two plates.

$\hookrightarrow$  doesn't depend of  $q$  or  $V$ , rather, the dimensions of the plate.


$$C = \frac{\epsilon_0 A}{d} \quad \epsilon_0 \rightarrow \text{permittivity of material between plates}$$

$A \rightarrow$  surface area of each plate

$d \rightarrow$  distance between plates

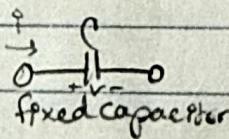

fixed capacitor

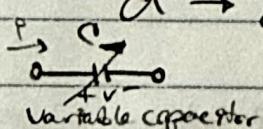

variable capacitor


$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$W = \frac{1}{2} CV^2 = \frac{q^2}{2C}$$

$\star$  a capacitor is DC current

$\star$  a voltage can't change abruptly

Non-ideal capacitor:

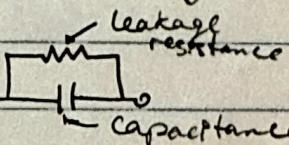

Ex; Calc charge stored on a 3-pF capacitor w/ 20V across it



$$q = 3 \cdot 10^{-12} \cdot 20 = 60 \text{ pC}$$

energy stored:

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 3 \cdot 10^{-12} \cdot 400 = 600 \text{ pJ}$$


## 6.3 series and parallel capacitors

Parallel:

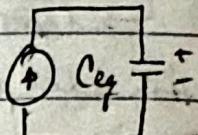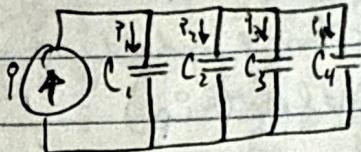

$$C_{eq} = C_1 + C_2 + C_3 + C_4 + \dots + C_N$$

Series:

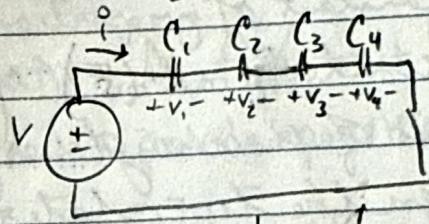


$$C_{eq} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \dots + \frac{1}{C_N}$$

two capacitors in series:  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$
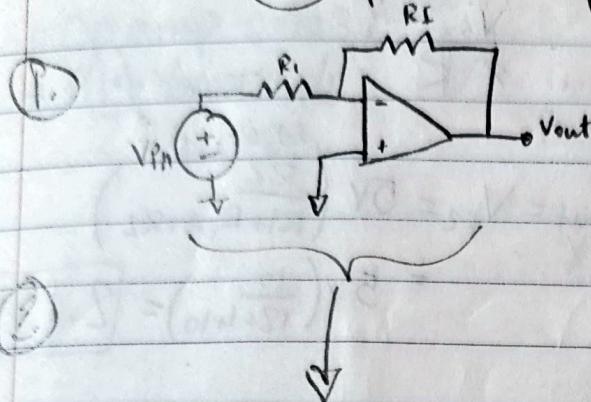
# Op-Amp HW

Seth Ricks


$$R_1 = 2\text{ k}\Omega \quad R_F = 10\text{ k}\Omega \quad V_{in} = 2V$$




$$\begin{aligned} V_{out} &= V_{in} \left( -\frac{R_F}{R_1} \right) \\ &= (2V) \left( -\frac{10}{2} \right) = \boxed{-10V} \end{aligned}$$

$$R_1 = 2\text{ k}\Omega \quad V_{out} = 8V \quad V_{in} = -1V$$
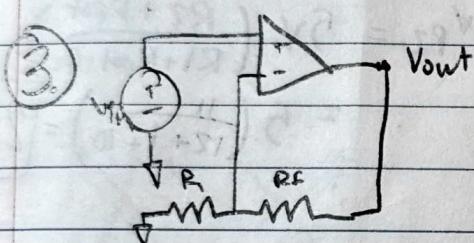
$$\begin{aligned} V_{out} &= V_{in} \left( -\frac{R_F}{R_1} \right) \\ -\left( \frac{V_{out}}{V_{in}} \right) (R_1) &= R_F = \boxed{10\text{ k}\Omega} \end{aligned}$$



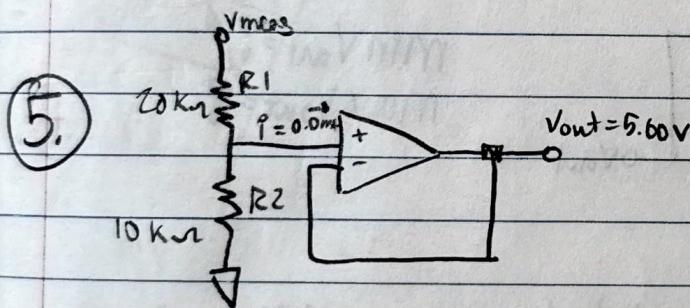
$$\begin{aligned} \frac{V_{out}}{V_p} &= \left( 1 + \frac{R_F}{R_1} \right) \\ V_{out} &= \left( 1 + \frac{10}{2} \right) (2) = \boxed{12V} \end{aligned}$$



$$V_{R2} = V_{out} = 5.60V$$

$$V_{out} = V_{meas} \left( \frac{R_2}{R_1 + R_2} \right)$$
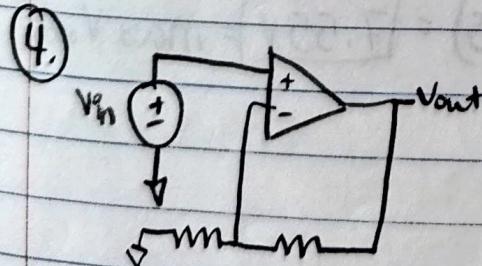
$$V_{meas} = V_{out} \left( \frac{R_1 + R_2}{R_2} \right) = 15V$$




$$\frac{V_{out}}{V_p} = \left( 1 + \frac{R_F}{R_1} \right)$$

$$\begin{aligned} V_{out} &= 8V \\ R_1 &= 2\text{ k}\Omega \\ V_{in} &= 1V \end{aligned}$$

$$\begin{aligned} \left( \frac{V_{out}}{V_p} - 1 \right) (R_1) &= R_F \\ R_F &= \boxed{14\text{ k}\Omega} \end{aligned}$$

(6)

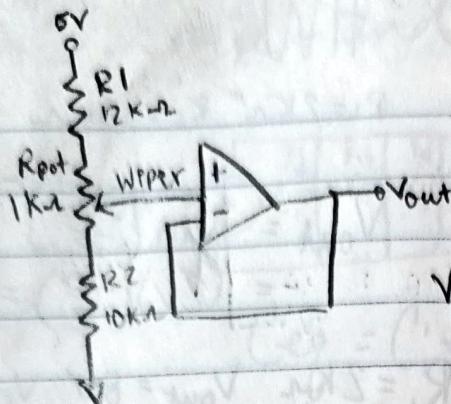


$$V_{out} = ?$$

\*1/R

above wiper  $\rightarrow 1\text{k}\Omega$

$$\begin{aligned} V_{out} &= V_{R2} = 5V \left( \frac{R2}{R1 + R_{pot} + R2} \right) \\ &= 5V \left( \frac{10}{12 + 1 + 10} \right) = [2.17V] \end{aligned}$$

(7.)

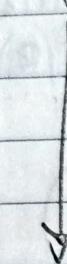


$$V_{out} = ?$$

\*1/R, below wiper  $\rightarrow 1\text{k}\Omega$

$$\begin{aligned} V_{out} &= V_{R2} = 5V \left( \frac{R2 + R_{pot}}{R1 + R_{pot} + R2} \right) \\ &= 5 \left( \frac{11}{12 + 1 + 10} \right) = [2.39V] \end{aligned}$$

(8.)

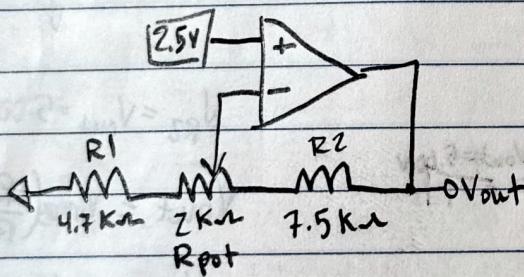

$$\min V_{out} = ?$$

$$\max V_{out} = ?$$

If resistance to the right of wiper is  $2\text{k}\Omega$ :

$$V_{out} = \left( 1 + \frac{7.5}{6.7} \right) (2.5) = [5.30V] = \min V_{out}$$

If resistance to the left of wiper is  $2\text{k}\Omega$ :


$$V_{out} = \left( 1 + \frac{9.5}{4.7} \right) (2.5) = [7.55V] = \max V_{out}$$

# OP Amp Summary


Opamp rules:

- 1)  $V_m = V_p$
- 2)  $I_{in} = 0A$

non-inverting:

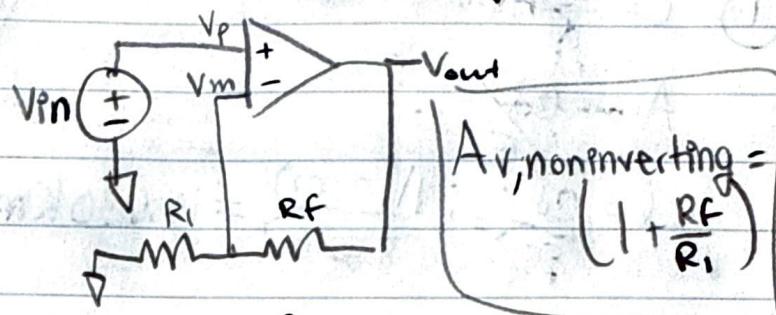
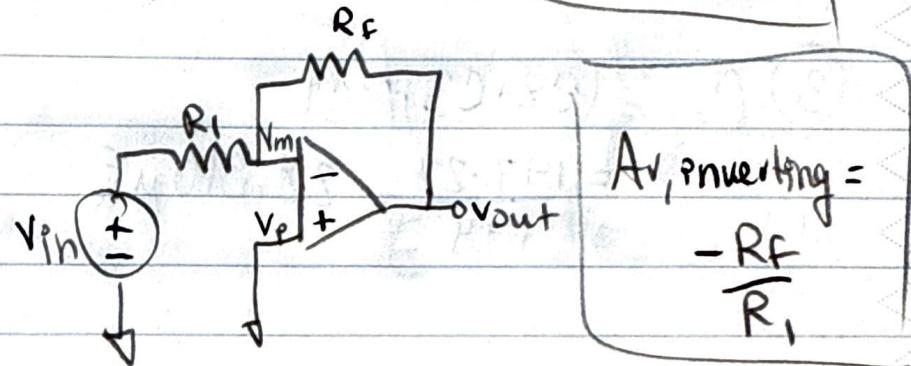
$$A_{V, \text{noninverting}} = \left(1 + \frac{R_F}{R_i}\right)$$



$$A_{V, \text{inverting}} = -\frac{R_F}{R_1}$$


# Capacitor HW

$$C = \frac{\epsilon A}{d}$$

$$A = \frac{Cd}{\epsilon}$$

$$l = \sqrt{\frac{Cd}{\epsilon}} = \frac{11(0.00)}{8.85 \times 10^{-12}} = 10.630 \text{ Km}$$
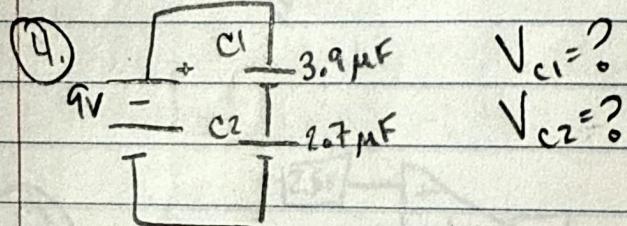
$$\begin{aligned} ③ C_{eq} &= (C_2 + C_3) // C_1 \\ &= \frac{147 \cdot 27}{147 + 27} = 22.810 \mu\text{F} \end{aligned}$$




Series capacitors have the same separated charge

$$\begin{aligned} q_f &= CV \\ q_f &= C_{eq} V = \left( \frac{3.9 \cdot 2.7}{3.9 + 2.7} \right) (9) \\ &= 141.359 \mu\text{C} \end{aligned}$$

$$V_{c1} = \frac{q_{eq}}{C_1} = 3.682 \text{ V}$$

$$V_{c2} = \frac{q_{eq}}{C_2} = 5.318 \text{ V}$$
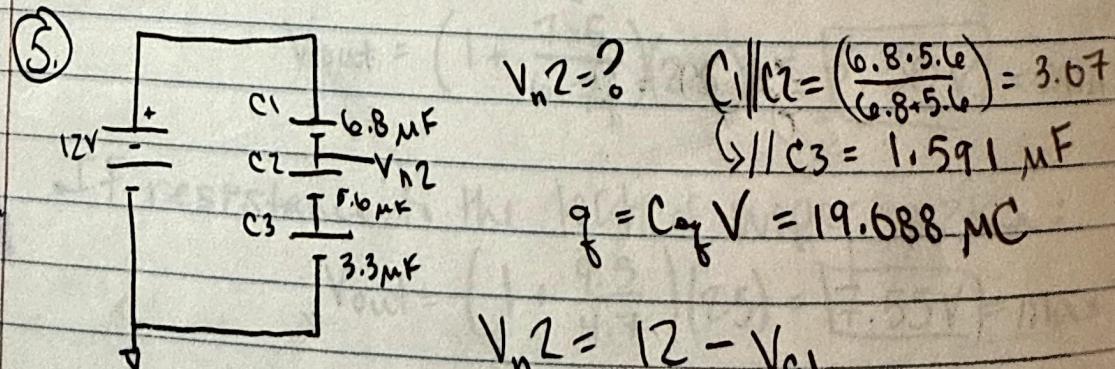
$$V_{c1} + V_{c2} = 9 \text{ V} \checkmark$$



$$C_1 // C_2 = \left( \frac{6.8 \cdot 5.6}{6.8 + 5.6} \right) = 3.07$$


$$C_1 // C_2 // C_3 = 1.591 \mu\text{F}$$

$$q_f = C_{eq} V = 19.688 \mu\text{C}$$

$$V_{n2} = 12 - V_{c1}$$

$$V_{c1} = q_f / C_1 = 2.867 \text{ V}$$

$$V_{n2} = 9.193 \text{ V}$$

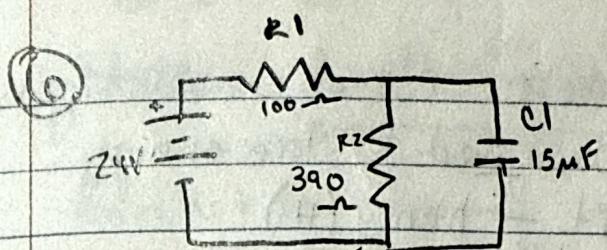

$$W = \frac{1}{2} CV^2 = \frac{q^2}{2C}$$

$$V_{C1} = V_{R2} = 24V \left( \frac{R2}{R1+R2} \right) = 19.102V$$

$$W_{C1} = \frac{1}{2} C_1 V_{C1}^2 = \frac{1}{2} (15\mu F) (19.102V)^2$$

$$W_{C1} = 2.7 \text{ mJ}$$

Class 2/27/2023

$$\begin{array}{c} +Q \\ | \\ | \\ | \\ | \\ -Q \end{array} \xrightarrow{\text{non-polarized}} \begin{array}{c} + \\ | \\ | \\ | \\ | \\ - \end{array} \xrightarrow{\text{polarized}} \begin{array}{c} + \\ | \\ | \\ | \\ | \\ - \end{array} \quad E = \epsilon_r \epsilon_0$$

$$\epsilon_0 = \text{air vacuum} = 8.85 \times 10^{-12} \text{ F/m}$$

air: 1      barium tetrinitrate: 1,000


glass: 4-10

$$i_c(t) = C \frac{dv_c}{dt}$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(\tau) d\tau + v(t_0)$$

$$W = \frac{1}{2} Cv^2 \quad (\text{Joules}) \quad \begin{matrix} \text{Energy stored} \\ \text{in capacitor} \end{matrix}$$

## Ch. 4 Inductors

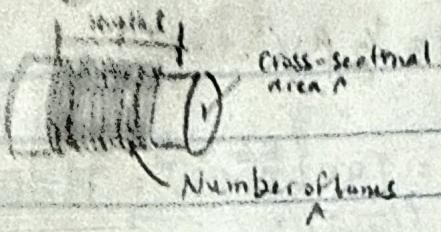

Inductor - coil of conducting wire designed to store energy unit - henry (H)

opposition to the change of current flow  $\frac{V}{A}$


$$L = \frac{N^2 A}{l}$$

$N \rightarrow \# \text{ of turns}$

$A \rightarrow \text{cross-sectional area}$


$l \rightarrow \text{length}$

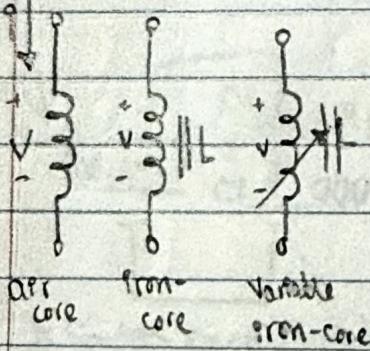$M \rightarrow \text{permeability of the core}$




Energy stored:

$$W = \frac{1}{2} L I^2$$

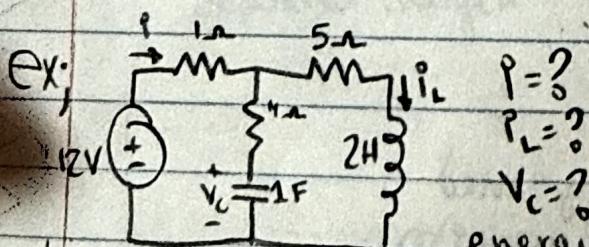



energy stored by capacitor and inductor?

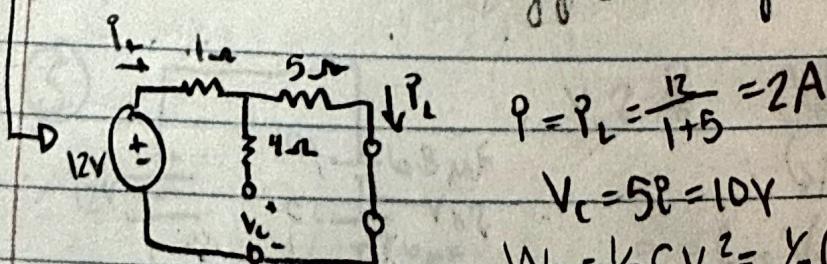

Inductors resist fast changes in current

## 6.5 Series and Parallel Inductors

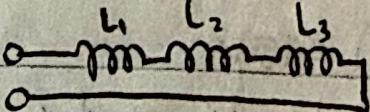Series:   $L_{\text{eq}} = L_1 + L_2 + L_3 + \dots + L_N$

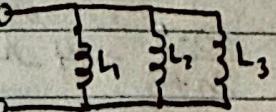Parallel:   $\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$

So, basically same as resistors.


## 7.1 Introduction

"First order circuit"  $\rightarrow$  resistor and capacitor  
 $\left\{ \begin{array}{l} \text{RC circuit} \\ \text{RL circuit} \end{array} \right. \rightarrow \text{resistor and inductor}$

Two ways to excite  $\rightarrow C$  &  $L$  are charged, or  
 ↳ Dependent sources
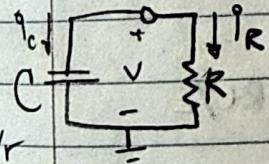
## 7.2 The source-free RC circuit

\* Current in the ways??  $\rightarrow$  dc source disconnected




Initial voltage:  $V(0) = V_0$ .

$$V(0) = \frac{1}{C} CV_0^2$$

$$i_C + i_R = 0$$

$$C \frac{dv}{dt} + \frac{V}{R} = 0 \rightarrow \frac{dv}{dt} + \frac{V}{RC} = 0$$

$$\text{Ans } V(t) = V_0 e^{-t/RC}$$


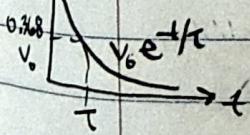


Time constant  $\rightarrow$  time required for the response to decay to a factor of  $1/e$  or 36.8%

$$\tau = RC$$

$$\text{So, } V(t) = V_0 e^{-t/\tau}$$

A circuit:  $5\tau$  to charge.

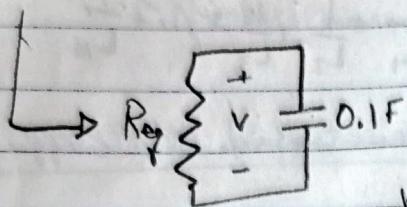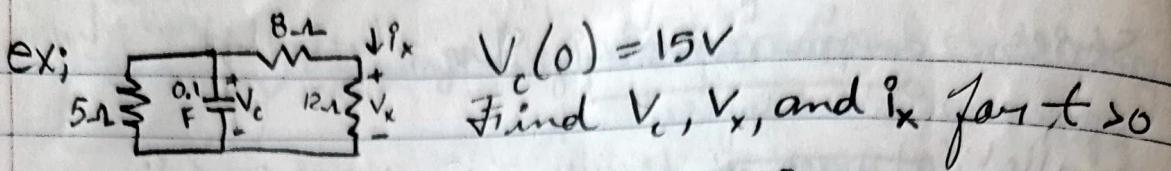

$$R_{eq} = \frac{20+5}{20+5} = 4\Omega$$


$$\tau = R_{eq} C = 4(0.1) = 0.4s$$

$$V_c = V = V(0)e^{-t/\tau} = 15e^{-t/0.4}V = 15e^{-2.5t}V$$

- Voltage div.  $V_x = \frac{12}{12+8}V = 0.6(15e^{-2.5t}) = 9e^{-2.5t}V$

- Ohm's Law  $i_x = \frac{V_x}{12} = 0.75e^{-2.5t}A$

### 7.3 The Source-Free RL circuit:

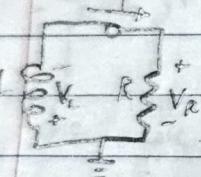

$$i(0) = I_0$$


$$W(0) = \frac{1}{2}LI_0^2$$

$$V_L + V_R = 0$$


$$L \frac{di}{dt} + Ri = 0$$

$$\tau = \frac{L}{R} \rightarrow i(t) = I_0 e^{-t/\tau}$$



$$\Rightarrow i(t) = I_0 e^{-Rt/L}$$

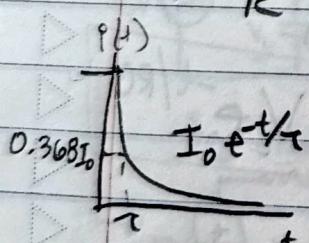

$$q(t+\tau) = 0.368q(t)$$

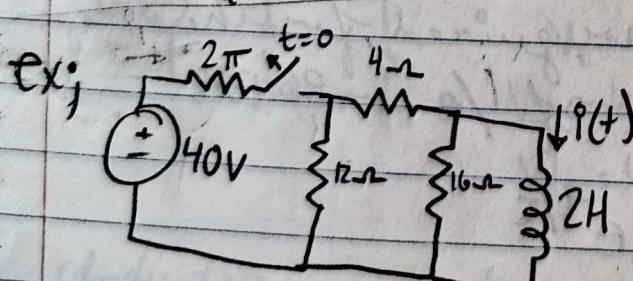

Find  $i(t)$  for  $t > 0$

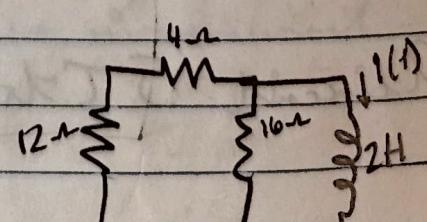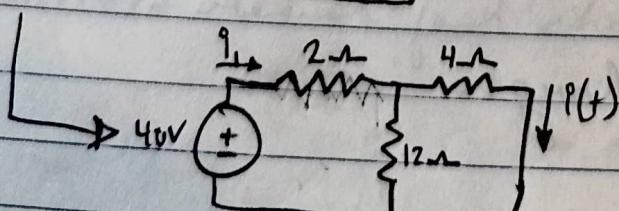

$t < 0$

( $\text{AC circuit}$ ) combine  $12\Omega + 4\Omega \rightarrow 3\Omega$

$$I_1 = \frac{40}{2+3} = 8A$$

$$i(0) = i(t) = \frac{12}{12+4} I_1 = 6A, t < 0$$


$$(t \geq 0) \rightarrow R_{\text{eq}} = 8\Omega, \quad T = \frac{L}{R_{\text{eq}}} = \frac{1}{4}s$$

$$i(t) = i(0)e^{-1/t} = 6e^{-4t} A$$

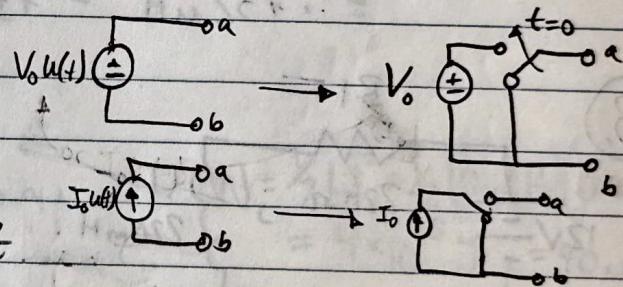7.4 Singularity Functions: (or switching functions)  
functions that are either discontinuous or have discontinuous derivatives

Unit Step function:  $u(t)$  is 0 for  $t < 0$ , and 1 for  $t \geq 0$

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$$




Derivative of unit step function

step function  $\rightarrow$  unit impulse function  $\delta(t)$

$$\delta(t) = \frac{d}{dt} u(t) = \begin{cases} 0, & t < 0 \\ \text{undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$

$$\int_0^{\infty} \delta(t) dt = 1$$

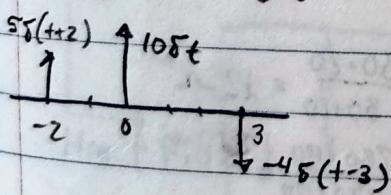


$$\int_a^b f(t)(t-t_0) dt = f(t_0)$$

at functional point where impulse occurs

Integrating unit step function  $\rightarrow$  unit ramp function
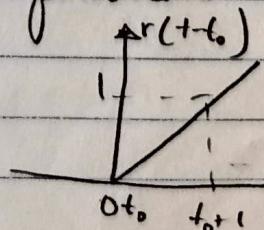
$$r(t) = \begin{cases} 0, & t \leq 0 \\ 1, & t \geq 0 \end{cases}$$



# Inductors HW

Seth Ricks

1.

Four inductors in series.

$$L_1 = 120 \mu\text{H}, L_2 = 47 \mu\text{H}, L_3 = 750 \text{nH}, L_4 = 560 \mu\text{H}$$

$$L_{\text{eq}} = 120 \times 10^{-6} + 47 \times 10^{-6} + 750 \times 10^{-9} + 560 \times 10^{-6}$$

$$= 7.27 \times 10^{-4} = 727 \mu\text{H}$$

2.

Four inductors in parallel.

$$L_1 = 120 \mu\text{H}, L_2 = 47 \mu\text{H}, L_3 = 750 \text{nH}, L_4 = 560 \mu\text{H}$$

$$= 750 \mu\text{H}$$




$$L_1 \parallel L_2 = \frac{120 \cdot 47}{120 + 47} = 33.77$$

$$L_3 \parallel L_4 = \frac{750 \cdot 560}{750 + 560} = 0.749$$

$$(L_1 \parallel L_2) \parallel (L_3 \parallel L_4)$$

$$= 732 \mu\text{H} = 732 \text{nH}$$

3.

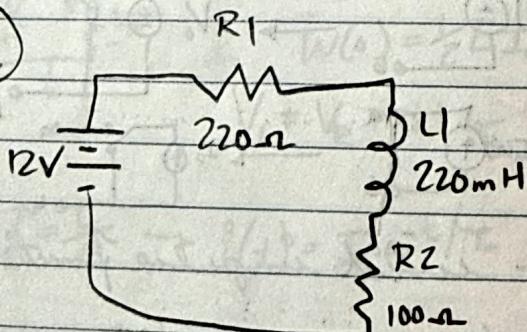


$$i = \frac{12V}{330 \Omega} A = 0.0364 A$$

$$W = \frac{1}{2} L i^2 = \frac{1}{2} (0.22 \text{ H}) (0.0364)^2$$

$$= 1.54 \times 10^{-4} J$$

$$= 154 \mu\text{J}$$

4.

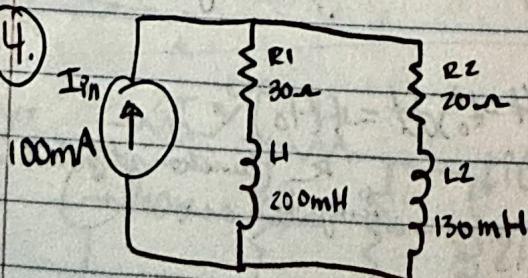


$$R_{\text{eq}} = \frac{30 \cdot 20}{30 + 20} = 12 \Omega$$

$$L_{\text{eq}} = \frac{200 \cdot 130}{220 + 130} = 78.79 \text{ mH}$$


$$W = \frac{1}{2} L i^2 = \frac{1}{2} (0.07879) (.1^2)$$

$$= 3.940 \times 10^{-4} J$$


$$= 394 \mu\text{J}$$

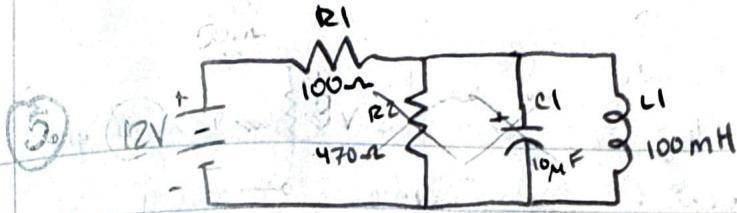

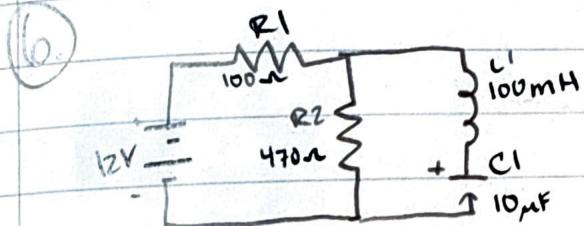
$$W = \frac{1}{2} L I^2 = \frac{1}{2} (0.1) \left(\frac{12}{100}\right)^2 = 7.2 \times 10^{-4} \text{ J} = 720 \mu\text{J}$$



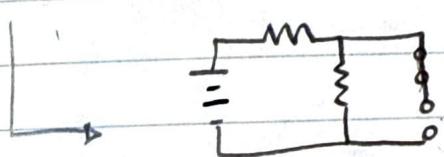
$$\begin{aligned} V_{R2} &= V_{C1} \\ V_{R2} &= 12V \left( \frac{R_2}{R_1 + R_2} \right) = 12V \left( \frac{470}{570} \right) \\ &= 9.895V \end{aligned}$$


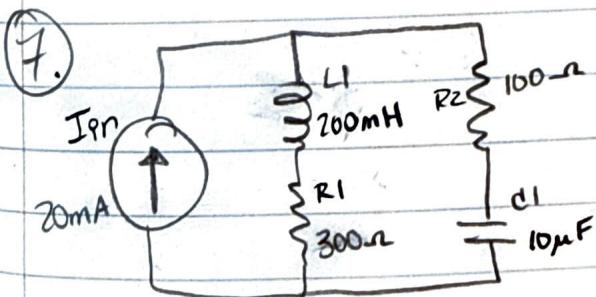
$$\begin{aligned} W &= \frac{1}{2} C_1 V_{C1}^2 = \frac{1}{2} (10 \mu\text{F}) (9.895)^2 \\ &= 490.0 \mu\text{J} \end{aligned}$$



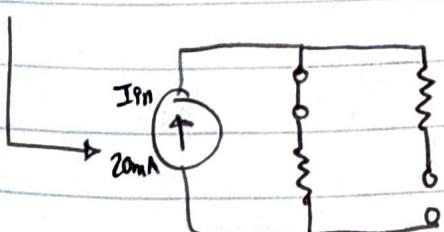
$$\begin{aligned} W_L &= \frac{1}{2} L I^2 = \frac{1}{2} (0.2 \text{ H}) (0.02 \text{ A})^2 \\ &= 4 \times 10^{-5} \text{ J} = 40 \mu\text{J} \end{aligned}$$



$$\begin{aligned} W_C &= \frac{1}{2} C_1 V_{C1}^2 \\ V_{C1} &= V_{R1} = (300 \Omega \cdot 0.02 \text{ A}) = 6 \text{ V} \\ W_C &= \frac{1}{2} (10 \times 10^{-6} \text{ H}) (6 \text{ V})^2 \\ &= 180 \mu\text{J} \end{aligned}$$


$$W_T = W_L + W_C = 220 \mu\text{J}$$

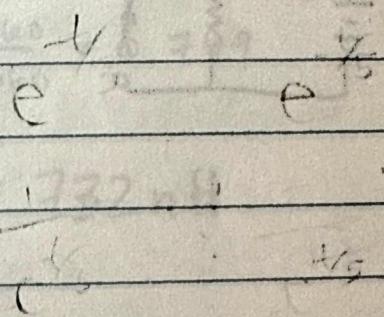Question: Voltage across capacitor  
in this circuit is independent of the  
resistor???



# Source Free RC and RL Circuits HW

1.

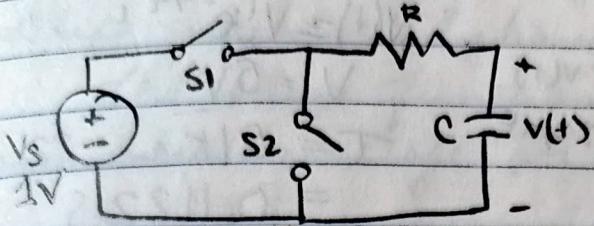

$$V(t) = V_0 e^{-t/\tau}$$


$$V(0) = 1V$$

$$V(\tau) = e^{-1}$$


$$V(3\tau) = e^{-3}$$

$$V(5\tau) = e^{-5}$$


$$V(10\tau) = e^{-10}$$

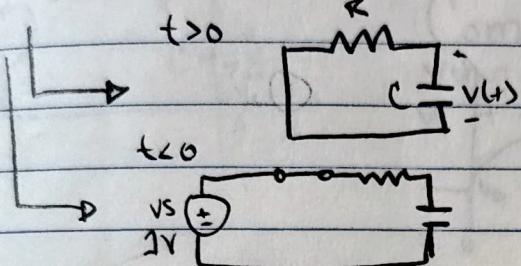

$t < 0$

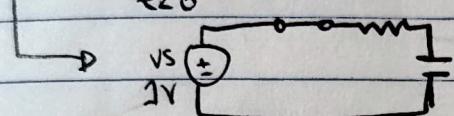

2.

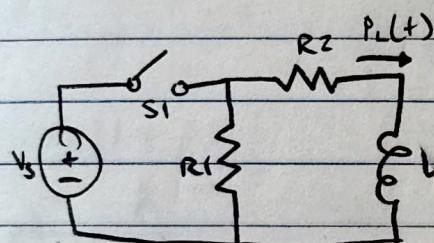

$$i_{L}(0) = 0.5A$$

$$i(t) = I_0 e^{-t/\tau}$$


$$i(\tau) = 0.5e^{-1}$$

$$i(3\tau) = 0.5e^{-3}$$

$$i(5\tau) = 0.5e^{-5}$$


$$i(10\tau) = 0.5e^{-10}$$

3.

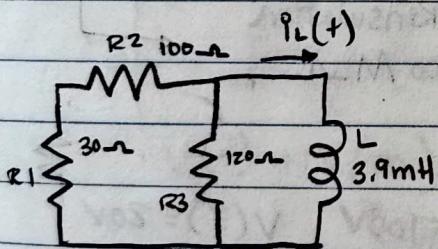

$$\tau = \frac{L}{R} = \frac{3.9 \text{ mH}}{62.4 \text{ ohm}} = 62.5 \text{ ms}$$

4.

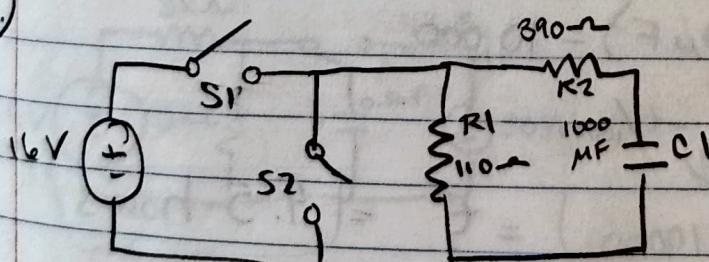


$$V(t) = V_0 e^{-t/\tau}$$

$$R_{eq} = \frac{390 \cdot 110}{390 + 110} = 78 \text{ ohm}$$


$$\tau = R_{eq} \cdot C = 0.078 \text{ s}$$

$$V(0) = 16V \left( \frac{R_1}{R_1 + R_2} \right) = 3.52V$$

$$V(t) = 3.52 e^{-t/0.078}$$

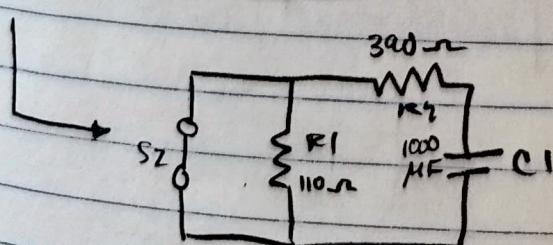

(5)

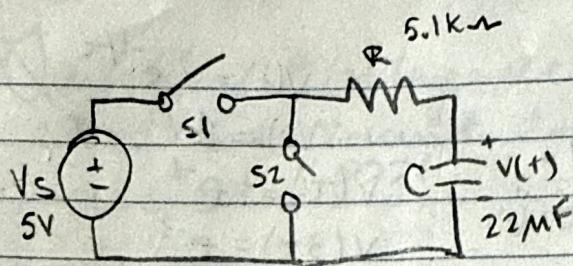

$$V(?) = 2.2 \text{ V}$$

$$V(t) = V_0 e^{-t/\tau}$$


$$V_0 = 5 \text{ V}$$

$$\begin{aligned} \tau &= 5.1 \text{ k}\Omega \cdot 22 \mu\text{F} \\ &= 0.1122 \text{ s} \end{aligned}$$

$$2.2 \text{ V} = 5 \text{ V} e^{-t/0.1122}$$

$$\begin{aligned} t &= -\ln\left(\frac{2.2}{5}\right) \cdot 0.1122 \\ &= 0.092 \text{ s} \\ &= 92 \text{ ms} \end{aligned}$$

(6.)

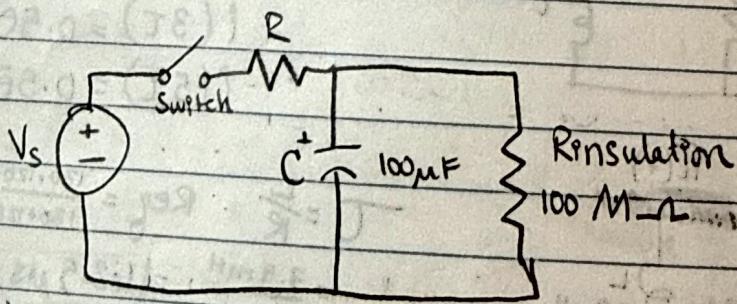

Time (hrs) for  $V_s: 100 \text{ V} \rightarrow 20 \text{ V}$        $V(0) = 100 \text{ V}$        $V(?) = 20 \text{ V}$


$$\tau = RC = (100 \text{ M}\Omega)(100 \mu\text{F}) = 10,000$$

$$20 \text{ V} = 100 \text{ V} \cdot e^{-t/10,000}$$

$$-\left(\ln\left(\frac{1}{5}\right) \cdot 10,000\right) = t = \boxed{4.5 \text{ hours}}$$

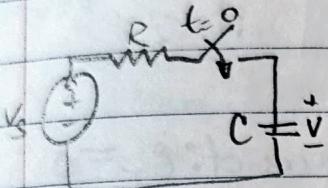
## 7.5 Step response of an RC circuit

Step response - behavior when the excitation is the step function, which may be voltage or current. Sudden voltage or current



Complete response:  $V(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{RC}}, t \geq 0 \end{cases}$

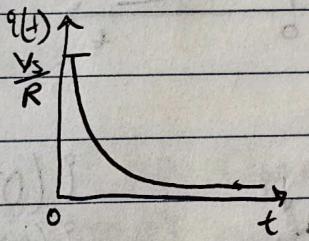
This is if it is charged initially. Otherwise  $V_0 = 0$ .



Complete response = Natural response + forced response  
 store energy independent source  
 temporary part permanent part  
 transient response steady-rate response

$$V(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$$

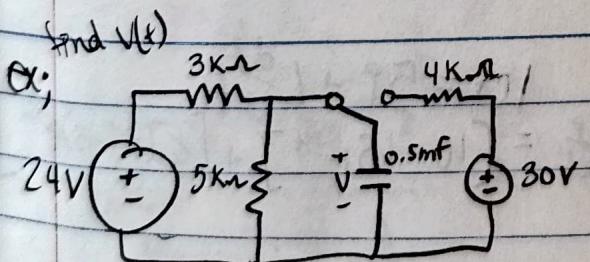↑ final  $V_\infty$       ↑ initial  $V_0$       ↑ time constant




$$V(0^-) = \frac{5}{5+3}(24) = 15V = V(0)$$

$$\tau = R_{TH} C = 2s$$



$$V(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$$

$$= 30 + (15-30)e^{-t/2} = 30 - 15e^{-0.5t} V$$

## 7.6 Step response of an $RC$ circuit

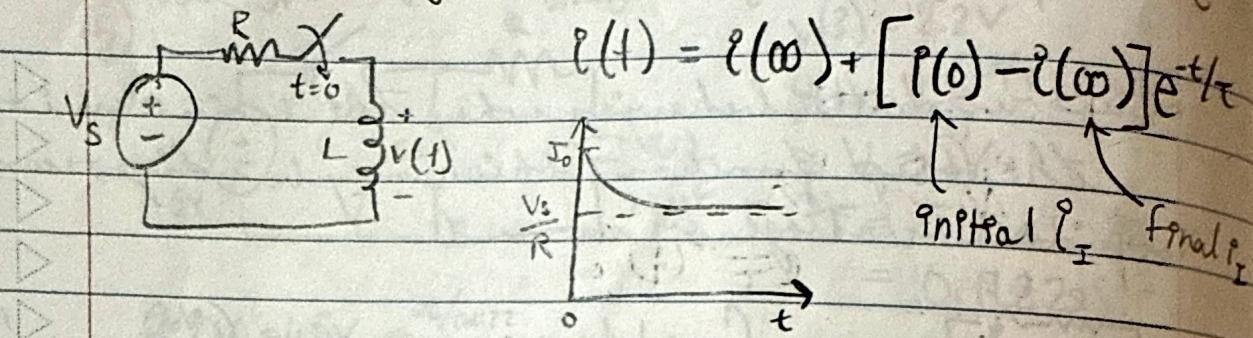

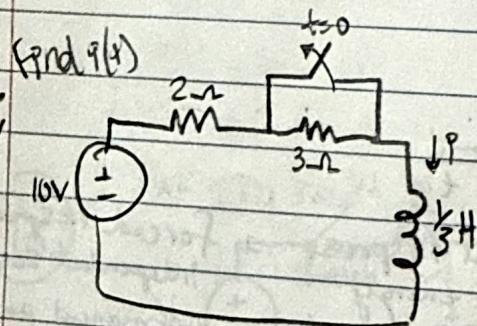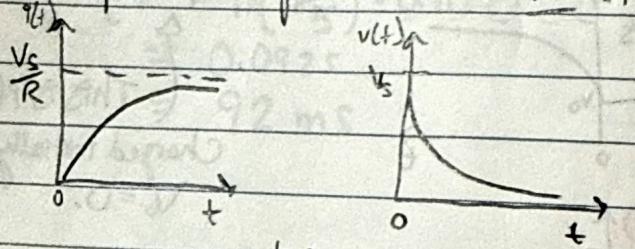Step  $RL$  responses for no initial current:  $i_r = 0$



$$i(0^-) = \frac{10}{2} = 5A = i(0)$$

$$i(\infty) = \frac{10}{2+3} = 2A$$

$$R_{TH} = 2+3 = 5\Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{3}{5} = \frac{1}{15}s$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= 2 + (5-2)e^{-15t} = 2 + 3e^{-15t} A, t \geq 0$$

Check: for  $t > 0$ , KVL:  $10 = 5i + L \frac{di}{dt}$

$$5i + L \frac{di}{dt} = [10 + 15e^{-15t}] + [3(3)(-15)e^{-15t}]$$


Instantaneous value = Final + [Initial - Final]  $e^{-(t-t_0)/\tau}$

(63.2%)

36.8%


## 7.9 Applications

### Delay Circuits

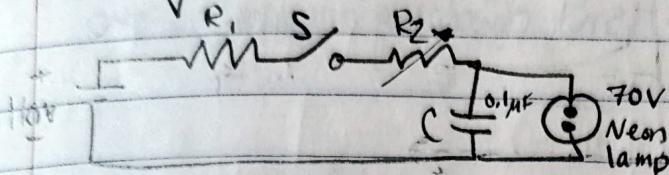

When S is closed, C charges until it reaches 70V, which then fires through lamp quickly and restarts. Can make the light flash several times a second.


### Photoflash Unit

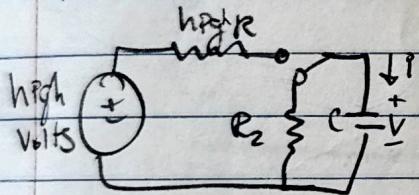

Cap. charges slowly through high  $R_1$ , ( $5R_1C$ ) and then discharges quickly through low  $R_2$  ( $5R_2C$ )


### Relay Circuits

- magnetically controlled switch

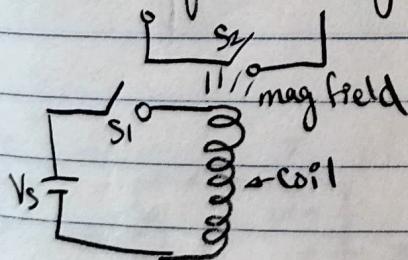


time to switch  $\rightarrow$  relay delay time

### Automobile Ignition Circuit

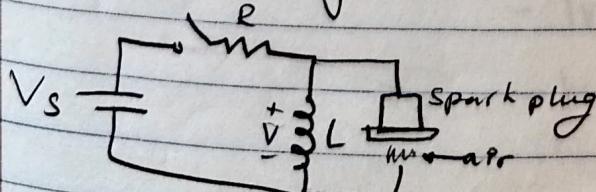

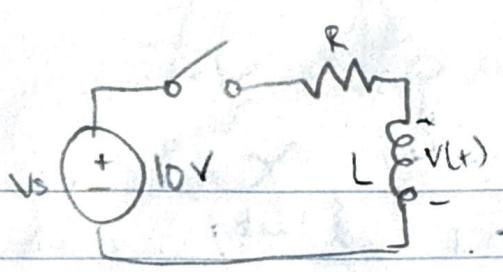Each cylinder is ignited at proper times w/ inductor. When switch is opened suddenly, large V created through a lot of Amps. Causes air to ignite. (gas)




$$V(0) = 10V$$

- Current = 0 because A can't change instantaneously

$$V(0) = 0, \text{ because } V(t) = L \frac{di}{dt} \rightarrow \frac{di}{dt}$$

isn't changing anymore so  $\rightarrow 0$


# Step Response of RC and RL Circuits

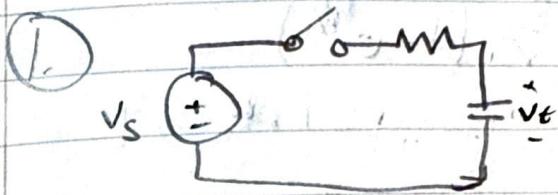

$$V(t=\tau) = V_s(1 - e^{-1}) \quad \checkmark$$

$$V(t=3\tau) = V_s(1 - e^{-3}) \quad \checkmark$$
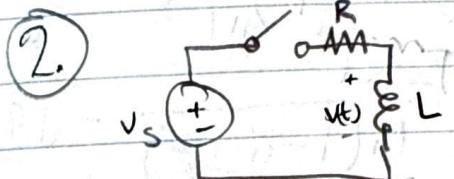
$$V(t=5\tau) = V_s(1 - e^{-5}) \quad \checkmark$$



$$R = 100\text{ }\Omega$$


$$V_s = 1\text{ V}$$

$$i(t) = \frac{V_s}{R} + \left(0 - \frac{V_s}{R}\right)e^{-t/\tau_A}$$

$$i(t=\tau) = \frac{V_s}{100}(1 - e^{-1})\text{ A}$$

$$i(t=3\tau) = \frac{V_s}{100}(1 - e^{-3})\text{ A}$$

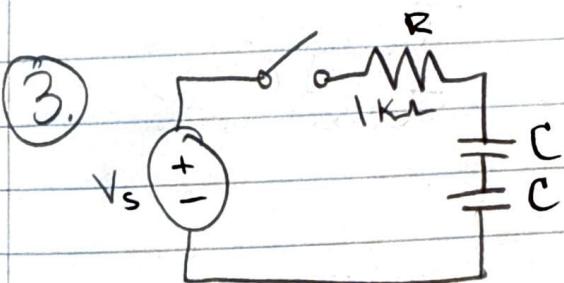
$$i(t=5\tau) = \frac{V_s}{100}(1 - e^{-5})\text{ A}$$



$$RC = \tau = 1\text{ ms} \quad C_{eq} = C_1$$

$$C = ?$$

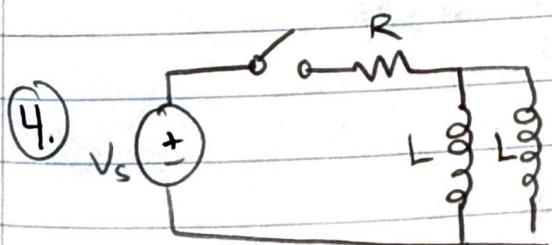
$$C = \frac{1\text{ ms}}{1\text{ k}\Omega} \cdot 2 = 2\text{ }\mu\text{F}$$



$$L = 10\text{ mH} \quad L_{eq} = 5\text{ mH}$$

$$R = ? \quad L/R = 50\text{ }\mu\text{s}$$
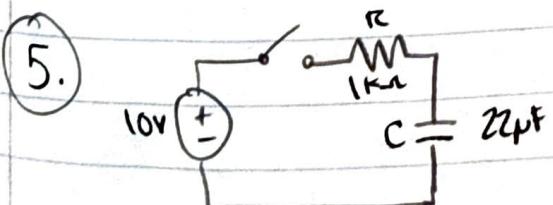
$$R = 5\text{ mH}/50\text{ }\mu\text{s} = 100\text{ }\Omega$$




C is discharged at  $t=0^-$   
 $t \rightarrow 5\text{ V}^+$

$$5\text{ V} = 10\text{ V} (1 - e^{-t/\tau})$$

$$- \ln\left[-\left(\frac{1}{2}\text{ V} - 1\right)\right] \cdot \tau = t$$

$$- \ln\left(1 - \frac{1}{2}\text{ V}\right) \cdot (22\text{ }\mu\text{F})(1\text{ k}\Omega) = 0.015 \quad t = 15\text{ ms}$$

6.

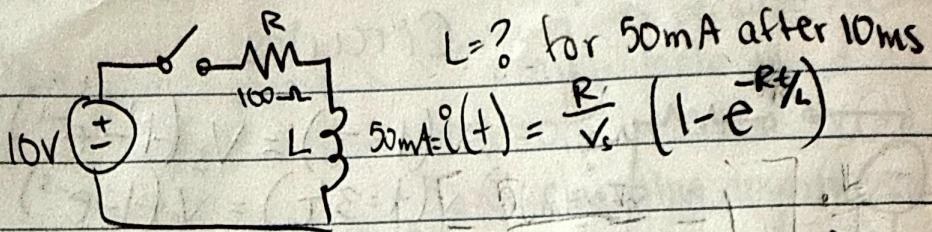


$$50\text{mA} = i(t) = \frac{R}{V_s} \left(1 - e^{-\frac{Rt}{L}}\right)$$

$$\ln \left[ - \left( i(t) \cdot \frac{V_s}{R} - 1 \right) \right] = - \frac{Rt}{L}$$

$$L = \frac{-Rt}{\ln(1 - i(t) \frac{V_s}{R})} = 199.5\text{H}$$

7.

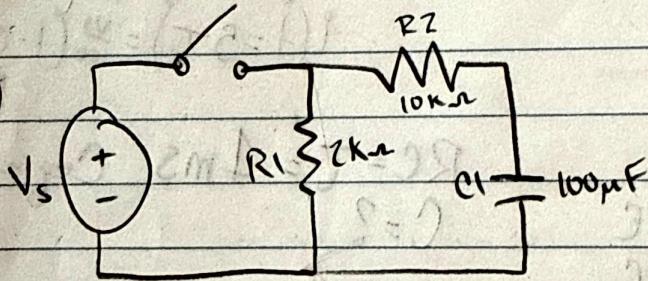

$$T_{\text{charging}} = ?$$

$$T_{\text{discharging}} = ?$$

While charging, the only resistor in question is  $R_2$ ?

$$T = R_2 C_1 = 7.0\text{s}$$

While discharging, resistors in series

$$R_{\text{eq}} = 12\text{k}\Omega$$

$$T = 1.2\text{s}$$

# 9.1 / 9.2 Sinusoids



Sinusoid - a signal that has the form of the sine or cosine function  
 ↳ alternating current!!

$$V(t) = V_m \sin \omega t$$

$V_m$  = Amplitude of sinusoid

$\omega$  = angular frequency in rad/s


$\omega t$  = "argument" of sinusoid

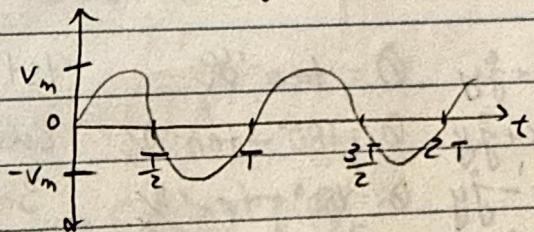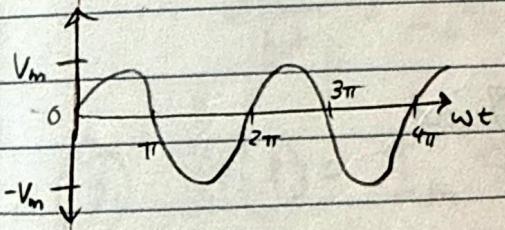

$$T = \frac{2\pi}{\omega}$$

$v(t)$  repeats itself every  $T$  seconds, so  $v(t+T) = v(t)$   
 (it's a periodic function) frequency  $\rightarrow f = \frac{1}{T}$   
 $\omega = 2\pi f$
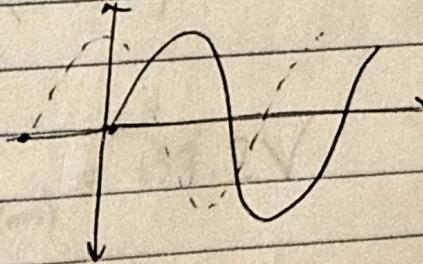
$$v(t) = V_m \sin(\omega t + \phi) \quad \xrightarrow{\text{"phase"}}$$



$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$ , where  $C = \sqrt{A^2 + B^2}$ ,  $\theta = \tan^{-1} \frac{B}{A}$

$$\text{ex: } 3 \cos \omega t - 4 \sin \omega t = 5 \cos(\omega t + 53.1^\circ)$$

Imaginary part  $\rightarrow$  phase  
 real part  $\rightarrow$  magnitude

## B.1 Representation of Complex numbers

$$z = x + jy, \text{ where } j = \sqrt{-1}$$

real      imaginary

Imaginary

real

Polar  $z = r \angle \theta$  ← angle w/ real axis, where  $r = \sqrt{x^2 + y^2}$

magnitude

$$\theta = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \theta, y = r \sin \theta$$

$$z = x + jy = r \angle \theta = r \cos \theta + j r \sin \theta$$

$$z = x + jy \quad \theta = \tan^{-1} \frac{y}{x} \quad 1\text{st Quad}$$

$$z = -x + jy \quad \theta = 180^\circ - \tan^{-1} \frac{y}{x} \quad 2\text{nd}$$

$$z = -x - jy \quad \theta = 180^\circ + \tan^{-1} \frac{y}{x} \quad 3\text{rd}$$

$$z = x - jy \quad \theta = 360^\circ - \tan^{-1} \frac{y}{x} \quad 4\text{th}$$

exponential or  $z = r e^{j\theta}, r = \sqrt{x^2 + y^2}, \theta = \tan^{-1} \frac{y}{x}$

# Sinusoids + Complex Numbers HW

$$① \quad v(t) = 170 \sin(120\pi t) V$$

a.) Peak-to-peak voltage = 350

$$b.) \text{frequency} = \frac{120\pi}{2\pi} = 60 \text{ Hz}$$

$$c.) \text{Period } T = \frac{2\pi}{120\pi} = \frac{1}{60} \text{ s}$$

$$② \quad v(t) = V_m \cos(2\pi f t) V$$

$$\frac{dv(t)}{dt} = -2\pi f V_m \sin(2\pi f t) V/s$$

$$③ \quad q(t) = I_m \sin[2\pi f t] A$$

$$\frac{dq}{dt} = 2\pi f I_m \cos[2\pi f t] A/s$$

$$④ \quad v(t) = V_m \cos(\omega t) V ; V_m = ? , f = 60 \text{ Hz} , v(2ms) = 100V$$

$$\omega = \frac{\omega}{2\pi} = 60 \text{ Hz}$$

$$\omega = 120\pi \text{ rad/s}$$

$$V_m = \frac{v(t)}{\cos \omega t} = \frac{100V}{\cos(120\pi \text{ rad/s} \cdot 2ms)} = 137.2V$$

$$⑤ \quad 60 - j30$$

$$a.) \quad r = \sqrt{60^2 + 30^2} = \sqrt{4500} = 10\sqrt{45}$$

$$\theta = 360^\circ - \tan^{-1}\left(\frac{30}{60}\right) = 333.4^\circ$$

$$z = 10\sqrt{45} \angle 333.4^\circ$$

$$b.) \quad 24 + j15$$

$$r = \sqrt{24^2 + 15^2} = \sqrt{801}$$

$$\theta = \tan^{-1}\left(\frac{15}{24}\right) = 32.01^\circ$$

$$z = \sqrt{801} \angle 32.01^\circ$$



(6.)  $a = r \cos \theta$   
 $b = r \sin \theta$

a.)  $120 \angle 32^\circ$

$$a = 120 \cos 32^\circ = 101.77$$

$$b = 120 \sin 32^\circ = 63.59$$

$$z = 101.77 + j63.59$$

b.)  $100 \angle 0.5\pi$

$$a = 100 \cos \frac{\pi}{2} = 0$$

$$b = 100 \sin \frac{\pi}{2} = 100$$

$$z = j100$$

(7.)  $\frac{3+j6}{3-j2} \cdot \frac{3+j2}{3+j2} = \frac{9+j18 + j6 + 12(-1)}{9 - (j2)^2}$


$$= -\frac{3+j24}{13} = -\frac{3}{13} + \frac{j24}{13}$$

## 9.3 Phasors

Phasor: complex number that represents amplitude and phase of a sinusoid

Imaginary numbers!
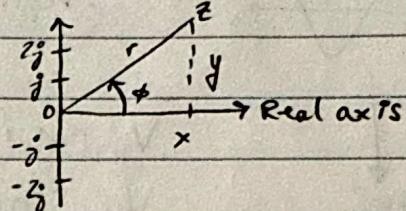
$$Z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$



Operations:

$$\text{addition: } Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\text{subtraction: } Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$\text{Mult: } Z_1 Z_2 = r_1 r_2 / \phi_1 + \phi_2$$

$$\text{Div: } \frac{Z_1}{Z_2} = \frac{r_1}{r_2} / \phi_1 - \phi_2$$

$$\text{Reciprocal: } \frac{1}{Z} = \frac{1}{r} / -\phi$$

$$\text{Square root: } \sqrt{Z} = \sqrt{r} / \phi/2$$

$$\text{Complex Conjugate: } Z^* = x - jy = r / -\phi = r e^{-j\phi}$$

$\hookrightarrow j^* = -j$

Euler's identity for phasor representation

$$e^{j\phi} = \cos \phi + j \sin \phi \quad \leftarrow \text{Proof in appendix B}$$

$$\cos \phi = \text{Re}(e^{j\phi}) \quad \rightarrow \text{"real" part of}$$


$$\sin \phi = \text{Im}(e^{j\phi}) \quad \rightarrow \text{"imaginary" part of}$$

$$\text{given } v(t) = V_m \cos(\omega t + \phi)$$

$$v(t) = \text{Re}(V e^{j\omega t}), \text{ where } V = V_m e^{j\phi} = V_m \angle \phi$$

$V$  is the phasor representation of the sinusoid  $v(t)$ . It's a complex representation of the magnitude and phase of a sinusoid.

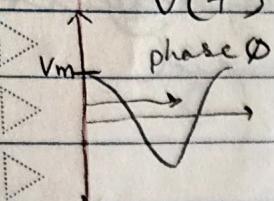- Mathematical equivalent of a sinusoid with the time dependence dropped.



Sinusoid

$$v(t) = V_m \cos(\omega t - \phi)$$

Time-domain representation

vector  
↓  
amplitude  
angle added  
phaser-domain  
representation

$$V_m |\phi|$$

$$V_m |\phi - 90^\circ|$$

$$I_m |\phi|$$

$$I_m |\phi - 90^\circ|$$

$$\begin{aligned} & V_m \cos(\omega t + \phi) \\ & V_m \sin(\omega t + \phi) \\ & I_m \cos(\omega t + \phi) \\ & I_m \sin(\omega t + \phi) \end{aligned}$$



Differentiating a sinusoid is equivalent to multiplying its corresponding phasor by  $j\omega$


$$\frac{dv}{dt} \leftrightarrow j\omega v$$

Integrating a sinusoid is the same as dividing its phasor by  $j\omega$

$$\int v dt \leftrightarrow \frac{v}{j\omega}$$

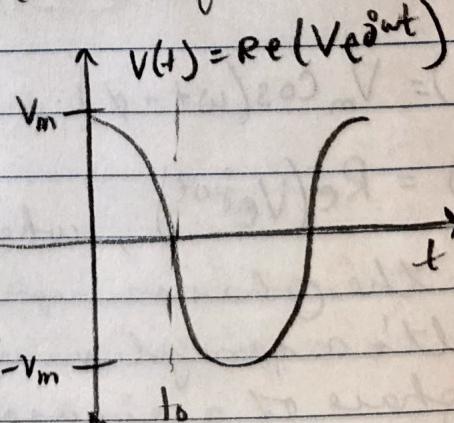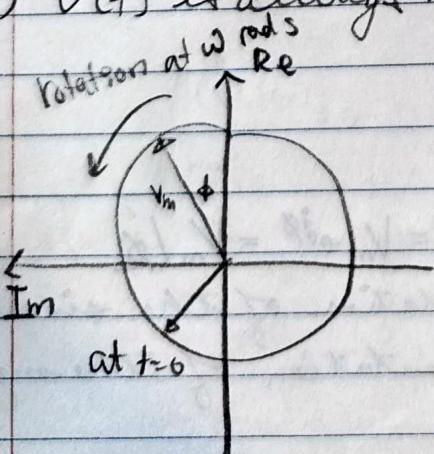- 1.)  $v(t)$  is instantaneous or time domain representation, while  $V$  is frequency or phasor domain representation
- 2.)  $v(t)$  is time dependent, while  $V$  is not
- 3.)  $v(t)$  is always real (no complex) while  $V$  is



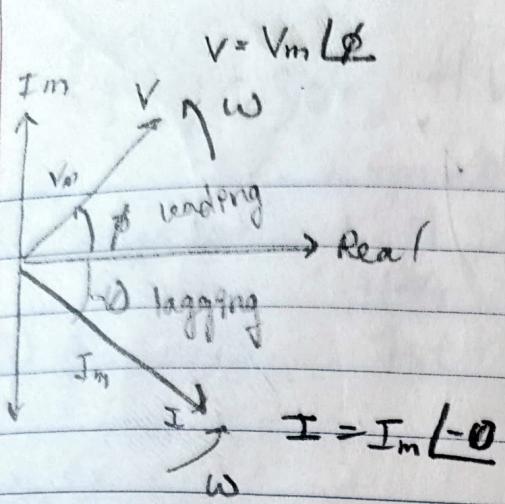

starts at 0 and goes w

$$\text{ex: } P = 6 \cos(50t - 40^\circ) A$$

$$I = 6 L -40^\circ A$$

$$V = -4 \sin(30t + 50^\circ) V$$

$$-\sin A = \cos(A + 90^\circ)$$

$$= 4 \cos(30t + 140^\circ) V$$

$$V = 4 L 140^\circ V$$

$$\text{ex: } V(t) = V_1(t) + V_2(t)$$

$$V_1(t) = 10 \cos(\omega t - 25^\circ) V$$

$$V_2(t) = 4 \sin(\omega t + 35^\circ)$$

$$10 L -25 + 4 L -55$$

$$V_1 = 10 \cos(-25) - j 10 \sin(-25) \\ = 9.06 - j 4.23$$

$$V_2 = 4 \cos(-55) - j 4 \sin(-55) \\ = 2.29 - j 3.28$$

$$V_1 + V_2 = 11.35 - j 7.51$$

$$V = 13.6 L -33.5^\circ V$$

# Phasor HW

Seth Ricks

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} \left( \frac{b}{a} \right)$$

① Regular  
Polar

$\theta = \tan^{-1} \left( \frac{b}{a} \right)$

Quadrant

original	$j(1+j)$	$j^2(1+j)$	$j^3(1+j)$	$j^4(1+j)$
$1+j$	$-1+j$	$-1-j$	$1-j$	$1+j$
$1 \angle \frac{\pi}{4}$	$1 \angle \frac{3\pi}{4}$	$1 \angle \frac{7\pi}{4}$	$1 \angle \frac{11\pi}{4}$	$1 \angle \frac{5\pi}{4}$
1st	2nd	3rd	4th	1st

②

a.)  $v(+)=12 \sin(\omega t + 45^\circ) V$

$$V = 12 \angle 45^\circ - 90^\circ = 12 \angle -45^\circ$$

b.)  $v(+)=9 \sin(\omega t - \frac{\pi}{3}) V$

$$V = 9 \angle -\frac{\pi}{3} - \frac{\pi}{2} = 9 \angle -60^\circ - 90^\circ = 9 \angle -150^\circ$$

c.)  $i(+)=i_1(+)+i_2(+)$

where  $i_1(+)=4 \sin(\omega t + \frac{\pi}{3})$  and  $i_2(+)=3 \cos(\omega t - \frac{\pi}{6}) A$

$$I_1 = 4 \angle \frac{\pi}{3} - \frac{\pi}{2} = 4 \angle -\frac{\pi}{6} = 4 \angle -30^\circ$$

$$I_2 = 3 \angle \frac{\pi}{6} = 3 \angle -30^\circ$$


$$I_1 = 3.46 - j2 \quad I_2 = 2.60 - j1.5$$

$$I_1 + I_2 = 6.06 - j3.5$$

$$= 7 \angle -30^\circ$$
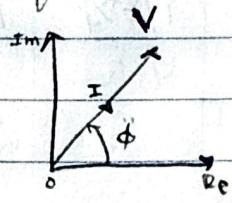
## 9.4 Phasor relationships for circuit elements



- If current through resistor  $R$  is  $i = I_m \cos(\omega t + \phi)$



$$V = IR = R I_m \cos(\omega t + \phi)$$


$$V = R I_m \angle \phi$$

$$V = RI$$

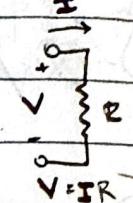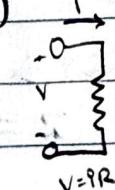

$$V = IR$$

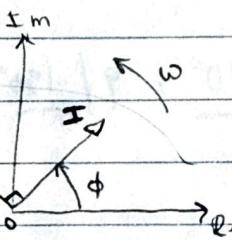- For the inductor  $L$ , assume current  $i = I_m \cos(\omega t + \phi)$




$$V = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

$$= \omega L I_m \cos(\omega t + \phi + 90^\circ)$$


$$= \omega L I_m \angle \phi + 90^\circ$$

$$V = j\omega L I$$

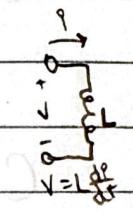


$$V = j\omega L I$$

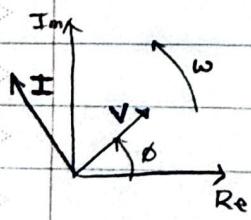- For the capacitor  $C$ , assume voltage  $v = V_m \cos(\omega t + \phi)$



$$i = C \frac{dv}{dt}$$
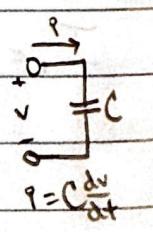
$$I = j\omega CV \rightarrow V = \frac{I}{j\omega C}$$



$$V = \frac{I}{j\omega C}$$

### Element

$R$

$L$

$C$

### Time Domain

$$V = RI$$

$$V = L \frac{di}{dt}$$

$$i = C \frac{dv}{dt}$$

### Frequency Domain

$$V = RI$$

$$V = j\omega L I$$

$$V = \frac{I}{j\omega C}$$

## 9.5 Impedance and Admittance

$$V = RI \quad V = j\omega L I \quad V = \frac{I}{j\omega C}$$

can be written as

$$\underline{\underline{Z}} = R \quad \underline{\underline{Z}} = j\omega L \quad \underline{\underline{Z}} = \frac{1}{j\omega C}$$

So, Ohm's law in phasor form for any element

$$Z = \underline{\underline{Z}} \quad \text{or} \quad V = Z I$$

$Z$  is a frequency-dependent quantity  $\rightarrow$  impedance  
 measured in ohms.

$$Z = R + jX = |Z| \angle \theta, \text{ where } |Z| = \sqrt{R^2 + X^2}, \theta = \tan^{-1}\left(\frac{X}{R}\right)$$

$$R = |Z| \cos \theta, \quad X = |Z| \sin \theta$$

Reciprocal of impedance  $\rightarrow$  admittance, siemens (S) or mhos

$$Y = \frac{1}{Z} = \frac{I}{V}$$

$$Y = (G + jB) \rightarrow \text{susceptance}$$

Conductance

$$G + jB = \frac{1}{R + jX}$$

$$\text{and} \quad G = \frac{R}{R^2 + X^2} \quad \text{and} \quad B = \frac{X}{R^2 + X^2}$$

Impedance and admittance of Passive elements


Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = \frac{1}{j\omega C}$

Always  $\underline{\underline{Z}}$   $|_{90^\circ}$



$\rightarrow$  Short at DC  
 $\omega = 0$

Always  $\underline{\underline{Z}}$   $|_{-90^\circ}$

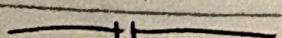

$\rightarrow$  Open at high frequencies  
 $\omega = \infty$


Without  $j \rightarrow$  reactance

Reactance is mag of impedance

$\rightarrow$  Open at DC  
 $\omega = 0$

$\rightarrow$  Short at high frequencies  
 $\omega = \infty$

ex:

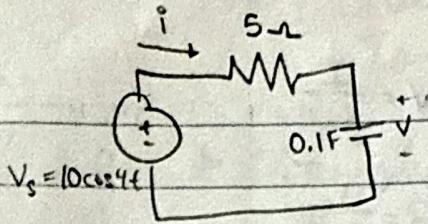

$$V_s = 10 / 0^\circ \text{ V}$$

$$Z = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \Omega$$


$$V = I Z_c = \frac{I}{j\omega C} = \frac{1.789 / 26.57^\circ}{j4 \times 0.1} \\ = \frac{1.789 / 26.57^\circ}{0.4 / 90^\circ} = 4.47 / -63.43^\circ \text{ V}$$

$$I = \frac{V_s}{Z} = \frac{10 / 0^\circ}{5 - j2.5} = \frac{10(5 + j2.5)}{5^2 + 2.5^2} \\ = 1.6 + j0.8 = 1.789 / 26.57^\circ \text{ A}$$

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

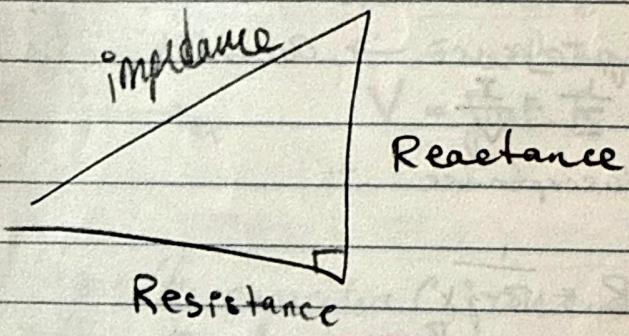(notice  $i(t)$  leads  $v(t)$  by  $90^\circ$ , as expected)



# Impedance HW

① Reactance  $X_C$  of a  $2.7 \mu F$  capacitor at frequency  $150\text{Hz}$ .

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 150 \cdot 2.7 \times 10^{-6}} = 392.98 \Omega$$

② Capacitance of Capacitor w/  $200\Omega$  reactance at  $20\text{kHz}$

$$X_C = \frac{1}{\omega C} \quad C = \frac{1}{\omega X_C} = \frac{1}{2\pi \cdot 20 \times 10^3 \cdot 200} = 39.79 \text{ nF}$$

③ Frequency at which  $0.1 \mu F$  capacitor has a reactance  $100\Omega$

$$X_C = \frac{1}{2\pi f C} \quad f = \frac{1}{2\pi \cdot C \cdot X_C} = \frac{1}{2\pi \cdot 100\Omega \cdot 0.1 \times 10^{-6} \text{ F}} = 15.92 \text{ kHz}$$

④ Reactance  $X_L$  of  $270 \mu H$  inductor at frequency of  $1\text{MHz}$


$$X_L = \omega L = 2\pi \cdot 10^6 \text{ Hz} \cdot 270 \times 10^{-6} \text{ H} = 1.697 \text{ k}\Omega$$

⑤ Inductance of an inductor that has a reactance  $250\Omega$  at  $20\text{kHz}$

$$X_L = \omega L \quad L = \frac{X_L}{2\pi f} = \frac{250\Omega}{2\pi \cdot 20 \times 10^3} = 1.99 \text{ mH}$$


⑥ Frequency at which a  $1.5 \text{ mH}$  inductor that has a reactance  $100\Omega$
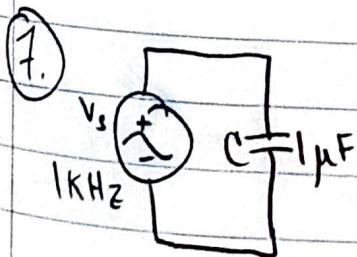
$$X_L = \omega L = 2\pi f L \quad f = \frac{X_L}{2\pi L} = \frac{100\Omega}{2\pi \cdot 1.5 \times 10^{-3}} = 10.61 \text{ kHz}$$



Impedance  $Z_C = ?$

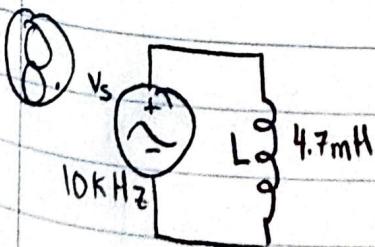
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2\pi f C} = -j \cdot \frac{1}{2\pi \cdot 10^3 \text{ Hz} \cdot 10^{-6} \text{ F}} = -j159.15 \Omega$$



Impedance  $Z_L = ?$

$$Z_L = j\omega L = j2\pi f L = j2\pi \cdot 10^4 \text{ Hz} \cdot 4.7 \times 10^{-3} \text{ H} = j295.31 \Omega$$

(9.)

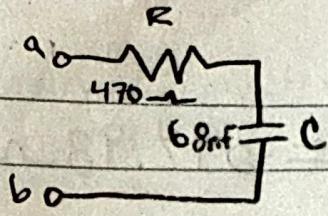

impedance = ? frequency = 5 kHz

$$\begin{aligned} Z &= R + \frac{1}{j\omega C} = 470 - \frac{1}{j2\pi f C} \\ &= 470 + \frac{1}{j2\pi \cdot 5 \cdot 10^3 \cdot 68 \cdot 10^{-9}} \\ &= 470 - j468.10 \end{aligned}$$

$$|Z| = \sqrt{R^2 + X^2} = \sqrt{470^2 - 468.10^2} \\ = 663 \Omega$$

$$\theta = \tan^{-1}\left(\frac{-468.10}{470}\right) = -44.88^\circ$$

$$Z = 663 \angle -44.88^\circ$$

## 9.6 Kirchhoff's Laws in the Frequency Domain


$$\text{KVL: } V_1 + V_2 + \dots + V_n = 0$$

translate to  $V_1 + V_2 + \dots + V_n = 0$

$$\text{KCL: } i_1 + i_2 + \dots + i_n = 0$$

translate to  $I_1 + I_2 + \dots + I_n = 0$


## 9.7 Impedance Combinations

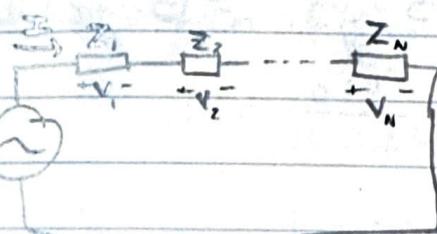

$$\text{KVL: } V = V_1 + V_2 + \dots + V_N = I(Z_1 + Z_2 + \dots + Z_N)$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N$$


If  $N=2$ ,

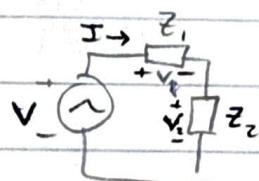

(Voltage division)


$$V_1 = \frac{z_1}{z_1 + z_2} V, \quad V_2 = \frac{z_2}{z_1 + z_2} V$$

If in //:

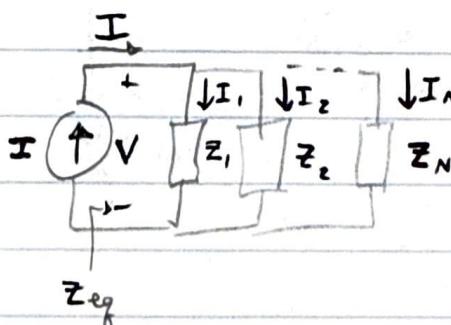

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

If  $N=2$ ,

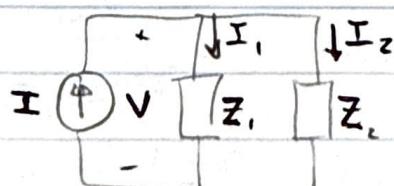


(current division)

$$I_1 = \frac{z_2}{z_1 + z_2} I, \quad I_2 = \frac{z_1}{z_1 + z_2} I$$

$$Y_{eq} = X \angle 0^\circ$$

$$\frac{1}{Y_{eq}} = \frac{1 \angle 0^\circ}{X \angle 0^\circ} = \frac{1}{X} \angle 0 - 0^\circ$$

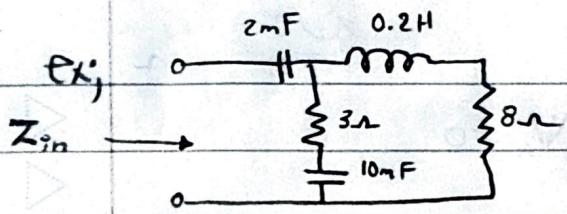Find input impedance. Assume circuit  
operates w/  $\omega = 50 \text{ rad/s}$



$Z_1$  = Impedance of  $2\text{-mF cap.}$

$Z_2$  = Impedance of  $3\text{-}\Omega$  resistor  
w/  $10\text{mF-cap}$

$Z_3$  = Impedance of the  $0.2 \text{ H}$   
inductor in series with  $8\text{-}\Omega$  resis.

$$Z_1 = \frac{1}{j\omega C} = -j10\Omega ; \quad Z_2 = 3 + \frac{1}{j\omega C} = (3-j2)\Omega$$


$$Z_3 = 8 + j\omega L = (8 + j10)\Omega$$

$$Z_{in} = Z_1 + Z_2 // Z_3 = -j10 + \frac{(3-j2)(8+j10)}{11+j8} = 3.22 - j11.07\Omega$$

# Impedance HW 2

Seth  
Ricks

①

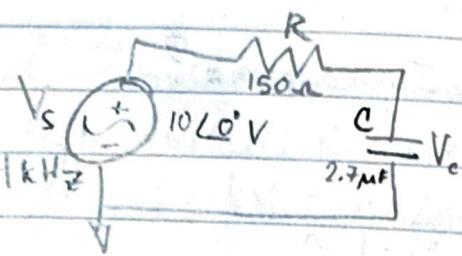

$$I = \frac{V_s}{Z_{eq}}$$

$$\omega = 1 \text{ kHz}$$

$$Z_{eq} = 150 + -j \cdot \frac{1}{\omega C} = 150 - j \cdot 2\pi(10^3) \cdot 2.7 \cdot 10^{-6}$$

$$= 150 - j 58.946 \Omega$$

$$|Z| = \sqrt{150^2 + (58.946)^2} = 161.166 \Omega$$


$$\theta = \tan^{-1}\left(-\frac{58.946}{150}\right) = -21.45^\circ$$

$$I = \frac{10 L 0^\circ}{161.166 L -21.45^\circ} = 62 \text{ mA } [21.45^\circ]$$

$$V_c = I Z_c = \frac{I}{j\omega C} = \frac{62 \text{ mA } [21.45^\circ]}{j(2\pi)(10^3 \text{ Hz})(2.7 \times 10^{-6} \text{ F})} = \frac{62 \text{ mA } [21.45^\circ]}{j 0.01696}$$

$$V_c = \frac{62 \text{ mA } [21.45^\circ]}{0.01696 / -90^\circ} = 3.669 / 111.45^\circ$$

②

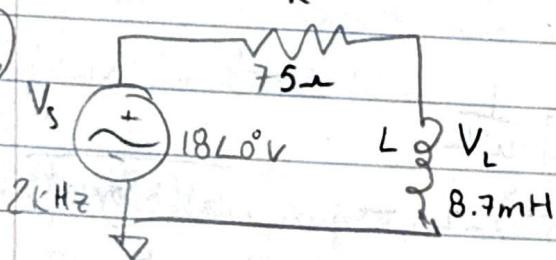

$$Z_{eq} = 75 + j\omega L$$

$$= 75 + j(2\pi)(2 \times 10^3)(8.7 \times 10^{-3})$$

$$= 75 + j 109.327$$


$$|Z| = \sqrt{75^2 + (109.327)^2} = 132.58$$

$$\theta = \tan^{-1}\left(\frac{109.327}{75}\right) = 55.55^\circ$$

$$I = \frac{V_s}{Z_{eq}} = \frac{18 L 0^\circ}{132.58 / 55.55^\circ} = 135.77 \text{ mA } [-55.55^\circ]$$

$$V_L = I Z = 135.77 \text{ mA } [-55.55^\circ] \cdot 109.327 / 90^\circ = 14.84 / 34.45^\circ \checkmark$$

(3.)

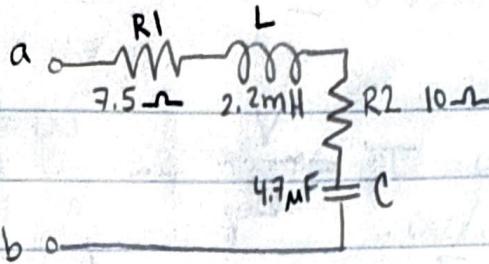

$$f = 1 \text{ kHz}$$

Impedance = ?


$$\begin{aligned} Z_{eq} &= 7.5 \Omega + 10 \Omega + -j \frac{1}{\omega C} + j \omega L \\ &= 17.5 - j \frac{1}{(2\pi)(10^3)(4.7 \times 10^{-6})} + j (2\pi)(10^3)(2.2 \times 10^{-3}) \\ &= 17.5 - j 33.863 + j 13.823 = 17.5 - j 20.040 \end{aligned}$$

$$|Z| = \sqrt{17.5^2 + (-20.040)^2} = 26.605$$

$$\theta = \tan^{-1} \left( \frac{-20.040}{17.5} \right) = -48.871^\circ$$

$$Z_{eq} = 26.605 \angle -48.871^\circ \Omega$$

(4.)

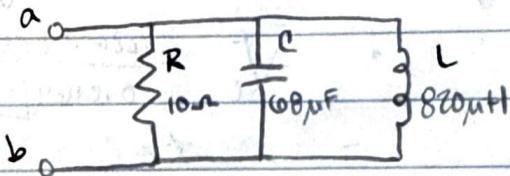

$$f = 1 \text{ kHz}$$

Admittance = ?

$$Y_{eq} = \frac{1}{10 \Omega} + j \omega C \Omega + -j \frac{1}{\omega L}$$

$$= \frac{1}{10 \Omega} + j (2\pi)(10^3)(168 \times 10^{-6}) \Omega - j \frac{1}{(2\pi)(10^3)(820 \times 10^{-6})} \Omega$$

$$= 0.1 + j 0.427 \Omega - j 0.194 \Omega$$

$$= 0.1 + j 0.233 \Omega$$

$$|Y| = \sqrt{0.1^2 + 0.233^2} = 0.253 \text{ Siemens}$$

$$\theta = \tan^{-1} \left( \frac{0.233}{0.1} \right) = 66.772^\circ$$


$$Y_{eq} = 0.253 \angle 66.772^\circ \text{ S}$$

## 11.1 / 11.2 Instantaneous and Average Power

Instantaneous Power - Power at any instant in time

$$P(t) = V(t) I(t); V(t) = V_m \cos(\omega t + \phi_v); I(t) = I_m \cos(\omega t + \phi_i)$$
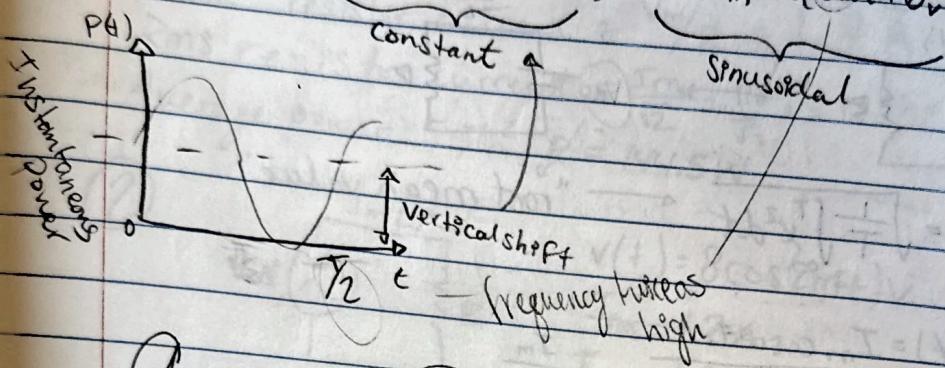
$$P(t) = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \phi_v + \phi_i)$$



Average Power:  $P = \frac{1}{2} \operatorname{Re}[V I^*] = \frac{1}{2} V_m I_m \cos(\phi_v - \phi_i)$

Resistive load - Absorbs power at all times ( $\phi_r = 0^\circ$ )

Reactive load ( $L$  or  $C$ ) - Absorbs zero average power ( $\phi_r - \phi_i = \pm 90^\circ$ )

Ex: Calc average power absorbed by an impedance  $Z = 30 - j70 \Omega$  when  $V = 120/0^\circ$  applied across it.

$$I = \frac{V}{Z} = \frac{120/0^\circ}{30 - j70} = \frac{120/0^\circ}{76.16 \angle -66.8^\circ} = 1.576 \angle 66.8^\circ A$$

$$P = \frac{1}{2} V_m I_m \cos(\phi_r - \phi_i) = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ) = 37.24 W$$

Resistor Power dissipated:


$$\frac{1}{2} V_m I_m$$

Capacitor / Inductor

$$0$$
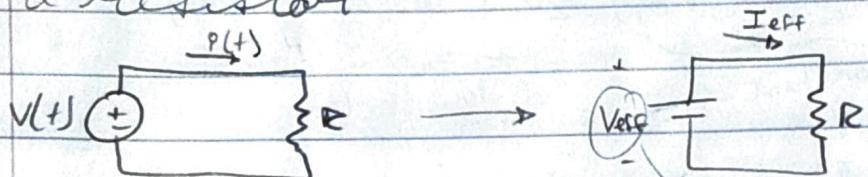
## 11.4 Effective or RMS value

Effective value of a periodic current is the dc current that delivers the same average power to a resistor



$$X_{\text{eff}} = X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

"root mean value"

For  $i(t) = I_m \cos \omega t$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt} = \frac{I_m}{\sqrt{2}}$$

$$V_m \cos \omega t : V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_p) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_p) = V_{\text{rms}} V_{\text{rms}} \cos(\theta_v - \theta_p)$$

$$\text{Arg.-Power by resistor: } P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$

RMS is NOT Average Voltage or Current.

It is used to find average power!

# AC Power HW

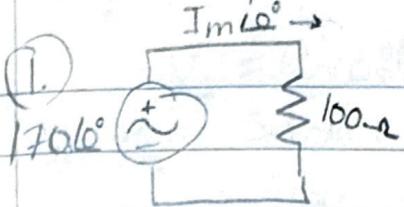


$$f = 120 \text{ Hz} \quad \text{Peak Voltage} = 170 \text{ V}$$

$$\text{average resistor current} = 0$$

$$\text{Peak resistor current} = \frac{V_m}{R} = 1.7 \text{ A}$$

$$\text{Rms resistor current} = \frac{I_m}{\sqrt{2}} = \frac{1.7}{\sqrt{2}} \text{ A} = 1.202 \text{ A}$$
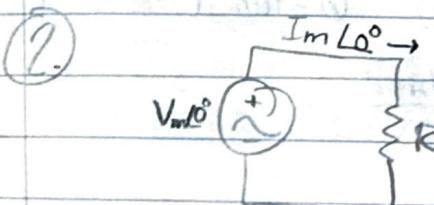
$$\text{Average power} = I_{\text{rms}}^2 R = 144.5 \text{ W}$$




$$v(t) = 8 \cos(2\pi ft) \text{ V}$$

$$I_{\text{rms}} = 1.2 \text{ A}$$

$$I_m = 1.2 \cdot \sqrt{2} \text{ A} = 1.697 \text{ A}$$

$$R = \frac{V_m}{I_m} = \frac{8}{1.697} \Omega = 4.714 \Omega$$

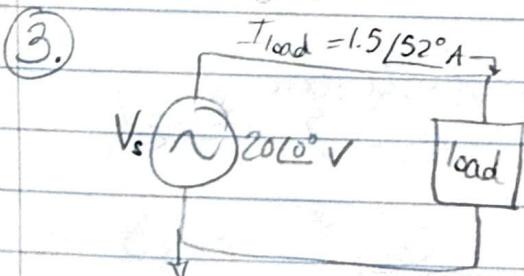
$$P_{\text{avg}} = I_{\text{rms}}^2 R = (1.2)^2 (4.714) = 6.788 \text{ W}$$



$$Z_{\text{load}} = \frac{20 60^\circ}{1.5 52^\circ} = 13.33 52^\circ \Omega$$

$$I_{\text{rms}} = \frac{1.5}{\sqrt{2}}$$
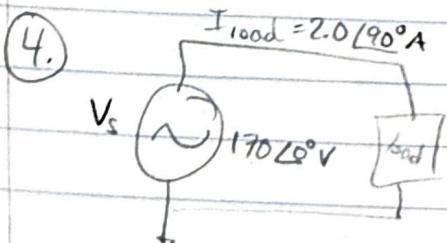
$$P_{\text{avg}} = I_{\text{rms}}^2 R = \left(\frac{1.5}{\sqrt{2}}\right)^2 (13.33) \cos(-52^\circ) \\ = 9.235 \text{ W}$$




$$Z_{\text{load}} = \frac{170 60^\circ}{2.0 90^\circ} = 85 90^\circ \Omega$$

$$I_{\text{rms}} = \frac{2.0}{\sqrt{2}}$$

$$P_{\text{avg}} = I_{\text{rms}}^2 R (\cos(-90^\circ)) = 0 \text{ W}$$

(5)

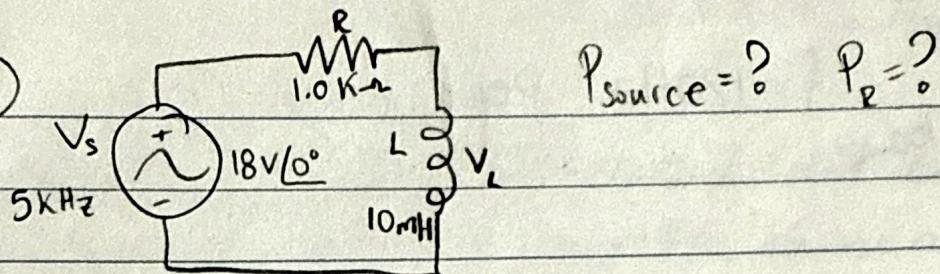

$$P_{\text{source}} = ? \quad P_R = ?$$

$$P_{\text{source}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$Z_{\text{eq}} = Z_R + Z_L = 1.0 \text{ k}\Omega + j(2\pi)(5 \times 10^3)(10 \times 10^{-3}) = 100 + j100\pi \text{ }\Omega$$

$$|Z_{\text{eq}}| = \sqrt{100^2 + (100\pi)^2} = 1048.187 \text{ }\Omega \quad \theta = \tan^{-1}\left(\frac{100\pi}{100}\right) = 17.441^\circ$$

$$I = \frac{V_o}{R} = \frac{18 / 0^\circ}{1048.187 / 17.441^\circ} = 0.0172 \angle 17.441^\circ$$

$$P_{\text{source}} = \frac{1}{2} (18)(0.0172) \cos(0 + 17.441^\circ) = 0.1477 \text{ W}$$

$$P_R = I_{\text{ms}}^2 R \cos(\theta_v - \theta_i) = \frac{(0.0172)^2}{\sqrt{2}} \cos(17.441^\circ) = 141 \mu\text{W}$$

$$= 0.1477 \text{ W}$$

Question: Difference between these two?

lab

$$V_s = 10 \angle 0^\circ V$$

$$\begin{aligned} Z_{eq} &= 5.1 \times 10^3 \Omega - j(2\pi 300)(0.1 \times 10^{-6}) \\ &= 5100 - j5305.16 \Omega \end{aligned}$$

$$|Z| = \sqrt{5100^2 + 5305.16^2} = 7359 \Omega$$

$$\theta = \tan^{-1}\left(\frac{-5305.16}{5100}\right) = -46.13^\circ$$

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ V}{7359 \angle -46.13^\circ \Omega} = 1.36 \text{ mA} \angle +46.13^\circ$$

$$\begin{aligned} Z_c &= -j5305.16 \Omega \\ &= 5305.16 \angle -90^\circ \Omega \end{aligned}$$

$$\begin{aligned} 1.36 \text{ mA} \angle +46.13^\circ &\star 5305.16 \angle -90^\circ \Omega \\ &= 7.21 \angle -43.87^\circ \end{aligned}$$

$$V_s = X \angle 0^\circ V$$

$$\frac{V_s}{Z_c} = \frac{X \angle 0^\circ V}{Y \angle 0^\circ} \quad 0 - 0 = 0$$

$$Z_L = Y \angle 0^\circ \Omega$$


$$I = -0^\circ$$

jxxv
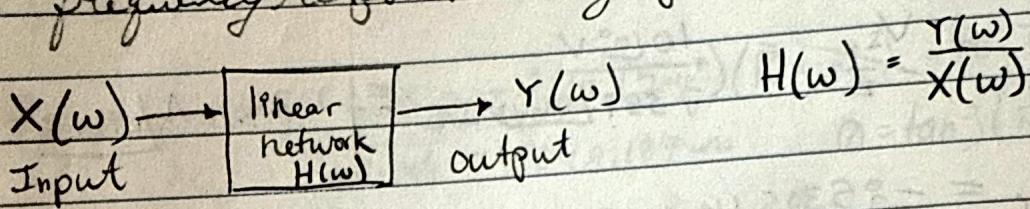
# 14.1 / 14.2 Transfer Function

Frequency response - the variation in a circuit's behavior with change in signal frequency

Transfer function  $H(\omega) \rightarrow$  (network function)  
Frequency response  $\rightarrow$  graph  $H(\omega)$  vs  $\omega$



$H(\omega) = \text{Voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$   $H(\omega) = \text{Transfer Impedance} = \frac{V_o(\omega)}{I_i(\omega)}$

$H(\omega) = \text{Current gain} = \frac{I_o(\omega)}{I_i(\omega)}$   $H(\omega) = \text{Transfer Admittance} = \frac{I_o(\omega)}{V_i(\omega)}$



$H(\omega) = H(\omega)/\phi$

$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$

↑ num. polynomial  
↓ denom. polynomial

A zero is a root of num. poly, and results in zero value of the function. A pole as a root of the denom. poly, is a value for which the function is infinite.

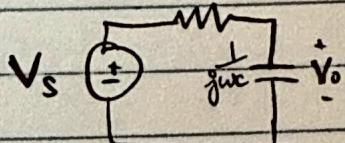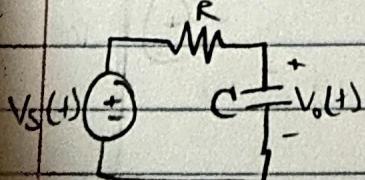ex; obtain  $V_o/V_s$  and frequency response. Let  $V_s = V_m \cos \omega t$



$$H(\omega) = \frac{V_o}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$H = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

$$\theta = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

## 14.3 The Decibel Scale

$$G = \text{Number of bels} = \log_{10} \frac{P_2}{P_1}$$

"Gain"  
has no units

$$\text{1/10th of a bel} \rightarrow G_{dB} = 10 \log_{10} \frac{P_2}{P_1} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{Used for Power}$$

$$\text{If } P_2 = 2P_1 \rightarrow G_{dB} = 10 \log_{10} 2 \approx 3 \text{ dB}$$

$$G_{dB} = 20 \log_{10} \frac{V_2}{V_1}, \quad G_{dB} = 20 \log_{10} \frac{I_2}{I_1} \quad * \text{ for } R_{out} = R_{in}$$

used for voltage / current

$$* R_{out} + R_{in}: A_{v dB} = 20 \log_{10} \left( \frac{R_{in}}{R_{out}} \right) - 10 \log_{10} \left( \frac{R_{in}}{R_{out}} \right)$$

## 14.4 Bode Plots:

Bode plots - semilog plot of the magnitude (in decibels) and phase (in degrees) of a transfer function versus frequency.

$$H = H/\phi = H e^{j\theta}$$

$$\ln H = \ln H + \ln e^{j\theta} = \ln H + j\theta$$

$$H_{dB} = 20 \log_{10} H$$

# Transfer Function HW

①

$$30\text{mW} \rightarrow 10\text{W}$$

$$G_{\text{dB}} = 10 \log_{10} \left( \frac{10}{30 \times 10^{-3}} \right) = 25 \text{ dB}$$

②

$$10\mu\text{V} \rightarrow 10\text{mV}$$

$$G_{\text{dB}} = 20 \log_{10} \left( \frac{10 \times 10^{-3}}{10 \times 10^{-6}} \right) = 60 \text{ dB}$$

③

$$1\text{V } 1\text{MHz} \rightarrow 1\text{mV } 1\text{MHz}$$

$$G_{\text{dB}} = 20 \log_{10} \left( \frac{10 \times 10^{-3}}{1} \right) = -40 \text{ dB}$$

④ Determine peak sinusoidal voltage

$$V_{\text{im}} \rightarrow [40 \text{ dB}] \rightarrow V_{\text{om}} = 1\text{V}$$

$$G_{\text{dB}} = 20 \log_{10} \left( \frac{1\text{V}}{V_{\text{im}}} \right)$$

$$10 \frac{G_{\text{dB}}}{20} = \frac{1}{V_{\text{im}}} \rightarrow V_{\text{im}} = 10^{-\frac{G_{\text{dB}}}{20}} = 10\text{mV}$$

⑤ Determine peak output voltage

$$V_{\text{im}} \rightarrow [42 \text{ dB}] \rightarrow [38 \text{ dB}] \rightarrow V_{\text{om}}$$


$$G_{\text{dB}} = 20 \log_{10} \left( \frac{V_{\text{out}}}{1\text{e-3}} \right)$$

$$V_{\text{out}} = 10^{\frac{G_{\text{dB}}}{20}} \cdot 1\text{e-3}$$

$$V_{\text{om}} = 10^{\frac{G_{\text{dB}}}{20}} \cdot 0.1259\text{V}$$

$$= \underline{\underline{10\text{V}}}$$

⑥ Determine voltage gain

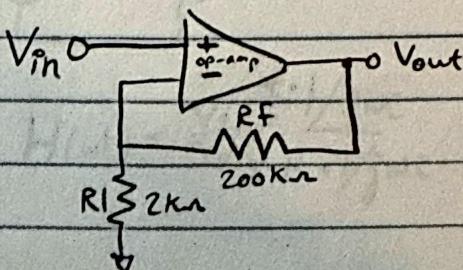

$$A = \left( 1 + \frac{R_F}{R_1} \right)$$



$$G_{\text{dB}} = 20 \log_{10} \left( 1 + \frac{R_F}{R_1} \right)$$

$$= 40.086 \text{ dB}$$

\* Gain if input is 120Hz 1V, output 120Hz 3mV

$$A_{v_{dB}} = 20 \log_{10} \left( \frac{3mV}{V} \right) = -50.5 \text{ dB}$$

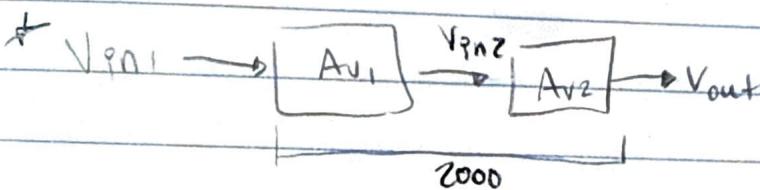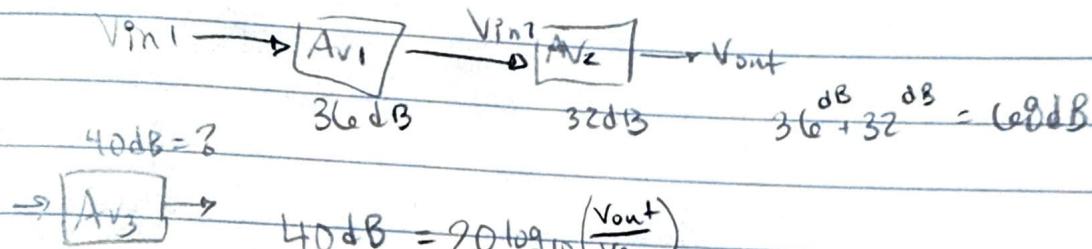$\text{dB} < 0 \rightarrow \text{attenuation}$



$$A_{v_{total}} = 20 \log_{10} (2000) = 46.0 \text{ dB}$$

$$-25 \text{ dB}$$

$$= A_{v2-dB} = 41 \text{ dB}$$

$$Av_2 = 10^{\frac{41}{20}} = 112$$