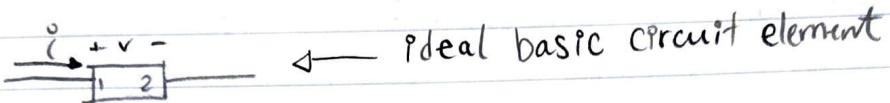


# \* It's Review time! \*

## 1.4 Voltage & Current

Voltage  $v = \frac{dw}{dq}$   $v = \text{voltage}$   $w = \text{energy in J}$   $q = \text{charge in coulombs}$

Current  $i = \frac{dq}{dt}$   $i = \text{current in amps}$   $q = \text{charge}$   $t = \text{time}$



ex: No charge at left terminal of element for  $t < 0$ . at  $t=0$ , 5A current begins to flow.





$$q(t) = \int_0^t i(x)dx = \int_0^t 5dx = 5x \Big|_0^t = 5t \text{ C for } t > 0$$

Total charge in 10 seconds  $\rightarrow 50 \text{ C}$
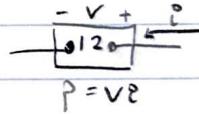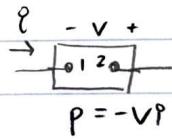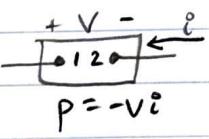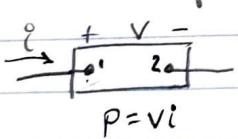
## 1.6 Power & Energy

Power  $P = \frac{dw}{dt}$   $P = \text{power in watts}$   $w = \text{energy in joules}$   
 $t = \text{time}$

$$P = \left(\frac{dw}{dq}\right) \left(\frac{dq}{dt}\right) = Vi$$



$P > 0 \rightarrow \text{element being charged}$

$P < 0 \rightarrow \text{power is extracted}$

2.2 Ohm's Law  $V = IR$

$$V = IR$$





$$V = -IR$$

Conductance  $\rightarrow G = \frac{1}{R}$


Power in terms of current for resistor  $\rightarrow P = I^2 R$   
 " " " " voltage " "  $\rightarrow P = \frac{V^2}{R} = V^2 G$

2.1 Voltage & Current source


Are the following valid?

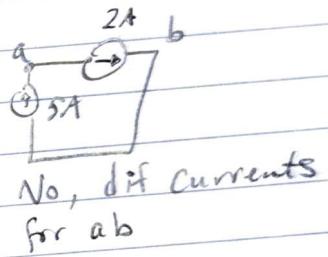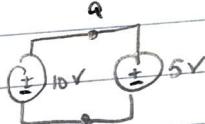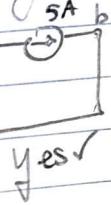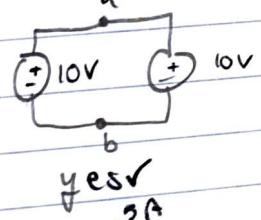

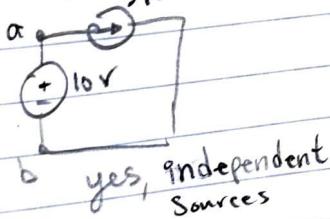(Same concept w/ combined dependent & independent sources.)



**1.8** There is no charge at the left terminal for  $t < 0$ . At  $t = 0$  a current of  $29e^{-1000t}$  mA enters left.

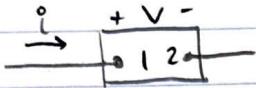**Part A**

$$q(t) = \int_0^t i(x) dx = \int_0^t 0.029 e^{-1000t} dt = 0.029 \int e^{-1000t} dt$$

$$u = -1000t$$

$$\frac{du}{dt} = -1000$$

$$dt = -\frac{du}{1000}$$

$$= 0.029 \int e^u \cdot -\frac{du}{1000} = -\frac{0.029}{1000} \int e^u du = \frac{-0.029}{1000} e^u$$

$$= -\frac{0.029}{1000} e^{-1000t}$$

$$* \quad \frac{0.029}{1000} = \frac{0.029}{1000} e^{-1000t} \mu C$$

$$= [q(t) = 29(1 - e^{-1000t}) \mu C]$$

**Part B**

$$\text{as } t \rightarrow \infty, q(t) \rightarrow [29 \mu C]$$

**Part C** If the current is stopped at  $t = 0.4$  ms, how much charge has accumulated at the left terminal.

$$\text{as } t \rightarrow 0.4 \text{ ms}, q(t) = 29(1 - e^{-1000(0.0004)}) = [9.56 \mu C]$$


$$^{\circ}A = -25^{\circ}$$

Seth Ricks

1.14

Part A

Which car has the dead battery?

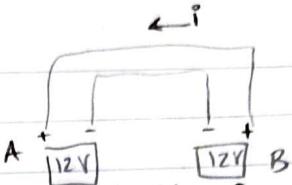

Car A

→ This is because the current is entering the positive terminal of A

Part B Assume  $i = 30A$

If the connection is maintained for 1 min, how much energy is transferred to the dead battery?


$$1 \text{ min} = 60 \text{ s} \quad P = \frac{dw}{dt}$$

$$\begin{aligned} P &= VI = 12V \cdot 30A = 360W = 360 \text{ J/s} \cdot 60\text{s} \\ &= 21600 \text{ J} \\ &= 21.6 \text{ kJ} \end{aligned}$$

Seth Ricks

Problem 2.4


Assume  $i = 13A$

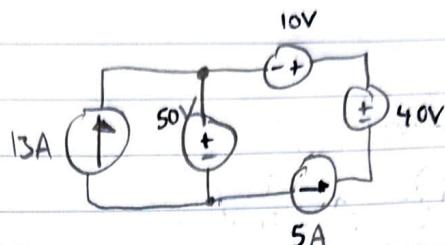

Part A Is the interconnection in ↑ valid?

Yes, the interconnection is valid. The independent power and current sources are properly aligned.

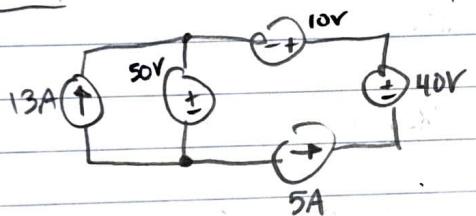
Part B Find the total power developed by the current sources.



$$50V \cdot 13A + 20 \cdot 5A = 750W$$

750 W

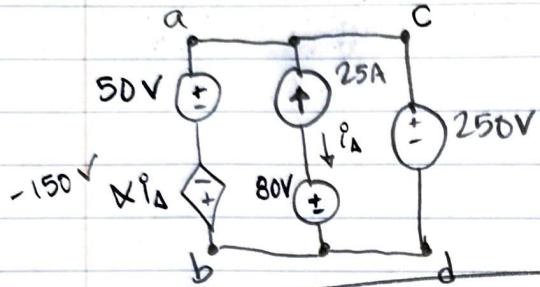Problem 2.8 Suppose that  $\propto = 6.0$





Part A Determine voltage drop from the top terminal to the bottom terminal,  $V_{ab}$ , in the left hand branch and,  $V_{cd}$  in the right hand branch of the circuit. Determine each voltage drop based on the elements in the corresponding branch and the middle branch.

$$i_A = -25 \text{ A} \quad \propto = 6.0 \quad \propto i_A = -150$$

$$V_{ab} = 200 \text{ V} , \quad V_{cd} = 250 \text{ V}$$

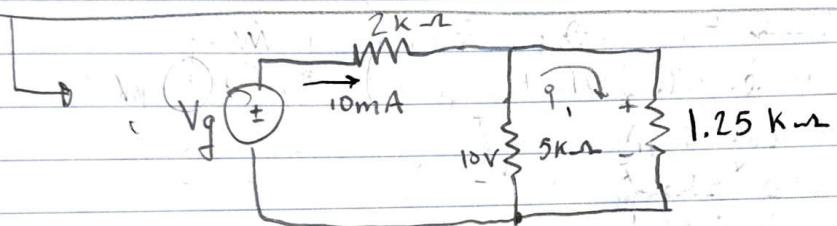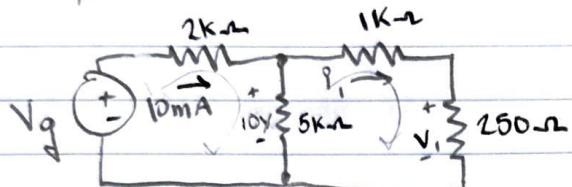**2.18** Part A Find  $i_1$

The current  $i_x$  in the circuit shown is 10 mA, and the voltage  $V_g$  is 10V



$$(1.25 \times 10^3) i_1 + (5 \times 10^3)(i_1 - i_x) = 0$$

$$(6.25 \times 10^3) i_1 - (5 \times 10^3)(10 \times 10^{-3}) = 0$$

$$i_1 = \frac{50}{6.25 \times 10^3} = 8 \text{ mA} = 8.00 \text{ mA}$$

**Part B** Find  $V_1$

$$V_1 = i_1 R_1 = 8.00 \text{ mA} \cdot 250 \Omega = 8 \times 10^3 \cdot 250 = 2 \text{ V}$$

$$= 2.00 \text{ V}$$

**Part C** Find  $V_g$

$$-V_g + (2 \times 10^3)(10 \times 10^{-3}) + 10V = 0$$

$$-V_g + 20 + 10 = 0$$


$$V_g = 30.0 \text{ V}$$

**Part D** Find the magnitude of the power supplied by the voltage source

$$P = Vi = (30.0 \text{ V})(10 \times 10^{-3} \text{ A}) = 0.3 \text{ W}$$

### Problem 2.32

Suppose that  $V_g = 280V$

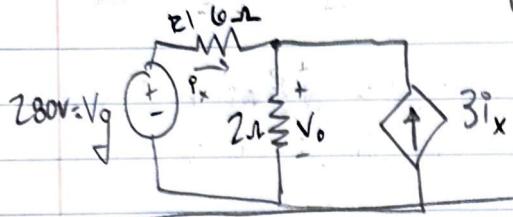

### Part A

Find  $V_o$

$$V_o = i_x \cdot R_o = (4i_x)(2\Omega) = 8i_x \text{ V}$$

$$V_{R1} = i_x \cdot 6\Omega = 6i_x \text{ V}$$

$$280V = (6i_x + 8i_x) \text{ V} = 14i_x \text{ V} = 20 = i_x$$

$$\boxed{V_o = 160V}$$

### Part B


Find the magnitude of the total power supplied  
in the circuit.

$$P_{vg} = V_i = 280V \cdot 20A = 5600 \text{ W} = 5.60 \text{ kW}$$

$$P_{dep\ source} = V_i = V_o \cdot 3i_x = 160 \cdot 60 = 9600 \text{ W} \\ = 9.60 \text{ kW}$$

$$\boxed{P_T = 15.2 \text{ kW}}$$

## Video Solution Problem

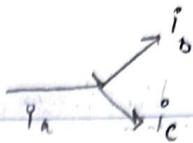

### Part A

A circuit node has current  $i_a$  entering and currents  $i_b$  and  $i_c$  exiting,  $i_a = 5\text{mA}$  &  $i_b = 9\text{mA}$ .

$$i_c = ?$$


$$i_a = i_b + i_c$$

$$5\text{mA} = 9\text{mA} - 4\text{mA}$$

$$i_c = -4\text{mA}$$

## The Voltage Divider

when no load attached

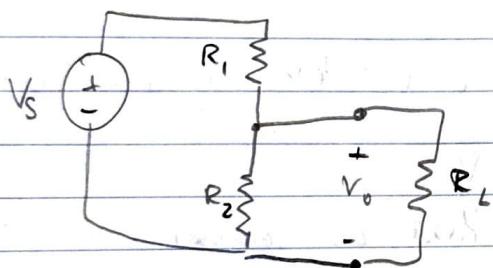

$$V_o = \frac{R_2}{R_1 + R_2} V_s$$

when load,

$$V_o = \frac{R_2}{R_1(1 + \frac{R_2}{R_L}) + R_2} V_s$$

### Part A/

find  $R_2$ ;  $V_s = 18V$ ,  $R_1 = 50\text{k}\Omega$ ,  $V_o = 6V$   
(No load)

$$V_o = \frac{R_2}{R_1 + R_2} V_s \rightarrow \frac{V_o}{V_s} = \frac{R_2}{R_1 + R_2}$$

$$\frac{V_o}{V_s} R_1 + \frac{V_o}{V_s} R_2 = R_2$$

$$\frac{V_o}{V_s} R_1 = R_2 - \frac{V_o}{V_s} R_2$$

$$= R_2 \left(1 - \frac{V_o}{V_s}\right)$$

$$R_2 = \frac{V_o}{V_s} R_1 \cdot \frac{1}{1 - \frac{V_o}{V_s}} = \frac{6}{18} \left(\frac{50 \times 10^3}{18}\right) \cdot \frac{1}{1 - \frac{6}{18}}$$

$$= 25000 \Omega = \boxed{25\text{K}\Omega}$$

## The Voltage Divider, Part B

Out of  $R_L = 300\text{ k}\Omega$ ,  $200\text{ k}\Omega$ ,  $100\text{ k}\Omega$   
 which is the most different output voltage from  $V_o = 6\text{ V}$ ?

$$V_o = \frac{R_2}{R_1(1 + \frac{R_2}{R_L}) + R_2} V_s \quad R_2 = 25\text{ k}\Omega$$

$$V_s = 18\text{ V} \quad R_1 = 50\text{ k}\Omega$$

$$R_L = 300\text{ k}\Omega \rightarrow V_o = 5.684$$

$$R_L = 200\text{ k}\Omega \rightarrow V_o = 5.538$$

$$R_L = 100\text{ k}\Omega \rightarrow V_o = 5.143$$

## Part C

Change  $R_1$  and  $R_2$  so that  $V_o = 6\text{ V}$  when the load resistance is  $R_L = 200\text{ k}\Omega$ . The actual output voltage must not drop below  $5.4\text{ V}$  when  $R_L = 100\text{ k}\Omega$ . What is the smallest resistor value that can be used for  $R_1$ ?

$$V_o = 6\text{ V} ; R_L = 200\text{ k}\Omega \quad V_o \geq 5.4\text{ V} \text{ when } R_L = 100\text{ k}\Omega$$

$$V_o = \frac{R_2}{R_1(1 + \frac{R_2}{R_L}) + R_2} V_s \quad R_2 = \frac{V_o R_1}{V_s} \cdot \frac{1}{1 - \frac{V_o}{V_s}}$$

$$R_2 = \frac{R_1 R_L V_o}{R_L (V_s - V_o) - R_1 V_o} = \frac{R_1 (200 \cdot 10^3) 6}{(200 \cdot 10^3)(18 - 6) - R_1 (6)} = \frac{R_1 \cdot 1.2 \cdot 10^6}{(2.4 \cdot 10^6) - 6 R_1}$$


$$R_2 = \frac{R_1 R_L V_o}{R_L (V_s - V_o) - R_1 V_o} = \frac{R_1 (100 \cdot 10^3) 5.4}{(100 \cdot 10^3)(18 - 5.4) - R_1 (5.4)} =$$

$$= \frac{R_1 \cdot 0.54 \cdot 10^6}{(1.2 \cdot 10^6) - 5.4 R_1}$$

$$R_1 = 66.7\text{ k}\Omega$$

\*Extra credit problem \*

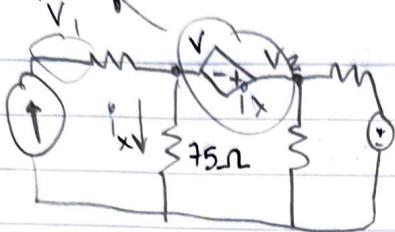Supernode = two nodes connected by a "floating" voltage source  
↳ ungrounded




$$V_2 - V = V_x$$

↳ Supernode gets its own equation  
 $P_x = \frac{V_x \cdot 0}{75}$

# Chapter 3

## 3.1 Resistors in Series

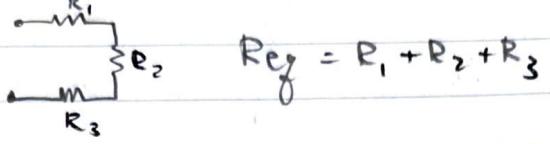


$$R_{eq} = R_1 + R_2 + R_3$$
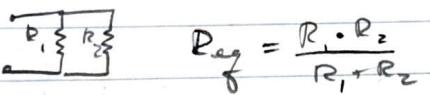
## 3.2 Resistors in Parallel




$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$



$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


$$G_{eq} = \sum_{i=1}^k G_i = G_1 + G_2 + \dots + G_k$$

## 3.3 The Voltage-Divider

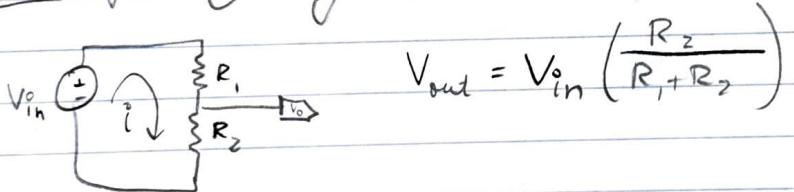

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$


Voltage Divider w/  $R_L$

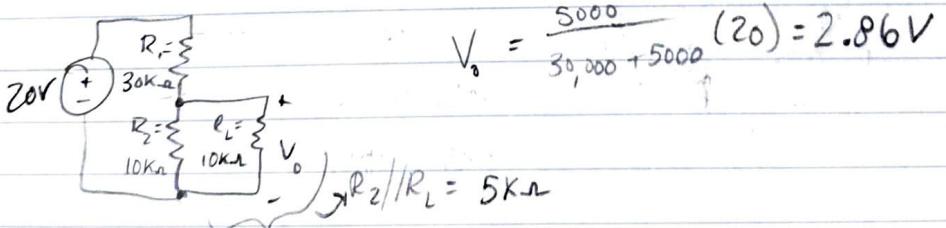

$$V_0 = \frac{5000}{30,000 + 5000} (20) = 2.86V$$

$$\Rightarrow R_2/R_L = 5k\Omega$$


### 3.3 Current Divider circuit

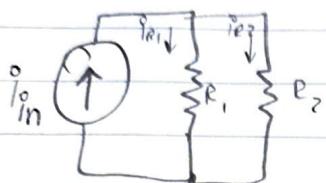

$$i_{R_1} = i_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$i_{R_2} = i_{in} \left( \frac{R_1}{R_1 + R_2} \right)$$


### 3.4 Voltage Division

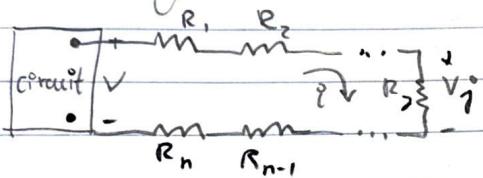

$$V_j = i R_j = \frac{R_j}{R_{\text{eq}}} V$$

% of total

### Current Division

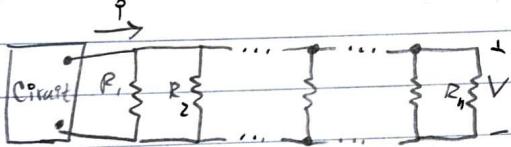


$$i_j = \frac{V}{R_j} = \frac{R_{\text{eq}}}{R_j}$$

Same but  
 $R_{\text{eq}} < R_j$


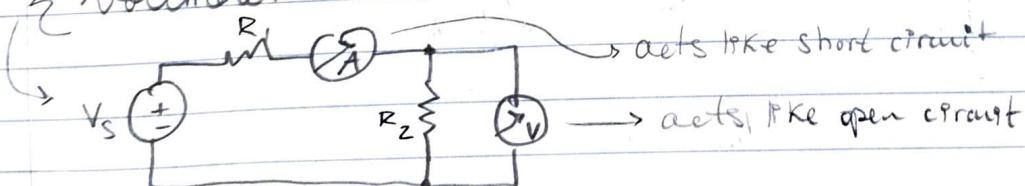
### 3.5 Measuring Voltage and Current

ammeter  $\rightarrow$  measures current. Put in series  $\rightarrow \approx R_{\text{eq}} = 0$

voltmeter  $\rightarrow$  measures voltage. Put in parallel  $\rightarrow \text{ideal } R_{\text{eq}} = \infty$




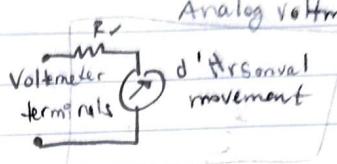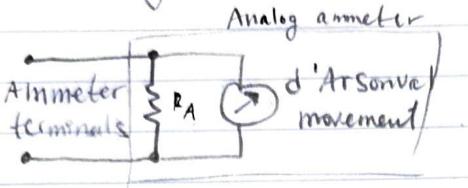Analog Meters  $\rightarrow$  based on coil in d'Arsonval movement



Digital Meters  $\rightarrow$  measure from discrete points in time

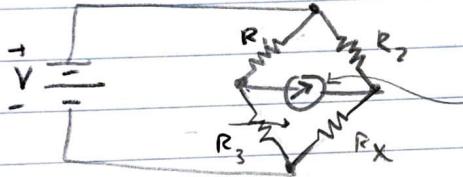
### 3.6] Measuring Resistance - The Wheatstone Bridge



microamp detector called  
a galvanometer

To find  $R_x$ , we adjust  $R_3$  until there is no current in the galvanometer. Then,

$$R_x = \frac{R_2}{R_1} R_3$$

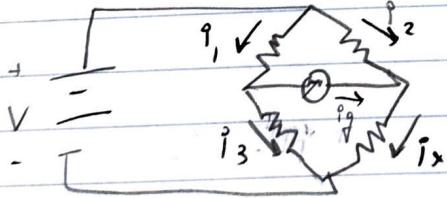


If  $i_g = 0$ , then  $i_2 = i_x$   
and  $i_1 = i_3$


$\Delta$  - to -  $\gamma$

$\pi$  - to -  $T$
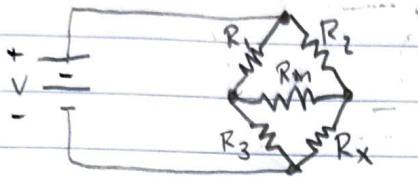
### 3.7 Delta-to-Wye (Pi-to-Tee) Equivalent Circuits




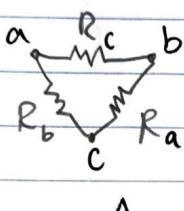$R_1, R_2, R_m \}$  }  $\rightarrow$  delta interconnection  
 $R_3, R_m, R_x \}$  } or pi " "




$\Delta$

{ or }

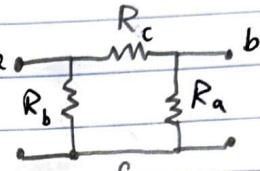


$\pi$

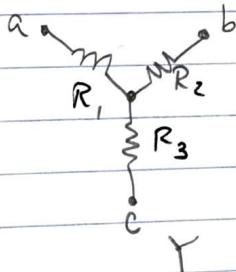$R_1, R_m, R_3 \}$  }  $\rightarrow$  wye ( $\gamma$ ) interconnection  
 $R_2, R_m, R_x \}$  } or tee ( $T$ ) interconnection





$\gamma$  { or }

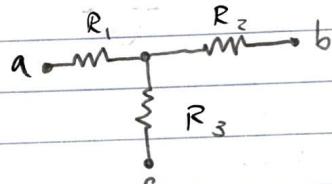

$T$

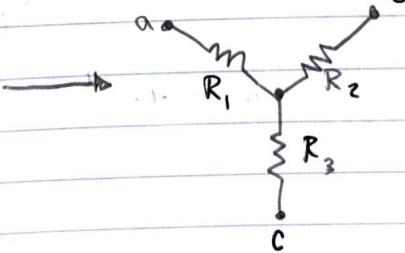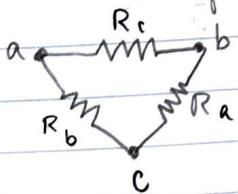$\Delta$  - to -  $\gamma$  transformation





$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


Reverse :  $\text{Y} \rightarrow \Delta$

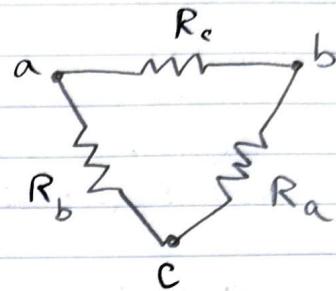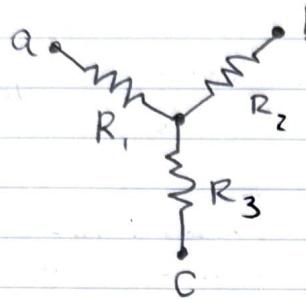

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

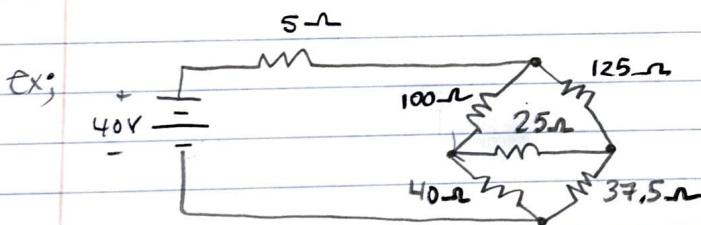
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



$$R_1 = \frac{100 \cdot 125}{250} = 50 \Omega$$

$$R_3 = \frac{100 \cdot 25}{250} = 10 \Omega$$
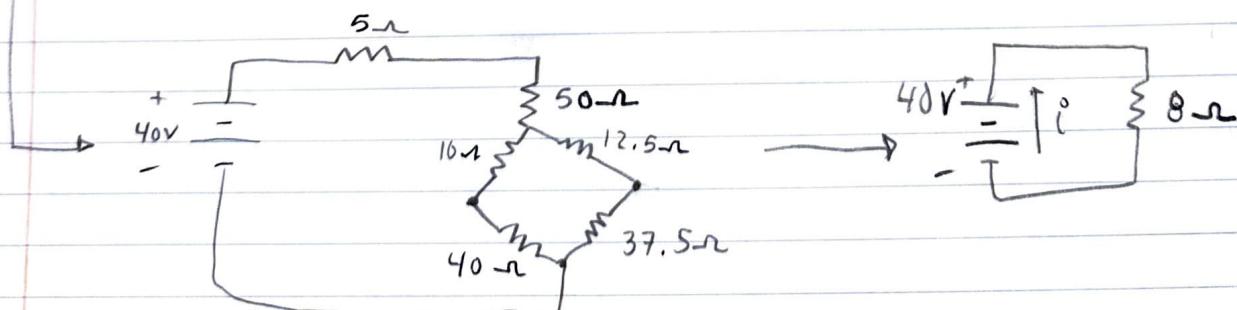
$$R_2 = \frac{125 \cdot 25}{250} = 12.5 \Omega$$



## 4.1 Terminology

Planar circuit → a circuit that can be drawn with no overlapping branches

node → where two elements combine

essential node → where three or more elements join

path → a trace of elements, none included twice


branch → path that connects two nodes

essential branch → a path that connects two essential nodes

loop → path whose last node is same as starting

mesh → loop that doesn't include another loop

## 4.2 - 4.4 Node-Voltage Method

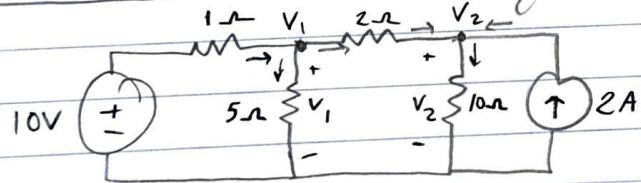

$$\text{node 1: } \frac{V_1 - 10}{1} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0 \quad \text{(10V)}$$


$$\text{node 2: } \frac{V_2 - V_1}{2} + \frac{V_2}{10} - 2 = 0 \quad \text{(2A)}$$

$$\text{Solve} \rightarrow V_1 = 9.09V, V_2 = 10.91V$$

$$\frac{10 - V_1}{1} = \frac{V_1}{5} + \frac{V_1 - V_2}{2}$$

$$\frac{V_1 - V_2}{2} + 2 = \frac{V_2}{10} \quad * \text{ Same answer!}$$
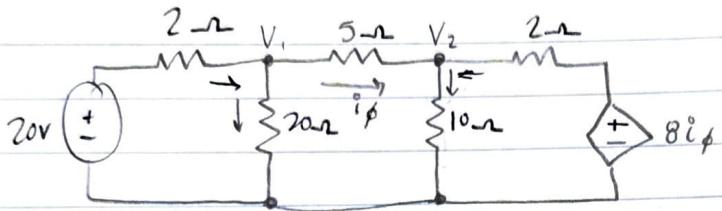
## The Node-Voltage Method and Dependent Source



$$\text{Node 1: } \frac{20 - V_1}{2} = \frac{V_1}{20} + i_\phi$$

$$i_\phi = \frac{V_1 - V_2}{5}$$

$$\text{Node 2: } \frac{V_2}{10} = i_\phi + \frac{8i_\phi - V_2}{2}$$

\* What the book has →  $\frac{V_1 - 20}{2} + \frac{V_1}{20} + \frac{V_1 - V_2}{5} = 0$


Solve →  $V_1 = 16V$     $i_\phi = 1.2A$   
 $V_2 = 10V$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{10} + \frac{V_2 - 8i_\phi}{2} = 0$$

$$i_\phi = \frac{V_1 - V_2}{5}$$


Basically, start at the node and minus next voltage.

Then = 0.

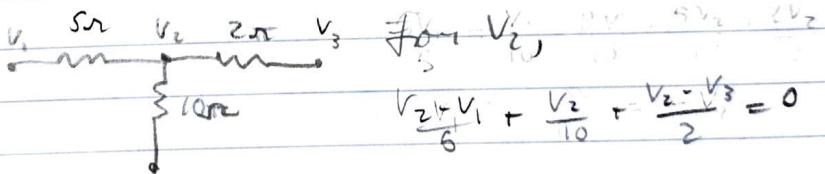

$$\frac{V_2 - V_1}{6} + \frac{V_2}{10} + \frac{V_2 - V_3}{2} = 0$$

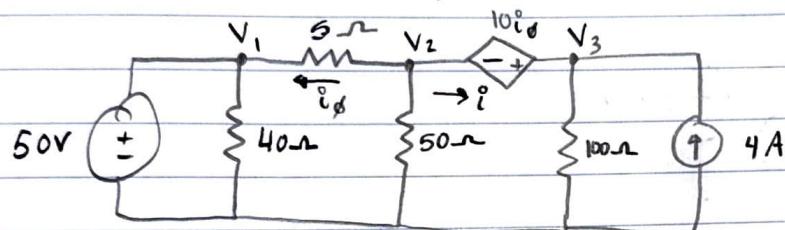4.4. Dependent voltage source between two nodes



\*Book equations\*

$$\text{Node 2: } \frac{V_2 - 50}{2} + \frac{V_2}{50} + i = 0$$

$$\text{Node 3: } \frac{V_3}{100} - i - 4 = 0$$

\*Add two equations\*


$$\frac{V_2 - 50}{2} + \frac{V_2}{50} + \frac{V_3}{100} - 4 = 0$$

Voltage source between two nodes → Supernode!

$$\text{Supernode equation: } V_3 - V_2 = 10i\phi \rightarrow i\phi = \frac{V_2 - 50}{5}$$

$$\text{Solve} \rightarrow V_2 = 60V, V_3 = 80V, i\phi = 2A$$

### 4.5 Mesh Current Method (Ans)

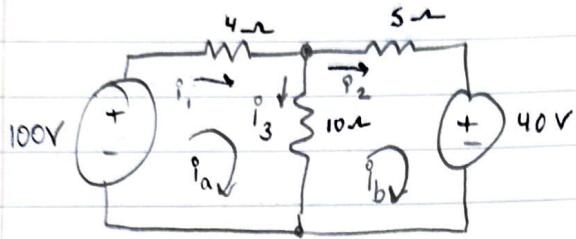


$$\text{Mesh 1 : } -100 + 4i_1 + 10(i_a - i_b) = 0$$

$$\text{Mesh 2 : } 5i_b + 40 + 10(i_b - i_a) = 0$$

$$\text{Solve} \rightarrow i_a = 10A, i_b = 4A$$

$$\begin{aligned}\text{Solve again} \rightarrow i_1 &= i_a = 10A \\ i_2 &= i_b = 4A \\ i_3 &= i_a - i_b = 6A\end{aligned}$$

### 4.8 Mesh Analysis Special cases

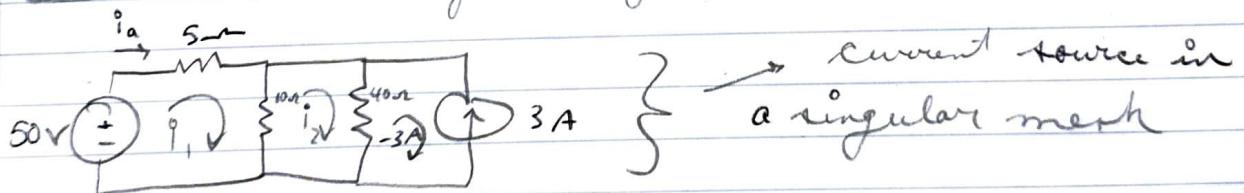


$$\begin{aligned}\text{Equations : } -50 + 5i_1 + 10(i_1 - i_2) &= 0 \\ 10(i_2 - i_1) + 40(i_2 - (-3)) &= 0\end{aligned}$$

$$\begin{aligned}\rightarrow i_1 &= 2A \\ i_2 &= -2A\end{aligned}$$

$$\begin{aligned}i_a &= i_1 = 2A \\ i_b &= i_1 - i_2 = 4A \\ i_c &= i_2 + 3 = 1A\end{aligned}$$

ex:

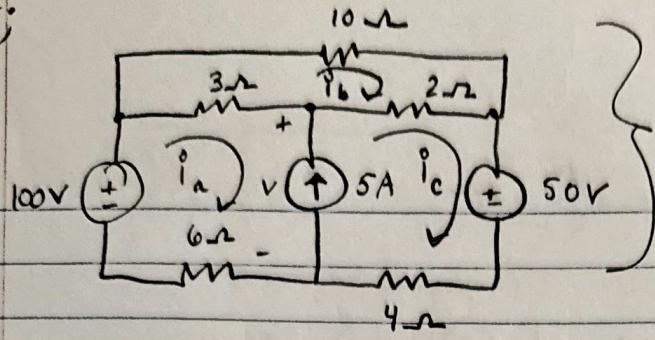


Current Source  
in two mesh

voltage  
drop across current  
source

$$\text{Mesh A: } -100 + 3(i_a - i_b) + v + 6i_a = 0$$

$$\text{Mesh C: } 50 + 4i_c - v + 2(i_c - i_b) = 0$$
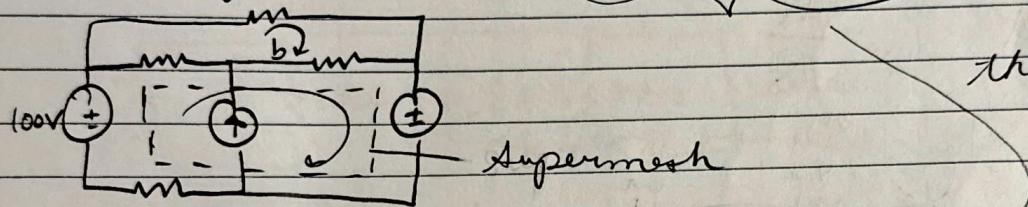
$$* \text{ add equations } * \rightarrow -50 + 9i_a - 5i_b + 6i_c = 0$$



$$\text{Supermesh: } -100 + 3(i_a - i_b) + 2(i_c - i_b) + 50 + 4i_c + 6i_a = 0$$

↓ Simplify →  $-50 + 9i_a - 5i_b + 6i_c = 0$


$$\text{Mesh b: } 10i_b + 2(i_b - i_c) + 3(i_b - i_a) = 0$$

$$* i_c - i_a = 5 * \leftarrow \text{Supermesh "constraint" equation}$$

Solve 3 equations (Supermesh, Mesh b, constraint)

$$\downarrow i_a = 1.75A, i_b = 1.25A, i_c = 6.75A$$

### 4.9 Source Transformation




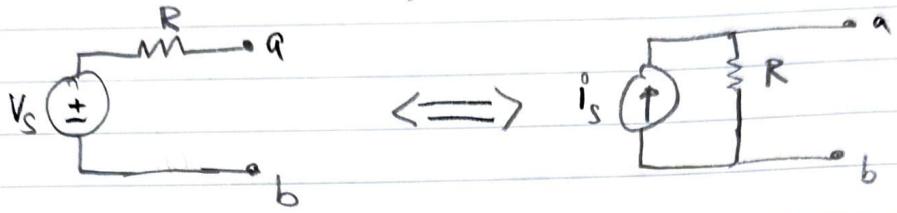




A resistor in series  
with a voltage source

A resistor in // with  
a current source



$$\star \quad i_s = \frac{V_s}{R}$$

ex; Simplification process

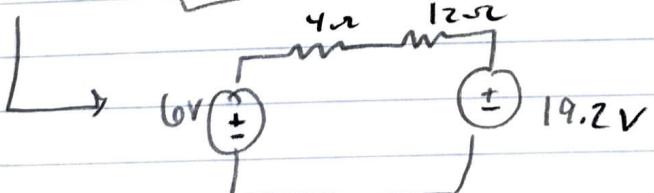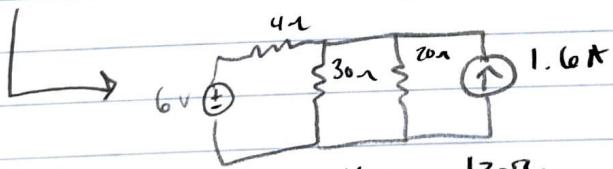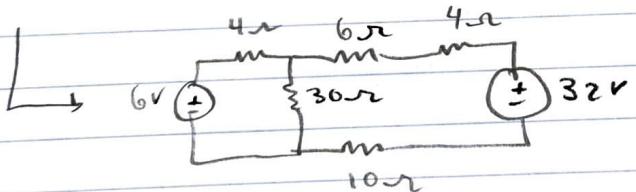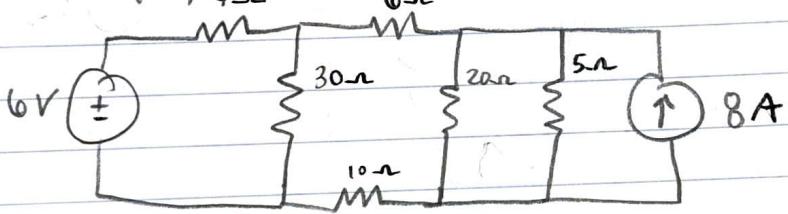

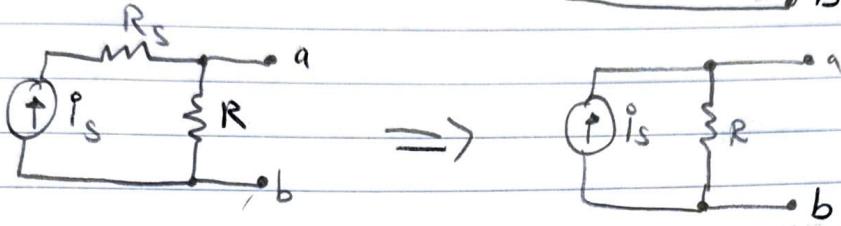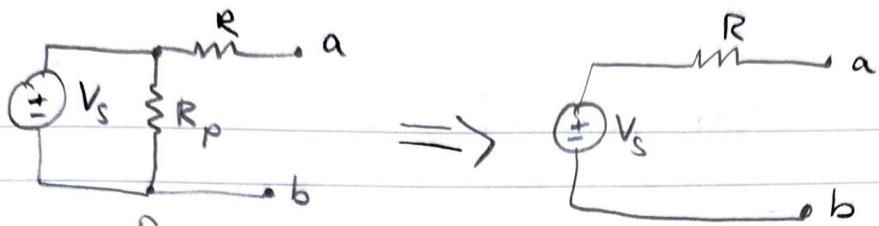

\* How is this possible ?? \*

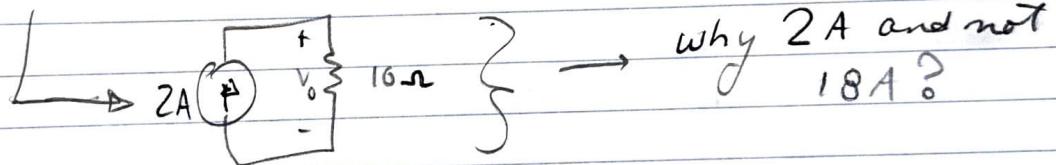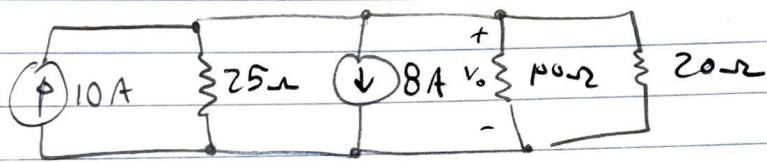


Seth Ricks

ECEN 250

1/16/2024

PS 2 : 3.18, 3.21,  
3.62, 4.12, 4.21,  
4.37

3.18

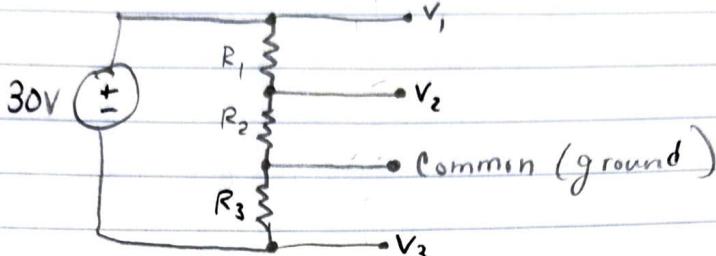

Part A

Select values  $R_1, R_2, R_3$

→ total power when divider unloaded = 30 W

$$\rightarrow V_1 = 15V ; V_2 = 5V ; V_3 = -15V$$

$$V_1 - \text{common} = 15$$

$$V_3 - \text{common} = -15V$$

$$V_2 - \text{common} = 5$$

$$V_{R1} = V_1 - V_2 = 10V \quad V_{R2} = V_2 = 5V \quad V_{R3} = |V_3| = 15V$$

$$P = 30W ; V = 30V \rightarrow i = 1A$$


$$i_{R1} = i_{R2} = i_{R3} = 1A \quad R_1 = \frac{V_{R1}}{i_{R1}} = \frac{10V}{1A} = 10\Omega$$

$$R_2 = \frac{V_{R2}}{i_{R2}} = \frac{5V}{1A} = 5\Omega$$


$$R_3 = \frac{V_{R3}}{i_{R3}} = \frac{15V}{1A} = 15\Omega$$

$$R_1 = 10\Omega ; R_2 = 5\Omega ; R_3 = 15\Omega$$

3.21

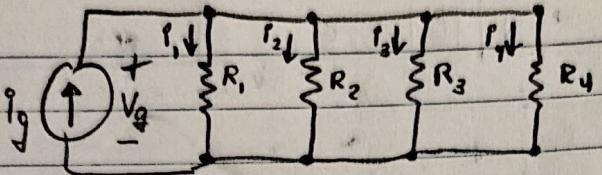
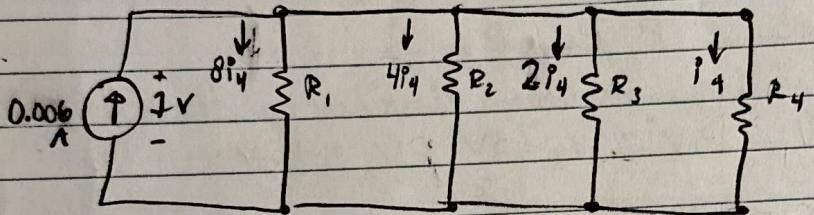
$$i_g = 6 \text{ mA}, V_g = 1 \text{ V}, i_1 = 2i_2, i_2 = 2i_3, i_3 = 2i_4$$



$$i_4 = i_4$$

$$i_3 = 2i_4$$

$$i_2 = 2i_3 = 2(2i_4) = 4i_4$$

$$i_1 = 2i_2 = 2(2i_3) = 4i_3 = 4(2i_4) = 8i_4$$

$$8i_4(R_1) = 4i_4(R_2) = 2i_4(R_3) = i_4(R_4)$$

$$8R_1 = 4R_2 = 2R_3 = R_4$$

$$8i_4 + 4i_4 + 2i_4 + i_4 = 0.006 \text{ A}$$

$$15i_4 = 0.006 \text{ A}$$

$$i_4 = 0.4 \text{ mA} = 0.0004 \text{ A}$$

$$R_4 = \frac{V}{I} = \frac{2V}{0.0004A} = 2500 \Omega = 2.50 \text{ k}\Omega$$


$$2R_3 = R_4 = 2500 \Omega$$

$$R_3 = 1250 \Omega = 1.25 \text{ k}\Omega$$



$$4R_2 = 2500 \Omega \rightarrow R_2 = 625 \Omega = 0.625 \text{ k}\Omega$$

$$8R_1 = 2500 \Omega \rightarrow R_1 = 312.5 \Omega = 0.313 \text{ k}\Omega$$

3.62

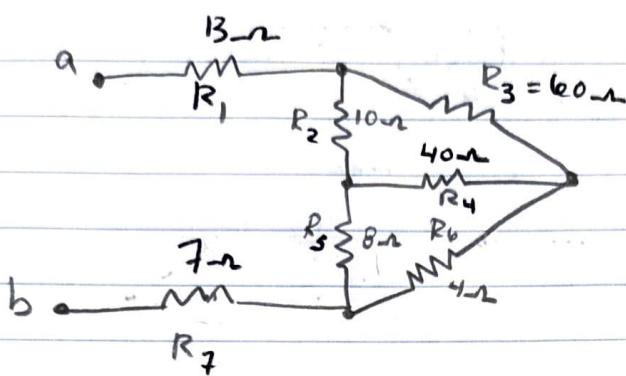

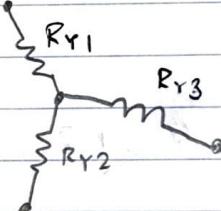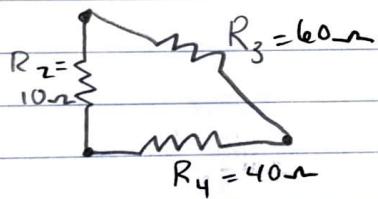Part A Simplify  $R_2$ ,  $R_3$ , and  $R_4$  by using  
A-to-Y transformation




$$R_{Y1} = \frac{(R_2)(R_3)}{R_4 + R_3 + R_2} = \frac{(10)(60)}{40 + 60 + 10} = \frac{600}{110} = 5.45 \Omega$$

$$R_{Y3} = \frac{(R_3)(R_4)}{R_4 + R_3 + R_2} = \frac{(60)(40)}{110} = \frac{2400}{110} = 21.8 \Omega$$



$$R_{Y2} = \frac{(R_2)(R_4)}{R_4 + R_3 + R_2} = \frac{(10)(40)}{110} = 3.64 \Omega$$

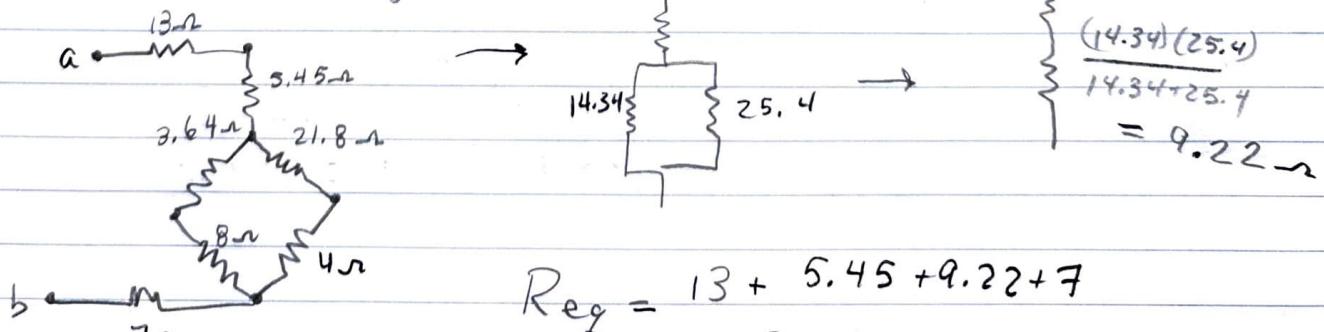Part B Find equivalent resistance  $R_{ab}$



$$\begin{aligned} R_{eq} &= 13 + 5.45 + 9.22 + 7 \\ &= 34.67 \Omega \\ &\approx 33.5 \Omega \end{aligned}$$

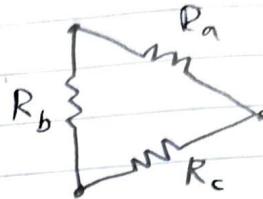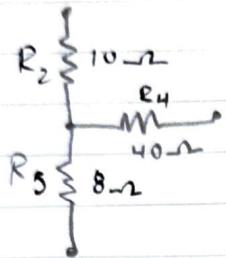
Part C Simplify by  $\Delta$ -to- $\Gamma$  or  $\Gamma$ -to- $\Delta$  rule /  $R_2, R_4, R_5$



$$R_a = \frac{R_2 R_4 + R_4 R_5 + R_5 R_2}{R_5} = \frac{(10)(40) + (40)(8) + (8)(10)}{8} = 100 \Omega$$

$$R_b = \frac{800}{R_4} = \frac{800}{40} = 20 \Omega \quad R_c = \frac{800}{R_2} = \frac{800}{10} = 80 \Omega$$

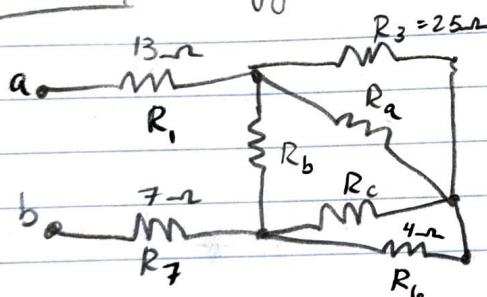Part D Suppose  $R_3 = 25 \Omega$ . Find  $R_{ab}$ .



$$R_3 // R_a = \frac{(25)(100)}{125} = 20 \Omega$$

$$R_6 // R_c = \frac{(4)(80)}{84} = 3.81 \Omega$$

$23.81 \Omega$

$$23.81 // R_b = \frac{(23.81)(20)}{43.81} = 10.87 \Omega$$


$$R_1 + \downarrow + R_7 = 30.87 \Omega = 30.9 \Omega$$

Part E

Two  $\Delta$ -to- $\Gamma$  or  $\Gamma$ -to- $\Delta$   
that can be used:

$$\frac{R_4 - R_5 - R_6}{R_5 - R_4 - R_6}$$

HP Prime

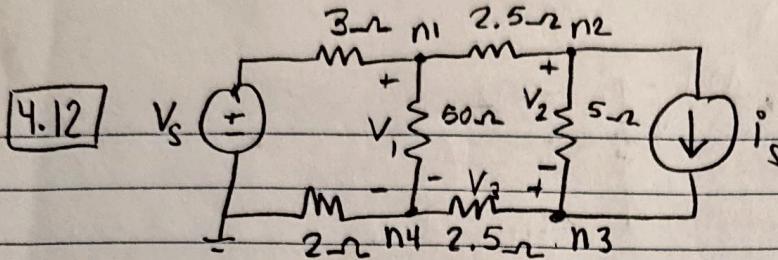

$$V_s = 830; i_s = 12.0 \text{ A}$$

Part A Use the node voltage method to find  $V_1$ ,

$$\text{Node 1: } \frac{n_1 - V_s}{3} + \frac{n_1 - n_4}{50} + \frac{n_1 - n_2}{2.5} = 0 \rightarrow \frac{n_1 - 830}{3} + \frac{n_1 - n_4}{50} + \frac{n_1 - n_2}{2.5} = 0 \\ (\frac{1}{3} + \frac{1}{50} + \frac{1}{2.5})n_1 - \frac{830}{3} - \frac{1}{50}n_4 - \frac{1}{2.5}n_2 = 0$$

$$\text{Node 2: } \frac{n_2 - n_1}{2.5} + \frac{n_2 - n_3}{5} + i_s = 0 \rightarrow \frac{n_2 - n_1}{2.5} + \frac{n_2 - n_3}{5} + 12.0 = 0 \\ -\frac{1}{2.5}n_1 + (\frac{1}{2.5} + \frac{1}{5})n_2 - \frac{1}{5}n_3 + 12.0 = 0$$

$$\text{Node 3: } \frac{n_3 - n_2}{5} + \frac{n_3 - n_4}{2.5} - i_s = 0 \rightarrow \frac{n_3 - n_2}{5} + \frac{n_3 - n_4}{2.5} - 12.0 = 0 \\ 0 + (-\frac{1}{5})n_2 + (\frac{1}{5} + \frac{1}{2.5})n_3 - \frac{1}{2.5}n_4 = 12$$

$$\text{Node 4: } \frac{n_4 - n_3}{2} + \frac{n_4 - n_1}{50} + \frac{n_4 - n_2}{2.5} = 0 \rightarrow \frac{n_4 - n_3}{2} + \frac{n_4 - n_1}{50} + \frac{n_4 - n_2}{2.5} = 0$$

$$V_1 = n_1 - n_4 = \boxed{500 \text{ V}}$$

$$n_1 = 632 \quad n_3 = 272 \quad \frac{1}{50} + 0 - \frac{1}{2.5} + (\frac{1}{2} + \frac{1}{50} + \frac{1}{2.5}) = 0 \\ n_2 = 492 \quad n_4 = 132$$

Part B Use the node voltage method to find  $V_2$

$$V_2 = (n_2 - n_3) + (n_3 - n_4) \\ = (492 - 272) + (272 - 132) = \boxed{360 \text{ V}}$$

Part C Use the node voltage method to find  $V_3$


$$V_3 = n_3 - n_4 = 272 - 132 = \boxed{140 \text{ V}}$$

Part D How much power does the 830V voltage source deliver to the circuit?

$$i = \frac{V_4}{2} = \frac{132}{2} = 66 \text{ A}$$

$$P = 830 \cdot 66 = 54780 = \boxed{54.8 \text{ kW}}$$

4.21

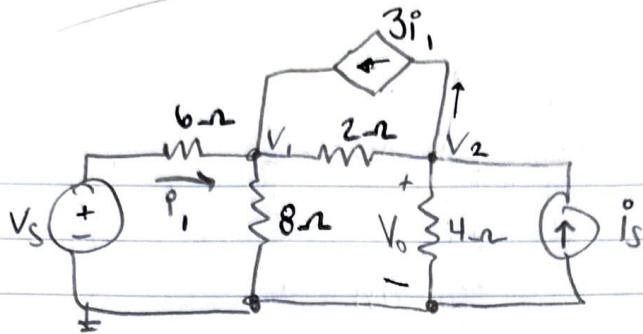

$$V_s = 78V, i_s = 6A$$

Part A Use node-voltage method to find  $V_o$

$$\text{Node 1 : } \frac{V_1 - V_s}{6} - 3i_1 + \frac{V_1 - V_2}{2} + \frac{V_1}{8} = 0$$

$$\text{Node 2 : } \frac{V_2 - V_1}{2} + \frac{V_2}{4} - i_s + 3i_1 = 0$$

$$i_1 = \frac{V_s - V_1}{6}$$

$$\begin{aligned} \text{Equation solver} \rightarrow & V_1 = 48 \\ & V_2 = 20 \\ & V_o = 20V \end{aligned}$$

Part B Find power absorbed by dependent source

$$V_1 - V_2 = V_o$$

$$P = 28V \cdot 3(5)A = 420W$$

$$48 - 20 = 28V$$


Part C Find the total power developed by the independent sources

$$P_{es} = V_o \cdot i_s = 20 \cdot 6 = 120W$$

$$P_{vs} = V_s \cdot i_1 = 78V \cdot 5A = 390W$$

$$120 + 390 = 510W$$

4.37

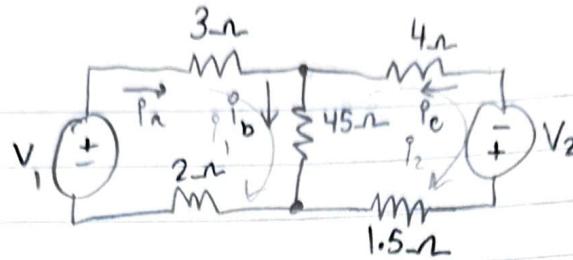

$$V_1 = 55V$$

$$V_2 = 88V$$

Part A

Find the value of  $i_a$

$$\text{Mesh 1: } -55 + 3i_1 + 45(i_1 - i_2) + 2i_1 = 0$$

$$\text{Mesh 2: } -88 + 1.5i_2 + 45(i_2 - i_1) + 4i_2 = 0$$

$$\begin{aligned} -55 + 3i_1 + 45i_1 - 45i_2 + 2i_1 &= 0 \\ 50i_1 - 45i_2 - 55 &= 0 \end{aligned}$$

$$\begin{aligned} -88 + 1.5i_2 + 45i_2 - 45i_1 + 4i_2 &= 0 \\ -45i_1 + 50.5i_2 - 88 &= 0 \end{aligned}$$

\* Equation Solver

$$\rightarrow i_a = i_b = 13.5A$$

Part B

Find the value of  $i_b$

13.5A

$$i_a = 13.5A$$

$$i_c = 13.75A$$

$$|i_a + i_b| = |i_c|$$

$$|i_b| = 5.275 - 44A = 0$$

$$i_b = -0.275A$$

$$i_a < i_c$$

$$i_a > i_b$$

$$i_a > i_b$$

$$|i_b| = 5.275 - 44A = 0$$

$$i_b = -0.275A$$

$$13.5 + i_b = 13.75$$

$$50i_1 + 13.75 = 55$$

$$i_1 = 15.4A$$

Part C

Find the value of  $i_c$

$$(50i_1 - 45i_2 - 55 = 0) \cdot 45$$

$$(-45i_1 + 50.5i_2 - 88 = 0) \cdot 50$$

$$2250i_1 - 2025i_2 - 2475 = 0$$

$$-2250i_1 + 2525i_2 - 4400 = 0$$

$$500i_2 - 6875 = 0$$

$$i_2 = 13.75$$

$$i_p = -i_2 = \boxed{-13.8A}$$

Part D

Find  $i_a$  if  $V_2$  is reversed

$$(50i_1 - 45i_2 - 55 = 0) \cdot 45$$

$$(-45i_1 + 50.2i_2 + 88 = 0) \cdot 50$$

$$2250i_1 - 2025i_2 - 2475 = 0$$

$$-2250i_1 + 2525i_2 + 4400 = 0$$

$$500i_2 + 1925 = 0$$

$$i_2 = -3.85$$


$$50i_1 - 45(-3.85) - 55 = 0$$

$$50i_1 + 118.25 = 0$$

$$i_1 = \boxed{-2.365 = i_a}$$

Part E

Find  $i_b$  if  $V_2$  is reversed

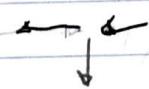

$$i_b = i_c - i_a$$

$$3.85 - 2.365 = \boxed{1.49A}$$


Part F

Find  $i_c$  if  $V_2$  is reversed

$$i_2 = i_c = \boxed{3.85A}$$

## (Video Solution Problem)

**Part A**

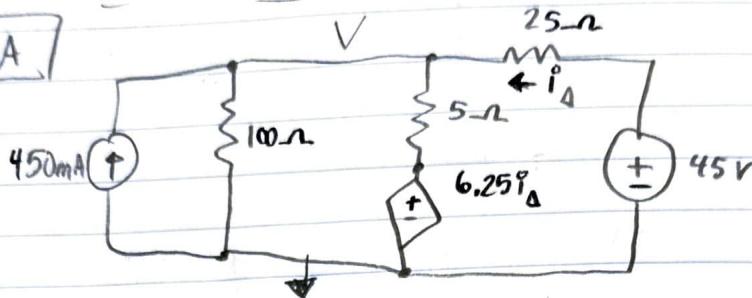

For the circuit analysed in the video, what is the power dissipated by the  $25\Omega$  resistor?

$$-0.45 + \frac{V}{100} + \frac{V - 6.25i_A}{5} + \frac{V - 45}{25} = 0$$


$$i_A = \frac{45 - V}{25}$$

$$-0.45 + \frac{V}{100} + \frac{V - 6.25 \left( \frac{45 - V}{25} \right)}{5} + \frac{V - 45}{25} = 0$$

$$V = 15$$

$$P_R = V_R \cdot i_R = (45 - 15) \cdot \left( \frac{45 - 15}{25} \right) = 30 \cdot 1.2 = \boxed{36 \text{ mW}}$$

4.12 → class


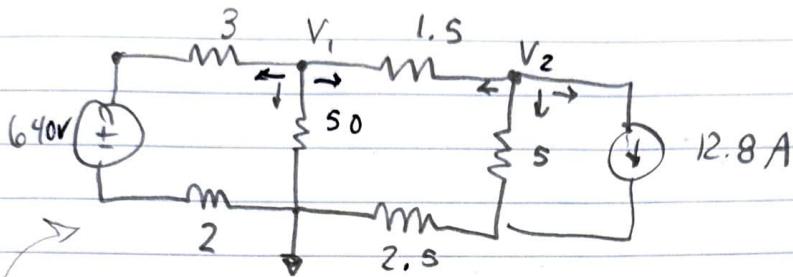


5 is the total resistance in the mesh

$$V_1 - 640 + \frac{V_1}{5} + \frac{V_1 - V_2}{2.5} = 0 \quad (5)$$

$$\frac{V_2 - V_1}{2.5} + \frac{V_2 - V_3}{5} + 12.8 = 0$$

Voltage across  $3\Omega$ ?

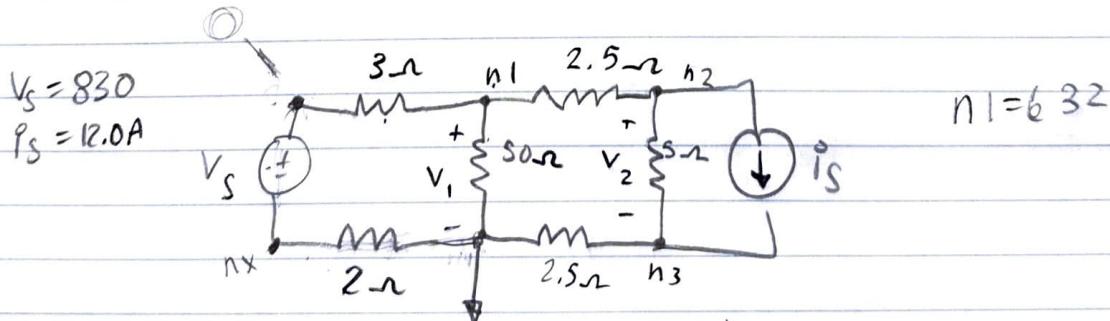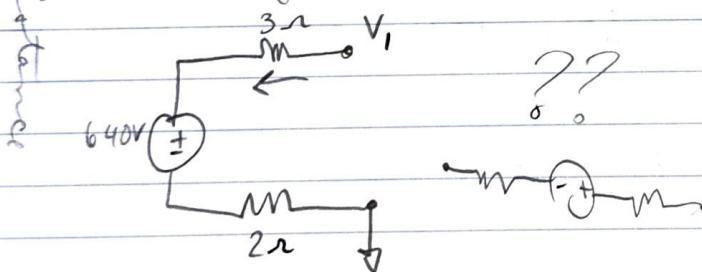

$$n1: \frac{n1 - 830}{5} + \frac{n1}{5} + \frac{n1 - n2}{2.5} = 0 \quad (5)$$

$$n2: \frac{n2 - n1}{2.5} + \frac{n2 - n3}{5} + 12 = 0$$

$$n3: \frac{n3}{2.5} + \frac{n3 - n2}{5} - 12 = 0$$

$$V_{3n} - V_{2n} + V_{2n} = 0 \quad n_x = 0$$



$$V_s = -V_{3n} + V_{2n}$$

$$632 = 2(V_{3n} + V_{2n})$$

4.10

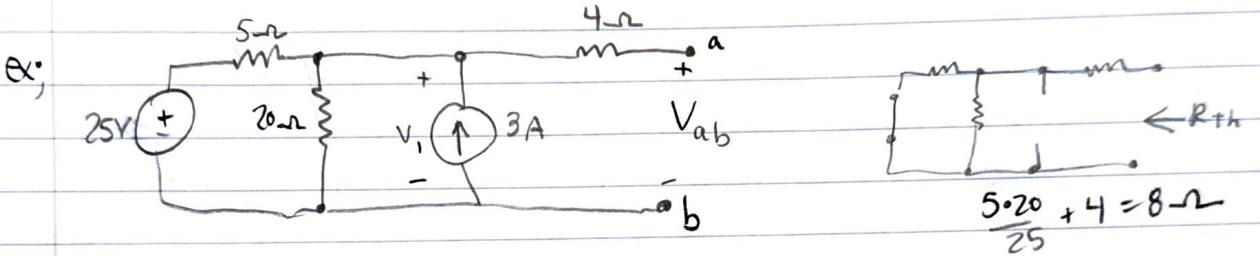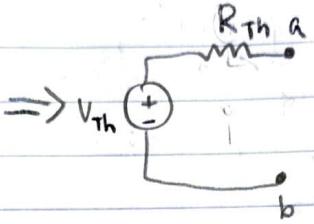
## Thevenin and Norton Equivalents

A resistive network containing independent & dependent sources



$$\text{Step 1 KCL: } \frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0 \rightarrow V_1 = 32 = V_{ab} = V_{Th} = 32$$

Step 2 Place short circuit across  $ab$

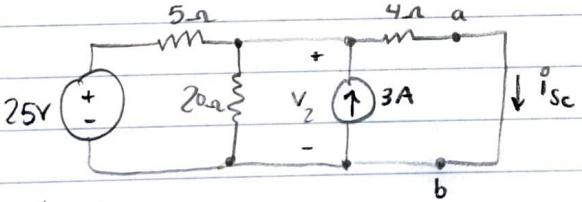

Find  $V_2$


$$\frac{V_2 - 25}{5} + \frac{V_2}{20} - 3 + \frac{V_2}{4} = 0$$

$$V_2 = 16V$$

$$\therefore i_{sc} = \frac{16}{4} = 4A$$

$$\text{Step 3 Find } R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32}{4} = 8\Omega$$
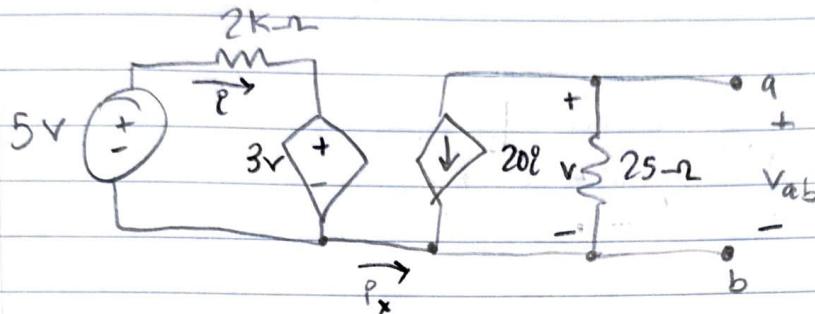
## Thevenin Equivalent w/ Dependent Source




$i_x$  must be zero bc there is no return path

$$V_{Th} = V_{ab} = (-20i)(25) = -500i \quad (-20i \text{ bc current flows from + to -})$$

$$i = \frac{5-3}{2000} = \frac{5-3V_{Th}}{2000}$$

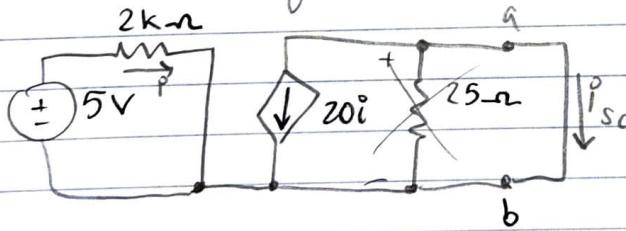\* Combine two equations  $\rightarrow V_{Th} = -5V$




$$i_{sc} = -20i$$


$$i = \frac{5}{2000} = 2.5mA \quad i_{sc} = -50mA$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{-5}{-0.05} = 100\Omega$$

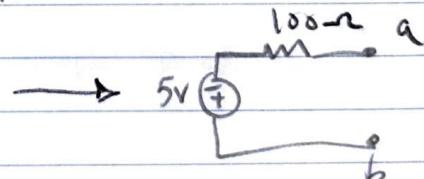(take away dependent voltage source bc  $V=0$ )



Finding  $R_{TH}$  using a test source

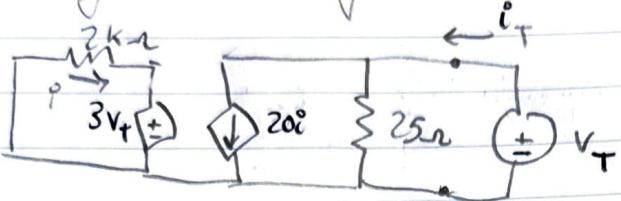


$$i_T = \frac{v_T}{25} + 20i \quad i = -\frac{3v_T}{2000}$$

$$i_T = \frac{v_T}{25} + 20 \left( \frac{-3v_T}{2000} \right)$$

$$\frac{v_T}{i_T} = 100\Omega = R_{TH}$$

# Norton's Theorem

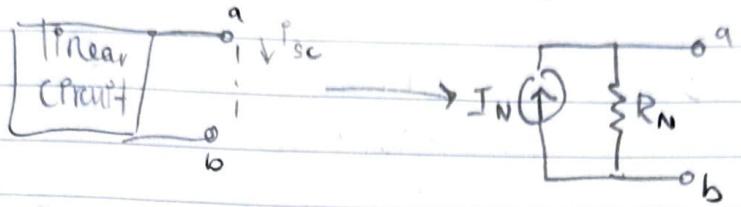




$$R_N = R_{TH}$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$

$$V_{OC} = V_{TH}$$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} = R_N$$


If you short ab,  $I_{SC} = I_N$

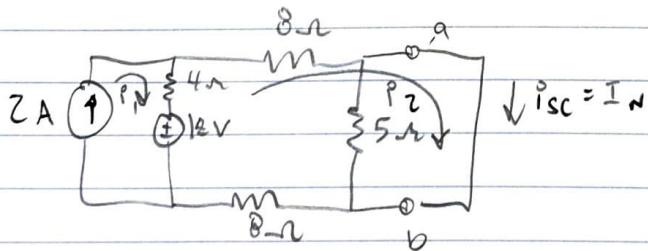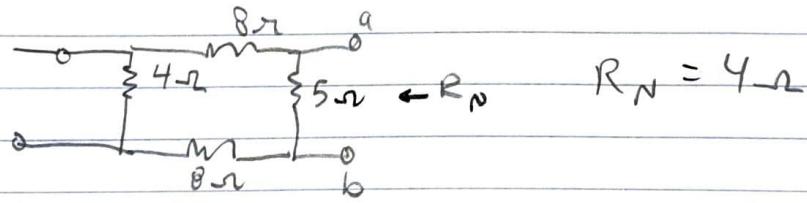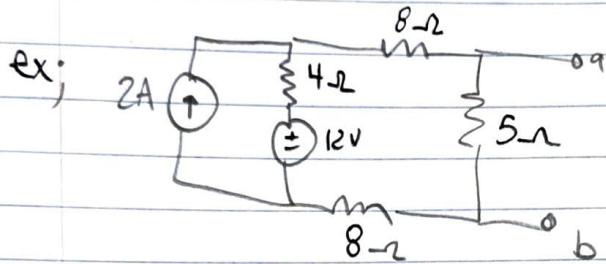

$$I_1 = 2A$$

$$20I_2 - 4I_1 - 12 = 0$$

$$I_2 = 1A = I_{SC} = I_N$$

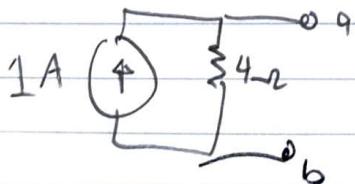

Summary:

Thevenin:

w/ no dep source → turn off Pndep. Sources  
find  $R_{TH}$   
find  $V_{TH}$  (Nodal Analysis)

w/ dep source → turn off indep. Sources  
add simple voltage to ab  
find  $R_{TH}$   
find  $V_{TH}$

Norton:

w/ no dep source → turn off indep. sources  
find  $R_N$

Short circuit

find  $I_N$  (current Analysis)


w/ dep → "  $\rightarrow I_{SC}$   
add simple voltage source

find  $R_N$

Short circuit

find  $I_N = I_{SC}$


## 4.12 Maximum Power Transfer

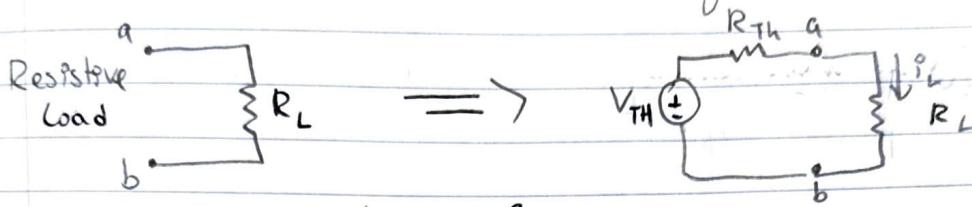

$$P = i^2 R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

Maximum Power  $\rightarrow R_L = R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_L}$$

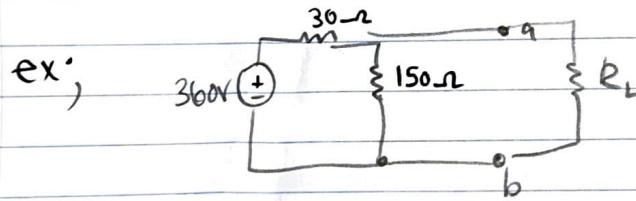


$$R_{TH} = \frac{(30)(150)}{180} = 25 \Omega$$

$$V_{TH} = V_{150\Omega} = 360 \left( \frac{150}{180} \right) = 300V$$

$$P_{max} = \frac{300^2}{4 \cdot 25} = 900W$$


### 4.13 Superposition

ex:

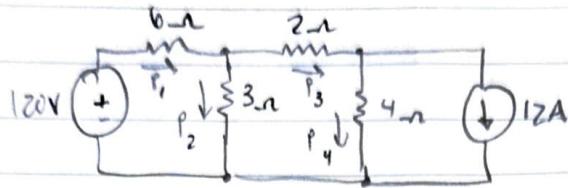

Find branch currents

\* Take out 12A source first

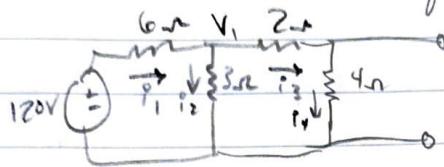

$$\frac{V_1 - 120}{6} + \frac{V_1}{3} + \frac{V_1}{2+4} = 0$$


$$V_1 = 30V$$

$$I_1 = \frac{120 - 30}{6} = 15A$$

$$I_2 = \frac{30}{3} = 10A$$

$$I_3 = I_4 = \frac{30}{6} = 5A$$

\* Take out voltage source

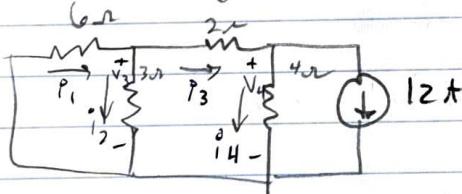

$$\frac{V_3}{3} + \frac{V_3 - V_4}{6} + \frac{V_3 - V_4}{2} = 0 \quad \left. \begin{array}{l} V_3 = -12V \\ V_4 = -24V \end{array} \right\}$$

$$\frac{V_4 - V_3}{2} + \frac{V_4}{4} + 12 = 0$$

$$I_1 = \frac{-V_3}{6} = \frac{12}{6} = 2A$$

$$I_2 = \frac{V_3}{3} = -4A$$



$$I_3 = -12 + 24 = 6A$$

$$I_4 = \frac{V_4}{4} = -6A$$

\* Add together  $I_1 = 17A$   $I_2 = 6A$   
 $I_3 = 11A$   $I_4 = -1A$


Superposition w/ dependent source

Find  $V_o$

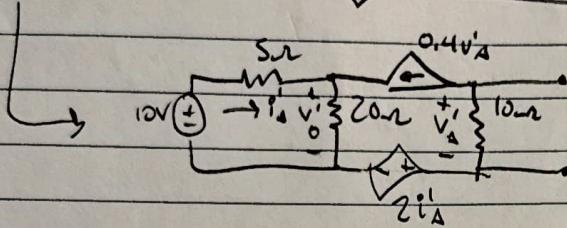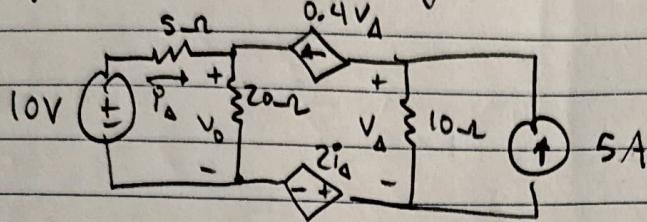

$$\text{So } V'_a = (0.4V'_A)(10) \rightarrow V'_A \text{ must be zero}$$
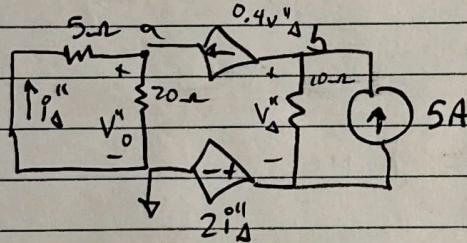
$$\text{Also, } V'_o = \frac{20}{25} 10 = 8V$$



$$\text{Node } a: \frac{V''_o}{20} + \frac{V''_o}{5} - 0.4V''_A = 0 \rightarrow 5V''_o - 8V''_A = 0$$

$$\text{Node } b: 0.4V''_A + \frac{V''_b - 2V''_o}{10} - 5 = 0 \rightarrow 4V''_A + V''_b - 2V''_o = 50$$

$$\text{also: } V''_b = V''_A + 2i''_A$$


$$\therefore 5V''_A = 50 \rightarrow V''_A = 10$$

$$5V''_o = 80 \rightarrow V''_o = 16V$$

$$V_o = V'_o + V''_o = 8 + 16 = \underline{24V}$$

4.40 Use the mesh-current method to find the power delivered by the 280V source in the circuit.

Suppose  $V = 280V$

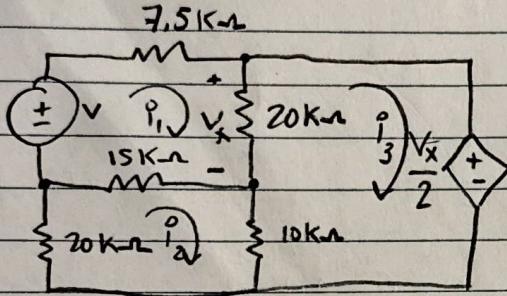

$$\begin{aligned} \text{Mesh 1: } & -V + 7.5i_1 + 20(i_1 - i_3) + 15(i_1 - i_2) = 0 \\ & -V + 7.5i_1 + 20i_1 - 20i_3 + 15i_1 - 15i_2 = 0 \\ & (7.5 + 20 + 15)i_1 - 15i_2 - 20i_3 = V = 280 \end{aligned}$$

$$\begin{aligned} \text{Mesh 2: } & 15(i_2 - i_1) + 10(i_2 - i_3) + 20i_2 = 0 \\ & 15i_2 - 15i_1 + 10i_2 - 10i_3 + 20i_2 = 0 \\ & -15i_1 + (15 + 10 + 20)i_2 - 10i_3 = 0 \end{aligned}$$

$$\text{Mesh 3: } \frac{V_x}{2} + 10(i_3 - i_2) + 20(i_3 - i_1) = 0$$

$$V_x = 20(i_1 - i_3) \quad 10(i_1 - i_3) + 10(i_3 - i_2) + 20(i_3 - i_1) = 0$$

$$V_i = 0.014$$

$$i_2 = 0.007$$

$$i_3 = 0.0105$$

$$P_V = 0.014 \cdot 280 = 3.92W$$

$$10i_1 - 10i_3 + 10i_3 - 10i_2 + 20i_3 - 20i_1 = 0$$

$$-10i_1 - 10i_2 + 20i_3 = 0$$


$$P = 7.947 \cdot 280 =$$

2/  
10



4.6e2






Part.A

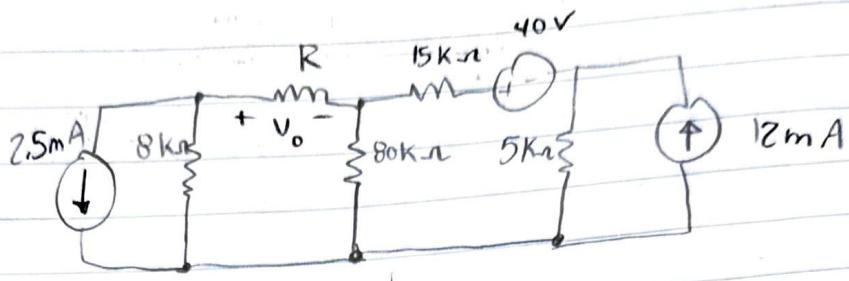

$$R = 12 \text{ k}\Omega$$

$$i_s = \frac{v_s}{R} \quad v_s = i_s R$$

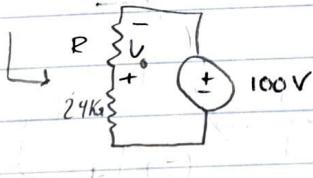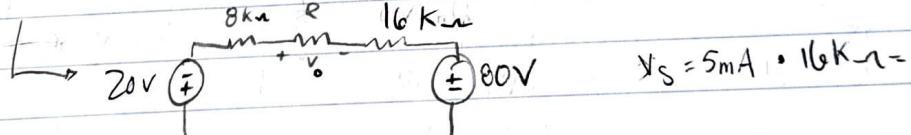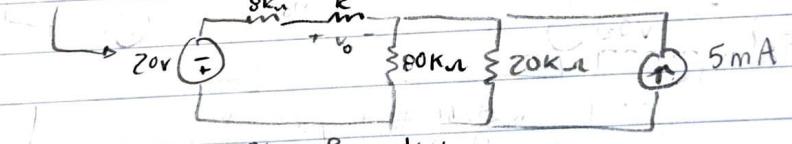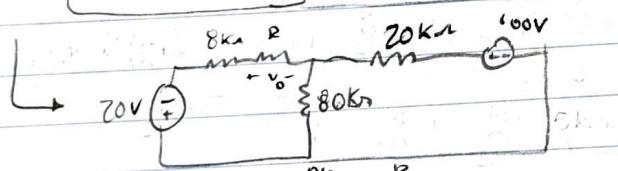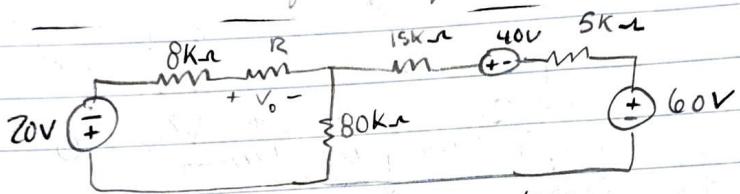Make a series of transformations to find the voltage  $V_o$ .




$$V_o = 100 \left( \frac{12}{12 \text{ k}\Omega + 24 \text{ k}\Omega} \right)$$

$$V_o = -33.3 \text{ V}$$

5:30

243

3/10

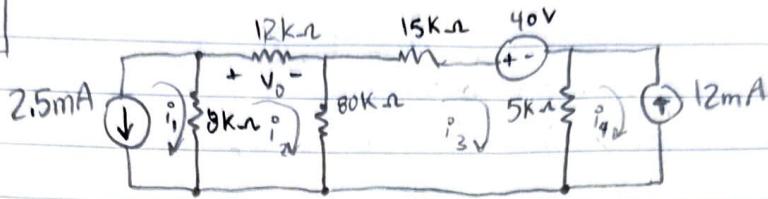Part B

Find the voltage  $V_0$  in the circuit using the mesh-current method.

$$i_1 = -2.5\text{ mA}$$

$$8(i_2 - i_1) + 12(i_2) + 80(i_2 - i_3) = 0$$

$$i_4 = -12\text{ mA}$$

$$8i_2 - 8i_1 + 12i_2 + 80i_2 - 80i_3 = 0$$

$$-8i_1 + 100i_2 - 80i_3 = 0$$

$$20 + 100i_2 - 80i_3 = 0$$

$$15i_3 + 40 + 5(i_3 - i_4) + 80(i_3 - i_2) = 0$$

$$100i_2 - 30i_3 = -20$$

$$15i_3 + 40 + 5i_3 - 5i_4 + 80i_3 - 80i_2 = 0$$

$$-30i_2 + 100i_3 + 60 = -40$$

$$-80i_2 + 100i_3 - 5i_4 = -40$$

$$-80i_2 + 100i_3 = -100$$


$$i_2 = 0.002777$$

$$V_0 = 12 \times 10^3 \cdot i_2 = \boxed{33.3\text{ V}}$$

5:30

243

3/10

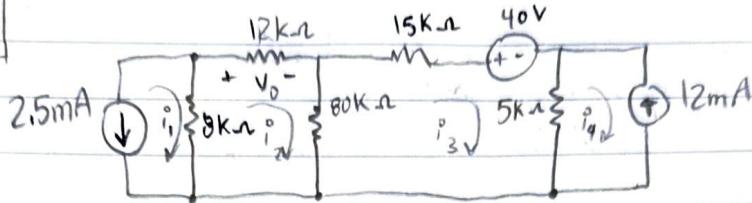**Part B**

Find the voltage  $V_o$  in the circuit using the mesh-current method.

$$i_1 = -2.5\text{mA}$$

$$i_4 = -12\text{mA}$$

$$8(i_2 - i_1) + 12(i_2) + 80(i_2 - i_3) = 0$$

$$8i_2 - 8i_1 + 12i_2 + 80i_2 - 80i_3 = 0$$

$$-8i_1 + 100i_2 - 80i_3 = 0$$

$$20 + 100i_2 - 80i_3 = 0$$

$$100i_2 - 80i_3 = -20$$

$$15i_3 + 40 + 5(i_3 - i_4) + 80(i_3 - i_2) = 0$$

$$15i_3 + 40 + 5i_3 - 5i_4 + 80i_3 - 80i_2 = 0$$

$$-80i_2 + 100i_3 - 5i_4 = -40$$


$$-80i_2 + 100i_3 + (-40) = -40$$

$$-80i_2 + 100i_3 = -100$$

$$i_2 = 0.002777$$

$$V_o = 12 \times 10^3 \cdot i_2 = \boxed{33.3\text{V}}$$

4.608

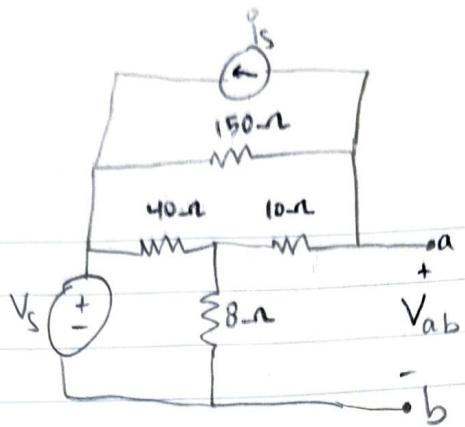


$$V_s = 380\text{V}$$

$$i_s = 2\text{A}$$

4/13

Part B

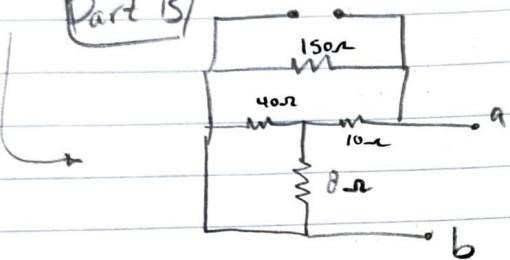


$$\frac{40 \cdot 8}{48} = \frac{20}{3} \rightarrow \frac{20}{3} + 10 = \frac{50}{3}$$

$$\frac{\frac{50}{3} \cdot 150}{\frac{50}{3} + 150} = 15\ \Omega$$

$$R_{Th} = 15\ \Omega$$

Part A

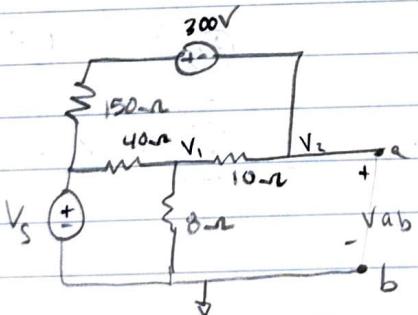

$$V_s = i_s R$$

$$V_s = 2 \cdot 150 = 300\text{V}$$

$$\frac{V_1 - 380}{40} + \frac{V_1}{8} + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_2 - 380 + 300}{150} = 0$$


$$\frac{V_2 - V_1}{10} + \frac{V_2 - 80}{150} = 0$$

$$V_1 = 64\text{V}$$


$$V_2 = 65.0\text{V}$$

5/10

4.81

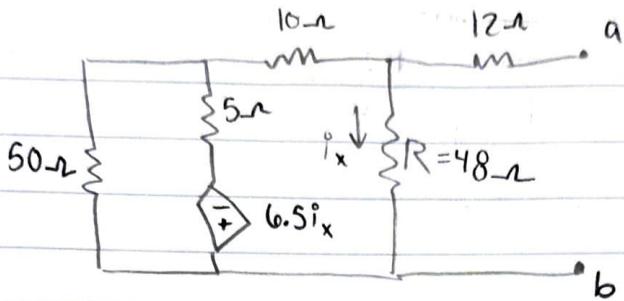

Part B Find Thevenin Resistance

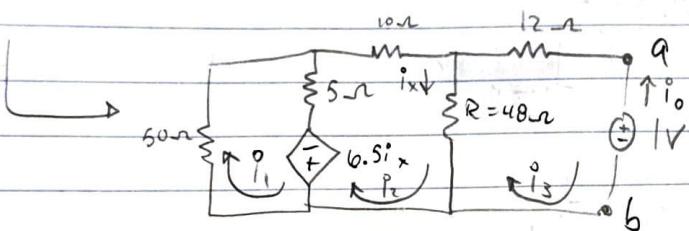

$$\text{Mesh 1: } -(6.5i_x + 50i_1 + 5(i_1 - i_2)) = 0 \quad i_x = i_2 - i_3$$

$$-6.5(i_2 - i_3) + 50i_1 + 5(i_1 - i_2) = 0$$

$$-6.5i_2 + 6.5i_3 + 50i_1 + 5i_1 - 5i_2 = 0 \rightarrow 55i_1 - 11.5i_2 + 6.5i_3 = 0$$

$$\text{Mesh 2: } 6.5i_x + 5(i_2 - i_1) + 10i_2 + 48(i_2 - i_3) = 0$$

$$(6.5(i_2 - i_3) + 5(i_2 - i_1) + 10i_2 + 48(i_2 - i_3)) = 0$$

$$6.5i_2 - 6.5i_3 + 5i_2 - 5i_1 + 10i_2 + 48i_2 - 48i_3 = 0 \rightarrow -53i_1 + 69.5i_2 - 6.5i_3 = 0$$


$$\text{Mesh 3: } 48(i_3 - i_2) + 12i_3 + 1 = 0$$

$$48i_3 - 48i_2 + 12i_3 + 1 = 0 \rightarrow -48i_2 + 60i_3 = -1$$


$$i_3 = -0.045 \text{ A} \quad R_{TH} = \frac{1}{i_0} = 22.2 \text{ ohms}$$

$$i_0 = 0.045 \text{ A}$$

6/10

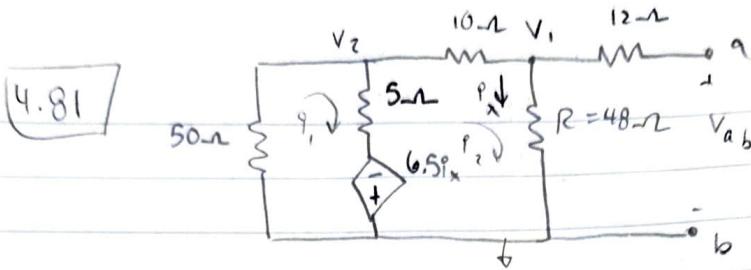

Part A Find Thevenin Voltage

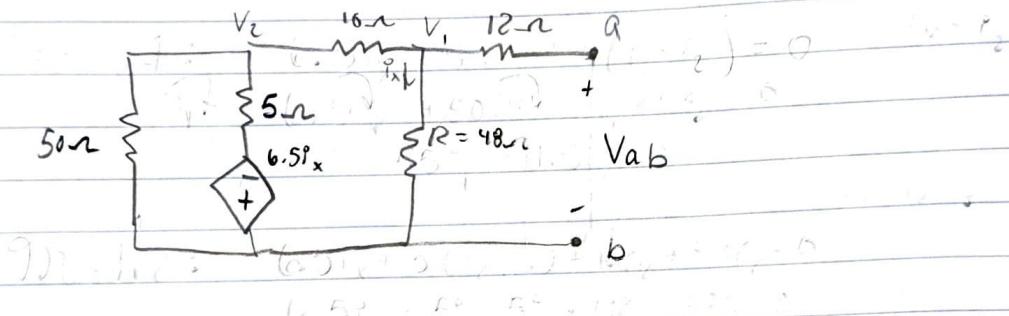

$$\frac{V_2}{50} + \frac{V_2 + 6.5ix}{5} + \frac{V_2 - V_1}{10} = 0$$


$$\frac{V_1 - V_2}{10} + \frac{V_1}{48} = 0$$

$$V_1 = 0 ; V_2 = 0$$

$$V_{ab} = V_1 = \boxed{0 \text{ Volts}}$$

$$V_1 =$$

4.84

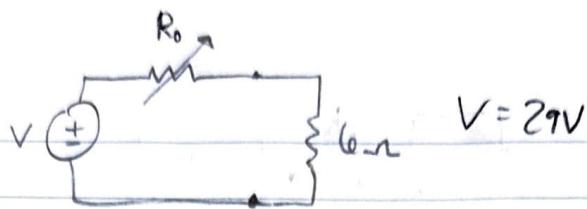

7/10

Part A Find the value of the variable resistor  $R_o$  that will result in Maximum power dissipation in the 6 ohm resistor

$$\text{Max power} \rightarrow [R_o = 0 \Omega]$$

Part B What is the maximum power that can be delivered to the 6 ohm resistor?


$$\cancel{P_{\max} = \frac{V_{Th}^2}{4R_L}} \quad V_{Th} = 29 \left( \frac{6}{12} \right) = 14.5$$

$$I = \frac{V}{R} = \frac{29}{6} \quad P = VI = \frac{29}{6} \cdot 29 = \boxed{140 \text{ W}}$$

\* I don't understand why we learned this if it's not applicable

8/10


4.96

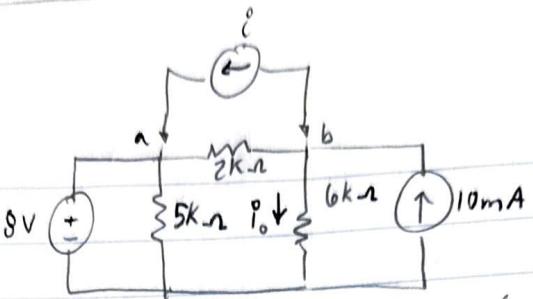

Before the current source  $i$  is attached, the current  $I_o$  is calculated to be 3.5 mA. Take  $i = 5.0 \text{ mA}$ .

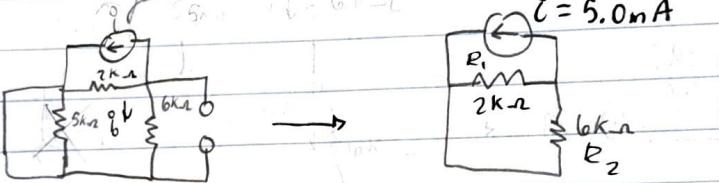Part A / Use superposition to find the value of  $I_o$  after the current source is attached.

w/ voltage + 10mA CS,  $I_o = 3.5 \text{ mA}$



$$I_{R2} = I_{in} \left( \frac{R_1}{R_1 + R_2} \right) = 5.0 \text{ mA} \left( \frac{2000}{2000 + 6000} \right) = 0.00125 = 1.25 \text{ mA}$$

$$I = -1.25 \text{ mA}$$

$$I_T = 3.5 \text{ mA} - 1.25 \text{ mA} = 2.25 \text{ mA}$$


$$I_2 = 0.00533$$

$$I_1 = 3.5 \text{ mA}$$

$$I = 2.25 \text{ mA}$$

Part B

Find  $i_0$  when all sources are on

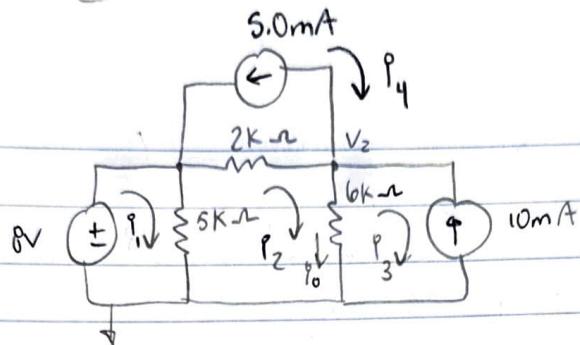

9/10

$$\frac{V_2}{6000} + \frac{V_2 - 8}{2000} - 0.01 + 0.005 = 0$$

$$\left(\frac{1}{6000} + \frac{1}{2000}\right)V_2 - \frac{8}{2000} - 0.01 + 0.005 = 0$$


$$\left(\frac{1}{6000} + \frac{1}{2000}\right)V_2 = \frac{8}{2000} + 0.01 - 0.005 \\ = 0.009$$

$$V_2 = 13.5 \text{ V}$$

$$i_0 = 13.5 \text{ V} / 6000 \Omega = \boxed{2.25 \text{ mA}}$$
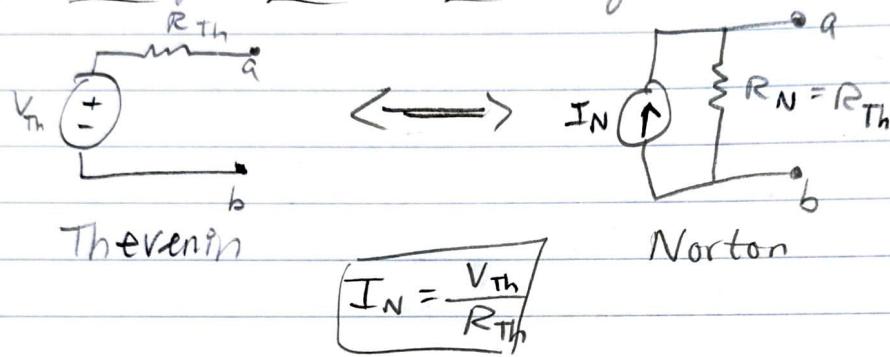
## Video Solution Problem: Finding a Norton Equivalent


Once the Thevenin equivalent circuit is found, which formula is used to find the Norton equivalent source?



$$I_N = \frac{V_{Th}}{R_{Th}}$$


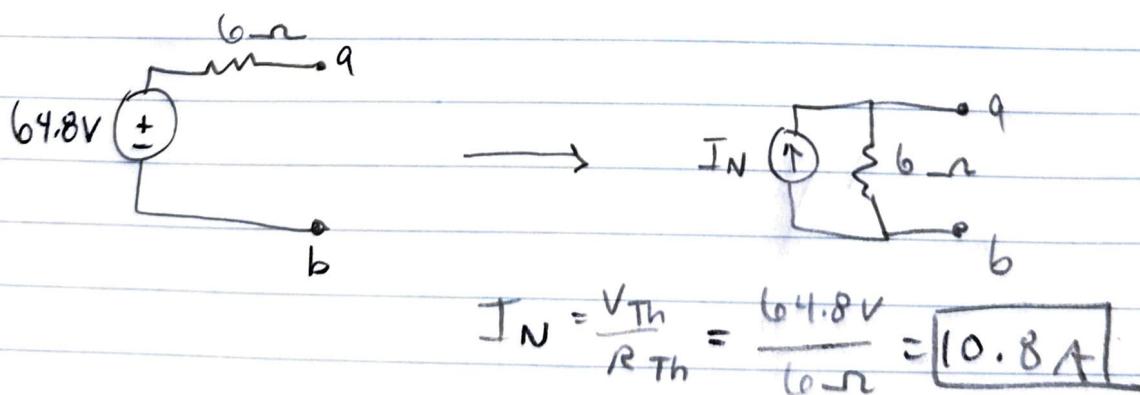
## Video Solution Problem: Finding a Thevenin Equivalent

What is current source value for the Norton equivalent of the circuit in the Assessment Problem?



$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{64.8V}{6\text{-}\Omega} = 10.8A$$

# Chapter 5 : Operational Amps

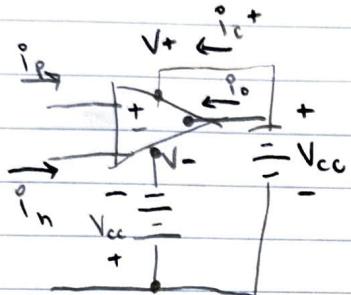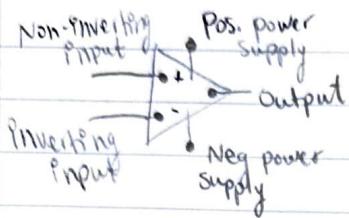

OP amp rules:

$$V_p = V_n$$


$$I_p = I_n = 0$$

## Analyzing an Ideal op amp

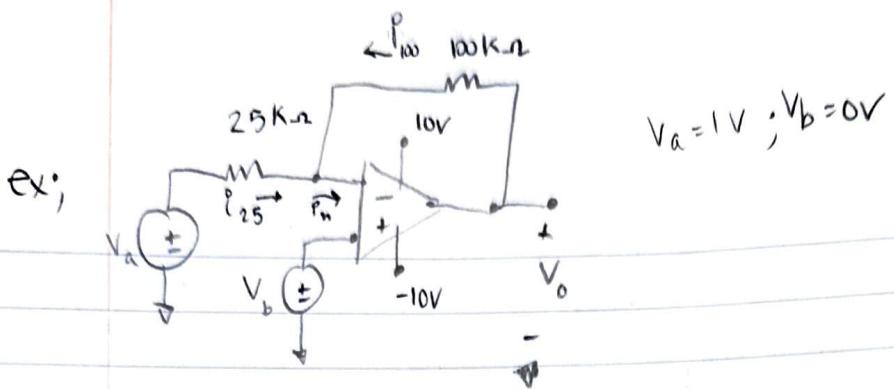1. Check for a negative feedback path
2. Write KCL equation at inverting input terminal
3. Solve KCL equation and use solution to find op amp's output voltage
4. Compare the op amp's output voltage to the power supply voltage

if input is  $\text{M}\text{M}$  but  $V_{cc}$  isn't high enough  $\rightarrow \text{N}\text{N}$   
("saturated")

\* Positive terminal is the leader,  
 negative is the follower \*




$$i_{25} + i_{100} - i_n = 0$$

$$i_{25} = \frac{V_a - V_n}{25,000} = \frac{1 - 0}{25,000} = \frac{1}{25,000}$$

$$i_{100} = \frac{V_o}{100,000}$$


$$\frac{1}{25,000} + \frac{V_o}{100,000} = 0 \quad V_o = -4V$$

### 5.3 The Inverting-Amp Circuit

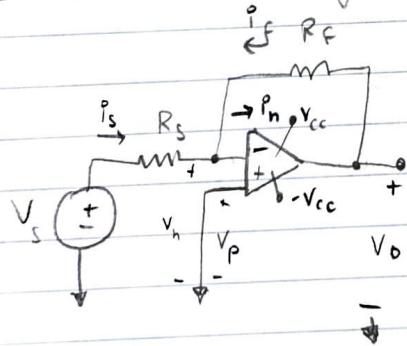


$$V_o = -\frac{R_f}{R_s} V_s \quad A_v = -\frac{R_f}{R_s}$$

Open-loop gain  $\rightarrow = \infty$

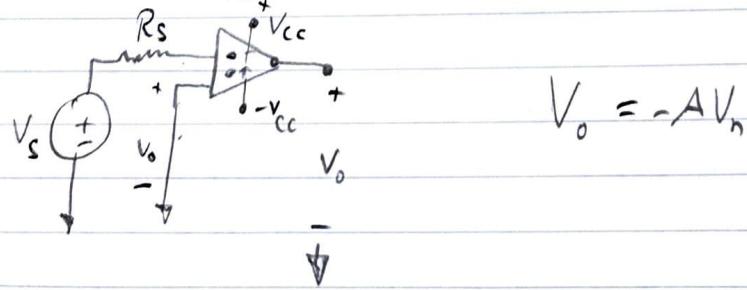

$$V_o = -A V_h$$


## 5.4 The summing-amplifier circuit

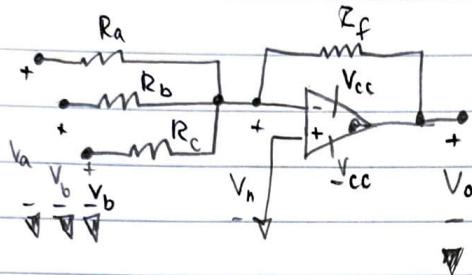

$$V_o = - \left( \frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_s \right)$$

The output is an inverted, scaled sum of the inputs


## 5.5 Non-inverting Amplifier circuit

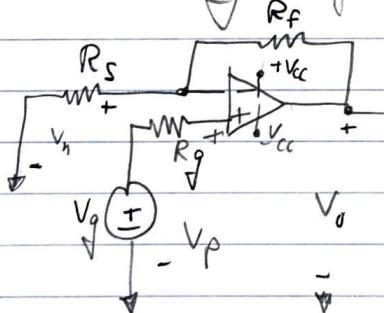

$$V_o = \frac{R_s + R_f}{R_s} V_g$$

If  $R_s \rightarrow 0$ ,  $A = 1$

## 5.6 The Difference Amplifier Circuit

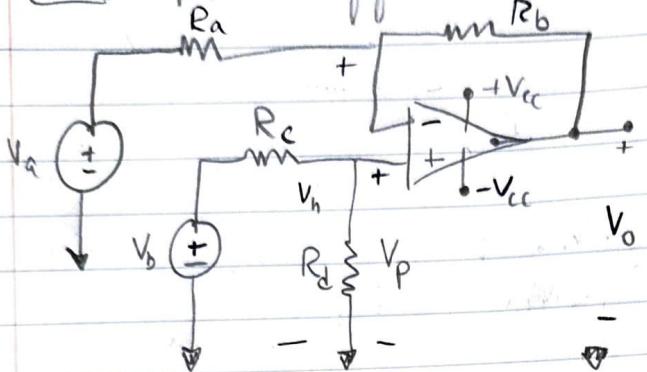

\* Takes the difference times the gain =  $V_o$

$$V_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} V_b - \frac{R_b}{R_a} V_a$$

*(ideal)*

\* If  $\frac{R_a}{R_b} = \frac{R_c}{R_d}$  \*  $\rightarrow V_o = \frac{R_b}{R_a} (V_b - V_a)$

Let's look at this circuit with respect to two other voltages


$$V_{dm} = V_b - V_a \rightarrow \text{differential mode input}$$

$$V_{cm} = (V_a + V_b)/2 \rightarrow \text{common mode input}$$

$$V_o = \left[ \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} \right] V_{cm} + \left[ \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)} \right] V_{dm}$$

$$= A_{cm} V_{cm} + A_{dm} V_{dm}$$

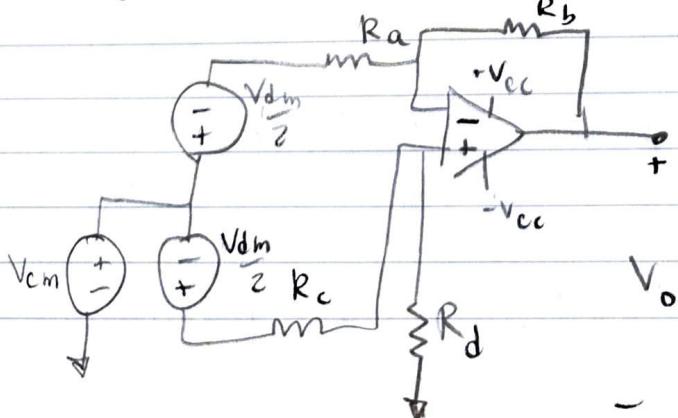\* if  $R_c = R_a$  &  $R_d = R_b$   $\rightarrow V_o = 0 V_{cm} + \left( \frac{R_b}{R_a} \right) V_{dm}$



## Common mode rejection ratio (CMRR)

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|, \text{ larger CMRR} \rightarrow \text{larger to ideal}$$

ex; Design difference amplifier that has a gain of 8, and  $\pm 8V$  power supplies, using ideal op amp

$$V_o = \frac{R_b}{R_a} (V_b - V_a) = 8(V_b - V_a) \quad \text{so } \frac{R_b}{R_a} = 8$$


example solution:  $R_c = R_a = 1.5k\Omega$ ;  $R_d = R_b = 12k\Omega$

If  $V_a = 1V$ , what range for  $V_b$  will allow it to remain in its linear operating region?

$$V_o = \frac{R_b}{R_a} (V_b - V_a) \rightarrow \frac{V_o}{8} + 1 = V_b \rightarrow \begin{aligned} &\frac{8}{8} + 1 = 2V && \text{max } ++ \\ &-\frac{8}{8} + 1 = 0V && \text{min } - \end{aligned}$$

$0V \leq V_b \leq 2V$

ex,

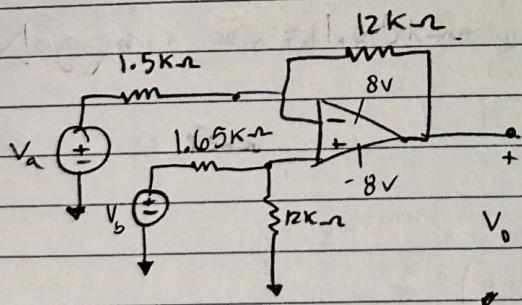

$$A_{cm} = \frac{(1500)(12000) - (12000)(1650)}{1500(1650 + 12000)} = -0.0879$$

$$A_{dm} = \frac{12000(1500 + 12000) + 12000(1650 + 12000)}{2(1500)(1650 + 12000)} = 7.956$$


$$CMRR = \left| \frac{7.956}{-0.0879} \right| = 90.5$$

5.7

## Realistic Model for the Op Amp


yayyy

Op Amp

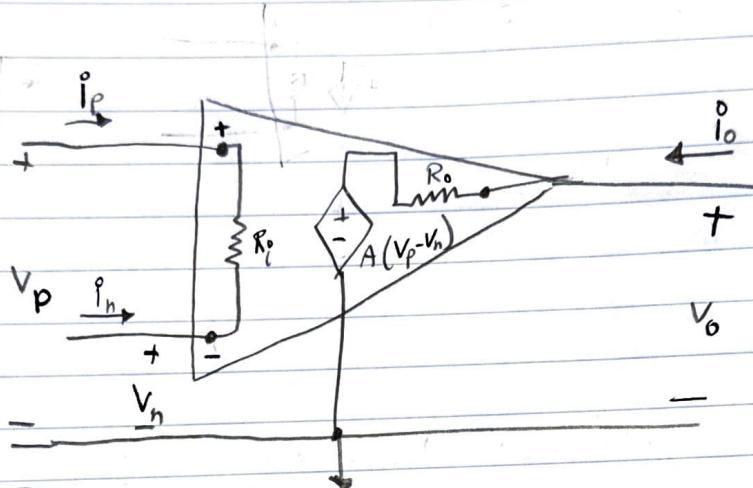

$$\left. \begin{array}{l} V_n = V_p \\ i_n = i_p = 0 \end{array} \right\} \text{invalid assumptions}$$

Realistic inverting amplifier:

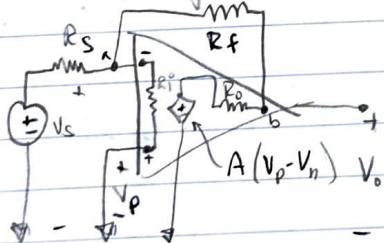


$$V_o = \frac{-A + (R_o/R_f)}{R_f \left( 1 + A + \frac{R_o}{R_p} \right) + \left( \frac{R_s}{R_p} + 1 \right) + \frac{R_o}{R_f}} V_s$$

$$\left. \begin{array}{l} R_o \rightarrow 0 \\ R_i \rightarrow \infty \\ A \rightarrow \infty \end{array} \right\} \rightarrow V_o = -\frac{R_f}{R_s} V_s$$

\* If  $R_L$  load at  $V_o$ , then

$$V_o = \frac{-A + (R_o/R_s)}{R_f \left( 1 + A + \frac{R_o}{R_p} + \frac{R_o}{R_L} \right) + \left( 1 + \frac{R_o}{R_L} \right) \left( 1 + \frac{R_s}{R_p} \right) + \frac{R_o}{R_f}} V_s$$

## Realistic non-inverting amplifier

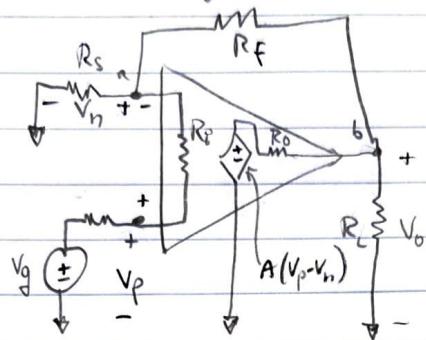

$$V_o = \frac{[(R_f + R_s) + (R_s R_o / A R_i)] V_g}{R_s + \frac{R_o}{A} (1 + K_r) + \frac{R_f R_s + (R_f + R_s)(R_i + R_g)}{A R_i}}$$

where  $K_r = \frac{R_s + R_g}{R_i} + \frac{R_f + R_s}{R_L} + \frac{R_f R_s + R_f R_g + R_g R_s}{R_i R_L}$

\* reduces to  $V_o = \frac{R_s + R_f V_g}{R_s}$  when  $\rightarrow \begin{cases} R_o \rightarrow 0 \\ A \rightarrow \infty \\ R_i \rightarrow \infty \end{cases}$

\* when no  $R_L \rightarrow V_o = \frac{[(R_f + R_s) + R_s R_o / A R_i] V_g}{R_s + \frac{R_o}{A} \left(1 + \frac{R_s + R_g}{R_i}\right) + \frac{1}{A R_i} [R_f R_s + (R_f + R_s)(R_i + R_g)]}$


Seth  
Ricks

ECEN 250  
2/1/2024

HW#4

1/3

## Inverting OpAmp Circuit

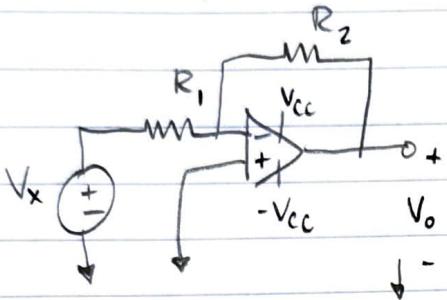

Part A Determine  $V_o$  when  $R_1 = 7.4 \text{ k}\Omega$ ;  $R_2 = 4.8 \text{ k}\Omega$ ;  
 $V_x = 320 \mu\text{V}$ ;  $V_{cc} = 10\text{V}$

$$i_{R1} = \frac{V_x}{R_1}, \quad i_{R2} = \frac{V_o}{R_2}$$

$$\frac{V_x}{R_1} + \frac{V_o}{R_2} = 0 \\ V_o = -\frac{V_x}{R_1} \cdot R_2 = \frac{-320 \times 10^{-6}}{7.4 \times 10^3} \cdot 4.8 \times 10^3 = -294 \mu\text{V}$$

Part B Determine  $R_2$  such that  $V_o = -m \times V_x$   
Assume  $m = 69$ ,  $R_1 = 4.6 \text{ k}\Omega$ ,  $V_{cc} = 15\text{V}$  and that  
the opamp is in its linear region of operation

$$V_o = -\frac{R_2}{R_1} V_x = -m V_x = -69 V_x \\ -69 = -\frac{R_2}{R_1}, \quad R_2 = 69 R_1 = 69 \times 4.6 \text{ k}\Omega = 317,400 \text{ V} = 317.4 \text{ k}\Omega$$

Part C What value of  $V_x$  will lead to saturation of the  
Opamp?


$$V_o = -\frac{R_2}{R_1} V_x = 69 V_x$$

$$15 \text{ V} = 69 V_x$$

$$V_x = 0.217 \text{ V}$$

7/13

## Non-inverting Op-Amp circuit

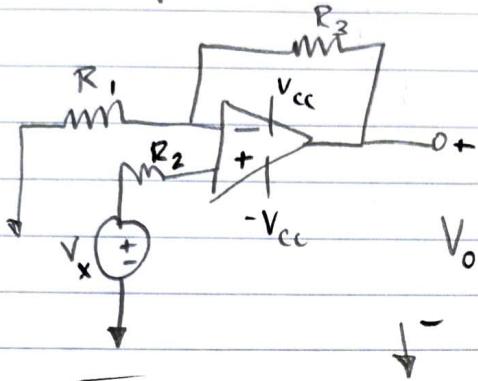

Part A Determine  $V_0$  when  $R_1 = 4.6\text{ k}\Omega$ ,  $R_2 = 1.8\text{ k}\Omega$ ,  
 $R_3 = 60\text{ k}\Omega$ ,  $V_x = 90\text{ mV}$ ,  $V_{cc} = 10\text{ V}$

$$V_0 = \frac{R_1 + R_3}{R_1} V_x = \frac{4.6 \times 10^3 + 60 \times 10^3}{4.6 \times 10^3} \cdot 90 \times 10^{-3} = \boxed{1.260\text{ mV}}$$

Part B Determine  $R_1$  such that  $V_0 = m \cdot V_x$ .  
 $m = 18$ ,  $R_2 = 4\text{ k}\Omega$ ,  $R_3 = 25\text{ k}\Omega$

$$V_0 = 18 V_x = \frac{R_1 + 25,000}{R_1} V_x$$

$$18 = \frac{R_1 + R_3}{R_1}$$


$$18R_1 - R_1 = R_3$$

$$17R_1 = R_3$$

$$R_1 = \frac{25,000}{17} = 1470\text{ }\Omega = \boxed{1.47\text{ k}\Omega}$$

3/13

## Analysis of ideal Op-Amp Circuits

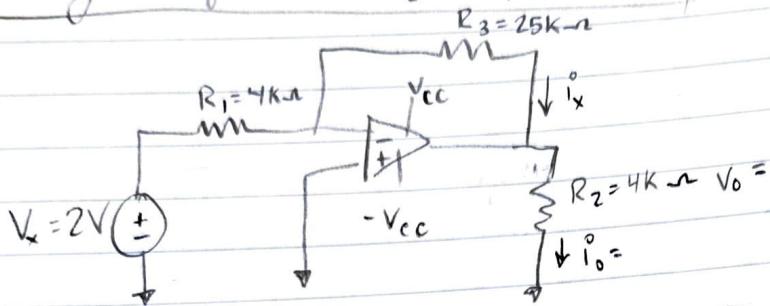

Part A  $V_o = ? ; i_x = ? ; i_o = ?$

$$\frac{0 - V_o}{R_3} + \frac{0 - V_x}{R_1} = 0$$

$$-\frac{V_o}{R_3} + \frac{-V_x}{R_1} = 0$$

$$-\frac{V_o}{R_3} = \frac{V_x}{R_1}$$

$$V_o = \frac{V_x}{R_1} \cdot R_3$$

$$= -\frac{2}{4,000} \cdot 25,000$$

$$V_o = -12.5V$$

$$i_x = \frac{0 - V_o}{R_3} = 0.0005A$$

$$i_o = \frac{V_o - 0}{R_2} = 0.003125A$$

\* How can there be current traveling up from ground if there is no current source?  
\* How can  $i_x$  be + if  $V_o$  is -?

Part B Determine the range of  $V_x$  so that it is linear region.  
 $R_1 = 6k\Omega$ ;  $R_2 = 9k\Omega$ ;  $R_3 = 40k\Omega$ ;  $V_{cc} = 15V$

$$V_o = -\frac{R_3}{R_1} V_x$$

$$V_{o\min} : V_o = -15V$$

$$V_x = V_o \cdot -\frac{R_1}{R_3} = (-15) \cdot -\frac{6,000}{40,000} = 2.25V$$

$$V_{o\max} : V_o = 15V$$

$$V_x = V_o \cdot -\frac{R_1}{R_3} = 15 \cdot -\frac{6,000}{40,000} = -2.25V$$

4/13


Part C Determine  $V_o$  when  $V_x = 3V$ ,  $I_x = 1.0\text{mA}$ ,  $R_1 = 5\text{k}\Omega$ ,  $R_2 = 45\text{k}\Omega$ ,  $R_3 = 3\text{k}\Omega$

$$V_o = -\frac{R_3}{R_1} V_x = \frac{-3000}{5000} \cdot 3 = -1.8V$$

$$I_x^0 = 1.0 \times 10^{-3} = -\frac{V_0}{R_3} \quad V_0 = -I_x^0 \cdot R_3 = -(1.0 \times 10^{-3})(3,000) = -3.0 \text{ V}$$

$$\text{hint: } I_x + \frac{V_o}{R_2} - \frac{V_x}{R_2} = 0 \quad V_o = \left( \frac{V_x}{R_2} - I_x \right) R_2 \\ = V_x - I_x R_2 = 3 - (1.0 \times 10^{-3})(45,000) \\ = \boxed{-42 V}$$

5/13

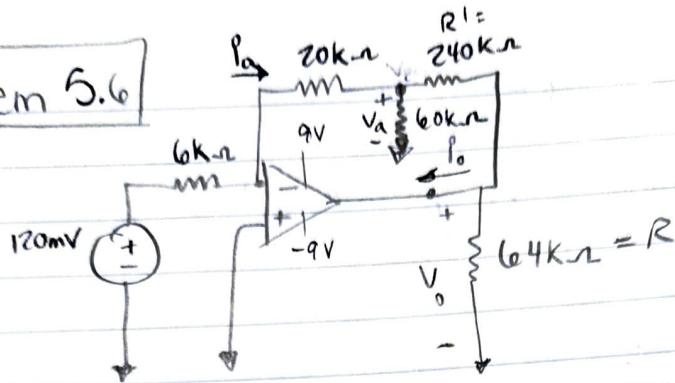Problem 5.6Part B Calculate  $V_a$ 

$$\frac{0 - 120\text{mV}}{6\text{k}\Omega} + \frac{0 - V_a}{20\text{k}\Omega} = 0$$

$$V_a = -\frac{120\text{mV}}{6\text{k}\Omega} \cdot 20\text{k}\Omega = \boxed{-0.40\text{V}}$$

Part C Calculate  $V_o$ 

$$\frac{V_a}{6\text{k}\Omega} + \frac{V_a}{20\text{k}\Omega} + \frac{V_a - V_o}{240\text{k}\Omega} = 0$$

$$240\text{k}\Omega \left( \frac{V_a}{6\text{k}\Omega} + \frac{V_a}{20\text{k}\Omega} + \frac{V_a - V_o}{240\text{k}\Omega} \right) = V_o = \boxed{-6.80\text{V}}$$

5.6

Part A

6/13

Calculate  $i_a$ 

$$\frac{120\text{mV}}{6\text{k}\Omega} = i_a = \boxed{20.0\mu\text{A}}$$

Part D


Calculate  $i_o$ 

$$\frac{V_o}{R} + \frac{V_o - V_a}{240\text{k}\Omega} + i_o^o = 0$$

$$i_o^o = \frac{-V_o}{R} - \frac{V_o - V_a}{240\text{k}\Omega} = \boxed{133\mu\text{A}}$$

7/13

5.7

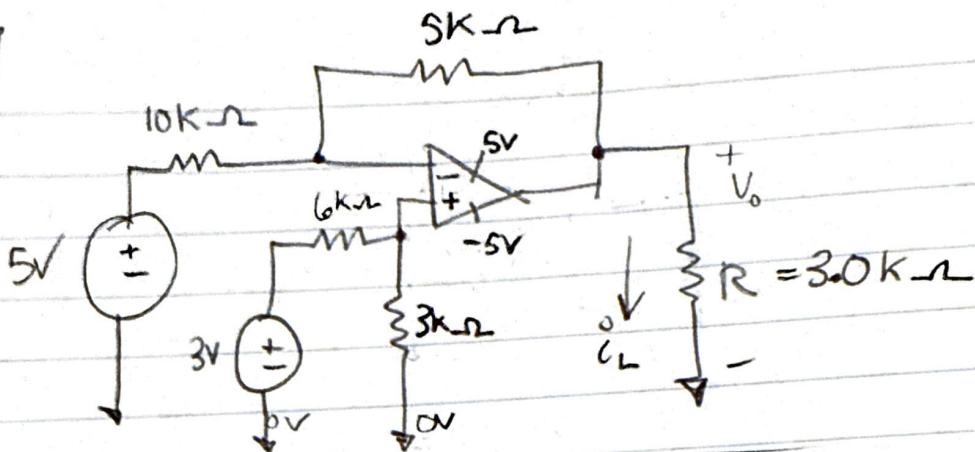

Part A)

Find  $i_L$

Voltage divider

$$V_P = \left( \frac{3\text{k}\Omega}{6\text{k}\Omega + 3\text{k}\Omega} \right) 3V = 1V$$

$$V_P = V_n = 1V$$

$$\frac{1-5}{10\text{k}\Omega} + \frac{1-V_o}{5\text{k}\Omega} = 0$$


$$\frac{-4}{10\text{k}\Omega} + \frac{1}{5\text{k}\Omega} = \frac{V_o}{5\text{k}\Omega}$$

$$V_o = 5\text{k}\Omega \left( \frac{-4}{10\text{k}\Omega} + \frac{1}{5\text{k}\Omega} \right) \\ = -1V$$

$$i_L = -1V / 3,000 \boxed{-0.333\text{mA}}$$

8/13

## Summing Op Amp Circuit

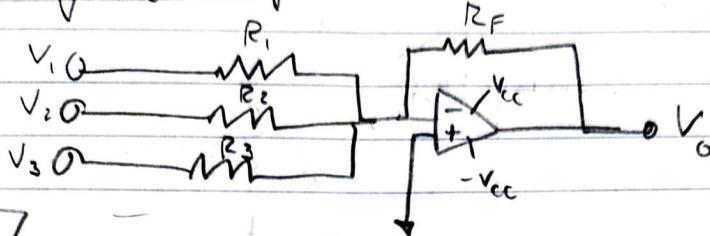

### Part A

Determine  $V_0$  when  $R_1 = 1.2\text{k}\Omega$ ,  $R_2 = 9.8\text{k}\Omega$ ,  
 $R_3 = 7.2\text{k}\Omega$ ,  $R_F = 100\text{k}\Omega$ ,  $V_1 = 20\text{mV}$ ,  $V_2 = 70\text{mV}$ ,  
 $V_3 = 150\text{mV}$ ,  $V_{cc} = 5\text{V}$

$$V_0 = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

$$= - \left( \left( \frac{100,000}{1,200} \cdot 20 \times 10^{-3} \right) + \left( \frac{100,000}{9.800} \cdot 70 \times 10^{-3} \right) + \left( \frac{100,000}{7.200} \cdot 150 \times 10^{-3} \right) \right)$$

$$= -4.464\text{V}$$

### Part B

Determine  $R_1$ ;  $R_2$ ;  $R_3$  AT

$$V_0 = (m_1 \cdot V_1 + m_2 \cdot V_2 + m_3 \cdot V_3)$$

$$m_1 = 5; m_2 = 8; m_3 = 3; R_F = 120\text{k}\Omega$$

$$m_1 = 5 = \frac{R_F}{R_1} \rightarrow R_1 = \frac{R_F}{5} = \frac{120,000}{5} = 24,000\text{\Omega} = 24\text{k}\Omega$$

$$m_2 = 8 = \frac{R_F}{R_2} \rightarrow R_2 = \frac{R_F}{8} = 15\text{k}\Omega$$

$$m_3 = 3 = \frac{R_F}{R_3} \rightarrow R_3 = \frac{R_F}{3} = 40\text{k}\Omega$$

### Part C

Determine range of  $V_1$  to op amp  $\Rightarrow$  linear region

$$R_1 = 3.4\text{k}\Omega, R_2 = 7.2\text{k}\Omega, R_3 = 7.8\text{k}\Omega, R_F = 200\text{k}\Omega, V_2 = 60\text{mV},$$

$$V_3 = 210\text{mV}, V_{cc} = 10\text{V}$$

$$\text{Min: } -10 = - \left( \left( \frac{200,000}{3,400} \right) V_1 + \left( \frac{200,000}{7.200} \right) 60 \times 10^{-3} + \left( \frac{200,000}{7.800} \right) 210 \times 10^{-3} \right)$$


$$V_1 = 0.650\text{V} = 650\text{mV}$$

$$\text{Max: } 10 = \dots$$

$$V_1 = -0.290 = -290\text{mV}$$

9/13

5.12

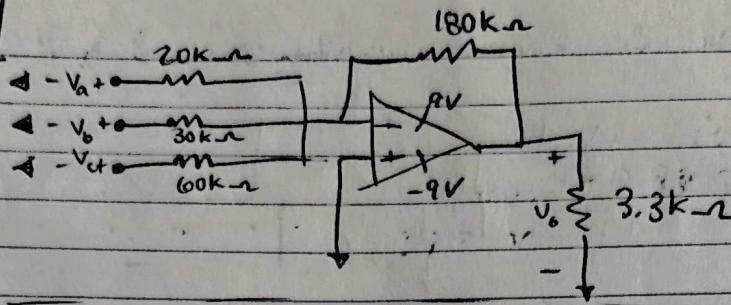

**Part A** The circuit is an example of an inverting summing amplifier.

**Part B** Find  $V_o$  if  $V_a = 0.5V$ ,  $V_b = 1.5V$ ,  $V_c = -3.3V$

$$V_o = - \left( \frac{R_F}{R_a} V_a + \frac{R_F}{R_b} V_b + \frac{R_F}{R_c} V_c \right)$$

$$= - \left( \frac{180,000}{20,000} \cdot 0.5 + \frac{180,000}{30,000} \cdot 1.5 + \frac{180,000}{60,000} \cdot -3.3V \right)$$

$$\boxed{V_o = -3.6V}$$

**Part C** If  $V_a = 0.5V$ ,  $V_b = 1.5V$ , min  $V_c$ ?

$$-9 = - \left( \frac{180,000}{20,000} \cdot 0.5 + \frac{180,000}{30,000} \cdot 1.5 + \frac{180,000}{60,000} V_c \right)$$

$$\boxed{V_c = -7.50V}$$

**Part D**

$$-9 = - \left( \frac{180,000}{20,000} \cdot 0.5 + \frac{180,000}{30,000} \cdot 1.5 + \frac{180,000}{60,000} V_c \right)$$

$$\boxed{V_c = -1.50V}$$

10/13


## Video : Analyzing Non-inverting Amplifier

$$-3.97V \leq V_g \leq 3.97V$$

$$V_o = 2.52 V_g = 10V$$

$$100^2 \cdot 30,000 = P_{30k\Omega} = 3.33mW$$

5.27

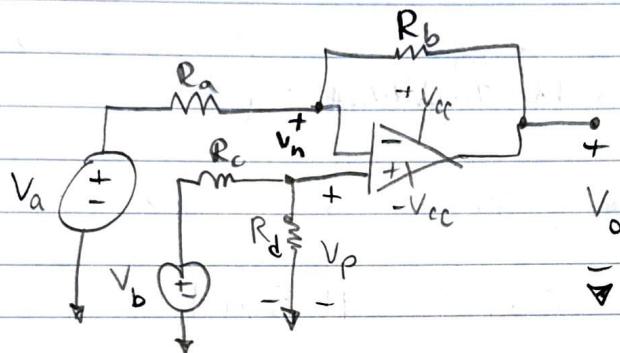

$$R_a = 20k\Omega; R_b = 80k\Omega; R_c = 47k\Omega; R_d = 33k\Omega$$

$$V_a = 0.45V; V_b = 0.9V; V_{cc} = \pm 9V$$

Part A

Find  $V_o$

$$V_o = \frac{R_b(R_a + R_b)}{R_a(R_c + R_d)} V_b - \frac{R_b}{R_a} V_a$$

$$= \frac{33,000(20,000 + 80,000)}{(20,000)(47,000 + 33,000)} \cdot 0.9 - \frac{80,000}{20,000} \cdot 0.45 = 6.056V$$

u / B

5.27 Part B] Calculate resistance in  $V_a$ , using current passing through it

$$V_p = \left( \frac{R_d}{R_c + R_d} \right) V_b = \left( \frac{33\text{k}\Omega}{47\text{k}\Omega + 33\text{k}\Omega} \right) \cdot 0.9\text{V} \\ = 0.37125\text{V}$$

$$I_{R_a} = \frac{0.45 - V_p}{R_a} = 3.94\text{ }\mu\text{A}$$


$$R_{V_a} = \frac{V_a}{I_{R_a}} = \frac{0.45}{3.94\text{ }\mu\text{A}} = 114\text{ k}\Omega$$

Part C] Calculate resistance in  $V_b$

$$I_{R_c} = \frac{0.9\text{V} - 0.37125\text{V}}{47,000} = 11.3\text{ }\mu\text{A}$$

$$R_{V_b} = \frac{V_b}{I_{R_c}} = 80,000\text{ }\Omega = 80\text{ k}\Omega$$

5.34

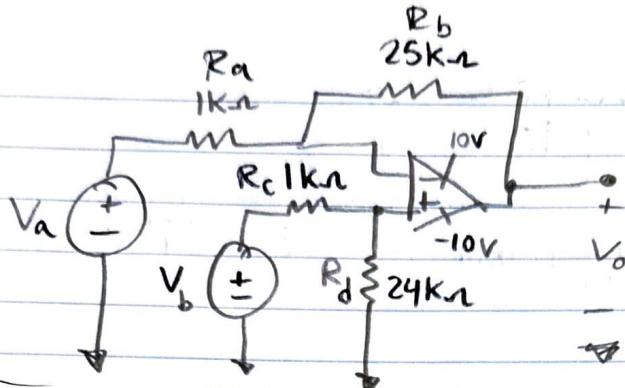

Part A Compute differential mode gain

$$A_{dm} = \left[ \frac{R_d(R_a + R_b) + R_b(R_c + R_d)}{2R_a(R_c + R_d)} \right] \\ = 24.98$$

Part B Compute Common mode gain


$$A_{cm} = \left[ \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} \right] \\ = -0.04$$

Part C Compute the CMRR

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{24.98}{-0.04} \right| = 624.5$$

13/13

5.39

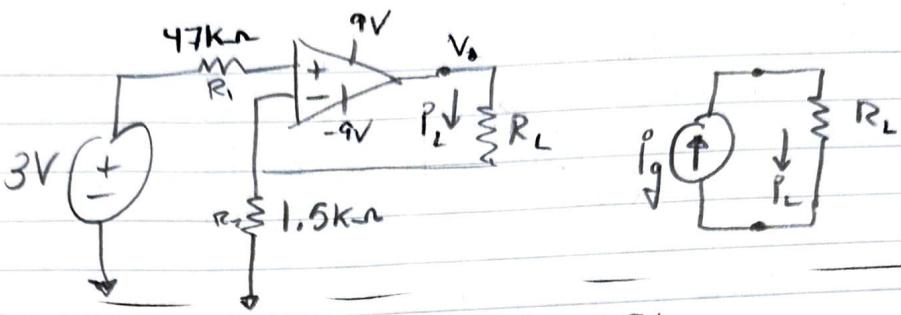

Part A Find value of  $i_L$  for  $R_L = 2.5\text{k}\Omega$

$$V_p = V_n \quad \frac{V_p - 3V}{47} = 0A \rightarrow V_p = 3V$$

$$\frac{V_n}{R_2} + \frac{V_n - V_o}{R_L} = 0$$


$$V_o = \left( \frac{V_n}{R_2} + \frac{V_n - V_o}{R_L} \right) R_L = \left( \frac{3}{1.5\text{k}\Omega} + \frac{3}{2.5\text{k}\Omega} \right) 2.5\text{k}\Omega = 8V$$

$$i_L = \frac{V_o - V_n}{R_L} = [2.00\text{mA}]$$

Part B Find the maximum value for  $R_L$  for which  $i_L$  will have the value in Part A


$$i_L = 2.00\text{mA} \quad V_o = ? \quad R_L = ?$$

$$\text{Max } V_o = 9V \quad (9V - 3V) / 2.00\text{mA} = [3.00\text{k}\Omega]$$

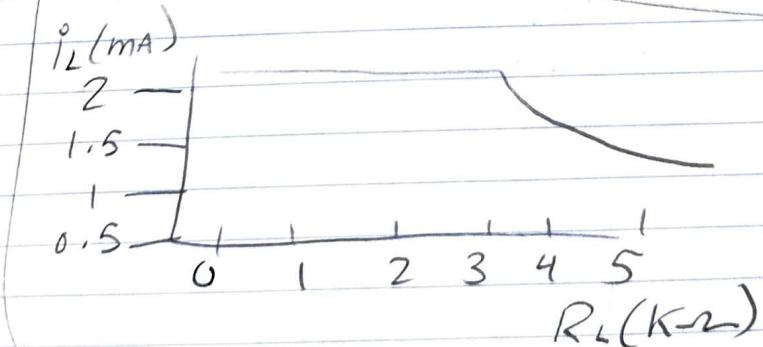
Part C

Choose the correct image
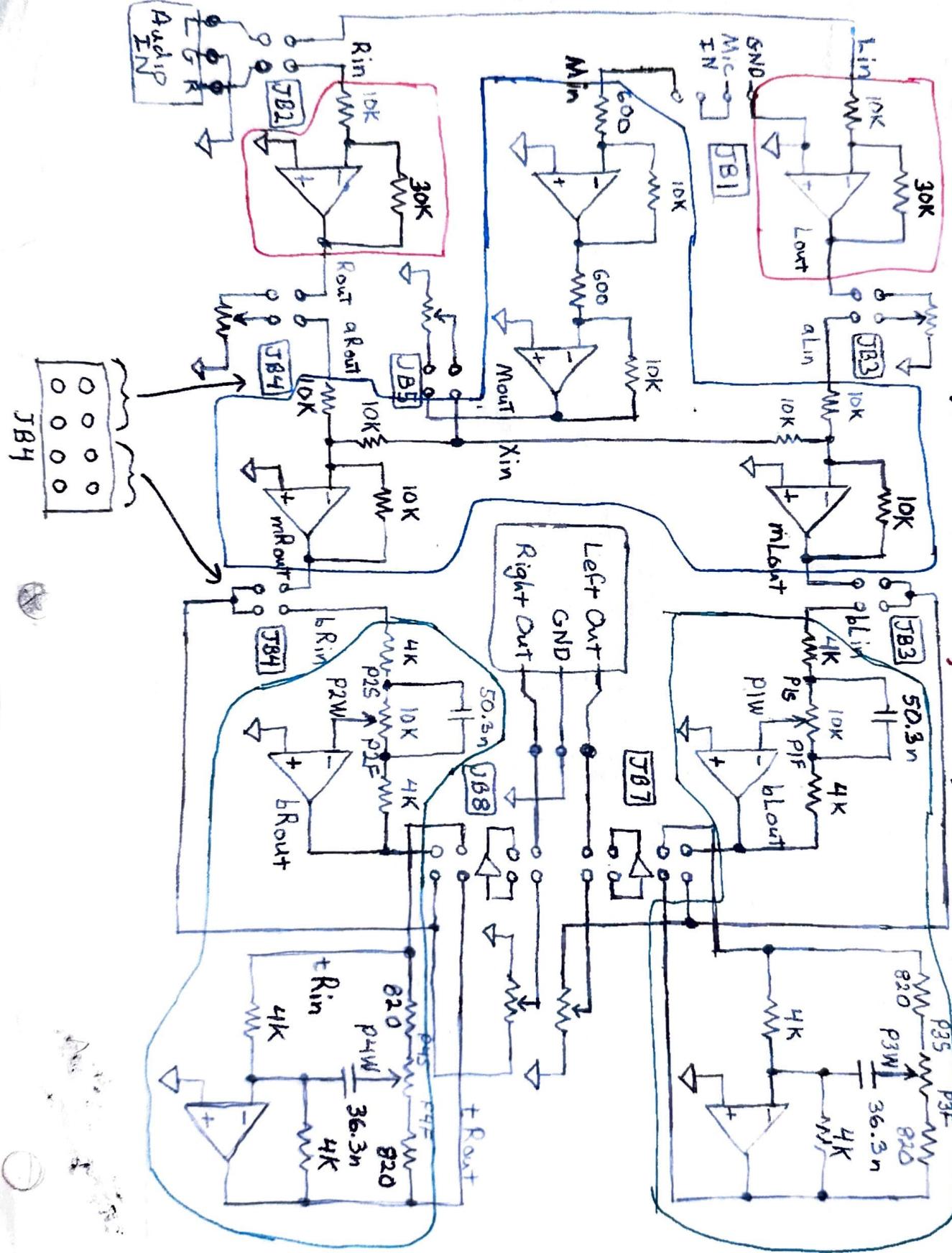
# ECEN 250 Audio Project - Buffer Board, Preamp/Mixer Board, Treble and Bass Board



Mother Board

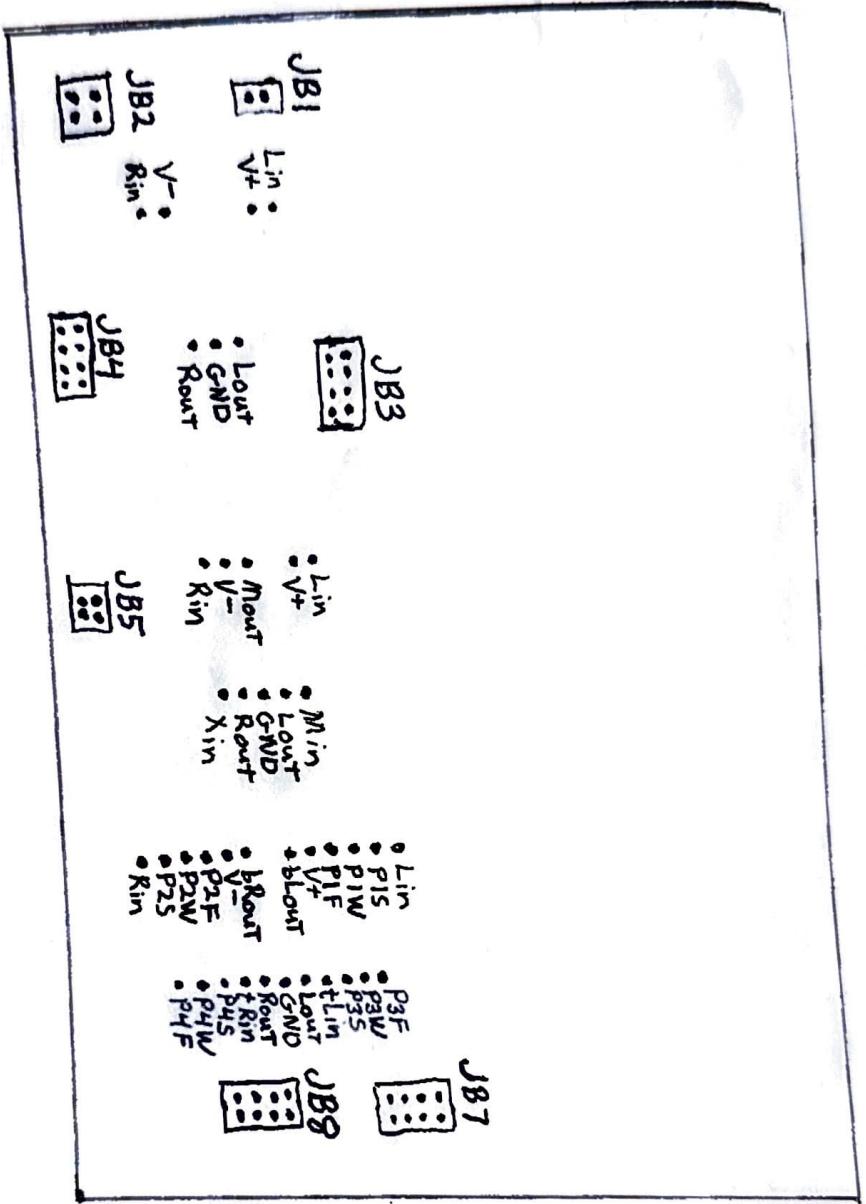

# Chapter 6

## 6.1 The inductor

- opposes change in current
- inductance measured in Henrys (H)

$$+ \xrightarrow{\frac{V}{L}} - \quad V = L \frac{di}{dt}$$


Voltage is constant  $\rightarrow$  voltage across = 0

\* Current can NOT change instantaneously

$$i(t) = \frac{1}{L} \int_0^t V dt + i(0) \quad : \text{Current}$$

$$\text{Power: } P = L i \frac{di}{dt}$$

$$\text{Energy: } W = \frac{1}{2} L I^2$$

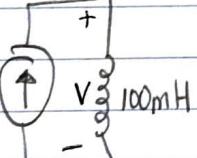
ex;   $i=0, t < 0$   
 $L = 10te^{-5t} A, t > 0$

At what time is current max?

$$\frac{di}{dt} = 10(-5te^{-5t} + e^{-5t}) = 10e^{-5t}(1-5t)$$

$$\text{when } \frac{di}{dt} = 0 \rightarrow t = 0.2s$$

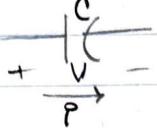6.2 The capacitor - stores electrical charge  
→ measured in Farads (F)



$$F = \frac{Q}{V}$$

Current:  $i = C \frac{dv}{dt}$

- capacitor behaves like an open circuit in constant voltage  
- voltage can't change instantaneously

Voltage:  $v(t) = \frac{1}{C} \int_{t_0}^t i d\tau + v(t_0)$


Power:  $p = vi = Cv \frac{dv}{dt}$

Energy:  $w = \frac{1}{2} Cv^2$

When power is positive → energy being stored  
negative → energy being dissipated


(6.3) Series-Parallel Combination of Conductance and Capacitance

Series

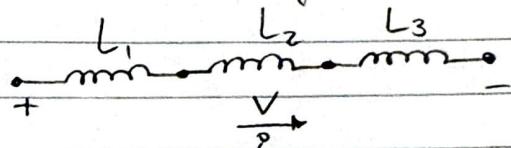

$$V = V_1 + V_2 + V_3 = (L_1 + L_2 + L_3) \frac{di}{dt} \rightarrow L_{eq} = \sum_{i=1}^n L_i$$


Parallel

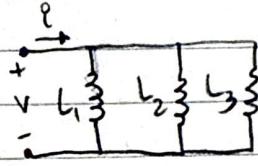

$$\frac{1}{L_{eq}} = \sum_{i=1}^n \frac{1}{L_i}$$


$$i(t_0) = \sum_{j=1}^n i_j(t_0)$$

Series

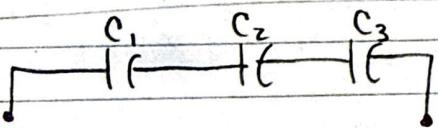


$$\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i} \quad V(t_0) = \sum_{j=1}^n V_j(t_0)$$

Parallel

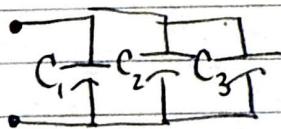


$$C_{eq} = \sum_{i=1}^n C_i$$

## [6.4] Mutual inductance

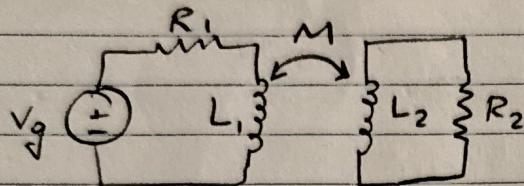


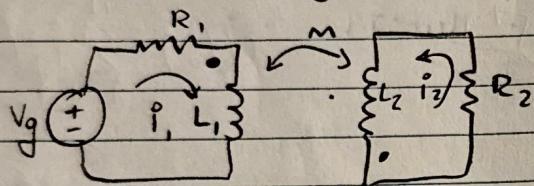Voltage across  $L_1 \rightarrow L_1 \left( \frac{di_1}{dt} \right)$   
 " "  $L_2 \rightarrow M \left( \frac{di_2}{dt} \right)$



$$\text{Mesh 1: } -V_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$$
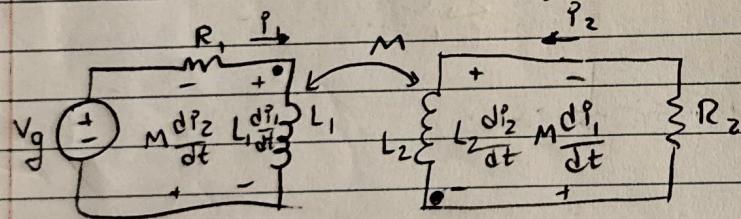
$$\text{Mesh 2: } i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$




Dot convention: When the reference direction for a current enters the dotted terminal of a coil, the reference polarity of the voltage that it induces in the other coil is positive at its dotted terminal.

$$M = K \sqrt{L_1 L_2} \quad K \rightarrow \text{"coefficient of coupling"}$$

$$W(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

A Closer look at Mutual inductance

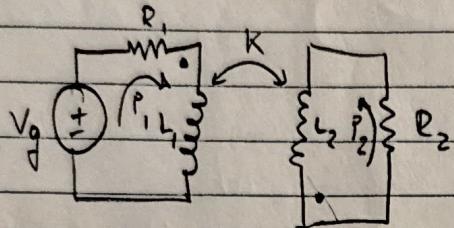

Part A Determine mutual inductance  $M$

$$L_1 = 3.0 \text{ H} ; L_2 = 2.0 \text{ H} ; R_1 = 9.0 \Omega ; R_2 = 8.0 \Omega ; k = 0.9$$

$$M = k \sqrt{L_1 L_2} = \boxed{2.20}$$

Part B Determine the energy stored in the coupled inductors at  $t = 0.2 \text{ s}$

$$K = 0.9 ; L_1 = 3.0 \text{ H} ; L_2 = 2.0 \text{ H} ; R_1 = 9.0 \Omega ; R_2 = 8.0 \Omega ; M = 0.9\sqrt{6} \text{ H}$$

$$i_1 = 6.04 \text{ A} ; i_2 = 4.25 \text{ A}$$

$$W(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

(since no t in  $i_1$  or  $i_2 \rightarrow$  doesn't matter)

$$= \boxed{16.2 \text{ J}}$$

Part C Determine energy stored at  $t = \infty$


$$i_1 = 4.74 \text{ A} ; i_2 = 2.11 \text{ A} ; K = 0.9 ; L_1 = 4.0 \text{ H} ; L_2 = 3.0 \text{ H} ; R_1 = 9.0 \Omega ; R_2 = 8.0 \Omega$$

$$W(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

$$= \boxed{20.4 \text{ J}}$$

2/14

## Mutual Inductance /

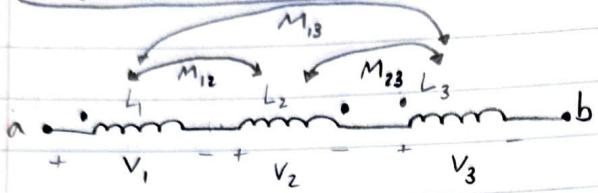

### Part A

Calculate equivalent inductance between ab

Assume  $M_{12} = M_{21} = 10.0 \text{ mH}$ ;  $M_{13} = M_{31} = 10.0 \text{ mH}$ ;  $M_{23} = M_{32} = 10.0 \text{ mH}$ ;  
 $L_1 = 3.00 \text{ mH}$ ;  $L_2 = 1.00 \text{ mH}$ ;  $L_3 = 6.00 \text{ mH}$

$$V_1 = L_1 \frac{di}{dt} - M_{12} \frac{di}{dt} + M_{13} \frac{di}{dt}$$

$$V_2 = L_2 \frac{di}{dt} - M_{12} \frac{di}{dt} - M_{23} \frac{di}{dt}$$

$$V_3 = L_3 \frac{di}{dt} + M_{13} \frac{di}{dt} - M_{23} \frac{di}{dt}$$

\* For the inductor you're on, if current enters dot, dot is +

↳ then all the other dots follow sign

↳ if current enters - terminal, subtract voltage & vice versa

$$V_T = (L_1 + L_2 + L_3) \frac{di}{dt} + (-2M_{12} + 2M_{13} - 2M_{23}) \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

$$L = \frac{V}{(i/dt)} = L_1 + L_2 + L_3 - 2M_{12} + 2M_{13} - 2M_{23} =$$


$$\boxed{-10.0 \text{ mH}}$$

3/4

11

**Part B**


Determine KVL equation for mesh 1

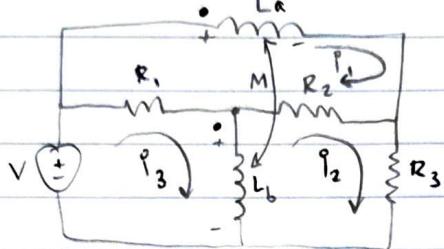

Current through inductor that produces voltage  $\rightarrow L_b$

$$\text{Mesh 1: } \boxed{L_a \frac{di_1}{dt} + R_2(i_1 - i_2) + R_1(i_1 - i_3) + M \frac{d(i_2 - i_3)}{dt} = 0}$$

minus bc respect to  $i_2$

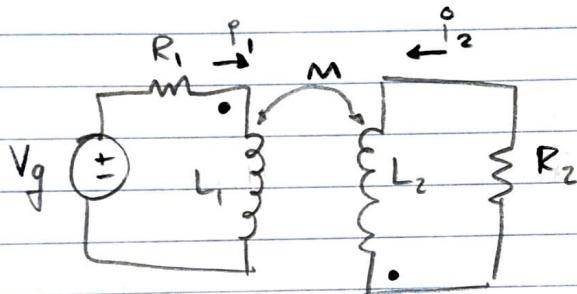**Part C**


Determine mesh equation for mesh 1.

$$\boxed{V_g = R_1 i_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}}$$

4/14

## The Capacitor

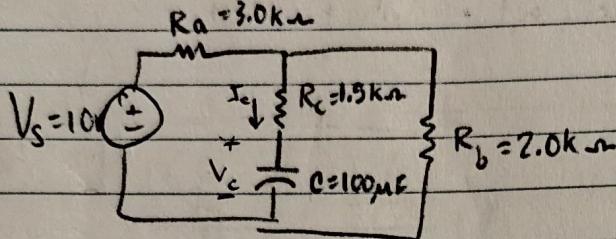**Part A** Connected for a long time. Current & voltage across capacitor?  $R_a = 3.0\text{ k}\Omega$ ;  $R_b = 2.0\text{ k}\Omega$ ;  $R_c = 1.5\text{ k}\Omega$ ;  $C = 100\mu\text{F}$ ;  $V_s = 10\text{ V}$





Capacitor under steady state  $\rightarrow$  open circuit

$$I_C = 0\text{ A} \quad V_{R_b} = V_C \rightarrow I_{R_c} = 0$$

$$V_{R_b} = 10\text{ V} \left( \frac{2.0\text{ k}\Omega}{5.0\text{ k}\Omega} \right) = 4.0\text{ V}$$


## Part B

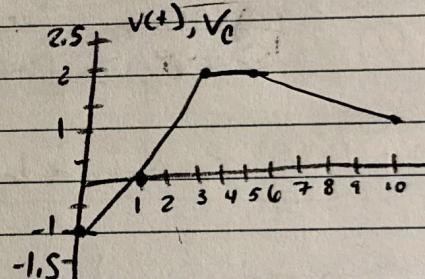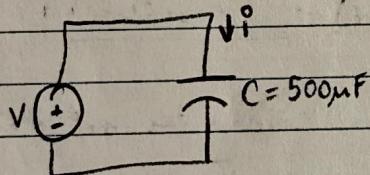


Create a sketch of current across the capacitor

$$I = C \frac{dV}{dt}$$
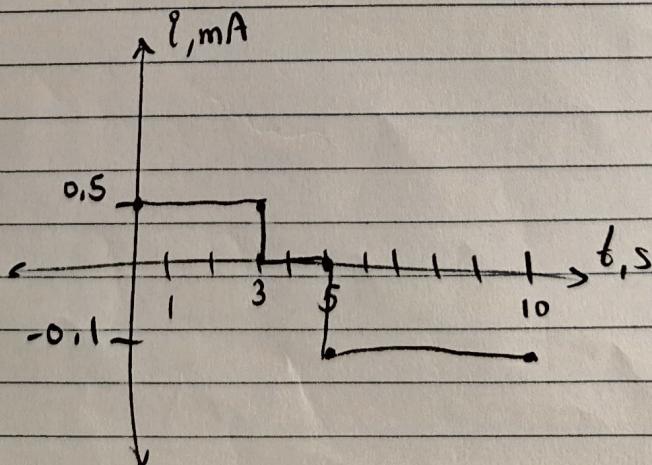
$$\frac{d(V_0)}{dt} = 1 \quad \frac{d(V_1)}{dt} = 1 \quad \frac{d(V_3)}{dt} = 0 \quad \frac{d(V_5)}{dt} = 0 \quad \frac{d(V_{10})}{dt} = -\frac{1}{5}$$




5/14

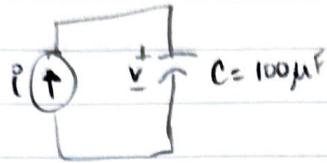Part C

$V_0 = 2V$ . If  $I(t) = 10 \cos(100t) A$ , what is  $V(t)$  across capacitor?

$$\begin{aligned} V(t) &= \frac{1}{C} \int_0^t I dt + V(t_0) \\ &= \frac{1}{100 \times 10^{-6}} \int_0^t 10 \cos(100t) dt + 1 = \left[ \frac{10}{100 \times 10^{-6}} \cdot \frac{\sin(100t)}{100} + 1 \right] = V(t) \\ &= 100 \sin(100t) + 1 \end{aligned}$$

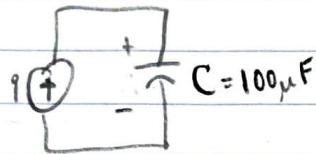Part D

What is the instantaneous power?

$$P = VI = (100 \sin(100t) + 1)(10 \cos(100t))$$


Part E Energy stored in capacitor at  $t=0$ ?

$$\begin{aligned} W &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} (100 \mu F) (100 \sin(100t) + 1)^2 \\ w(0) &= \frac{1}{2} (100 \times 10^{-6})(1) = 50 \mu J \end{aligned}$$

6/14

## The inductor

### Part A

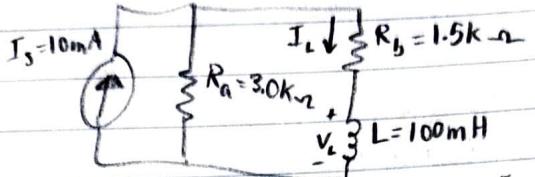



$$R_a = 3.0\text{k}\Omega; R_b = 1.5\text{k}\Omega; L = 100\text{mH}; I_S = 10\text{mA}$$

$$I_L = ? \quad V_L = ?$$


$$V_L = L \frac{di}{dt} = 0 \rightarrow \frac{di}{dt} = 0$$

$$I_L = I_S \left( \frac{R_a}{R_a + R_b} \right) = 10\text{mA} \left( \frac{3.0\text{k}\Omega}{3.0\text{k}\Omega + 1.5\text{k}\Omega} \right) = 0.67\text{mA}$$


### Part B

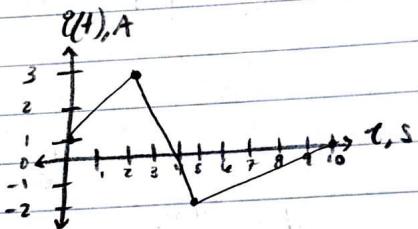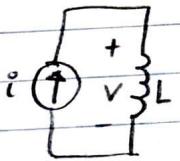

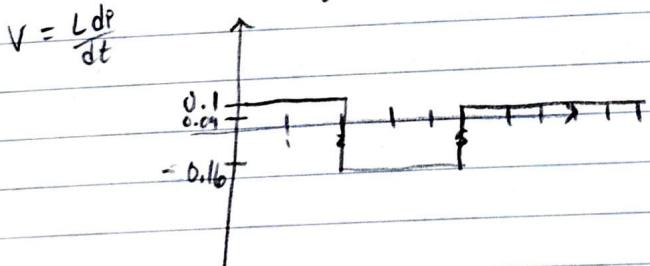Create a sketch of voltage across inductor



### Part C

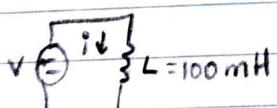

$I_0 = 10\text{mA}$ ,  $V(t) = 1e^{-10t} + 2e^{-5t} \text{V}$ , what is  $i(t)$  through inductor?

$$i(t) = \frac{1}{L} \int_0^t V(t) dt + i(0)$$

$$= \frac{1}{100 \times 10^{-3}} \cdot \int_0^t [1e^{-10t} + 2e^{-5t}] dt + 10 \times 10^{-3} / \text{A}$$

7/14


$$= \frac{1}{100 \times 10^{-3}} \cdot \left[ \frac{-e^{-10t}}{10} + \frac{-2e^{-5t}}{5} \right]_0^t + 10 \times 10^{-3} A$$

$$= \frac{1}{100 \times 10^{-3}} \cdot \left[ \left( -\frac{e^{-10t}}{10} - \frac{2e^{-5t}}{5} \right) - \left( -\frac{1}{10} - \frac{2}{5} \right) \right] + (10 \times 10^{-3})$$

$$= \frac{1}{100 \times 10^{-3}} \cdot \left[ \frac{1}{10} (-e^{-10t} - 4e^{-5t} + 5) \right] + (10 \times 10^{-3})$$

$$= -e^{-10t} - 4e^{-5t} + 5.01$$

$$q(t) = 1000 (-e^{-10t} - 4e^{-5t} + 5.01) \text{ mA}$$

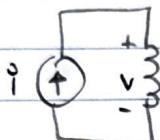**Part D**

$$L = 100 \text{ mH}$$


$$i = 2t^2 \text{ mA} = 0.002t^2 \text{ A}$$

Power absorbed?

$$P = VI$$

$$V = L \frac{di}{dt} = (100 \times 10^{-3}) \cdot (0.004t) \text{ V}$$

$$P = 0.8t^3 \mu \text{W}$$

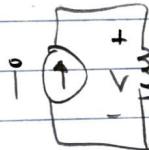**Part E**

$$L = 100 \text{ mH}$$

$$q = 2(2 - e^{-t/100}) \text{ mA}$$

$$= 2(2 - e^{-t/100}) / 1000 \text{ A}$$

$$w = \frac{1}{2} L i^2 = \frac{1}{2} (100 \times 10^{-3}) \left( \frac{4 - 2e^{-t/100}}{1000} \right)^2$$

$$= \frac{1}{2} (100 \times 10^{-3}) \left( \frac{2}{1000} \right)^2 = \boxed{200 \text{ nJ}}$$

8/14

Problem 6.3

The current in a 15 mH inductor is


$$i = 1A, t \leq 0$$

$$i = A_1 e^{-2000t} + A_2 e^{-8000t} A, t \geq 0$$

and  $V(0) = 60V$

Part A Choose expression for voltage for  $t \geq 0$

$$V = L \frac{di}{dt}$$

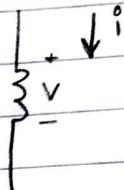

$$i(0) = 1A = A_1 + A_2$$

$$V(t) = L \left[ -2000A_1 e^{-2000t}, -8000A_2 e^{-8000t} \right]$$

$$V(t) = -30A_1 e^{-2000t} - 120A_2 e^{-8000t}$$

$$V(0) = 60 = -30A_1 - 120A_2$$

$$A_1 = 2; A_2 = -1$$

$$V(t) = -60e^{-2000t} + 120e^{-8000t}$$

Part B Find the time greater than zero, when the power at the terminals of the inductor is zero

$$P = VI = (-60e^{-2000t} + 120e^{-8000t}) / (2e^{-2000t} - e^{-8000t})$$

$$P=0 \rightarrow t = 116\mu s$$

9/14

## Problem 6.5 /

Current in a  $2H$  inductor is

$$i = 25A \quad t \leq 0$$

$$i = (B_1 \cos 5t + B_2 \sin 5t) e^{-t} \quad t \geq 0$$

Voltage across is 100V at  $t=0$

Part A Calculate power at the terminals of the inductor at  $t = 490\text{ms}$ .

$$25 = B_1 \quad i = (25 \cos 5t + B_2 \sin 5t) e^{-t}$$

$$V = L \frac{di}{dt} \quad i = 25 \cos 5t e^{-t} + B_2 \sin 5t e^{-t}$$

$$\frac{di}{dt} = -25 \cos 5t e^{-t} - 125 e^{-t} \sin 5t$$

$$+ B_2 [5 \cos 5t e^{-t} - e^{-t} \sin 5t]$$

$$V = 2 [-25 \cos 5t e^{-t} - 125 e^{-t} \sin 5t + 5B_2 \cos 5t e^{-t} - B_2 e^{-t} \sin 5t]$$

$$V = -50 \cos 5t e^{-t} - 250 e^{-t} \sin 5t + 10B_2 \cos 5t e^{-t} - 2B_2 e^{-t} \sin 5t$$

$$V(0) = 100 = -50 + 10B_2 \quad 50 = 10B_2$$

$$150 = 10B_2 \quad B_2 = 15$$

$$B_2 = 15$$

$$V = -50 \cos 5t e^{-t} - 250 e^{-t} \sin 5t + 150 \cos 5t e^{-t} - 30 e^{-t} \sin 5t$$

HAPPY  
VALENTINE'S  
DAY!

$$i = (25 \cos 5t + 15 \sin 5t) e^{-t}$$

$$P = VP$$


$$P(490\text{ms}) = 929 \text{ W}$$

With Pickle  
Isabel  
Mooney



Part B

The inductor is absorbing power.

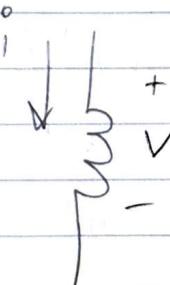

10/14


Video Solution Problem: Voltage, Current, Power, and Energy in an Inductor

Find the time when the power is maximum.

$$i_g = 18t e^{-10t} \quad v = 0.9 e^{-10t} (1 - 10t)$$

$$P = VI$$

$$P_{\max} = 0.029 \text{ s}$$

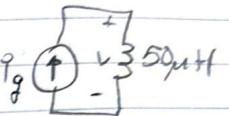

Problem (6.14)

The voltage of  $0.6 \mu\text{F}$  capacitor is zero for  $t < 0$ . For  $t \geq 0$ , the voltage is  $40e^{-15000t} \sin 30000t \text{ V}$

Part A | Find the initial current in the capacitor.

$$\frac{1}{C} \frac{dV}{dt} \quad V = \begin{cases} 0, & t < 0 \\ 40e^{-15000t} \sin 30000t, & t \geq 0 \end{cases}$$

$$i = C \frac{dv}{dt} \quad i(0) = C \frac{dv}{dt}(0) = [0.72 \text{ A}]$$

Part B | Find the power delivered to the capacitor at  $t = \frac{\pi}{80} \text{ ms}$

$$P(\frac{\pi}{8000}) = v(t)i(t) = [0.49 \text{ mW}]$$

Part C | Find energy stored at  $t = \frac{\pi}{80} \text{ ms}$

$$W = \frac{1}{2} CV^2$$

$$= \frac{1}{2} (0.6 \times 10^{-6}) (40e^{-15000t} \sin 30000t)^2$$

$$W(\frac{\pi}{80000}) = [126 \mu\text{J}]$$

11/14


Problem 6.19

The voltage across the terminals of  $400\text{nF}$  capacitor is

$$V = \begin{cases} 25\text{V}, & t \leq 0 \\ A_1 e^{-1500t} + A_2 e^{-1500t}, & t \geq 0 \end{cases}$$

The initial current is  $90\text{mA}$

Part A | What is the initial energy stored in the capacitor.

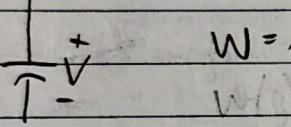  $W = \frac{1}{2} CV^2 = \frac{1}{2} (400 \times 10^{-9}) (25)^2 = [125\mu\text{J}]$

Part C | Evaluate the coefficient  $A_2$

$$25 = A_1(0)e^{-1500(0)} + A_2 e^{-1500(0)} \quad \boxed{A_2 = 25.0\text{V}}$$

Part B | Evaluate the coefficient  $A_1$

$$I = C \frac{dV}{dt} \quad \frac{dV}{dt} = A_1 \left( -1500 e^{-1500x} + e^{-1500x} \right) + 25(-1500 e^{-1500x})$$

$$I = (400 \times 10^{-9}) A_1 (- +) + (400 \times 10^{-9}) 25(-1500 e^{-1500x})$$

$$I(0) = 90 \times 10^{-3} = (400 \times 10^{-9}) A_1 + (400 \times 10^{-9})(25)(-1500)$$

$$225,000 = A_1 + 25(-1500)$$

$$\boxed{A_1 = 262,500 \text{V/S}}$$

Part D | Equation for capacitor current


$$I = (400 \times 10^{-9})(262,500)(-1500 e^{-1500x} + e^{-1500x}) + (400 \times 10^{-9})(25)(-1500 e^{-1500x})$$

$$= -157.5 \times e^{-1500x} + 0.105 e^{-1500x} + -0.015 e^{-1500x}$$

$$\boxed{I = -157.5 \times e^{-1500x} + 0.09 e^{-1500x} \text{A}}$$

12 / 14

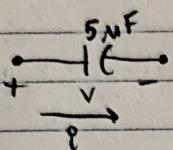Video Solution: Voltage, Current, Power in Capacitor




$$V = 500t e^{-2500t} \text{ V}$$






$$I = 2.5 e^{-2500t} (1 - 2500t) \text{ mA}$$

Find time  $t > 0$  when power is zero  
graphing  $\rightarrow t = 0.400 \text{ ms}$

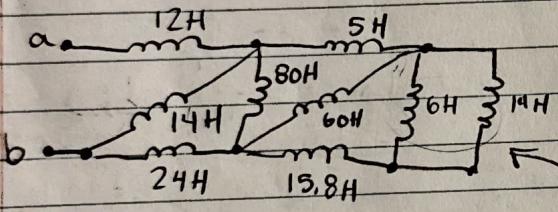Problem 6.23 Assume initial energy in inductors is zero



Part A Find equivalent inductance

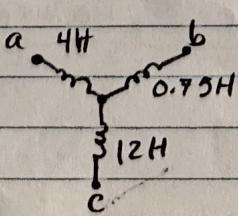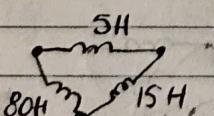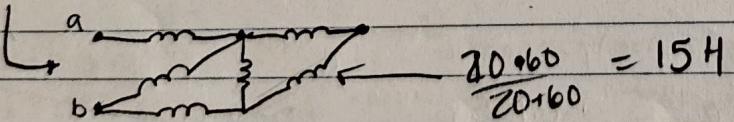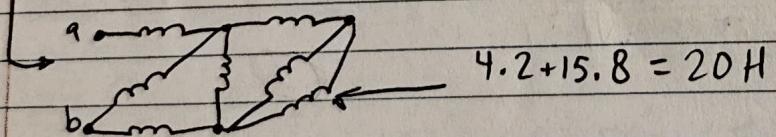
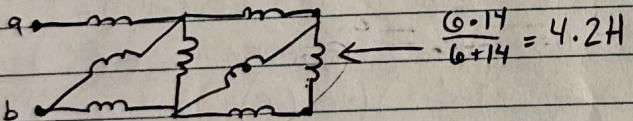


$$R_a = \frac{5+80}{100} = 4 \text{ H}$$

$$R_b = \frac{5+15}{100} = 0.75 \text{ H}$$

$$R_c = \frac{80+15}{100} = 12 \text{ H}$$





13/4

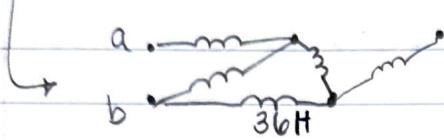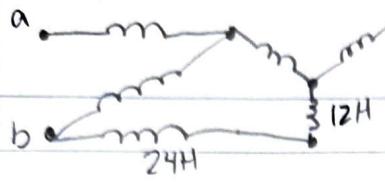

$$R_a = \frac{14+4+36}{14+4+36} = \frac{27}{28}$$

$$R_b = 9$$

$$R_c = \frac{18}{7}$$

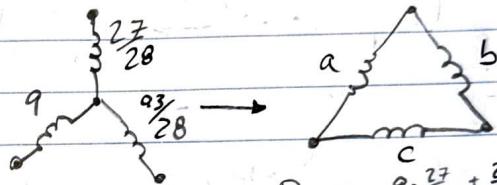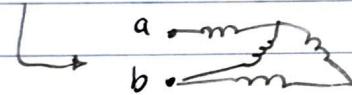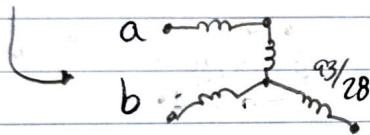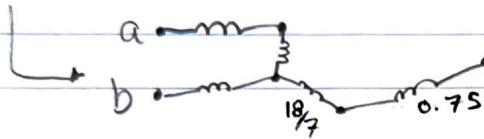


$$R_a = \frac{9 \cdot \frac{27}{28} + \frac{27}{28} \cdot \frac{93}{28} + 9 \cdot \frac{93}{28}}{\frac{9}{28}}$$

$$= \frac{10917}{868}$$

$$R_b = \frac{3639}{784}$$

$$R_c = \frac{1213}{28}$$

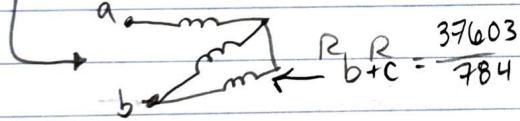

$$\frac{37603}{784} \cdot \frac{10917}{868} = \frac{279}{28}$$


$$\frac{37603}{784} + \frac{10917}{868} = \frac{279}{28}$$

$$\frac{615}{28} = 22.0 \text{ H}$$

14/14

Part B]

Find equivalent inductance

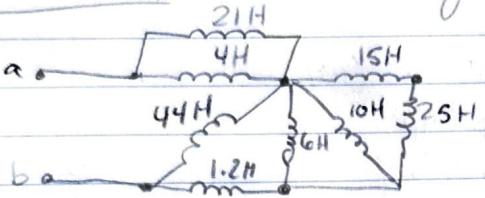

$$\xrightarrow{a \leftarrow} \frac{21+4}{21+4} = 3.36 \text{ H}$$

$$\xrightarrow{b \leftarrow} 15+25 = 40 \text{ H}$$

$$\xrightarrow{a \leftarrow} \frac{1}{40} + \frac{1}{10} + \frac{1}{6} \rightarrow L = \frac{24}{7} \text{ H}$$

$$\xrightarrow{b \leftarrow} \frac{24}{7} + 1.2 = \frac{162}{35} \text{ H}$$

$$\xrightarrow{a \leftarrow} \frac{1}{44} + \frac{1}{\frac{162}{35}} \rightarrow L = \frac{3564}{851} \text{ H}$$

$$\xrightarrow{b \leftarrow} \frac{3564}{851} + 3.36 = \boxed{7.55 \text{ H}}$$

# Chapter 9 introduction

## 9.1 The sinusoidal source


Sinusoidal voltage:  $v = V_m \cos(\omega t + \phi)$

amplitude:  $\pm V_m$

period:  $T$  (seconds)

frequency (cycles per second):  $f = \frac{1}{T}$

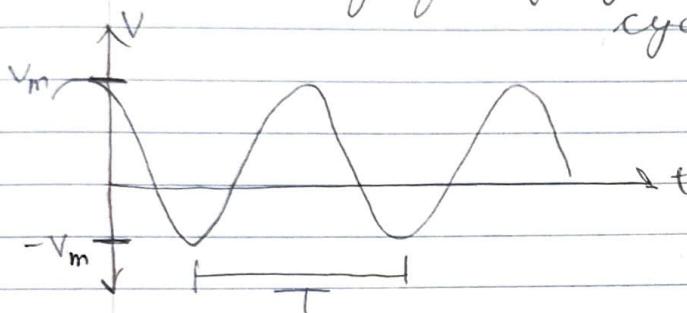cycle per second  $\rightarrow$  hertz (Hz)



angular frequency:  $\omega = 2\pi f = \frac{2\pi}{T}$  (rads/sec)

phase angle:  $\phi$

$\hookrightarrow$  determines  $t=0$

$$(\# \text{ degrees}) = \frac{180^\circ}{\pi} (\# \text{ rads})$$

$\hookrightarrow$  positive  $\rightarrow$  shift right

Negative  $\rightarrow$  shift left

$$\text{RMS value: } V_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$

$$\left\{ \text{Simplified} \right\} \rightarrow V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \quad (\text{used to calculate power})$$

$\hookrightarrow$  "root, mean, square"

$$\text{rms of } i \rightarrow I_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2 dt}$$

$$\sin(\omega t + \phi) = \cos(\omega t + \phi - 90^\circ)$$

Aleth Lewis Ricker

loves

Isabel Elisabeth Rooney Ricker


Seth  
Ricks

ECEN 250

HW#6

1/10

Problem 6.30

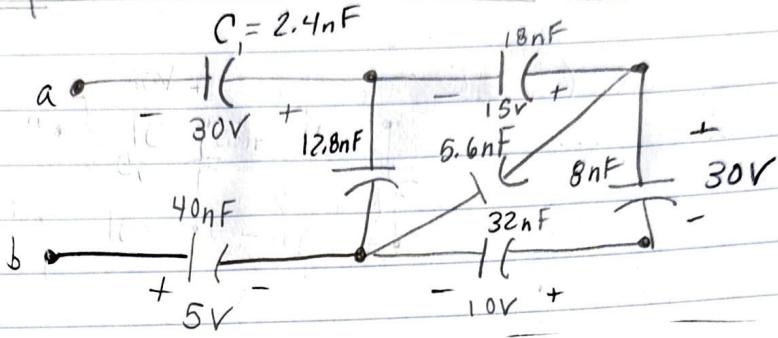

Part A / Find equivalent resistance

$$\frac{32 \cdot 8}{80} = 6.4 \text{nF}$$

$$6.4 + 5.6 = 12 \text{nF}$$


$$\frac{12 \cdot 18}{12+18} = 7.2 \text{nF}$$

$$7.2 + 12.8 = 20 \text{nF}$$

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{40} + \frac{1}{2.4} = 2.03 \text{nF} = C_{eq}$$

2/10

Part B

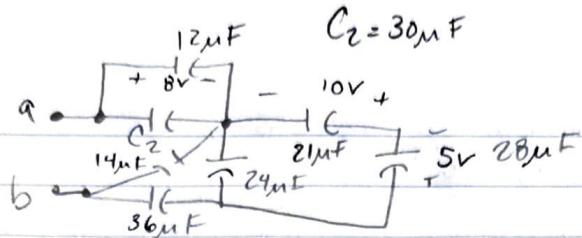

Find equivalent capacitance

$$\frac{21 \cdot 28}{21 + 28} = 12 \mu F$$

$$12 + 24 = 36 \mu F$$

$$\frac{36 \cdot 36}{36 + 36} = 18 \mu F$$



$$18 + 14 = 32 \mu F$$

$$12 + 30 = 42 \mu F$$

$$= 18.2 \mu F = C_{eq}$$

3/10

## Video : Combining Capacitors

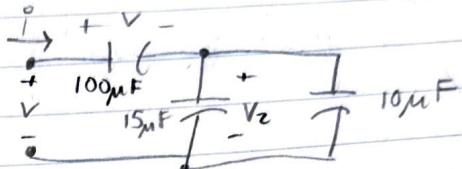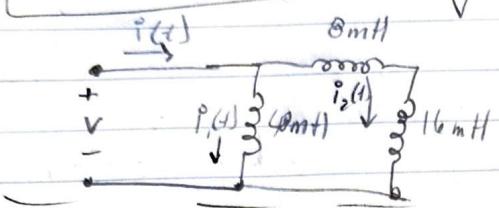

Part A / Find initial energy stored in  $C_{eq}$

$$L_{eq} = \frac{(8+16) \cdot 48}{8+16+48} = 16 \text{ mH}$$

$$W = \frac{1}{2} L I^2 \quad I = -0.4 \text{ A} \quad \rightarrow W = \frac{1}{2} (16) (-0.4)^2 \times 10^{-3} = 1.28 \text{ mJ}$$

Part B / Find initial energy stored in  $C_{eq}$



$$C_{eq} = \frac{(15+10) \cdot 100}{15+10+100} = 20 \mu\text{F}$$

$$W = \frac{1}{2} C V^2 \quad V = 5V \quad \rightarrow W = \frac{1}{2} (20 \times 10^{-6}) (5^2) = 250 \mu\text{J}$$

4/10



## Series-Parallel Combinations of Inductance & Capacitance

### Part A] Determine $L_{eq}$

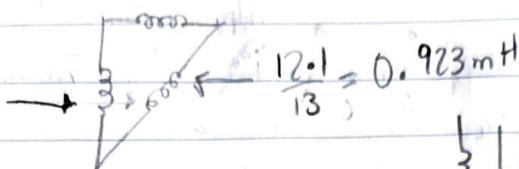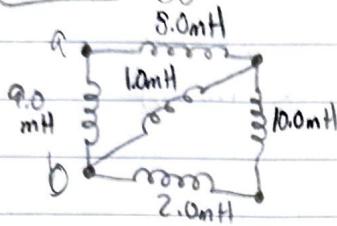


$$L_{eq} = \frac{(0.923+8) \cdot 9}{0.923+8+9} = 4.48 \text{ mH}$$

### Part B] Determine $L_{eq}$

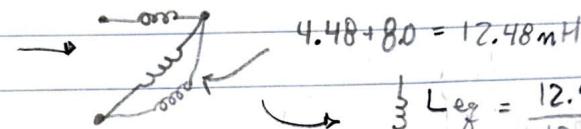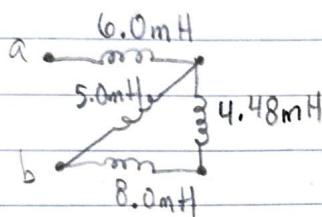


$$L_{eq} = \frac{12.48 \cdot 5}{12.48+5} + 6 = 9.57 \text{ mH}$$

### Part C] Determine $C_{ab}$

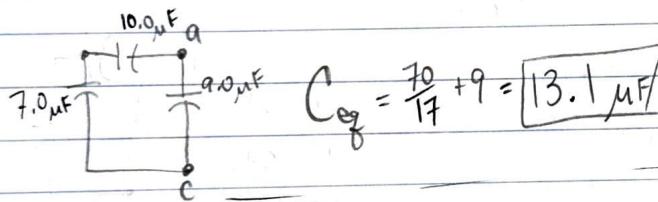


$$C_{eq} = \frac{70}{17} + 9 = 13.1 \mu\text{F}$$

### Part D] Determine $C_{bd}$

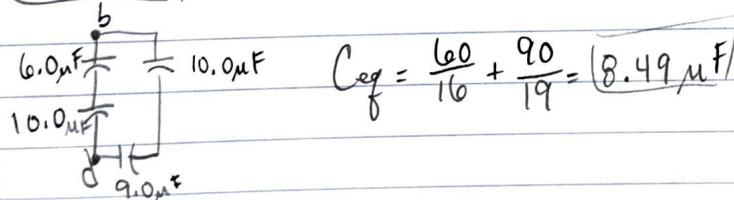


$$C_{eq} = \frac{60}{16} + \frac{90}{19} = 8.49 \mu\text{F}$$

### Part E] Determine $C_{ab}$

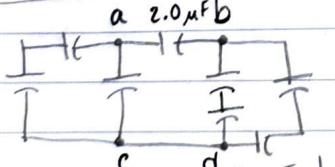

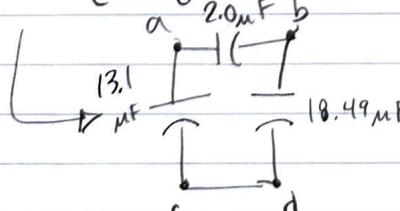
$$C_{ab} = \frac{13.1 \cdot 18.49}{13.1 + 18.49} = 3.548 \mu\text{F}$$



$$\frac{13.1 \cdot 8.49}{13.1 + 8.49} = 3.15 \mu\text{F}$$

5/10

### Part F

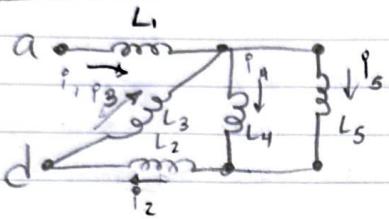


$$i_3 = -2.0 \text{ mA}, i_4 = 6.0 \text{ mA}, i_5 = 8.0 \text{ mA}, i_2 = ?$$

$$L_1 = 6.0 \text{ mH}, L_2 = 10.0 \text{ mH}, L_3 = 1.0 \text{ mH}, \\ L_4 = 7.0 \text{ mH}, L_5 = 1.0 \text{ mH}$$

$$i_2 = i_4 + i_5 = 14.0 \text{ mA}$$

$$i_1 + i_3 = i_4 + i_5 \rightarrow i_1 = i_4 + i_5 - i_3 = 6.0 + 8.0 - 2.0 = 12.0 \text{ mA}$$


### Part G

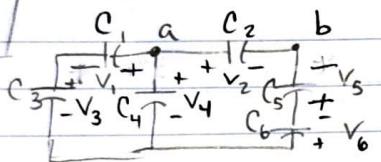

$$V_1 = -2.0 \text{ V}, V_3 = 1.0 \text{ V}, V_5 = -6.0 \text{ V}$$

$$V_6 = 7.0 \text{ V}, C_1 = 8.0 \mu\text{F}, C_2 = 3.0 \mu\text{F}, \\ C_3 = 10.0 \mu\text{F}, C_4 = 6.0 \mu\text{F}, C_5 = 5.0 \mu\text{F}, \\ C_6 = 6.0 \mu\text{F} \quad V_4 = ?$$


Determine  $V_2$  across ab

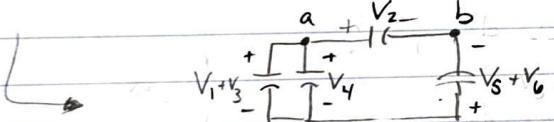

$$V_2 = V_1 + V_3 + V_5 + V_6 = 0 \text{ V}$$

6/10

Problem 6.38

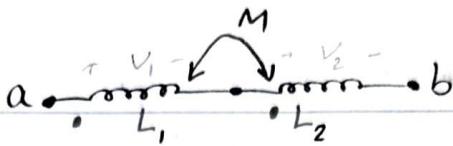

**Part A** The two coupled coils can be replaced by a single coil having an inductance of  $L_{ab}$ . Express  $L_{ab}$  in terms of  $L_1$ ,  $L_2$ , and  $M$  (Express  $V_{ab}$  as a function of  $i_{ab}$ )

$$V_1 = L_1 \frac{di}{dt} + M \frac{di_2}{dt} \quad V_2 = L_2 \frac{di}{dt} + M \frac{di_1}{dt}$$


$$V_{ab} = (L_1 + L_2 + 2M) \frac{di}{dt}$$

$$\boxed{L_{ab} = L_1 + L_2 + 2M}$$

**Part B** If  $L_2$  is Reversed, find  $L_{ab}$


$$\boxed{L_{ab} = L_1 + L_2 - 2M}$$

Problem 6.42, Part A

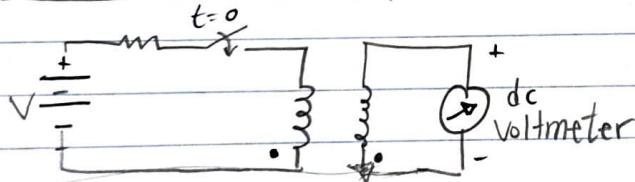

When  $t=0$ , the voltmeter is upscale. Replace the dot on the same terminal as the other, because of their positive relationship.

Video: Circuit w/ Mutually Coupled Coils

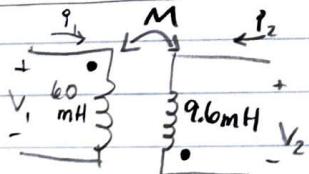

Find the energy when mutual inductance is max. ( $K=1$ )

$$W(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2 \quad i_1 = 10A; i_2 = 15A$$

$$M = K \sqrt{L_1 L_2}$$

$$= (1) \sqrt{60 \cdot 9.6} \cdot 10^{-6} = 0.024 H$$

$$= \frac{1}{2} (60 \times 10^{-3}) (10)^2 + \frac{1}{2} (9.6 \times 10^{-3}) (15)^2 - (0.024)(10)(15) \approx 0.48 J$$

$$1.2 = \checkmark - x(10)(15)$$


7/10

## Video : Analyzing Mutually Coupled Coils

Purpose of Dot Convention - Establish reference polarity

### Problem 9.1

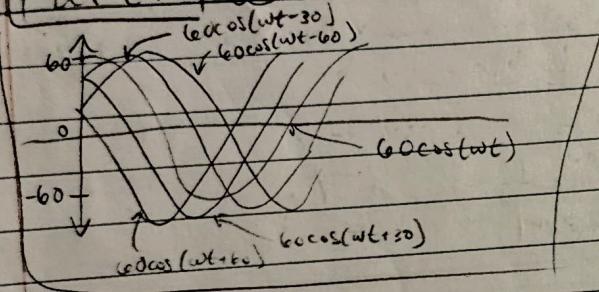**Part A** Determine sketches for  $i = 60\cos(\omega t + \phi)$  for  $\phi = 60^\circ, 30^\circ, 0^\circ, -30^\circ, -60^\circ$



**Part B** State whether the current function is shifting to the right or left as  $\phi$  becomes more negative.

→ Right as  $\phi$  becomes more negative

**Part C** What is the direction of the shift if  $\phi$  goes from  $0^\circ$  to  $30^\circ$ ?

→ Left

8/10

**Problem 9.5** Consider the sinusoidal voltage

$$V(t) = 290 \cos(120\pi t - 60^\circ) V$$

**Part A** What is the maximum amplitude of the voltage?

$$\rightarrow [290V]$$

**Part B** What is the frequency in hertz?

$$\hookrightarrow \omega = 2\pi f \rightarrow f = \frac{\omega}{2\pi} = \frac{120\pi}{2\pi} = [60.0 \text{ Hz}]$$

**Part C** What is the frequency in radians per second?

$$\hookrightarrow \omega = \frac{2\pi}{T} = \frac{2\pi}{f} = [377 \text{ rad/s}]$$

**Part D** What is the phase angle in radians?

$$-60^\circ \cdot \frac{\pi}{180} = [-1.05 \text{ rad}]$$

**Part E** Phase angle in degrees?  $\rightarrow [-60.0^\circ]$

**Part F** Period in milliseconds?  $T = \frac{1}{f} = [16.7 \text{ ms}]$

**Part G** First time after  $t=0$  that  $V=290$ ?

$$\hookrightarrow V(t) = 290 \cos(120\pi t - 60 \cdot \frac{\pi}{180})$$

$$V(t) = 290 \rightarrow [2.78 \text{ ms}]$$

**Part H** The sinusoidal function is shifted  $125/18 \text{ ms}$  to the right.  
What is the expression for  $V(t)$ ?

$$V(t) = 290 \cos(120\pi(t - \frac{125}{18}) - 60 \cdot \frac{\pi}{180})$$

$$= 290 \cos(120\pi t - \frac{25\pi}{6} - \frac{1}{3}\pi)$$

$$= 290 \cos(120\pi t - \frac{7\pi}{6}) = 290 \cos(120\pi t - \pi - \frac{1}{6}\pi)$$

$$V(t) = -290 \cos(120\pi t - \frac{\pi}{6})$$

**Part I**  $9 \text{ ms}$  shifted to the left for  $V(t) = 290 \sin(120\pi t)$

$$V(t) = 290 \cos(120\pi(t + x) - \frac{\pi}{3})$$

$$= 290 \cos(120\pi t + 120\pi x - \frac{\pi}{3})$$

$$120\pi x - \frac{\pi}{3} = -\frac{\pi}{2}$$

$$120\pi x = \frac{\pi}{6}$$

$$x = -\frac{1}{720} = -1.39 \text{ ms} \rightarrow +16.7 \text{ ms} = [15.3 \text{ ms}]$$

9/10

Problem 9.6  $V = 100\cos(240\pi t + 45^\circ) V$   
 $V = 100\cos(240\pi t + \frac{\pi}{4}) V$

Part A Find  $f$  in hertz

$$\hookrightarrow \omega = 2\pi f \quad 240\pi = 2\pi f \rightarrow f = 120 \text{ Hz}$$

Part B Find  $T$

$$\hookrightarrow T = \frac{1}{f} = \frac{1}{120} = 8.33 \text{ ms}$$

Part C Find  $V_m$

$$\hookrightarrow V_m = 100 \text{ V}$$

Part D Find  $V(0)$

$$\hookrightarrow V(0) = 70.7 \text{ V}$$

Part E Find  $\phi$  in degrees

$$\hookrightarrow \phi = 45^\circ$$

Part F Find  $\phi$  in radians

$$\hookrightarrow \phi = \frac{\pi}{4} \text{ rad}$$

Part G Find smallest positive  $t$  which  $V = 0$

$$0 = 100\cos(240\pi t + \frac{\pi}{4})$$

$$\frac{\pi}{2} = 240\pi t + \frac{\pi}{4}$$

$$\frac{\pi}{4} = 240\pi t$$

$$\cancel{100} = t = 1.04 \text{ ms}$$

Part H Find smallest positive  $t$  which  $\frac{dV}{dt} = 0$

$$\frac{dV}{dt} = -100\sin(240\pi t + \frac{\pi}{4}) \cdot 240\pi$$

$$= -24000\pi \sin(240\pi t + \frac{\pi}{4}) = 0$$

$$\sin(240\pi t + \frac{\pi}{4}) = 0$$

$$240\pi t + \frac{\pi}{4} = 0$$

$$240\pi t = -\frac{\pi}{4}$$

$$t = -1.04 \text{ ms} + \frac{\pi}{2}$$

$$\hookrightarrow t = 3.13 \text{ ms}$$

10/10

### The sinusoidal source

$$v(t) = 50 \cos(2000t - \frac{\pi}{4}) \text{ mV}$$

Part A/ Find amplitude  $\rightarrow [50 \text{ mV}]$

Part C/ Find frequency in hertz

$$2000 = 2\pi f \rightarrow f = \frac{1000}{\pi} \text{ Hz}$$

Part B/ Find Frequency in rad/sec

$$[2000 \text{ rad/sec}]$$

Part D/ Find period  $\rightarrow T = \frac{1}{f} = \frac{\pi}{1000} \text{ s} \rightarrow [T = 3.14 \text{ ms}]$

Part E/ Find phase angle in degrees  $\rightarrow [-45^\circ]$

Part F/ Find the value of the voltage source  
at  $t = 392.7 \mu\text{s}$

$$v(392.7 \mu\text{s}) = [50.0 \text{ mV}]$$

Part G/ Construct a cosine function to match  
the given plot.

$$\rightarrow i(t) = 25 \cos(1000t + 30^\circ) \text{ mA}, t \geq 0 \text{ ms}$$

$$i(0) = 21.651$$


$$21.651 = 25 \cos x$$

$$x = 30^\circ$$

$$T = (7.330 - 1.047) \times 10^{-3}$$

$$\omega = \frac{2\pi}{T} = 1000$$

## 9.2 The Sinusoidal Response

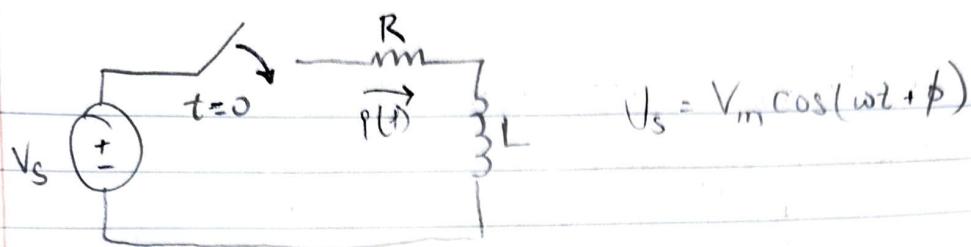

$$V_s = V_m \cos(\omega t + \phi)$$

$$L \frac{di}{dt} + RI = V_m \cos(\omega t + \phi)$$

$$i = \underbrace{\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t}}_{\text{Steady-state component}} + \underbrace{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)}_{\text{transient component}}$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

**Steady state:** cosine function, like circuit source

: frequency of solution = frequency of source

: max current amplitude =  $V_m / \sqrt{R^2 + \omega^2 L^2}$

: phase angle of current =  $\phi - \theta$ , voltage =  $\phi$

## 9.3 The Phasor

$$\text{Euler's identity } e^{\pm j\theta} = \cos \theta \pm j \sin \theta$$

$$\text{Phasor transform: } V = V_m e^{j\theta} = \underbrace{\Re\{V_m \cos(\omega t + \phi)\}}_{\text{the phasor transform of }} \xrightarrow{\text{"Frequency" domain}}$$


$$\text{Rectangular form: } V = V_m \cos \theta + j V_m \sin \theta$$

# \* Notes from 150 \*
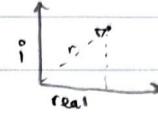
## Representation of Complex Numbers

$$Z = x + jy, \text{ where } j = \sqrt{-1}$$

polar:  $Z = r\angle\theta$ , where  $r = \sqrt{x^2 + y^2}$   
 $\theta = \tan^{-1} \frac{y}{x}$   
 $x = r\cos\theta, y = r\sin\theta$



$$\begin{aligned} a &= r\cos\theta \\ b &= r\sin\theta \\ Z &= a + jb \end{aligned}$$

$$Z = x + jy = r\angle\theta = r(\cos\theta + j\sin\theta)$$

$$Z = x + jy \quad \theta = \tan^{-1} \frac{y}{x} \rightarrow \text{1st Quad}$$

$$Z = -x + jy \quad \theta = \tan^{-1} \frac{y}{x} \rightarrow \text{2nd Quad}$$


$$Z = -x - jy \quad \theta = 180^\circ + \tan^{-1} \frac{y}{x} \rightarrow \text{3rd}$$

$$Z = x - jy \quad \theta = 360^\circ - \tan^{-1} \frac{y}{x} \rightarrow \text{4th}$$

$$\text{exponential: } Z = r e^{j\theta}, \quad r = \sqrt{x^2 + y^2}, \quad \theta = \tan^{-1} \frac{y}{x}$$

Phasors: complex number that represents amplitude and phase of a sinusoid
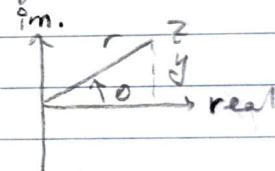
$$Z = x + jy = r\angle\theta = r(\cos\theta + j\sin\theta)$$



Operations:

$$\text{addition: } Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\text{subtraction: } Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$\text{mult: } Z_1 Z_2 = r_1 r_2 \angle (\theta_1 + \theta_2)$$

$$\text{Div: } Z_1 / Z_2 = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2)$$

$$\text{Reciprocal: } \frac{1}{Z} = \frac{1}{r} \angle -\theta$$

$$\text{Square root: } \sqrt{Z} = \sqrt{r} \angle \frac{\theta}{2}$$

$$\text{Complex conjugate: } Z^* = x - jy = r\angle -\theta = r e^{-j\theta}$$

$\hookrightarrow y^* = -y$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\cos\theta = \underbrace{\text{Re}(e^{j\theta})}_{\text{"real" part}}$$


$$\sin\theta = \underbrace{\text{Im}(e^{j\theta})}_{\text{"imaginary" part}}$$

$$V(t) = V_m \cos(\omega t + \phi)$$

$$\hookrightarrow V(t) = \text{Re}(V_m e^{j\omega t}), \text{ where } V = V_m e^{j\phi} = V_m \angle \phi$$


time-domain	phasor-domain
$v(t) = V_m \cos(\omega t + \phi)$	$V = V_m \angle \phi$

$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \phi)$	$I_m \angle \phi$
$I_m \sin(\omega t + \phi)$	$I_m \angle \phi - 90^\circ$

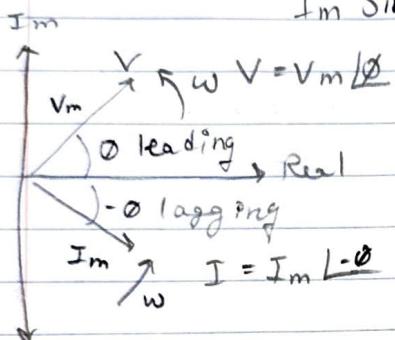

\* Can only convert cos to  $a+jb$
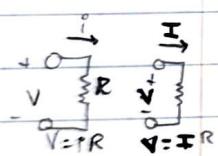
## 9.4 Phasor relationships for circuit elements



Element	Time Domain	Frequency Domain
$R$	$V = RI$	$V = R \angle 0^\circ I$

$L$	$V = L \frac{di}{dt}$	$V = j\omega L I$
-----	-----------------------	-------------------

$C$	$I = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$
-----	-----------------------	---------------------------

## 9.5 Impedance & Admittance

$$V = RI \quad V = j\omega L I \quad V = \frac{I}{j\omega C}$$

$$\rightarrow \frac{V}{I} = R \quad \frac{V}{I} = j\omega L \quad \frac{V}{I} = \frac{1}{j\omega C}$$

$$\therefore Z = \frac{V}{I} \quad \text{or} \quad V = ZI$$

$Z$  is a frequency-dependent quantity measured in ohms  
 ↳ impedance

$R = R_e(Z) \rightarrow$  resistance

$X = \text{Im}(Z) \rightarrow$  reactance

$$Z = R + jX = |Z|(\cos\theta + j\sin\theta), \text{ where } |Z| = \sqrt{R^2 + X^2}, \theta = \tan^{-1}\left(\frac{X}{R}\right)$$

$$R = |Z|\cos\theta, \quad X = |Z|\sin\theta$$



Reciprocal of impedance  $\rightarrow$  admittance, (Element (s))  
 ↳ or mhos



$$Y = \frac{G}{jB} \rightarrow$$
 susceptance

conductance

$$G + jB = \frac{1}{R + jX} \quad \text{or} \quad G = \frac{R}{R^2 + X^2} \quad \text{and} \quad B = \frac{-X}{R^2 + X^2}$$

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

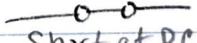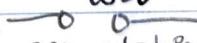Always  $X \perp 90^\circ$    $\rightarrow$    
 short at DC  
 $\omega=0$   
  
 open at high freq.  
 $\omega=\infty$

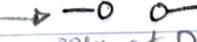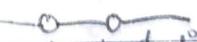
Always  $X \perp 90^\circ$    $\rightarrow$    
 open at DC  
 $\omega=0$   
  
 short at high frequencies  
 $\omega=\infty$

## 9.6 Kirchoff's Laws in the Frequency Domain

$$\text{KVL: } V_1 + V_2 + \dots + V_n = 0 \rightarrow V_1 + V_2 + V_n = 0$$

$$\text{KCL: } i_1 + i_2 + \dots + i_n = 0 \rightarrow I_1 + I_2 + \dots + I_n = 0$$


## 9.7 Impedance Combinations

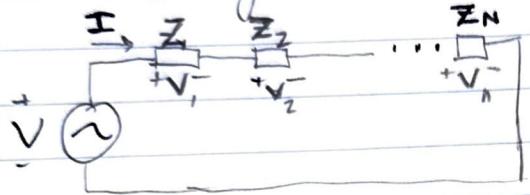

$$\text{KVL: } V = V_1 + V_2 + \dots + V_N = I(Z_1 + Z_2 + \dots + Z_N)$$

$$Z_{\text{eq}} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N$$


If  $N=2$

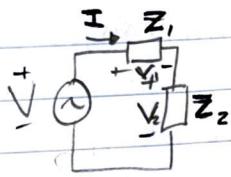

(Voltage Division)


$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

If in // :

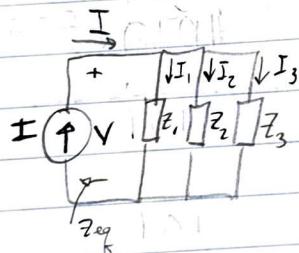

$$Y_{\text{eq}} = Y_1 + Y_2 + \dots + Y_N$$

If  $N=2$

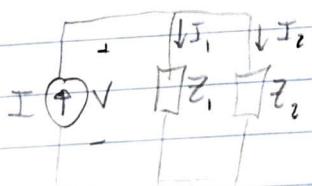

(Current Division)

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

$$Y_{\text{eq}} = Y_{\text{L0}}^{\circ}$$

$$\frac{1}{Y_{\text{eq}}} = \frac{1}{Y_{\text{L0}}^{\circ}} + \frac{1}{Y_{\text{L0}}^{\circ}} \cancel{Y_{\text{L0}}^{\circ}}$$

\* Delta-to-WYE is the same as before \*

Seth Ricks

ECEN 250

HW#7 1/8

Problem 9.7

$$V = V_m \sin \frac{2\pi}{T} t, 0 \leq t \leq T/2$$

Part A Find the rms value

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Video: Using the Phasor transform

Part A What does NOT appear in the phasor representation?  
↳ Frequency

Video: Frequency Domain of Inductor

Part A The phasor representation of an inductance corresponds to  
↳ an imaginary positive impedance

Problem 9.11

Part A

$$y = 100 \cos(300t + 45^\circ) + 500 \cos(300t - 60^\circ)$$

$$100 \angle 45^\circ + 500 \angle -60^\circ$$

$$x_1 = r \cos \theta = 100 \cos 45^\circ = \frac{100}{\sqrt{2}}$$

$$y_1 = r \sin \theta = 100 \sin 45^\circ = \frac{100}{\sqrt{2}}$$

$$x_2 = 500 \cos(-60^\circ) = 250$$

$$y_2 = 500 \sin(-60^\circ) = -250\sqrt{3}$$

$$Z_1 = \frac{100}{\sqrt{2}} + j \frac{100}{\sqrt{2}}$$

$$Z_2 = 250 + j(-250\sqrt{3})$$

$$Z_1 Z_2 = 320.71 + j(-362.30)$$

$$r = \sqrt{x^2 + y^2} = 483.86$$

$$\theta = \tan^{-1} \left( \frac{-362.30}{320.71} \right) = -48.48^\circ$$

$$y = 483.86 \cos(300t - 48.48^\circ) \checkmark$$

2/8

**Part B**

$$y = 250 \cos(377t + 30^\circ) - 150 \sin(377t + 140^\circ)$$

$$x_1 = 250 \cos 30^\circ = 125\sqrt{3}$$

$$y_1 = 250 \sin 30^\circ = 125$$

$$z_1 = 125\sqrt{3} + j125$$

$$z = 120.09 + 10.09j$$

$$r = 120.51 \quad \theta = \tan^{-1}\left(\frac{y}{x}\right) = 4.80^\circ$$

$$\boxed{y = 120.51 \cos(377t + 4.80^\circ)}$$

$$-150 \cos(377t + 50^\circ)$$

$$x_2 = -150 \cos 50^\circ = -96.42$$

$$y_2 = -150 \sin 50^\circ = -114.91$$

$$z_2 = -96.42 - 114.91j$$

**Part C**

$$y = (60 \cos(100t + 60^\circ)) - 120 \sin(100t - 125^\circ) + 100 \cos(100t + 90^\circ)$$

$$\rightarrow -120 \cos(100t - 215^\circ)$$

$$x_1 = 60 \cos 60^\circ = 30$$

$$y_1 = 60 \sin 60^\circ = 30\sqrt{3}$$

$$z_1 = 30 + 30\sqrt{3}j$$

$$x_2 = -120 \cos 215^\circ = 98.30$$

$$y_2 = -120 \sin 215^\circ = -68.83$$

$$z_2 = 98.30 - 68.83j$$

$$x_3 = 100 \cos 90^\circ = 0$$

$$y_3 = 100 \sin 90^\circ = 100$$

$$z_2 = 0 + 100j$$

$$z = 128.3 + 83.13j$$

$$r = 152.88 \quad \theta = 32.94^\circ$$

$$\boxed{y = 152.88 \cos(100t + 32.94^\circ)}$$

**Part D**

$$y = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$$

$$x_1 = 100 \cos 40^\circ = 76.60$$

$$y_1 = 100 \sin 40^\circ = 64.28$$

$$x_2 = -93.97$$

$$y_2 = 34.20$$

$$x_3 = 17.34$$

$$y_3 = -98.48$$


$$z = -0.01 + 0j$$

$$r \approx 0, \theta = 0$$

$$\boxed{y = 0}$$

3/8

Video : Circuit in Frequency Domain

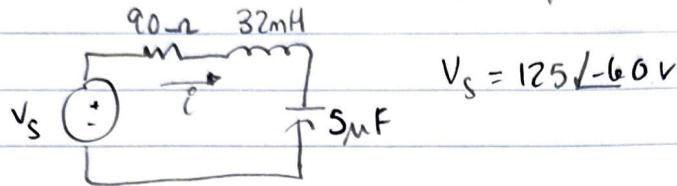

a.) Value of capacitance & current  $i$  w/ phase  $-105^\circ$

$$\theta = I_m \angle -105^\circ \text{A} \quad i = \frac{125 \angle -60^\circ}{|Z| \angle \theta_2} = \frac{125}{|Z|} \angle -60 - \theta_2$$

$$-105^\circ = -60 - \theta_2 \rightarrow \theta_2 = 45^\circ$$

Video : Impedance in Series and Parallel

Diagram of a parallel circuit consisting of a  $20\Omega$  resistor and a  $5\text{mH}$  inductor in parallel.

Combined resistance & reactance

$$\hookrightarrow Z = (Y_1 + Y_2)^{-1} = \left(\frac{1}{20} + \frac{1}{j\omega L}\right)^{-1} = \frac{j\omega L}{20 + j\omega L} \times \frac{20 - j\omega L}{20 - j\omega L}$$

x by Fancy 1

Video : Δ-to-Y in Frequency Domain

- The transformation involves only resistances

4/8

Problem 9.13 | The voltage across the terminals of a 5μF capacitor is  $22 \cos(4000t + 25^\circ)$  V

Part A Calculate the capacitive reactance.

$$Z = \frac{1}{j\omega C} = \frac{1}{j(4000)(5 \times 10^{-6})} = -50j \rightarrow -50.0 \angle -90^\circ$$

Part B Calculate impedance of capacitor

$$0 - 50.0j \angle -90^\circ$$

Part C Calculate Phasor current  $\mathbf{I}$

$$\mathbf{V} = \frac{\mathbf{I}}{j\omega C} \quad \mathbf{I} = \mathbf{V} j\omega C = 22 \angle 25^\circ \cdot j(4000)(5 \times 10^{-6})$$

- negative

$$= 0.44 \angle 115^\circ$$
$$= 0.44 \angle -65^\circ$$


Part D Find the steady state expression for the capacitor

$$i = 0.44 \angle 115^\circ \quad (\text{add } 180^\circ) \quad (\text{switch sign})$$

$$i = 0.44 \cos(4000t + 115^\circ) A$$

5/8

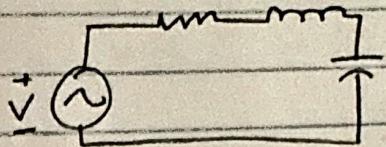Problem 9.20 A  $400\Omega$  resistor, a  $87.5\text{mH}$  inductor, and a  $3125\text{nF}$  capacitor are connected in series.  $V = 500 \cos(8000t + 60^\circ)\text{V}$



Part A Determine impedance of elements in frequency-domain

$$Z_L = j\omega L = j8000L ; Z_C = \frac{1}{j\omega C} = \frac{1}{j8000C} = -400\frac{1}{j}\Omega ; Z_R = 400\Omega$$
$$Z = 400 + 300j \rightarrow 500 \angle 36.87^\circ$$



Part B Find the phasor current

$$I_g = \dot{V}/Z = 500 \angle 60^\circ / 500 \angle 36.87^\circ = 1 \angle 23.13^\circ \text{A}$$

Part C  $i(t) = 1 \cos(8000t + 23.1^\circ) \text{A}$

6/8

## Problem 9.29

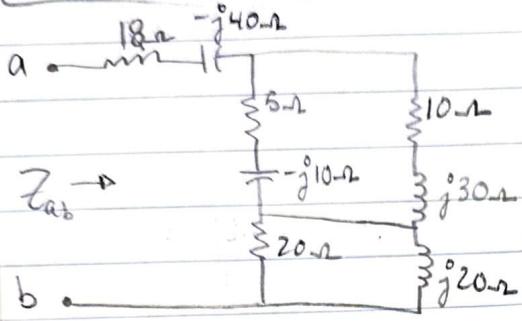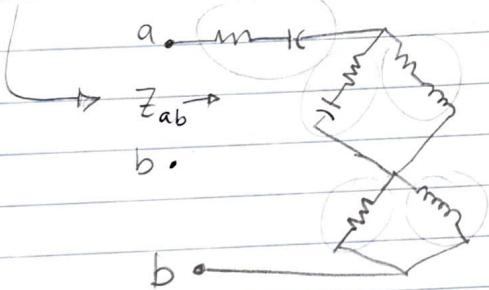Part A. Express  $Z_{ab}$  in polar form

$$\frac{(20)(j20)}{20+j20} + \frac{(5-j10)(10+j30)}{5-j10+10+j30} + 18-j40 = Z_{ab}$$

$$\frac{400j}{20+j20} + \frac{50+j150-j100+300}{15+j20} + 18-j40 = Z_{ab}$$

$$\frac{20j}{1+j} + \frac{350+j50}{15+j20} + 18-j40 = Z_{ab}$$

$$\frac{1-j}{1+j} \cdot \frac{20j}{1+j} + \frac{70+j10}{3+j4} + 18-j40 = Z_{ab}$$

$$\frac{20+j20j}{2} + \frac{70+j10}{3+j4} + 18-j40 = Z_{ab}$$

$$= 10+10j + \frac{250-j250}{25} + 18-j40 = Z_{ab}$$

$$10+10j + 10-j10 + 18-j40 = Z_{ab}$$

$$38-j40 = Z_{ab}$$

$$r = \sqrt{38^2 + (-40)^2} = 55.2$$


$$\theta = \tan^{-1}\left(\frac{-40}{38}\right) = -46.5^\circ$$

$$Z_{ab} = 55.2 \angle -46.5^\circ$$

7/8

Part B Express  $Z_{ab}$  in rectangular form  
 $[Z_{ab} = 38 - j40]$

Problem 9.37

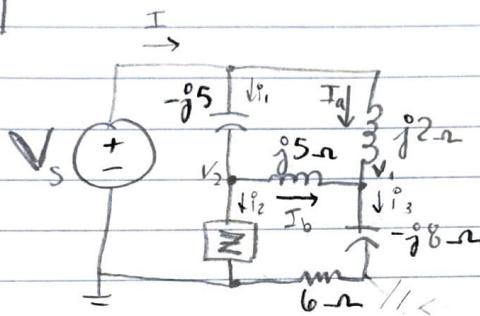

$$V_s = 80 \text{ } 0^\circ \text{ V}$$

$$I_a = 5 \text{ } -90^\circ \text{ A}$$

$$x = 5 \cos(-90^\circ) = 0$$

$$y = 5 \sin(-90^\circ) = -5 \text{ } +j0$$

Part A / Find  $I_b$

$$V_s - V_1 = (-j5)(j2) = 10 \text{ V}$$

$$V_1 = 70 \text{ V}$$

$$\frac{6+j8}{6+j8} \cdot \frac{V_1 - 0}{6-j8} = i_3 = 1 \text{ } 0^\circ$$

$$\frac{420 + 560j}{100} = i_3 = 4.2 + 5.6 \text{ } 0^\circ$$

$$i_3 = I_b + I_a$$

$$I_b = i_3 - I_a = 4.2 + 5.6 \text{ } 0^\circ - 4.2 + 5.6 \text{ } 90^\circ = 0$$

$$= 4.2 + 10.6 \text{ } 0^\circ + (5.6 \text{ } 90^\circ)$$

$$I_b = 4.2 + 10.6 \text{ } 0^\circ \text{ A}$$

Part B  $V_2 - V_1 = (4.2 + 10.6j) \cdot (j5)$

$$= 21j - 53 = -53 + 21j$$

$$V_2 = -53 + 21j + 70$$

$$V_2 = 17 + 21j$$

$$\frac{V_s - V_2}{-j5} = i_1$$

$$\frac{80 - 17 - 21j}{-j5} = i_1 = \frac{61.75 - 80j - 17j + 21}{5} = \frac{21 + 63j}{5} = 4.2 + 12.6j$$

$$\frac{V_2}{j5} = 2 + 12.6j$$

$$1.90 + 0.711j$$

8/8

$$I_1 = I_2 + I_b$$

$$I_1 = 4.2 + j12.6$$

$$I_b = 4.2 + 10.6j$$

$$I_2 = I_1 - I_b = 2j$$

$$Z = \frac{V_2}{I_2} = \frac{17+21j}{2j} \cdot \frac{-j}{j} = \frac{21-17j}{2} = |10.5-8.5j| \text{ } \angle -17^\circ$$

Class 2/26

Polar

$$20 \angle 30^\circ$$



Rectangular

$$x = 20 \cos 30^\circ = 10\sqrt{3}$$

$$10\sqrt{3} + 10j$$

$$16 \angle -130^\circ$$



$$-10.28 - 12.26j$$

$$12 + j30$$



$$32.31 \angle 68.20^\circ$$

$$16 \angle 20^\circ$$



$$2.11 \angle -138.12^\circ$$

$$-12.82$$



$$-2.16 + 0.15j$$

$$13 \angle 12^\circ$$



$$-6 \angle 16^\circ$$

Voltage Sources

$$120 \sin(60(2\pi)t + 30^\circ)$$

$$120 \cos(60(2\pi)t - 60^\circ)$$

$$120 \cos(120\pi t + 60^\circ)$$

Phasor form

$$120 \angle -60^\circ$$

$$120 \angle 60^\circ$$

$$22 \cos(100\pi t + 20^\circ) + 16 \sin(100\pi t - 60^\circ)$$

$$= 22 \cos(100\pi t + 20^\circ) + 16 \cos(100\pi t - 150^\circ)$$

$$= 22 \angle 20^\circ + 16 \angle -150^\circ = 50.07 \angle 13.22^\circ = 6.83 \angle -3.99^\circ$$

$$= [5.07 \cos(100\pi t - 13.22^\circ)] = 6.83 \cos(100\pi t - 3.99^\circ)$$

$$15 \cos(100t + 16^\circ) + 20 \cos(200t + 72^\circ)$$

$$15 \angle 16^\circ + 20 \angle 72^\circ = 34.95 \angle 19.43^\circ$$


$$= [34.95 \cos(100\pi t + 19.43^\circ)]$$

$$= 0.200 \cos(100t - 180^\circ) - 0.100 \cos(100t + 120^\circ)$$

$$= 0.2 \angle -180^\circ + -0.100 \angle 120^\circ = 0.30 \angle -176^\circ$$

$$= 0.30 \cos(100t - 176^\circ)$$
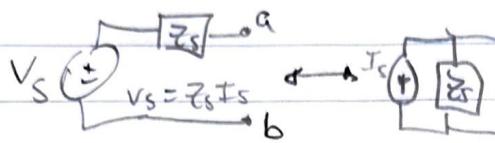
## 9.7 Source Transformation & TH equivalent



$V_s = Z_s I_s$

Same as before (for it they)  
to 1

## 9.8 Node voltage w/ frequency


↳ same as before to 1

## 9.9 Mesh Current Method

↳ same as before to 1

Just remember to  
convert!


## 9.12 Phasor Diagrams → you know this

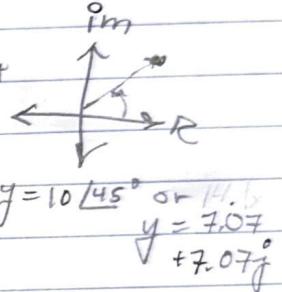
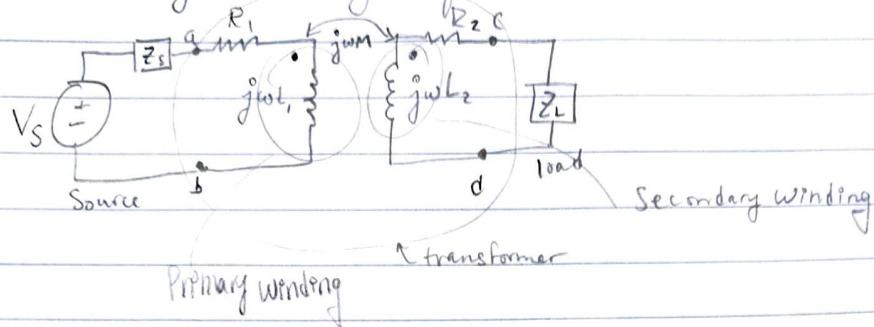
## 9.10 The Transformer (Linear)

- Used to eliminate DC signals

- Change voltage for transmission, distribution, "consumption"



$$V_s = (Z_s + R_1 + jwL_1) I_1 - jwM I_2$$

$$0 = -jwM I_1 + (R_2 + jwL_2 + Z_L) I_2$$

$$Z_{11} = Z_s + R_1 + jwL_1$$

$$Z_{22} = R_2 + jwL_2 + Z_L$$

$$\rightarrow I_1 = \frac{Z_{22}}{Z_{11} Z_{22} + w^2 M^2} V_s$$

$$\rightarrow I_2 = \frac{jwM}{Z_{22}} I_1$$

$$Z_{\text{internal}} = Z_{11} + \frac{w^2 M^2}{Z_{22}}$$

$$Z_{ab} = Z_{11} + \frac{w^2 M^2}{Z_{22}} - Z_s = \boxed{R_1 + jwL_1 + \frac{w^2 M^2}{(R_2 + jwL_2 + Z_L)}}$$

$$Z_r(\text{reflected imp.}) = \frac{w^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(wL_2 + X_L)]$$


"Reflected impedance"

Scaling factor for reflected impedance:

$$Z_{22}^* = \frac{w^2 M^2}{|Z_{22}|^2} = \frac{w^2 M^2}{|Z_{22}|^2}$$

$$Z_{22} = R_2 + R_L + j(wL_2 + X_L)$$

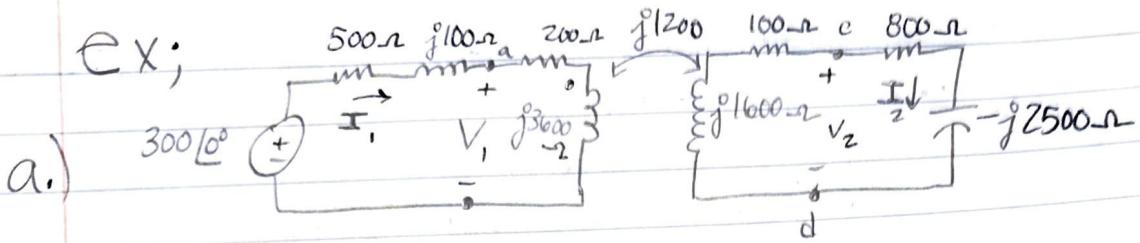( $Z_m$  is a factor of  $Z_r$  to some degree)



a.)

b.) Self-impedance of primary circuit:

$$Z_{11} = 500 + j100 + 200 + j3600 = 700 + j3700 \Omega$$

c.) Self-impedance of secondary circuit:

$$Z_{22} = 100 + j1600 + 800 - j2500 = 900 - j900 \Omega$$

d.) Impedance reflected into primary winding:

$$Z_r = \left( \frac{1200}{900 - j900} \right)^2 \cdot (900 + j900) = 800 + j800 \Omega$$

e.) Scaling factor:  $Z_{22}^* = 8/9$

f.) Impedance looking into terminals


$$Z_{ab} = 200 + j3600 + 800 + j800 = 1000 + j4400 \Omega$$

g.) Calculate the Thevenin equivalent w/ respect to the terminals of the load impedance

$$I_1 = \frac{300 \angle 0^\circ}{700 + j3700} = 79.67 \angle -79.29^\circ \text{ mA}$$

$$\begin{aligned} ? V_{Th} &= j1200 (79.67 \angle -79.29^\circ) \times 10^{-3} \\ &= 95.60 \angle 10.71^\circ \text{ V} \end{aligned}$$
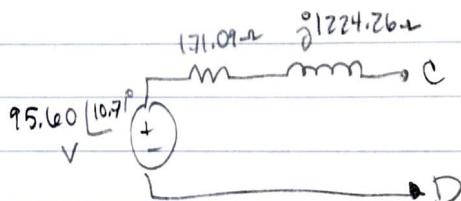
$$\begin{aligned} Z_{Th} &= 100 + j1600 + \left( \frac{1200}{700 + j3700} \right)^2 (700 - j3700) \\ &= 171.09 + j1224.26 \Omega \end{aligned}$$




# 9.11 The Ideal Transformer

ideal transformer - two coupled coils w/  $N_1$ ,  $N_2$  turns

1.) Coefficient of coupling  $\rightarrow K=1$

2.) Self-inductance of each coil is  $\infty \rightarrow L_1 = L_2 = \infty$

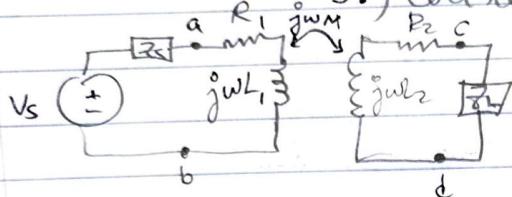3.) Coil losses due to parasitic resistance are negligible




$$Z_{ab} = R_1 + jwL_1 + \frac{w^2 M^2}{R_2 + jwL_2 + Z_L}$$

$$Z_{22} = R_2 + R_L + j(wL_2 + X_L) = R_{22} + jX_{22}$$

As  $L_1 \rightarrow \infty, L_2 \rightarrow \infty, K \rightarrow 1$


$$\begin{aligned} X_{ab} &= \left(\frac{N_1}{N_2}\right)^2 X_L \\ \frac{w^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} &= \frac{L_1}{L_2} R_{22} = \left(\frac{N_1}{N_2}\right)^2 R_{22} \\ Z_{ab} &= R_1 + \left(\frac{N_1}{N_2}\right)^2 R_2 + \left(\frac{N_1}{N_2}\right)^2 (R_L + jX_L) \end{aligned}$$

Voltage relationship :

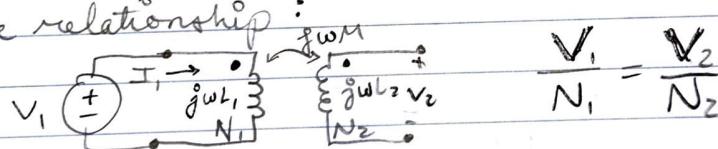


$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

Current rel. :

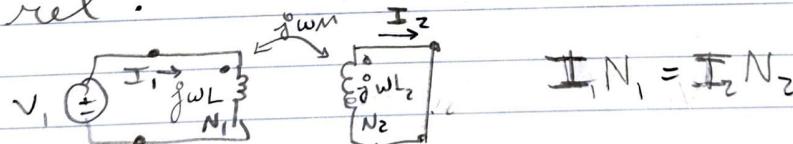

$$I_1 N_1 = I_2 N_2$$

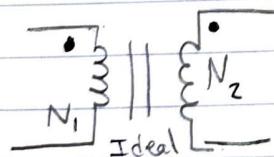

\*Symbol for  
Ideal transformer

## Dot convention for ideal Transformer

- If the coil voltages  $V_1$  &  $V_2$  are both + or both - ,

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$


- if  $I_1$  &  $I_2$  are both directed into or out of dots,

$$N_1 I_1 = -N_2 I_2$$




$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$N_1 I_1 = -N_2 I_2$$

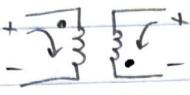

$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$N_1 I_1 = N_2 I_2$$

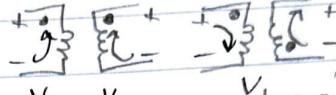

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$




$$N_1 I_1 = N_2 I_2$$

$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$


$$N_1 I_1 = -N_2 I_2$$

turn ratio :  $a = \frac{N_2}{N_1}$



3 ways to show turn ratio

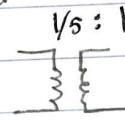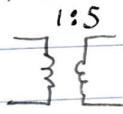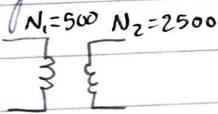
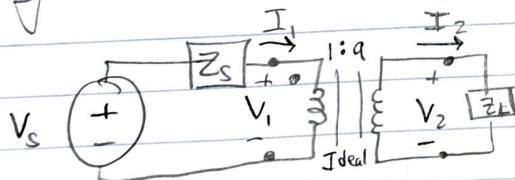
## Using an ideal Transformer for Impedance Matching


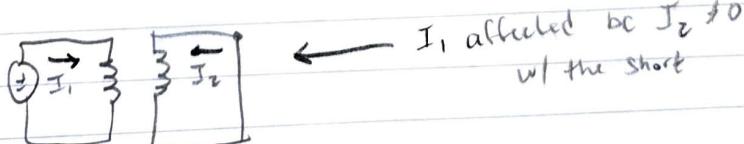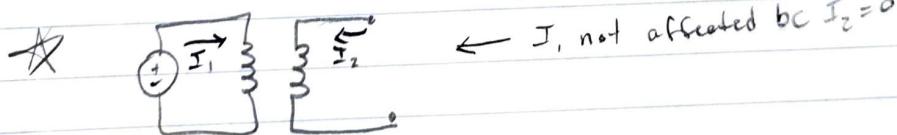
$$V_1 = \frac{V_2}{a} ; I_1 = a I_2 ; Z_{in} = \frac{1}{a^2} Z_L$$




Seth  
Ricks

ECEN 250


HW#8

1/7

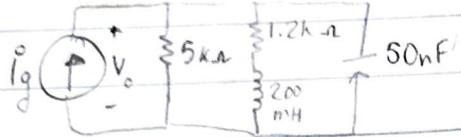Problem 9.35 The frequency of the source voltage in the circuit is adjusted so  $V_o$  is in phase with  $i_g$ .



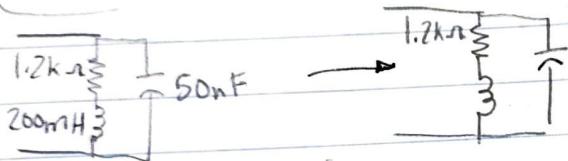Part A What is the value of  $\omega$  in rad/sec



$$Z_L = j\omega L$$

$$C = \frac{1}{j\omega C}$$

$$\begin{aligned} Y_{eq} &= \frac{1}{R + j\omega L} + j\omega C \\ &= \frac{1}{1 + (j\omega C)(R + j\omega L)} \cdot \frac{(R - j\omega L)}{(R - j\omega L)} = \frac{R - j\omega L + (j\omega C)(R + j\omega L)(R - j\omega L)}{R^2 + \omega^2 L^2} \\ &= \frac{R - j\omega L + (j\omega C)(R^2 + \omega^2 L^2)}{R^2 + \omega^2 L^2} \end{aligned}$$

$$= \frac{R}{R^2 + \omega^2 L^2} + \frac{-j\omega L + (j\omega C)(R^2 + \omega^2 L^2)}{R^2 + \omega^2 L^2}$$

$$0 = -j\omega L + (j\omega C)(R^2 + \omega^2 L^2)$$

$$= j\omega L + j\omega C R^2 + j\omega L^2 C$$

$$= WL + WCR^2 + W^3 L^2 C$$

$$0 = -L - CR^2 - W^2 L^2 C$$

$$W^2 L^2 C = -L - CR^2$$

$$W = \sqrt{\frac{L - CR^2}{L^2 C}}$$

$$= \sqrt{\frac{(200 \times 10^{-3}) - (50 \times 10^{-9})(1.2 \times 10^3)}{(200 \times 10^{-3})^2 (50 \times 10^{-9})}}$$


$$= 8,000 \text{ rad/s}$$

2/7

Part B

$$i_g = 7 \cos \omega t \text{ mA} \quad V_o(t) = V_o \cos(\omega t + \phi),$$

find  $V_o, \omega, \phi$

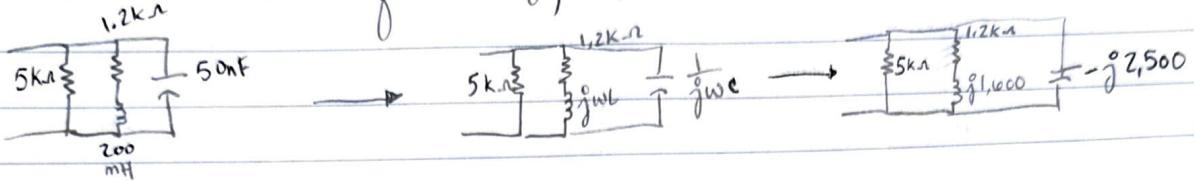

$$Z_{eg} = 5\text{k}\Omega // 1.2\text{k}\Omega + j1,600 // -j2,500$$

$$Z_{eg} = 2,000$$

$$V_o = 14 \cos(8,000t + 0)$$


(14,8000, 0)

Video: Node voltage w/ frequency

Finding  $V$  as a function of  $t$ ?

Write node-voltage equation

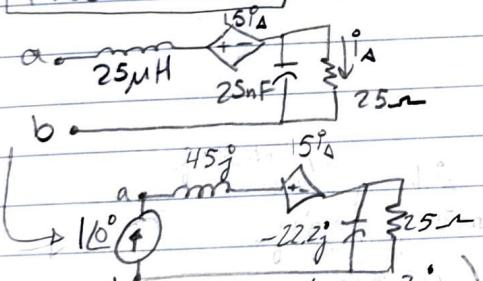Problem 9.51] Find  $Z_{ab}$  when frequency = 1.8 M rad/s



$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(1.8)(10^6)(25)(10^{-9})} = 22.2j$$

$$Z_L = j\omega L = j(1.8)(10^6)(25)(10^{-6}) = 45j$$

$$P_a = j \left( \frac{-22.2j}{25 - 22.2j} \right) = 0.441 - 0.496j$$

$$15^\circ / 10^\circ = 6.61 + 7.45j = V_{os}$$

$$15^\circ / 10^\circ = Z_{ps} = 6.61 - 7.45j$$

$$Z_{eg} = \frac{(25)(-22.2j)}{25 - 22.2j} + 6.61 - 7.45j + 45j = 17.6 + 25.1j = 30.7 \angle 58.0^\circ$$

$$V_{os} = 17.6 \text{ V}$$

$$V_{os} = 17.6 + 25.1j \text{ mV}$$

3/7

Video: Mesh method w/ frequency

Alternative for mesh current method

combine the two middle branches

Video: Source trans.


Part A] Find voltage across 30-Ω resistor

$$I = 4.47 \angle 26.565^\circ A$$




$$V_{L(t)} = I \cdot 30 = [-134.1 \cos(500t + 26.565) V]$$

Problem 9.54 /  $V_s = 80 \angle 0^\circ V$

Use node-voltage to find  $V_o$

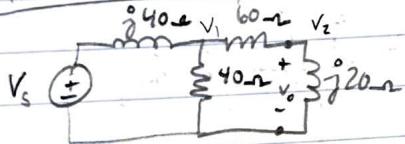

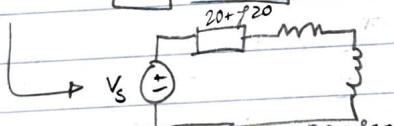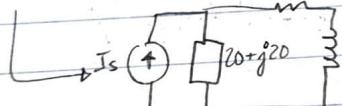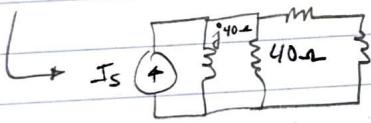
$$I_s = \frac{V_s}{Z} = \frac{80 \angle 0^\circ}{j40} = 2 \angle -90^\circ$$



$$V_s = I_s Z = 2 \angle -90^\circ \cdot (20 + j20)$$

$$= 56.57 \angle -45^\circ$$

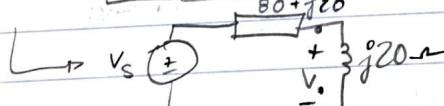


$$V_o = V_s \left( \frac{j20}{80 + j20 + j20} \right) = [12.65 \angle 18.4^\circ]$$

4/7

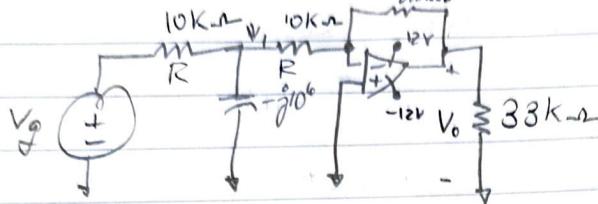Problem 9.69

$$V_g = 2.8 \cos 100t \text{ V}$$

$V(t) = V_0 \cos(\omega t + \phi)$ , where  $-180^\circ \leq \phi \leq 180^\circ$



$$1 \mu\text{F} = \frac{1}{j\omega C} = -j10^4$$

$$\begin{aligned} V_g &= 2.8 \angle 0^\circ \\ &= 2.8 + 0j \end{aligned}$$

Part A

$$\frac{V_1 - V_g}{10k\Omega} + \frac{V_1}{C} + \frac{V_1}{R} = 0$$

Find  $V_0$ 

$$\frac{V_1 - V_g}{R} + \frac{V_1}{C} + \frac{V_1}{R} = 0$$

$$\frac{V_1}{R} + \frac{V_1}{C} + \frac{V_1}{R} = \frac{V_g}{R}$$

$$V_1 \left( \frac{1}{R} + \frac{1}{C} + \frac{1}{R} \right) = \frac{V_g}{R} \rightarrow V_1 = \frac{V_g}{R} / \left( \frac{1}{R} + \frac{1}{C} + \frac{1}{R} \right) = 1.12 - 0.56j$$

2.75E-1

$$\frac{0 - V_1}{10k\Omega} + \frac{0 - V_0}{200k\Omega} = 0$$

$$\frac{-V_1}{200k\Omega} = \frac{V_1}{10k\Omega}$$

$$V_0 = \frac{-V_1}{10 \times 10^3} \cdot 200 \times 10^3 = 25.0 \angle 153^\circ$$

Part BFind  $\phi \rightarrow \phi = 153^\circ$ Part C Find  $\omega \rightarrow \omega = 100 \text{ rad/s}$

5/7

Video: Mesh method w/ frequency

Find the voltage across  $2\text{mH}$  inductor, + on left, with  $\mathbf{I}_1 = -0.8 - j1.6 \text{ A}$

$$\frac{\rightarrow}{\cancel{=}} \frac{\cancel{=}}{\cancel{=}}$$

$$Z = j\omega L = j300 \Omega$$

$$V = IZ = (-0.8 - j1.6)(j300) = -480 - 240j = 536.7 \angle -26.7^\circ$$

$$V(t) = 536.7 \cos(5000t - 26.7^\circ)$$


Video: Analyzing circuit w/ ideal transformer?

Which pair of equations is from the video?


$$\frac{V_1}{N_1} = -\frac{V_2}{N_2} \quad N_1 I_1 = -N_2 I_2$$

Video: Linear Transformer

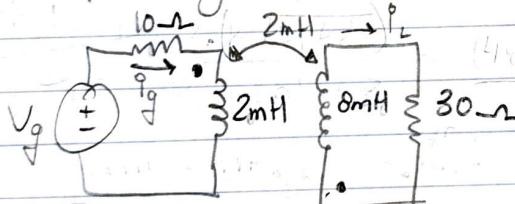Voltage across  $30\Omega$  resistor, positive at top



$$V_g = 70 \cos 5000t \text{ V}$$

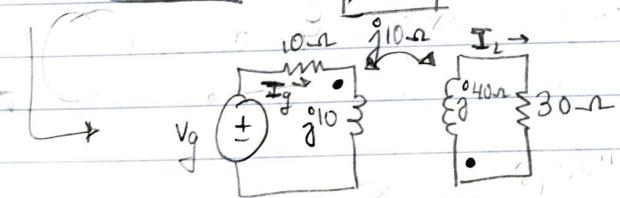

$$V_g = 70 \text{ } \textcircled{1} \text{ V}$$

$$-70 \text{ } \textcircled{1} + 10I_g + j10I_g + j10I_L = 0$$

$$30I_L + j40I_L + j10I_g = 0$$


$$I_g = 4 - j3 = 5 \angle -36.87^\circ$$

$$I_L = -1 \text{ A} = 1 \angle 180^\circ \text{ A}$$

$$V_{30\Omega} = -30 \cos(5000t + 180^\circ)$$

6/7

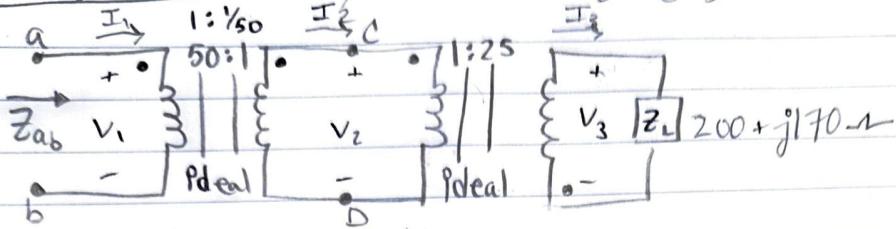Problem 9.80 / Find  $Z_{ab}$ ;  $Z_L = 200 + j170 \angle -$




$$V_1 = 50V_2$$

$$I_1 = \frac{1}{50} I_2$$

$$V_2 = -\frac{V_3}{25}$$

$$I_2 = -25 I_3$$

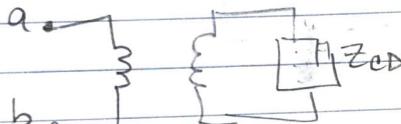
$$Z_{CD} = \left(\frac{N_1}{N_2}\right)^2 (200 + j170 \angle -) = \left(\frac{1}{25}\right)^2 (200 + j170 \angle -) = 0.32 + 0.272j$$



$$Z_{ab} = \left(\frac{N_1}{N_2}\right)^2 (0.32 + 0.272j) = (50)^2 \cdot (0.32 + 0.272j) = 800 + 680j \angle -$$

7/7

Problem 9.74

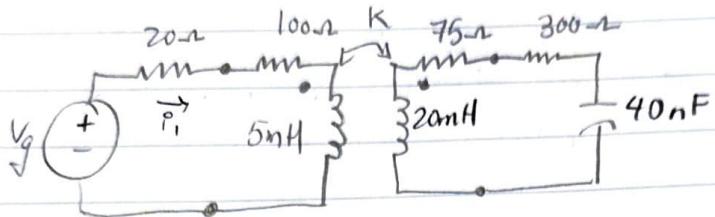

V<sub>g</sub> frequency: 48 krad/s

$$M = K\sqrt{L_1 L_2}$$

Part A What is the value of K?

$$Z_{L1} = j(5\text{mH})(48\text{k}) = j240\text{-}\Omega$$

$$Z_{L2} = j(20\text{mH})(48\text{k}) = j960\text{-}\Omega$$

$$Z_M = jK\sqrt{(5\text{mH})(20\text{mH})} \cdot 48\text{k} = jK480\text{-}\Omega$$

$$Z_C = -j\frac{1}{48\text{k}(40\text{nF})} = -j520.83\text{-}\Omega$$

$$\text{Mesh 1: } -V_g + 120i_1 + j240i_1 - jK480i_2 = 0$$

$$\text{Mesh 2: } 375i_2 - j520.83i_2 + j960i_2 - jK480i_1 = 0$$

$$i_2(375 - j520.83 + j960) = jK480i_1$$

$$i_2 = \frac{jK480i_1}{375 + j480}$$

$$\frac{V_g}{i_1} = Z_{in} = 120 + j240 + \frac{K^2 480^2}{375 + j480} = 120 + j240 + K^2(259.07 - j303.41)$$

$$\left| Z_{in} \right| = \sqrt{(120 + 259.07K^2)^2 + (240 - 303.41K^2)^2}$$

$$\frac{d|Z_{in}|}{dK} = 0 \rightarrow K = 0.512$$

Part B What is the peak amplitude of i<sub>1</sub> when  
 $V_g = 429 \cos(4.8 \times 10^4 t) \text{ V}$ ?

$$i_1 = \frac{V_g}{Z_{in}} = \frac{429 \cos(48,000t)}{120 + j240 + (0.512)^2(259.07 - j303.41)} = 1.74 \angle -40.5^\circ$$

$$|i_{1\text{peak}}| = 1.74 \text{ A}$$

## 12.1 Definition of Laplace Transform

$$F(s) = \int [f(t)]$$

→ transform from time to frequency domain


- We solve problem in frequency and then convert it back
- Functional Transform → of a specific function
- Operational " → specific math stuff

$$\mathcal{L}\{f(t)\} = \int_0^\infty f(t)e^{-st} dt \quad \begin{matrix} t \rightarrow \text{time domain} \\ s \rightarrow \text{frequency domain} \end{matrix}$$

## 12.2 The Step Function


$$Ku(t) = 0, t < 0$$

$$Ku(t) = K, t \geq 0$$

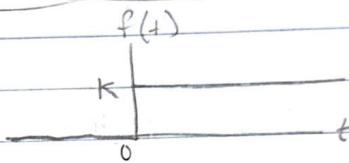


\* Not defined at  $t=0$ . If we need to, then we can say

$$Ku(0) = 0.5K$$

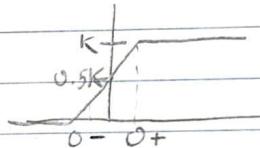

$$Ku(a-t) = k, t < a$$

$$Ku(a-t) = 0, t \geq a$$

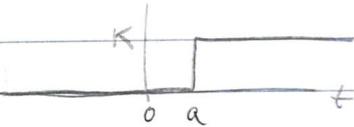


$$k \underbrace{[u(t-1) - u(t-3)]}_{\text{"turning on"}} = k, 1 < t < 3$$

"turning  
on"      "turning  
off"

ex; Using Step function for Finite Duration

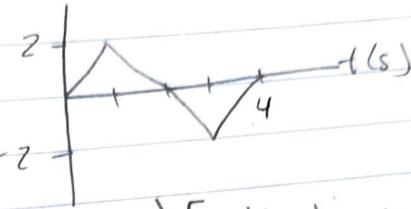
$$f(t) = \begin{cases} 0 & t \leq 0 \\ 2t & 0 \leq t \leq 1 \\ -2t+4 & 1 \leq t \leq 3 \\ 2t-8 & 3 \leq t \leq 4 \\ 0 & t \geq 4 \end{cases}$$



$$f(t) = 2t[u(t) - u(t-1)] + (-2t+4)[u(t-1) - u(t-3)] + (2t-8)[u(t-3) - u(t-4)]$$

### 12.3 The impulse Function

→ infinite amplitude, zero duration

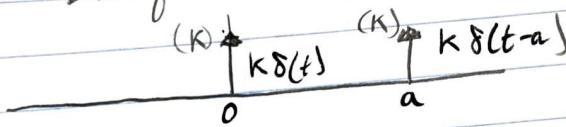


### 12.4 Functional Transform

Type	$f(t) (t > 0)$	$F(s)$
impulse	$\delta(t)$	1
step	$u(t)$	$\frac{1}{s}$
ramp	$t$	$\frac{1}{s^2}$
exponential	$e^{-at}$	$\frac{1}{s+a}$
Sine	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
Cosine	$\cos \omega t$	$\frac{1}{(s+a)^2}$
damped ramp	$t e^{-at}$	$\frac{s}{(s+a)^2}$
damped Sine	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
damped Cosine	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
	$\cosh at$	$= \frac{s}{s^2 - a^2}$
	$\sinh at$	$= \frac{a}{s^2 - a^2}$

## 12.5 Operational Transforms

Operation	$f(t)$	$F(s)$
Mult. by a constant	$Kf(t)$	$KF(s)$
Add/Sub	$f_1(t) \pm f_2(t) \dots$	$F_1(s) \pm F_2(s) \dots$
First der.	$f'(t)$	$sF(s) - f(0)$
Sec. der.	$f''(t)$	$s^2F(s) - sf(0) - f'(0)$
$n^{th}$ der.	$f^n(t)$	$s^nF(s) - s^{n-1}f(0) - s^{n-2}f'(0) - s^{n-3}f''(0) - \dots - f^{n-1}(0)$
integral	$\int_0^t f(x) dx$	$F(s)/s$
translation in time	$f(t-a)u(t-a), a > 0$	$e^{-as}F(s)$
translation in frequency	$e^{-at}f(t)$	$F(s+a)$
Scale changing	$f(at), a > 0$	$\frac{1}{a}F(\frac{s}{a})$
First der. (s)	$t f(t)$	$-F'(s)$
$n^{th}$ der. (s)	$t^n f(t)$	$(-1)^n F^{(n)}(s)$
S integral	$f(t)/t$	$\int_s^\infty F(u) du$

## 12.6 Applying the Laplace Transform

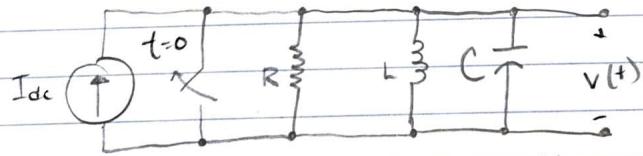

step function, current turns on at  $t=0$

Sum of currents :  $\frac{V(t)}{R} + \frac{1}{L} \int_0^t V(x) dx + C \frac{dV(t)}{dt} = I_{dc} u(t)$

Laplace Transform :  $\frac{V(s)}{R} + \frac{1}{L} \frac{V(s)}{s} + C [sV(s) - V(0)] = I_{dc} \left(\frac{1}{s}\right)$

time domain

$$V(s) = \frac{I_{dc}/C}{s^2 + (1/LC)}$$

$$V(t) = \mathcal{J}^{-1}[V(s)] \leftarrow \text{Next section}$$

$$\mathcal{J}[v] = V \quad \text{or} \quad v = \mathcal{J}^{-1}[V]$$

$$\mathcal{J}[i] = I \quad \text{or} \quad i = \mathcal{J}^{-1}[I]$$

$$\mathcal{J}[f] = F \quad \text{or} \quad f = \mathcal{J}^{-1}[F]$$

frequency domain

Seth  
Rocks

ECEN 250

HW #9

1



### The Step Function

Part A] plot function  $f(t) = 2t u(t) - 2(t-1)u(t-1) - 2(t-3)u(t-3) + 2(t-4)u(t-4)$  over  $0 \leq t \leq 5$

when  $t=0$ , all terms are 0

$t=1$ , only  $2t u(t)$  is nonzero (all others not turned on yet,  $2t u(t)$  is still on)

$$\hookrightarrow f(1) = 2$$

$t=3$ ;  $2t u(t) + -2(t-1)u(t-1)$  are on


$$\hookrightarrow f(3) = 2$$

$t=4$ , only  $2(t-4)u(t-4)$  is off (all other are on)

$$\hookrightarrow f(4) = 0$$

$t=5$ ; all terms are on

$$\hookrightarrow f(5) = 0$$

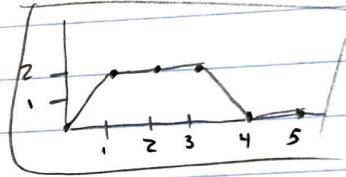

Part B] plot  $f(t) = 4u(t) - 7t u(t) + 12(t-1)u(t-1) - 8(t-2)u(t-2) + 4(t-3)u(t-3) - (t-4)u(t-4)$  over  $0 \leq t \leq 5$

$$t=0; f(0) = 4$$


$$t=1; f(1) = -3$$

$$t=2; f(2) = 2$$

$$t=3; f(3) = -1$$


$$t=4; f(4) = 0$$

$$t=5; f(5) = 0$$

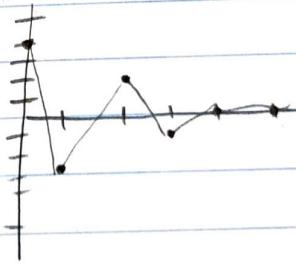

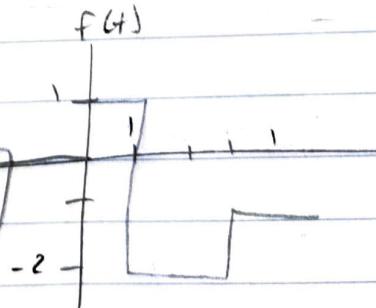Part C] make function for graph


$$f(t) = 1u(t) - 1u(t-1) + -2u(t-1) + 2u(t-3) - 1u(t-3)$$



(2)


### Problem 12.1

#### Part A

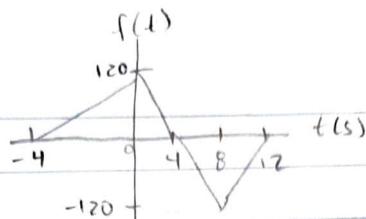


$$f(t) = (120 + 30t)[u(t+4) - u(t)] + (120 - 30t)[u(t) - u(t-8)] + (30t - 360)[u(t-8) - u(t-12)]$$

#### Part B

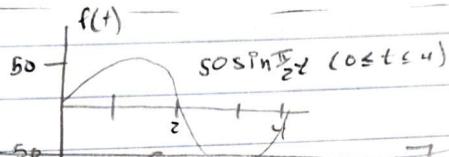

$$f(t) = (50 \sin \frac{\pi}{2} t)[u(t) - u(t-4)]$$


#### Part C

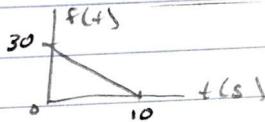

$$f(t) = (30 - 3t)[u(t) - u(t-10)]$$

### Problem 12.4

#### Part A

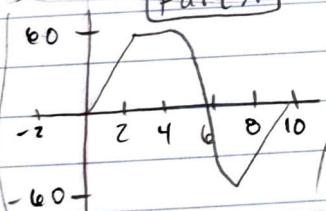

$$\begin{aligned} f(t) &= 0 \\ &= 30t \\ &= 60 \\ &= 60 \cos\left(\frac{\pi}{4}t - \pi\right) \\ &= 30t - 300 \\ &= 0 \end{aligned}$$

$$\begin{aligned} t \leq 0; \\ 0 \leq t \leq 2s \\ 2s \leq t \leq 4s \\ 4s \leq t \leq 8s \\ 8s \leq t \leq 10s \\ 10s \leq t \leq 00 \end{aligned}$$

#### Part B

$$\begin{aligned} f(t) &= 30t[u(t) - u(t-2)] + 60[u(t-2) - u(t-4)] + 60 \cos\left(\frac{\pi}{4}t - \pi\right)[u(t-4) - u(t-8)] \\ &\quad + (30t - 300)[u(t-8) - u(t-10)] \end{aligned}$$

(3)

## The Impulse Function

### Part A

$$f(t) = \begin{cases} 0, & t < -\epsilon \\ \frac{1}{2\epsilon}t, & -\epsilon < t < \epsilon \\ 1, & t > \epsilon \end{cases}$$

→ The total area under the first derivative is 1  
 In the limit  $\epsilon \rightarrow 0$ , the first derivative is zero everywhere except  $t=0$

### Part B

$$\int_{-\infty}^{\infty} (8t+7) \delta(t-4.0) dt$$

$$= 8(4.0) + 7 = 39$$

Problem 12.6 Explain why the following function generates an impulse function as  $\epsilon \rightarrow 0$

$$f(t) = \frac{e/\pi}{\epsilon^2 + t^2}, -\infty \leq t \leq \infty$$

\* As  $\epsilon \rightarrow 0$  the amplitude  $\rightarrow \infty$ ; and the area is independent of  $\epsilon$   
 i.e.  $A = \int_{-\infty}^{\infty} \frac{e}{\pi} \frac{1}{\epsilon^2 + t^2} dt = 1$

(4)

Problem 17.13 | Find Laplace Transform

Part A |  $f(t) = t$

$$\mathcal{L}[f(t)] = \left[ \frac{1}{s^2} \right]$$

Part B |  $f(t) = te^{-at}$

$$\mathcal{L}[f(t)] = \left[ \frac{1}{(s+a)^2} \right]$$

Part C |  $f(t) = \sin \omega t$

$$\mathcal{L}[f(t)] = \left[ \frac{\omega}{s^2 + \omega^2} \right]$$

Part D |  $f(t) = \cosh \beta t$

$$\mathcal{L}[f(t)] = \left[ \frac{s}{s^2 - \beta^2} \right]$$

Part E |  $f(t) = \sinh \beta t$

$$\mathcal{L}[f(t)] = \left[ \frac{\beta}{s^2 + \beta^2} \right]$$

Video : Partial Fraction

If  $f(s)$  is a rational function where the num. and denom. are of the same order, the  $\mathcal{L}^{-1}[f(s)]$  will always contain  
 ↳ [an impulse function]

Video : Partial Fraction

When the denominators of two terms in a partial fraction are complex conjugates, the associated  
 ↳ [also complex conjugates]

Video : Partial Fraction

Evaluating  $F(s)(s+1)$  at  $s = -1 \rightarrow$  why NOT zero?


↳ [Because  $F(s)$  has  $(s+1)$  in denominator]

Video | when  $(s+a)^2$  in denominator, what denominators in expansion?

↳  $(s+a)$  and  $(s+a)^2$

(5)

### Problem 12.28

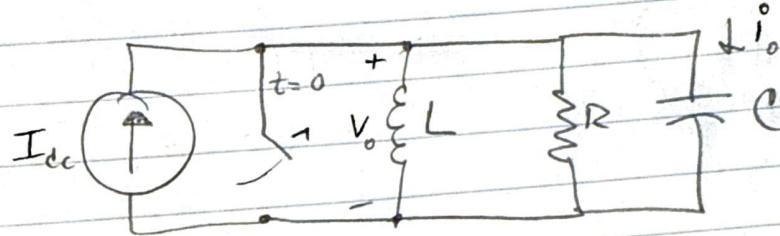

**Part A** Derive the integrodifferential equation that governs the behavior of the voltage  $V_o$ .

$$\int_0^t V_o(x) dx + \frac{V_o(t)}{R} + C \frac{dV_o(t)}{dt} = I_{dc} u(t)$$

**Part B**, find  $V_o(s)$

$$I[s] \rightarrow \frac{V(s)}{R} + \frac{1}{L} \frac{V(s)}{s} + C[sV(s) - V(0)] = I_{dc} \left( \frac{1}{s} \right)$$

$$V(s) = \frac{\frac{I_{dc}}{C}}{s^2 + (\frac{1}{RC})s + (\frac{1}{LC})}$$

**Part C**



$$I_o(s) = C \frac{dV_o(t)}{dt} \\ = C [sV(s) - V(0)]$$

$$= \boxed{\frac{I_{dc}s}{s^2 + (\frac{1}{RC})s + (\frac{1}{LC})}}$$

6

Problem 12.29

Part A

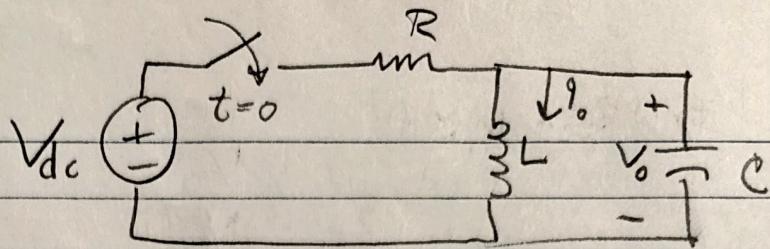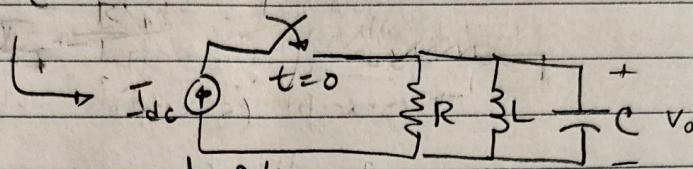Find  $V_0$  for  $t \geq 0$ 

$$I_{dc} = \frac{V_0}{R} + \frac{1}{L} \int_0^t V_0(x) dx + C \frac{dV_0}{dt}$$

$$V_{dc} = V_0 + \frac{R}{L} \int_0^t V_0 dt + RC \frac{dV_0}{dt} \quad \rightarrow (V_{dc} u(t))$$

Part B Find  $V_0(s)$ 

$$\frac{V_{dc}}{s} \rightarrow \frac{V_{dc}}{s} = V(s) + R/L \frac{V(s)}{s} + RC [sV(s) - V(0)]$$

$$\frac{V_{dc}}{s} V(s) + V(s) \left( \frac{R}{Ls} \right) + V(s) (RCs) - RCV(0)$$

$$\frac{V_{dc}}{s} = V(s) \left[ 1 + \frac{R}{Ls} + RCs \right]$$

$$V(s) = \frac{V_{dc}}{s + \frac{R}{L} + RCs^2}$$

Part C Find  $I_0(s)$ 

$$I_0 = \frac{1}{L} \int_0^t V_0(x) dx$$

$$I[I_0] = I_0 = \frac{1}{L} \frac{V(s)}{s} = \frac{V_{dc}}{s + \frac{R}{L} + RCs^2} \cdot \frac{1}{Ls} = \boxed{\frac{V_{dc}}{Ls^2 + Rs + RCLs^3}}$$

Video: Initial &amp; Final Value Theorem

If  $f(t)$  is the  $\mathcal{L}^{-1}[F]$ , then by the final value theorem, the long-term, steady-state value of  $f(t)$  equals  
 $\hookrightarrow$  the value of  $sF(s)$  as  $s$  approaches 0

# 12.7 inverse laplace

$u(t)$  is bc it is a real-world problem that starts at  $t=0$ !

Root type

Distinct real

repeated real

Distinct complex

Repeated complex

$$F(s)$$

$$\frac{K}{s+a}$$

$$\frac{K}{(s+a)^2}$$

$$\frac{K}{s+\alpha - j\beta} + \frac{K^*}{s+\alpha + j\beta}$$

$$\hookrightarrow \frac{K}{(s+\alpha - j\beta)^2} + \frac{K^*}{(s+\alpha + j\beta)^2}$$

$$f(t)$$

$$Ke^{-at} u(t)$$

$$Kte^{-at} u(t)$$

$$2|K| e^{-\alpha t} \cos(\beta t + \phi) u(t)$$

$$2t|K| e^{-\alpha t} \cos(\beta t + \phi) u(t)$$

$$\text{General: } \frac{K}{(s+a)^r}$$

$$\frac{Kt^{r-1} e^{-at}}{(r-1)!} u(t)$$

Partial fractions:

$$1.) \frac{Px+q}{(x-a)(x-b)}, a \neq b \quad \frac{A}{x-a} + \frac{B}{x-b}$$

$$2.) \frac{Px+q}{(x-a)^2} \quad \frac{A}{x-a} + \frac{B}{(x-a)^2}$$

$$3.) \frac{Px^2+qx+r}{(x-a)(x-b)(x-c)} \quad \frac{A}{x-a} + \frac{B}{x-b} + \frac{C}{x-c}$$

$$4.) \frac{Px^2+qx+r}{(x-a)^2(x-b)} \quad \frac{A}{x-a} + \frac{B}{(x-a)^2} + \frac{C}{x-b}$$

$$5.) \frac{Px^2+qx+r}{(x-a)(x^2+bx+c)} \quad \frac{A}{x-a} + \frac{Bx+C}{x^2+bx+c}$$

Non-factorable

$$6.) \frac{A(s+z_1)}{(s+\alpha - j\beta)(s+\alpha + j\beta)} = \frac{K}{s+\alpha - j\beta} + \frac{K^*}{s+\alpha + j\beta}$$

$$7.) \frac{A(s+z_1)}{(x+j\beta)^r} = \frac{K}{(s+\alpha - j\beta)^r} + \frac{K^*}{(s+\alpha + j\beta)^r}$$

# Klausur Ricks

$$\text{ex: } F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+16)} = \frac{120}{s} + \frac{48}{s+16} - \frac{72}{s+8}$$

$$f(t) = \mathcal{J}^{-1}[F(s)] = (120 - 78e^{-8t}, 48e^{-16t}) u(t)$$

$$\text{ex: } F(s) = \frac{100(s+3)}{(s+4)(s^2+6s+25)} = \frac{-12}{s+4} + \frac{6+8i}{s+3+4i} + \frac{6-8i}{s+3-4i} = \frac{-12}{s+4} + \frac{10\angle -53.13^\circ}{s+3+4i} + \frac{10\angle 53.13^\circ}{s+3-4i}$$

$$f(t) = \mathcal{J}^{-1}[F(s)] = [-12e^{-4t} + 20e^{-3t} \cos(4t - 53.13^\circ)] u(t)$$

$$\text{ex: } F(s) = \frac{100(s+25)}{s(s+5)^3} = \frac{20}{s} - \frac{400}{(s+5)^3} - \frac{100}{(s+5)^2} - \frac{20}{s+5}$$

$$f(t) = \mathcal{J}^{-1}[F(s)] = [20 - 200t^2 e^{-5t} - 100t e^{-5t} - 20e^{-5t}] u(t)$$

$$\text{ex: } F(s) = \frac{768}{(s^2+6s+25)^2} = \left[ \frac{-12}{(s+3-j4)^2} + \frac{-12}{(s+3+j4)^2} \right] + \left[ \frac{31\angle 90^\circ}{s+3-j4} + \frac{31\angle -90^\circ}{s+3+j4} \right]$$

$$f(t) = \mathcal{J}^{-1}[F(s)] = [-24te^{-3t} \cos 4t + 6e^{-3t} \cos(4t - 90^\circ)] u(t)$$

## 12.8 Poles and Zeros of $F(s)$

$$F(s) = \frac{k(s+z_1)(s+z_2) \dots (s+z_n)}{(s+p_1)(s+p_2) \dots (s+p_m)}$$

$-p_1, -p_2, -p_3, \dots, -p_m \rightarrow$  poles of  $F(s)$

$-z_1, -z_2, -z_3, \dots, -z_n \rightarrow$  zeros of  $F(s)$

## 12.9 Initial- and Final-Value Theorems

$$\text{Initial Value Theorem: } \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

$$\text{Final-Value Theorem: } \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

SETH  
RICKS

ECEN 250

HW#10 1

Problem 12.42

Part A

$$\text{Find } f(t) \text{ for } F(s) = \frac{6s^2 + 26s + 26}{(s+1)(s+2)(s+3)} = \frac{3}{s+1} + \frac{2}{s+2} + \frac{1}{s+3}$$

$$f^{-1}[F(s)] = [3e^{-t} + 2e^{-2t} + e^{-3t}] u(t) = f(t)$$

$$\text{Part B} \quad \text{Find } f(t) \text{ for } F(s) = \frac{13s^3 + 134s^2 + 392s + 200}{s(s+2)(s^2 + 10s + 24)} = \frac{6}{s} + \frac{4}{s+2} + \frac{2}{s+4} - \frac{1}{s+6}$$

$$f^{-1}[F(s)] = [6e^{-t} + 4e^{-2t} + 2e^{-4t} + e^{-6t}] u(t) = f(t)$$

$$\text{Part C} \quad \text{Find } f(t) \text{ for } F(s) = \frac{10(s^2 + 11s)}{(s+5)(s^2 + 10s + 169)}$$

$$= \frac{10}{s+5} + \frac{-25j}{s+5+12j} + \frac{25j}{s+5-12j} = \frac{10}{s+5} + \frac{4.17 \angle -90^\circ}{s+5+12j} + \frac{4.17 \angle 90^\circ}{s+5-12j}$$

$$f^{-1}[F(s)] = f(t) = [10e^{-5t} - 8.33e^{-5t} \cos(12t + 90^\circ)] u(t)$$

$$\text{Part D} \quad \text{Find } f(t) \text{ for } F(s) = \frac{56s^2 + 112s + 8000}{s(s^2 + 14s + 62s)} = \frac{25 \angle -16.3^\circ}{s} + \frac{24 \angle -71^\circ}{s+7+24j} + \frac{24 \angle 71^\circ}{s+7-24j}$$

$$f^{-1}[F(s)] = f(t)' = [8 + 50e^{-7t} \cos(24t - 16.3^\circ)] u(t)$$

Problem 12.45

Part A Find  $f(t)$  for  $F(s) = \frac{100(s+1)}{s^2(s^2+2s+5)}$

$$= \frac{20}{s^2} + \frac{12}{s} + \frac{-6-8j}{x+1+2j} + \frac{-6+8j}{x+1-2j} = \frac{20}{s^2} + \frac{12}{s} + \frac{10e^{-2+2j}}{x+1+2j} + \frac{10e^{-1-2j}}{x+1-2j}$$

$$\mathcal{J}^{-1}[F(s)] = f(t) = [20t + 12 + 20e^{-t} \cos(2t + 2.21)] \cdot u(t)$$

Part B Find  $f(t)$  for  $F(s) = \frac{40(s+2)}{s(s+1)^3}$

$$= \frac{80}{x} - \frac{40}{(x+1)^3} - \frac{80}{(x+1)^2} - \frac{80}{x+1}$$

$$\mathcal{J}^{-1}[F(s)] = f(t) = [80 - 20t^2 e^{-t} - 80t e^{-t} - 80 e^{-t}] u(t)$$


Part C Find  $f(t)$  for  $F(s) = \frac{5s^2+29s+32}{(s+2)(s+4)}$

$$= 5 - \frac{3}{x+2} + \frac{2}{x+4} \quad \mathcal{J}^{-1}[F(s)] = f(t) = [5\delta t - 3e^{-2t} + 2e^{-4t}] u(t)$$

Part D  $F(s) = \frac{2s^3+8s^2+2s-4}{s^2+5s+4} = 2x - 2 + \frac{4}{x+4}$

$$\mathcal{J}^{-1}[F(s)] = f(t) = [2\delta'(t) - 2\delta(t) + 4e^{-4t}] \cdot u(t)$$

(3)

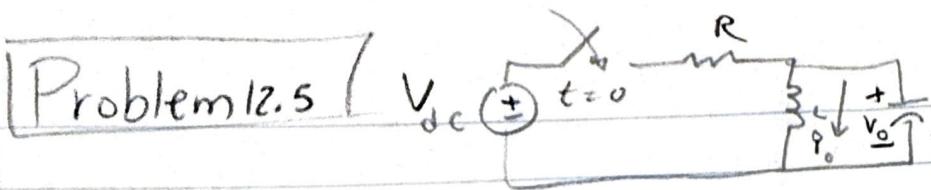

$$V_o(s) = \frac{V_{dc}/RC}{s^2 + (1/RC)s + (1/LC)} ; \quad T_o(s) = \frac{V_{dc}/RLC}{s[s^2 + (1/RC)s + (1/LC)]}$$

Part A Find final value of the voltage

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} SF(s) = 0$$

Part B Find initial value of the voltage

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} SF(s) = 0$$

Part D Find initial value of the current

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} SF(s) = 6$$

Part C Find final value of the current

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} SF(s) = V_{dc}/R$$

# 13.1 Circuit Elements in the S Domain


S-domain Voltage  $\rightarrow$  Volt-Seconds

" Current  $\rightarrow$  A-Seconds


" Ohms  $\rightarrow$  Ohms

Resistor  $\rightarrow$  the same

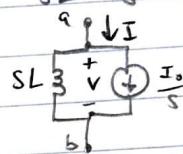
$$\text{Inductor} \rightarrow V = SLI - LI_0 \quad I = \frac{V}{SL} + \frac{I_0}{S}$$


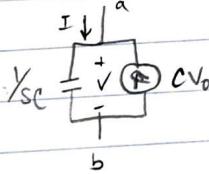
$$\text{Capacitor} \rightarrow I = SCV - CV_0$$


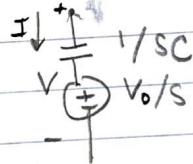
$$V = \left(\frac{1}{SC}\right)I + \frac{V_0}{S}$$



## 13.2 Circuit Analysis in the S Domain

- If no energy is stored in the capacitor or inductor,  
then  $V = ZI$


$$\hookrightarrow \text{so } Z_L = sL \text{ ohms}, \\ Z_C = \frac{1}{sC} \text{ ohms}$$

### Laplace Transform Method

- 1.) Determine initial conditions for Capacitors & inductors
- 2.) Laplace-transform independent V & I functions
- 3.) transform time domain to s domain
- 4.) Analyze S-domain circuit
- 5.) use initial & final value theorems to check voltages & currents
- 6.) Inverse-Laplace

ex; 500Ω resistor, 16mH inductor, 25nF capacitor in //

a.) Express total admittance

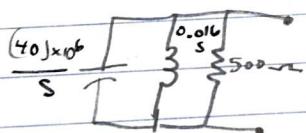


\* No initial conditions

$$Z_R = 500 \Omega$$

$$Z_L = 0.016s \Omega$$


$$Z_C = \frac{40 \times 10^6}{s} \Omega$$
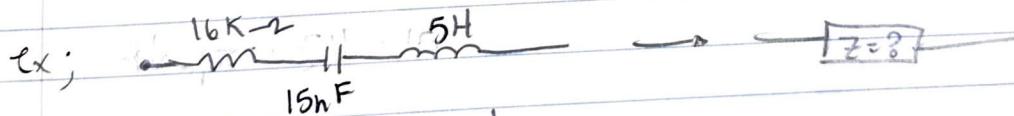
$$Y_{eq} = \frac{1}{500} + \frac{1}{0.016s} + \frac{s}{40 \times 10^6} = \frac{s^2 + 80,000s + 25 \times 10^8}{40 \times 10^6 s} \Omega^{-1}$$



$$Z = 16k\Omega + \frac{1}{(15 \times 10^{-9})s} + 5s$$
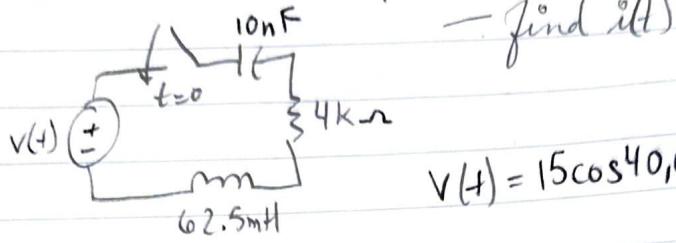
### 13.3.4 Circuit w/ a sinusoidal source




— find  $i(t)$

$$v(t) = 15 \cos 40,000t \text{ V}$$

\* Initial energy is zero
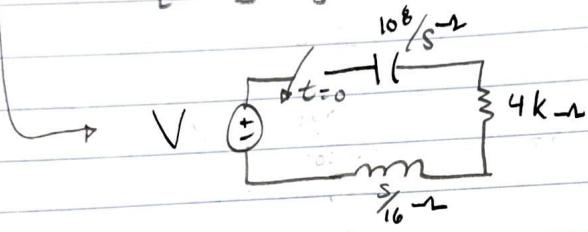
$$V = \int [v(t)] = \frac{15s}{s^2 + 40,000^2} \text{ V-S}$$




$$I = \frac{V}{Z} = \frac{240s^2}{(s^2 + 40,000^2)(s^2 + 64,000s + 16 \times 10^8)} \text{ A-S}$$

$$= \frac{1.875 \times 10^{-3}}{s - j40,000} + \frac{1.875 \times 10^{-3}}{s + j40,000}$$

$$+ \frac{3.125 \times 10^{-3} \angle -126.87^\circ}{s + 32,000 - j24,000} + \frac{3.125 \times 10^{-3} \angle 126.87^\circ}{s + 32,000 + j24,000}$$

$$\mathcal{I}^{\text{r}}[I] = [3.7 \cos 40,000t + 6.25 e^{-32,000t} \cos(24,000t - 126.87^\circ)] \text{ A(t) mA}$$
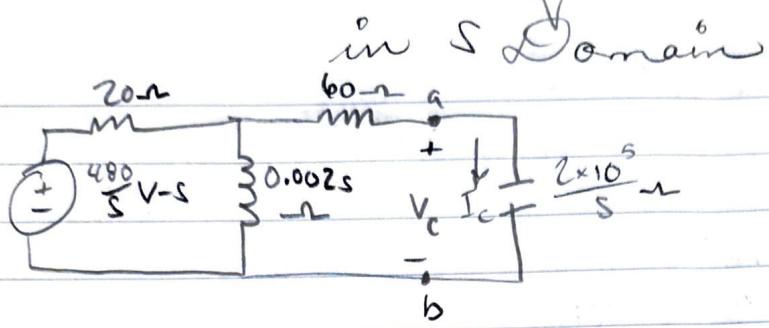
### 13.3.6 Creating a Thevenin Equivalent



- If ab is open, 60Ω resistor is turned off

$$\text{(Voltage Divider)} \quad V_{Th} = \frac{(480/s)(0.002s)}{20 + 0.002s} = \frac{480}{s+10^4}$$

$$Z_{Th} = 60 + \frac{(0.002s)(20)}{20 + 0.002s} = \frac{80(s+7500)}{s+10^4}$$

$$I_c = \frac{\frac{480}{s+10^4}}{\frac{80(s+7500)}{s+10^4} + \frac{2 \times 10^5}{s}} = \frac{6s}{(s+5000)^2} = \frac{-30,000}{(s+5000)^2} + \frac{6}{s+5000}$$

$$P_c = (-30,000t e^{-5000t} + 6e^{-5000t}) u(t) A$$

$$V_c = \frac{1}{sC} I_c = \frac{2 \times 10^5}{s} \cdot \frac{6s}{(s+5000)^2} = \frac{12 \times 10^5}{(s+5000)^2}$$

$$V_c = (12 \times 10^5 t e^{-5000t}) u(t) V$$

4

D

## Circuit Elements in the S-Domain

Part A) Find  $I(s)$


$$V(s) = \frac{50}{s+5000}$$

$$Z = 2.5 \text{ k}\Omega$$


$$I(s) = \frac{V(s)}{Z} = \frac{0.02}{s+5000}$$

Part B

$$I_o = 50 \text{ mA}$$

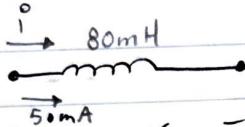


$$[0.08s, 0.004 \text{ V}]$$

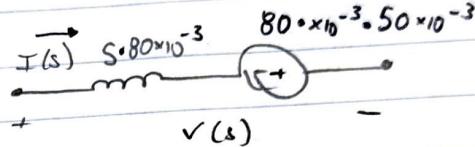

Part C

$$V_o = 25 \text{ V}$$

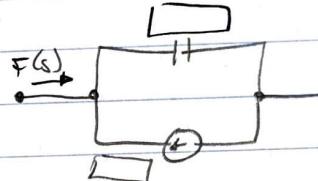

$$Y_{SC} = \frac{1}{s(200 \times 10^{-6})} = \frac{1}{s \cdot 5,000}$$

$$CV_o = (200 \times 10^{-6}) \cdot 25 = 0.005 \text{ A}$$

Part D

$$v(t) = 5 \cos 2000t \text{ V}$$


$$C = 2.5 \mu\text{F} \quad L = 50 \text{ mH}$$

$$\mathcal{I}[v(t)] = \frac{\frac{5s}{8}}{s^2 + 4 \times 10^6}$$


$$\mathcal{I}[C] = \frac{1}{sC} = \frac{1}{400000} \text{ A}$$

$$\mathcal{I}[I] = sL = 550 \cdot 10^{-3}$$

Part E

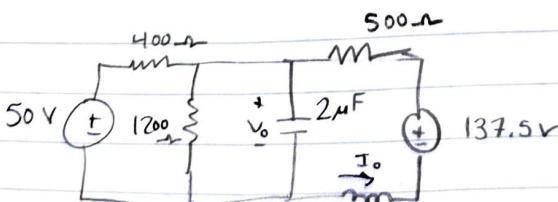
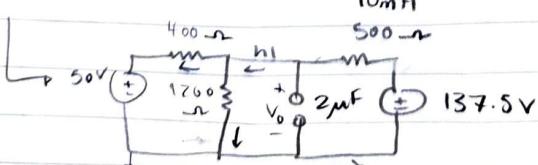
$$\frac{75}{1200} + \frac{75 - 50}{400} = I_o = 125 \text{ mA}$$




$$\frac{n_1}{1200} + \frac{n_1 - 50}{400} + \frac{n_1 - 137.5}{500} = 0$$

$$\frac{n_1}{1200} + \frac{n_1}{400} - \frac{50}{400} + \frac{n_1}{500} - \frac{137.5}{500} = 0$$

$$\frac{2n_1}{375} = 0.4$$

$$n_1 = 75 \text{ V}$$

(5)

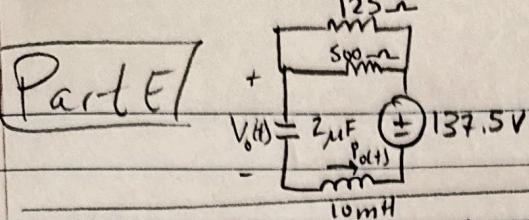


$$Z_R = 100 \quad Z_C = \frac{3 \times 10^6}{s} \quad Z_L = sL = 10 \times 10^{-3} s$$

$$V_c(s) = \frac{V_o}{s} = \frac{75V}{s}$$

$$V_L(s) = L I_o = 1.25mV \quad V(t) = 137.5 u(t) \quad (\text{bc of switch})$$

$$V(s) = \frac{137.5}{s}$$

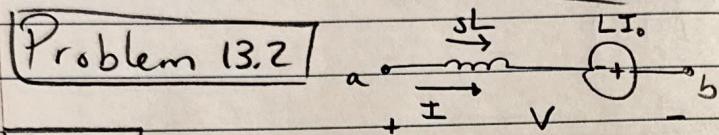
Part A

Find Norton equivalent of the circuit

$$I_n = -\frac{L I_o}{sL} = \boxed{-\frac{I_o}{s}}$$

Part B Calculate impedance equivalent

$$Z_n = \boxed{SL}$$

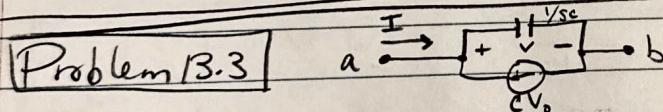Part A Find equivalent voltage

$$V_{Th} = C V_o \cdot \frac{1}{sC} = \boxed{\frac{V_o}{s}}$$

Part B Calculate equivalent impedance

$$Z_{Th} = \boxed{\frac{1}{sC}}$$

\* Why do the voltage sources not have resistance?

6

Problem 13.5 |  $16\text{k}\Omega$ ,  $5\text{H}$ ,  $1\text{SNT}$  in series

[Part A] Find s-domain impedance total

$$Z_R = 16\text{k}\Omega$$

$$Z_L = 5s$$

$$Z_C = \frac{6.7 \times 10^7}{s}$$

$$Z_T = \frac{s}{s} (s^2 + 3200s + 1.3 \times 10^7)$$

[Part B] Numerical pole

$$-p = 0 \text{ rad/s}$$

[Part C] Numerical zeros

$$-z_1, -z_2 = -1600 + 3280j, -1600 - 3280j \text{ rad/s}$$

(6)

$$F(s) = \frac{100(s+1)}{s^2(s^2+2s+5)} = \frac{K_1}{s^2} + \frac{K_2}{s} + \frac{K_3}{s+1+2j} + \frac{K_4}{s+1-2j}$$

$$100(s+1) = K_1 \left[ (s^2+2s+5) \right] + K_2 \left[ s \right] \left[ (s^2+2s+5) \right]$$

$$+ K_3 \left[ (s^2) \cdot (s+1-2j) \right] + K_4 \left[ (s^2) \cdot (s+1+2j) \right]$$

$$100s+100 = K_1 \left[ \underline{s^2+2s+5} \right] + K_2 \left[ \underline{s^3+2s^2+5s} \right] + K_3 \left[ \underline{s^3+s^2-2s^2j} \right] + K_4 \left[ \underline{s^3+s^2+2s^2j} \right]$$

$K_3s^3 + s^2[K_3 - 2K_3j]$   
 $K_3(1-2j)$

$$K_2 + K_3 + K_4 = 0$$

$$(K_1 + 2K_2 + (1-2j)K_3 + (1+2j)K_4) = 0$$

$$2K_1 + 5K_2 = 100$$

$$K_1 \cdot 5 = 100$$

$$\begin{bmatrix} 0 & \cancel{s^2(s^2+2s+5)} & \cancel{s^2} & \cancel{s+1+2j} \\ 0 & s^3(s^2+2s+5) & s^3 & s^2+5 \\ 0 & 100(s+1) & 100 & 0 \\ 2 & 5 & 0 & 0 \\ 5 & 0 & K_1 [0^3+2s^2+5s^3+100] & 0 \end{bmatrix}$$

$$\xrightarrow{\quad} \begin{bmatrix} 1000 & 20 \\ 0 & 0 & 12 \\ 0 & 10 & -6-8j \\ 0 & 0 & 1-6+8j \end{bmatrix}$$


## 13.4 The Transfer Function

→ The s-domain ratio of the Laplace transform of the output to the Laplace transform of the input

$$H(s) = \frac{Y(s)}{X(s)}$$

↑ output signal  
↓ input signal

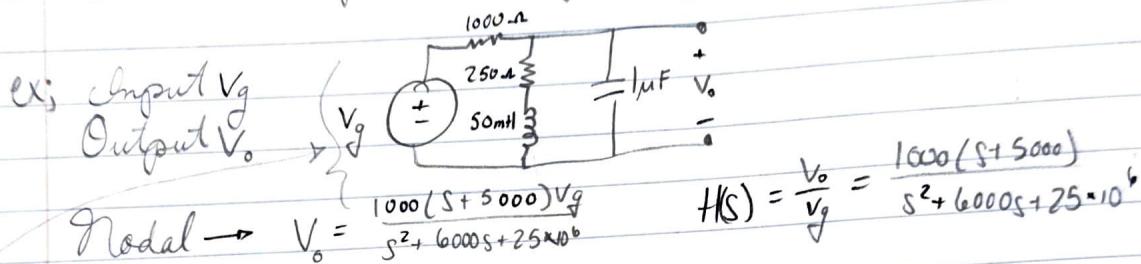→ Multiple equations can represent circuits, depending on what output and input signals are chosen.



## 13.5 The Transfer Function in Partial Fraction Expansion

$$Y(s) = H(s)X(s)$$

- Expanding  $H(s)$  and  $X(s)$  both into partial fractions leads to their poles and zeros.

↳  $H(s) \rightarrow$  transient response

↳  $X(s) \rightarrow$  steady-state response

• If circuit is delayed by a second, then

$$\hookrightarrow Y(s) = H(s)X(s)e^{-st}$$

• If circuit is unit impulse function

$$\hookrightarrow Y(s) = H(s)$$

ex; where  $V_g = 50\mu u(t) V$      $\mathcal{I}[V_g] = \frac{50}{s^2}$

$$H(s) = \frac{1000(S+5000)}{S^2 + 6000S + 25 \times 10^6} \rightarrow V_o = \frac{1000(S+5000)}{(S^2 + 6000S + 25 \times 10^6)} \cdot \frac{50}{s^2}$$

Partial fraction,  $\mathcal{I}^{-1} \rightarrow V_o = [10\sqrt{5} \times 10^{-4} e^{-3000t} \cos(4000t + 79.70^\circ) + (10t - 4) \times 10^{-4}] u(t) V$


Steady-state

transient


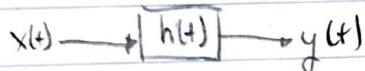
## 13.6 The Transfer Function and the Convolution Integral

→ Relate the output  $y(t)$  to the input  $x(t)$  of the circuit and the circuit's impulse  $h(t)$


$$y(t) = \int_{-\infty}^{\infty} h(\lambda)x(t-\lambda)d\lambda = \int_{-\infty}^{\infty} h(t-\lambda)x(\lambda)d\lambda$$



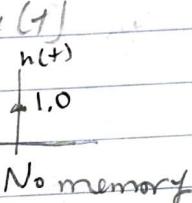
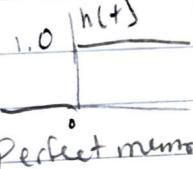
$x(t)$  can be represented as impulses, and the sum of those impulses =  $y(t)$



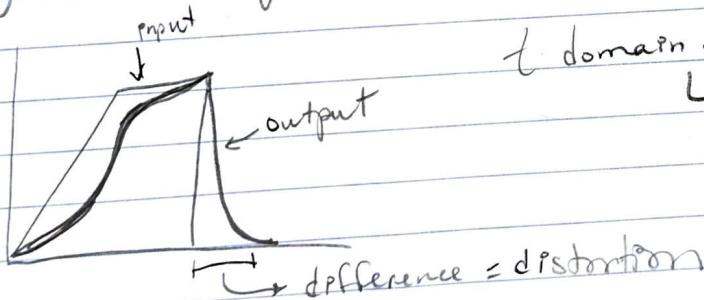→ The more memory, the more distortion between input and output



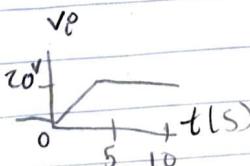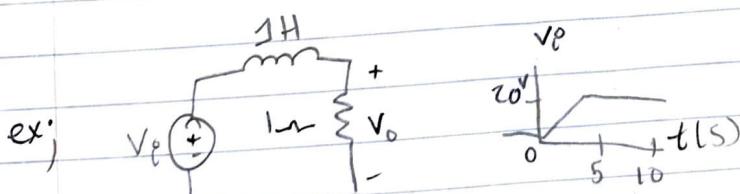t domain of s domain transfer function  
↳ "Impulse response"



$$V_o = \frac{1}{s+1} V$$

When  $V_i$  is the unit impulse  $\delta(t)$ ,  $V_o = 1$   
 $H(s) = \frac{V_o}{V_i}$  →  $V_o = h(t) = e^{-t} u(t)$   
 $h(\lambda) = e^{-\lambda} u(\lambda)$



Seth Ricks

ECEN 250


HW #11

①

Problem 13.8

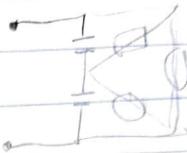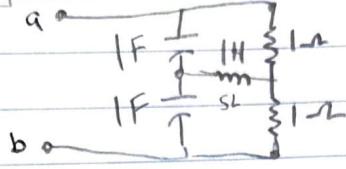


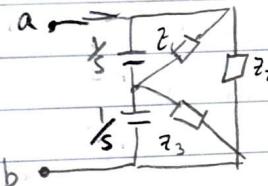Part A Express equivalent s-domain impedance




$$Z_1 = \frac{1+s}{s} = \frac{2s+1}{s} = Z_3 = 2s$$

$$Z_2 = \frac{2s+1}{2s^2}$$

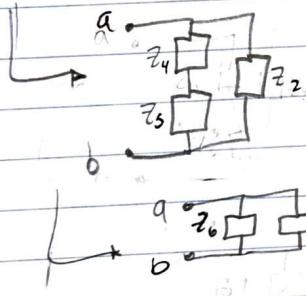

$$Z_4 = \frac{(2s+1)(\frac{1}{s})}{2s+1+s} = \frac{2+s}{2s+1+s} = \frac{2s+1}{s} = \frac{2s+1}{2s^2+s+1} = Z_5$$

$$Z_3 = Z_4 = \frac{4s+2}{2s^2+s+1}$$

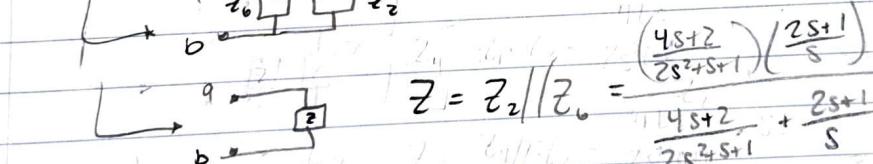

$$Z = Z_2 // Z_5 = \frac{\left(\frac{4s+2}{2s^2+s+1}\right)\left(\frac{2s+1}{s}\right)}{\frac{4s+2}{2s^2+s+1} + \frac{2s+1}{s}} = \frac{2}{s+1}$$

Part B Find the poles

$$\rightarrow P = -1$$

Part C Find the zeros

$$\rightarrow \text{no zeros}$$

$$\frac{4s^2+4s+1}{s+1} = \frac{4s^2+4s+1}{s+1} = \frac{4s^2+4s+1}{s+1}$$

$$4s^2+4s+1 = 4s^2+4s+1$$

$$\frac{4s^2+4s+1}{s+1} = \frac{4s^2+4s+1}{s+1}$$

$$4s^2+4s+1 = 4s^2+4s+1$$

### 3.7 The transfer function and the steady-state sinusoidal response

assuming the input  $x(t) = A \cos(\omega t + \phi)$

$$\text{and } Y(s) = H(s)X(s)$$

$$y_{ss}(t) = A |H(j\omega)| \cos[\omega t + \phi + \alpha(\omega)]$$

ex; given  $V_g = 120 \cos(5000t - 30^\circ) V$

$$\text{and } H(s) = \frac{1000 (s + 5000)}{s^2 + 6000s + 25 \cdot 10^6}$$


$$H(j\omega) = H(j5000) = \frac{1-j^1}{6} = \frac{\sqrt{2}}{6} \angle -45^\circ$$

$$\begin{aligned} y_{ss}(t) &= \frac{(120)\sqrt{2}}{6} \cos(5000t + 30^\circ - 45^\circ) \\ &= 20\sqrt{2} \cos(5000t - 15^\circ) V \end{aligned}$$

### 3.8 The Impulse Function in Circuit Analysis

We use 1.) capacitor circuit 2.) inductor series circuit to create an impulse function with a switching operation

ex;

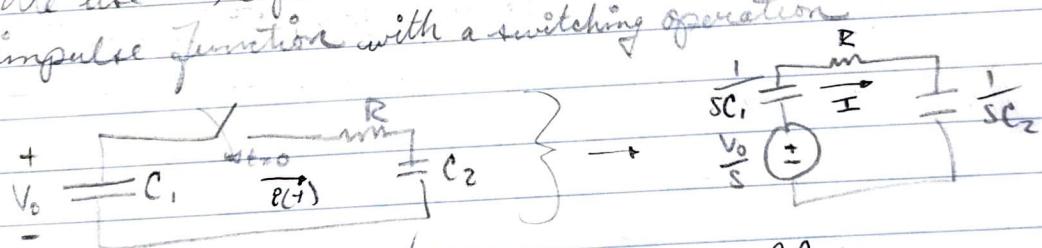

$$I = \frac{V_o/s}{R + 1/SC_1 + 1/SC_2} = \frac{V_o/R}{s + (1/RC_e)}$$

$$C_e = \frac{C_1 C_2}{C_1 + C_2}$$



$$\mathcal{Z}[I] = \left( \frac{V_o}{R} e^{-t/RC_e} \right) u(t)$$

$$q(\text{charge}) = \int_{0^-}^{0^+} \frac{V_o}{R} e^{-t/RC_e} dt = V_o C_e$$

as  $R \rightarrow 0$ ;  $t \rightarrow V_o C_e \delta(t)$

Problem 13.14 Part A

(2)

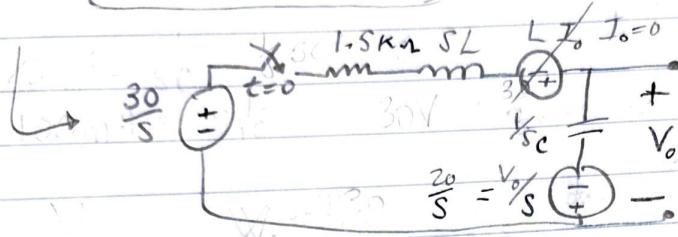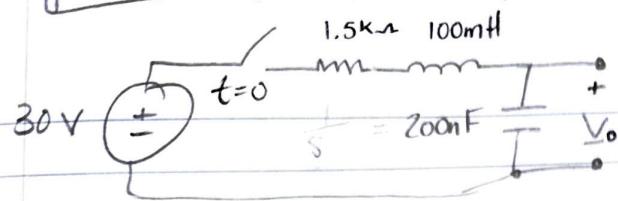

$$\frac{50}{s} \cancel{(1.5 \times 10^3 + SL + \frac{1}{SC})} = I$$

$$I/\cancel{SC} = \frac{50}{s} - \frac{100}{s+5000} + \frac{50}{s+10000}$$

$$V_o = \cancel{\frac{50}{s} (SL + 1.5 \times 10^3)} + \frac{30}{s} - \frac{100}{s+5000} + \frac{50}{s+10000}$$


Part B

$$V_o(t) = \mathcal{J}[V_o] = [30 - 100e^{-5000t} + 50e^{-10000t}] \text{ Volts}$$


(3)

**Problem 13.26** There is no initial energy at  $t=0$

**Part A** Find  $V_o$  for  $t \geq 0$

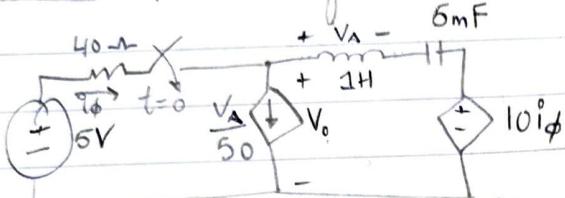

S-domain

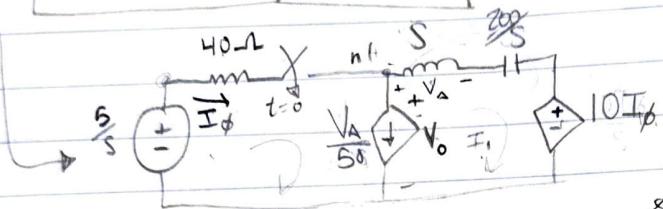

$$\begin{aligned} SL &= S \\ \frac{1}{SC} &= 200\% \end{aligned}$$

$$\text{Augment mesh: } I_0 - I_1 = \frac{V_A}{50}$$

$$I_1^+ = I_0^+ - \frac{V_A}{50}$$

$$I_1^- = I_0^- - \frac{I_1 S}{50}$$

$$I_1^+ + \frac{I_1 S}{50} = I_0^+$$

$$I_1 \left[ 1 + \frac{S}{50} \right] = I_0^+$$

$$I_1 = \frac{I_0^+}{S+50}$$

$$\Rightarrow I_1 = \frac{50I_0^+}{S+50}$$

$$\frac{5 - V_o}{40} = I_0^+$$

$$10I_0^+ = \frac{5 - V_o}{40} = \frac{5}{4S} - \frac{V_o}{4}$$

$$\Rightarrow \frac{V_o - 10I_0^+}{S + \frac{200}{S}} = I_1$$

$$I_1 = \frac{50I_0^+}{S+50} = \frac{50}{S+50} \left[ \frac{5 - V_o}{40} \right]$$

$$\frac{V_o - 10 \left[ \frac{5 - V_o}{40} \right]}{S + \frac{200}{S}} = \frac{V_o}{S+50} \left[ \frac{5 - V_o}{40} \right]$$

$$\frac{V_o - 10 \left[ \frac{5 - V_o}{40} \right]}{S + \frac{200}{S}} = \frac{50}{S+50} \left[ \frac{5 - V_o}{40} \right]$$

$$\begin{aligned} \left( S + 50 \right) \cdot \left[ V_o - 10 \left[ \frac{5 - V_o}{40} \right] \right] &= \left( S + \frac{200}{S} \right) \cdot \left[ 50 \left[ \frac{5 - V_o}{40} \right] \right] \\ \left( S + 50 \right) \cdot \left[ V_o - \frac{5}{4S} + \frac{V_o}{4} \right] &= \left( S + \frac{200}{S} \right) \cdot \left[ \frac{25}{4S} - \frac{5V_o}{4} \right] \end{aligned}$$

$$\begin{aligned} \frac{5S+50}{S+200} &= \frac{5-V_o S}{1+V_o S} \\ -V_o S^3 - 200V_o S + 5S^2 + 1000 &= V_o S^2 + 50V_o S^2 - S^2 - 50S \end{aligned}$$

$$-2V_o S^3 - 50V_o S^2 - 200V_o S = -6S^2 - 50S - 1000$$

$$V_o = \frac{-6S^2 - 50S - 1000}{-2S^3 - 50S^2 - 200S} = \frac{S}{x} - \frac{6}{x+5} + \frac{4}{x+20}$$

$$Y^{-1}[V_o] = [5 - 6e^{-5t} + 4e^{-20t}] u(t) V$$


**Part B** Does it make sense?

Yes, it does!!

4

### Problem 13.38

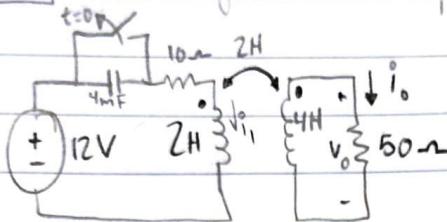Part A) Use Laplace Transform method to find  $i_o$



\* switch has been closed for a long time before opening at  $t=0$ .

Because it has been closed for a long time, both inductors act like a short.

$$\hookrightarrow i_o(0^-) = \frac{12}{10} = 1.2A$$

$$i_o(0^+) = 0A$$




$$v_c(0^-) = 0V \text{ (open, no charge)}$$

$$L\ddot{i}_o = 2.4V \quad \frac{1}{SC} = \frac{250}{S}$$

$$sL_1 = 2s \quad sM = 2s$$

$$sL_2 = 4s$$

S-domain,  
 $t \geq 0$

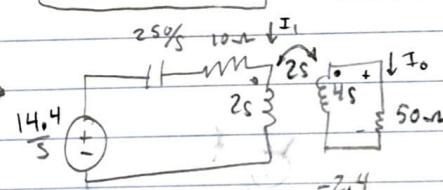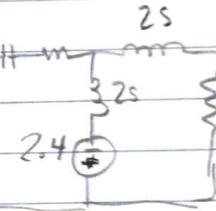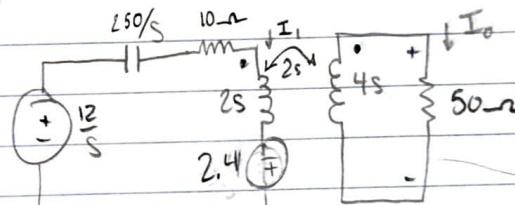

$$\text{Loop 1: } -\left(\frac{12}{s} + \frac{250}{s}\right)i_1 + 10i_1 + 2sI_1 - 2sI_o = 0 \quad \left(\frac{250}{s} + 10 + 2s\right)i_1 - 2sI_o = \frac{12}{s} + 2.4$$

$$\text{Mash 2: } 50I_o + 4sI_o - 2sI_1 = -\frac{2.4}{s} \quad -2sI_1 + (50 + 4s)I_o = -\frac{2.4}{s}$$


$$I_o = \frac{-\frac{3}{10}}{s+25} + \frac{\frac{3-6s}{20}}{s+5+10j} + \frac{\frac{3+6s}{20}}{s+5-10j}$$

$$I_o = \frac{3}{10}e^{-25t} + \frac{300\sqrt{5}}{20}e^{-5t} \cos(10t + 83.43^\circ) u(t) \text{ mA}$$


(5)

Problem (3.49)

Part A)

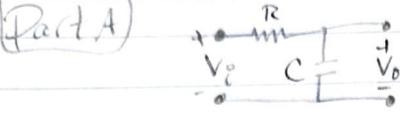

$$\text{Find } H(s) = V_o/V_i$$

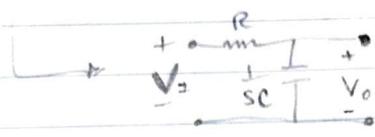


$$\frac{V_o}{V_i} = \frac{1}{sC}$$

$$\frac{V_o}{V_i} = \frac{1}{sCR + 1}$$

$$H(s) = \frac{1}{sCR + 1}$$

Part B)

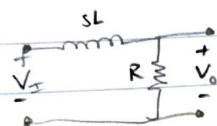

$$\frac{V_o}{V_i} = \frac{1}{sL + R}$$

$$\frac{V_o}{V_i} = \frac{1}{sL + R} = H(s)$$

Part C) If  $R = 47\Omega$  and  $H(s) = V_o/V_i = \frac{5000}{s+5000}$ , find C

$$\frac{1}{sCR + 1} = \frac{5000}{s+5000} = \frac{1}{sC(47) + 1} = \frac{5000}{C \cdot 235000s + 5000}$$

$$C \cdot 235000 = 1 \Rightarrow C = 4.26 \mu F$$

Part D) If  $R = 47\Omega$  and  $H(s) = \frac{5000}{s+5000}$ , find L


$$\frac{R}{sL + R} = \frac{5000}{s+5000} = \frac{47}{sL + 47} \cdot \frac{\frac{5000}{47}}{\frac{5000}{47}}$$

$$sL \frac{5000}{47} = 5000$$

$$L = 9.4 \text{ mH}$$

(6)

## Problem 13.56

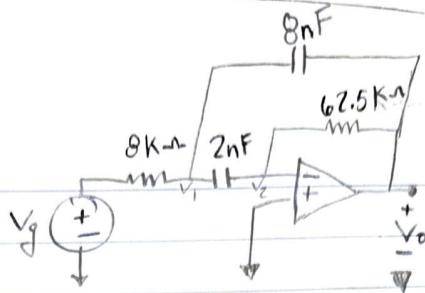
Part A) Derive  $H(s) = \frac{V_o}{V_g}$ 

$$V_p = 0; V_n = 0$$

$$\frac{1}{SC_1} = \frac{500 \times 10^6}{s} \quad \frac{1}{SC_2} = \frac{125 \times 10^6}{s}$$

$$R_1 = 8 \text{ k}\Omega$$

$$R_2 = 62.5 \text{ k}\Omega$$

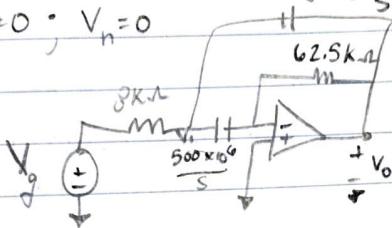

$$\frac{V_i - V_g}{R_1} + \frac{V_i - V_o}{SC_1} + \frac{V_i}{SC_2} = 0$$

$$\frac{-V_o}{R_2} + \frac{-V_i}{SC_1} = 0$$

$$\frac{V_i - V_g}{R_1} + V_i SC_1 + V_i SC_2 = 0$$

$$\frac{-V_o}{R_2} - V_i SC_1 = 0$$

$$-V_i = \frac{500 \times 10^6}{s} \cdot \frac{V_o}{62.5 \times 10^3}$$

$$-V_i SC_1 = -\frac{V_o}{R_2} \quad V_i = \frac{-V_o}{R_2 SC_1}$$

$$-V_i = \frac{8000 V_o}{s}$$

$$-V_i = \frac{-V_o}{R_2 SC_1} \quad V_i = \frac{V_o}{R_2 SC_1}$$

$$\frac{-V_i}{500 \times 10^6} + \frac{V_o - V_i}{125 \times 10^6} + \frac{V_g - V_i}{8000} = 0$$

$$\frac{8000 V_o}{s} + \frac{V_o + 8000 V_o}{125 \times 10^6} + \frac{V_g + 8000 V_o}{s} = 0$$

$$\frac{V_o}{62500} + \frac{V_o s + V_o}{125 \times 10^6} + \frac{V_g}{8000} + \frac{V_o}{s} = 0$$

$$V_o \left[ \frac{1}{62500} + \frac{s}{125 \times 10^6} + \frac{1}{15625} + \frac{1}{s} \right] = \frac{-V_g}{8000}$$

$$V_o = -15625 s$$

$$\frac{V_o}{V_g} = \frac{-15625 s}{s^2 + 1250000000}$$

Part B)  $-P_1 - P_2 = -5000 + 1.00 \times 10^4 j, -5000 - 1.00 \times 10^4 j$ 

Part C) Unit step response in milliseconds?

$$V_o(t) = -1.5625 e^{-st} \cos(10t - 90^\circ)$$

# Chapter 14: Intro to Frequency-Selective Circuits

7





- Grow as changes

$$H(s) = V_o(s) / V_i(s)$$

Passband - signals that pass from input to output

Stopband - signals that are blocked

Frequency response plot  $\rightarrow |H(j\omega)|$  vs.  $\omega \rightarrow$  magnitude plot  
 $\rightarrow \phi(j\omega)$  vs.  $\omega \rightarrow$  phase angle plot

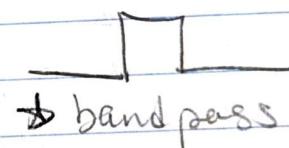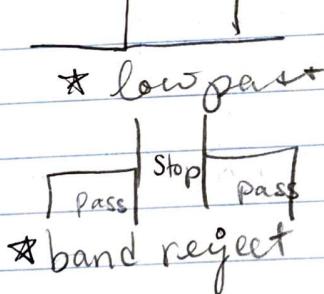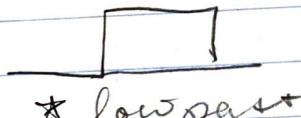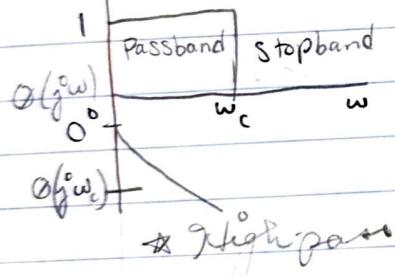

\* high pass



\* band reject

\* band pass

## 14.7 Two-part Filter

RL circuit & series RC circuit behave as low-pass

RL circuit

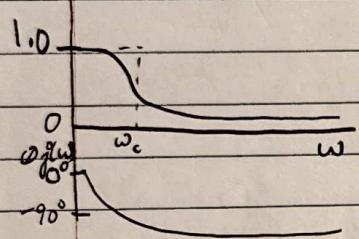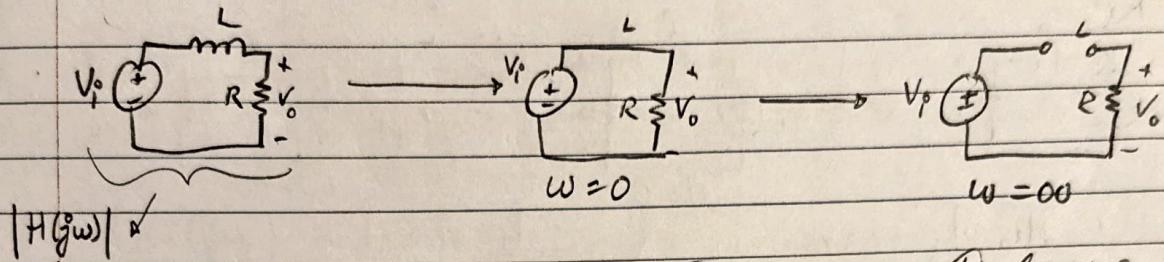


Cutoff Frequency Definition:

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{max}$$

Cutoff Frequency for RL Filters:

$$\omega_c = \frac{R}{L}$$


RC circuit

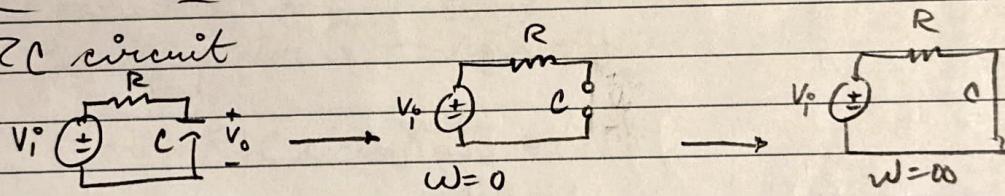

Transfer Function for Low-pass Filter

$$H(s) = \frac{\omega_c}{s + \omega_c}$$

Sdomain:

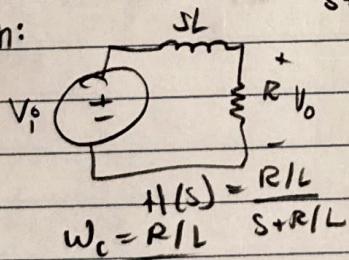

$$V_i \xrightarrow{\frac{R}{sC}} V_o \quad H(s) = \frac{1/RC}{s + 1/RC}$$


$\omega_c = 1/RC$

$$\tau = 1/\omega_c$$

$$\frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{\frac{1}{sC}}{\frac{RC + 1}{sC}} = \frac{1}{RC + 1} = \frac{1}{s + 1/RC}$$

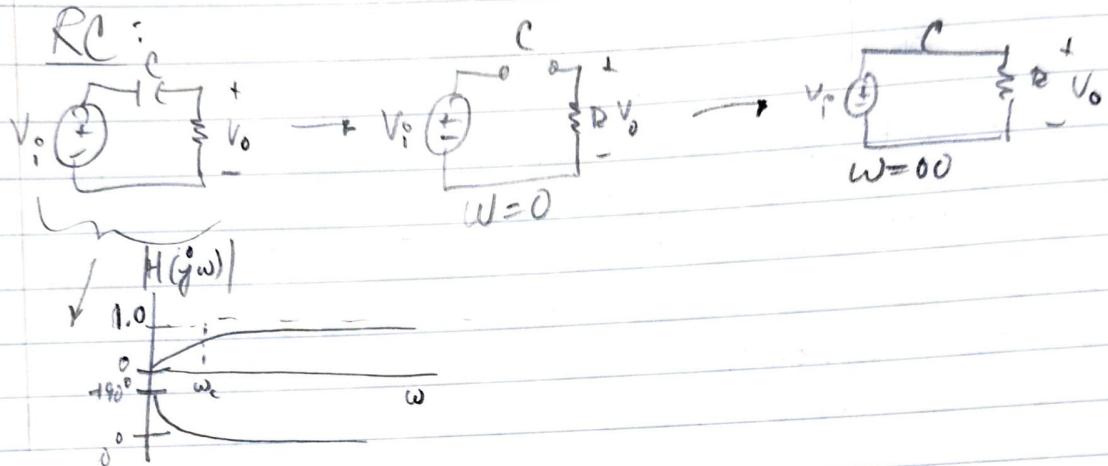
## 14.3 High-Pass Filter

RL circuit & RC circuit again, but  $V_o(s)$  is defined in a different place




Transfer Function for High-Pass Filter

$$H(s) = \frac{s}{s + \omega_c}$$

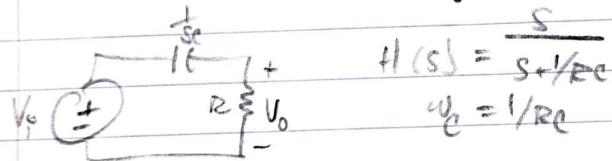

$$H(s) = \frac{s}{s + 1/Rc}$$

$$\omega_c = 1/Rc$$

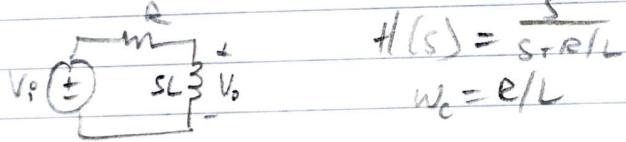

$$H(s) = \frac{s}{s + R/L}$$

$$\omega_c = R/L$$

# Class notes

$$\frac{V_o^2}{V_p^2}$$

$$dB \rightarrow 10 \log_{10} \frac{P_o}{P_p} \rightarrow 20 \log_{10} \frac{V_o}{V_p}$$

-20 dB → reduced by factor of 10


Zero → increases slope

Pole → decreases the slope

$$H(j\omega) = \frac{R/L}{j\omega + R/L}$$

$$\text{Magnitude: } |H(j\omega)| = \sqrt{\omega^2 + (R/L)^2}$$

# Bode Plots

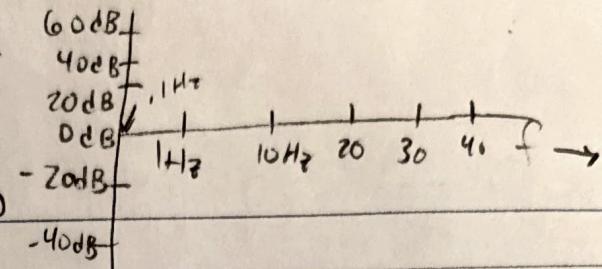

$$\text{phase: } \phi(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |1| = \frac{R/L}{\sqrt{\omega_c^2 + (R/L)^2}}$$

when  $\omega > \omega_c$ , plot goes down and starts approaching zero

## 14.4 Bandpass Filter

- two cutoff frequencies,  $\omega_{c1} \approx \omega_{c2}$

• Center frequency  $\omega_0 \rightarrow$  frequency where  $H(s)$  is purely real  
 - ↳ (resonant frequency) → where  $Z_L \approx Z_C$  cancel out





$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$$

$$H_{\max} = |H(j\omega_0)|$$

• Bandwidth  $B \rightarrow$  width of the passband

• quality factor  $Q \rightarrow$  ratio of center frequency to bandwidth

## A series RLC circuit

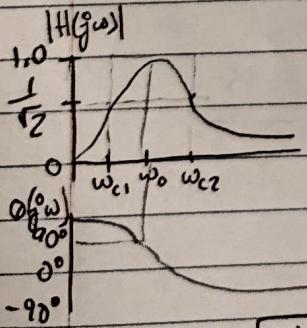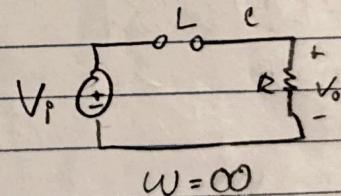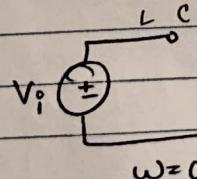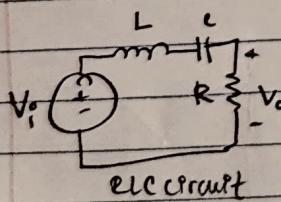

$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}$$

$$\phi(j\omega) = 90^\circ - \tan^{-1} \left[ \frac{\omega(R/L)}{(1/LC) - \omega^2} \right]$$

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{[(1/LC) - \omega^2]^2 + [\omega(R/L)]^2}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_0 = \sqrt{\omega_{c1} + \omega_{c2}}$$


$$\beta = \frac{\omega_{c2} - \omega_{c1}}{\omega_0}$$

$$\beta = \frac{R}{L}$$

$$\frac{3.5}{I=0.582} \quad 5.842$$

$$Q = \frac{\omega_0}{\beta} \quad Q = \sqrt{\frac{L}{R^2 C}}$$

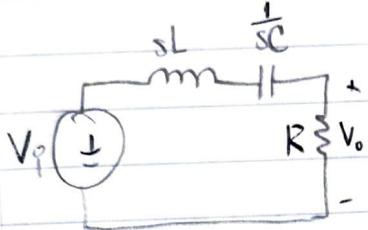
$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$



$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$$

$$\omega_0 = \sqrt{1/LC}$$

$$\beta = R/L$$

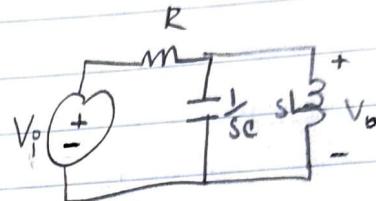

$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$\omega_0 = \sqrt{1/LC}$$


$$\beta = 1/RC$$

$$\Rightarrow H(s) = \frac{k\beta s}{s^2 + \beta s + \omega_0^2}$$

where  $k \cdot \beta$  depend on whether the series resistance of the voltage source is zero or nonzero

## 14.5 Bandreject Filter

RLC circuit

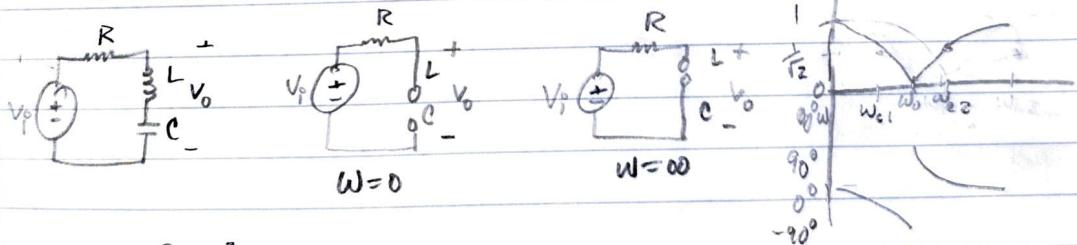


$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

$$H(s) = \frac{s^2 + 1/LC}{s^2 + (R/L)s + 1/LC}$$

$$\omega_0 = \sqrt{1/LC}$$

$$\beta = R/L$$

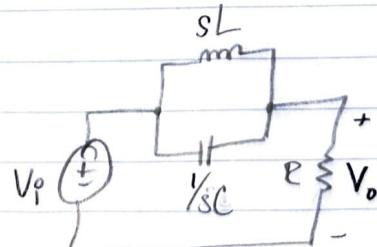

$$H(s) = \frac{s^2 + 1/LC}{s^2 + s/RC + 1/LC}$$

$$\omega_0 = \sqrt{1/LC} \quad \beta = 1/RC$$

[Problem 14.6] Use 25 mH inductor to design a low-pass RL passive filter with a cutoff frequency of 2.5 kHz

Part A) Resistor?

$$w_c = R/L \rightarrow R = L \cdot w_c = L \cdot 2\pi f = [393 \Omega]$$

Part B) Load w/ 750 Ω, what is cutoff frequency?

$$750 \parallel 393 = 257.07 \Omega$$

$$f_c = R/L \cdot \frac{1}{2\pi} = [1,642 \text{ Hz}]$$

Part C

Use [390 Ω] resistor from the given table

Part D) If you use  $\uparrow$ , then what is  $f_c$ ?

$$f_c = R/L \cdot \frac{1}{2\pi} = [2,483 \text{ Hz}]$$

(2)

11

Problem 14.10 Use  $35\text{nF}$  capacitor to design a low-pass passive filter w/ a cutoff frequency of  $160\text{ krad/s}$

Part A  $f_c$ ?  $f_c = \frac{\omega_0}{2\pi} = [25.5\text{ kHz}]$

Part B Filter resistor?  $R = \frac{1}{\omega_c C} = [179\text{ }\Omega]$

Part C Assume cutoff frequency can't increase more than 8%. Smallest load resistance?

$$1.08 \cdot f_c = 27,540\text{ Hz}$$


$$H(s) = \frac{V_o}{V_i} \quad \frac{1}{sC} \parallel R_2 = \frac{\frac{R_2}{sC}}{\frac{R_2}{sC} + R_2} = \frac{\frac{R_2}{sC}}{\frac{R_2 + sCR_2}{sC}} = \frac{sC}{sC + R_2} = \frac{R_2}{sC + R_2}$$

$$V_o = V_i \left[ \frac{\frac{R_2}{sC+1}}{R + \frac{R_2}{sC+1}} \right]$$

$$H(s) = \left[ \frac{\frac{R_2}{sC+1}}{R + \frac{R_2}{sC+1}} \right]$$

$$= \frac{\frac{R_2}{sC+1}}{\frac{R(R_2sC+1)+R_2}{R_2sC+1}} = \frac{\frac{R_2}{sC+1}}{\frac{R_2}{R_2sC+1} + R} = \frac{\frac{R_2}{sC+1}}{\frac{R_2}{RR_2sC+R+R_2}} = \frac{R_2}{RR_2sC+R+R_2}$$
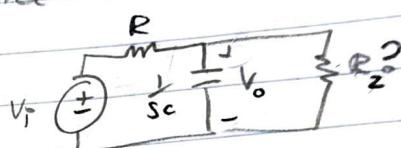
$$V_o = V_i \left[ \frac{R_2}{R + \frac{R_2}{sC+1}} \right] \quad H(s) = \frac{R_2}{s + \frac{R_2}{RR_2sC+R+R_2}}$$



$$2\pi f_c = \omega_c = \frac{R+R_2}{R_2 C} = \frac{1}{R_2 C} + \frac{1}{RC}$$

$$-\frac{1}{R_2 C} = \frac{1}{R_2} - 2\pi f_c$$

$$R_2 C = \frac{1}{R_2} - 2\pi f_c$$

$$R_2 = \frac{1}{\frac{1}{R_2} - 2\pi f_c} / C = [2128.7\text{ }\Omega]$$

Part D  $H(j\omega) = ?$  when  $\omega = 0$ ? (For part C)

$$H(j\omega) = H(j0) = \frac{R_2}{R+R_2} = [0.922]$$

(3)


**Problem 14.17** Design RC high-pass filter w/ cutoff frequency of 240 Hz using 100 nF capacitor.

**Part A** What is the  $\omega_c$ ?  $\omega_c = 2\pi f_c = \boxed{510 \text{ rad/s}}$

**Part B** Resistor value?  $\omega_c = \frac{1}{RC} \rightarrow R = \frac{1}{\omega_c C} = \boxed{1,631 \Omega}$

**Part C** Transfer function,  $H(s)$ ?  $H(s) = \frac{s}{s + \frac{1}{\omega_c}}$

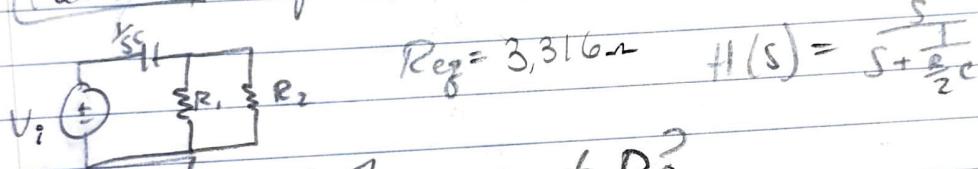**Part D** If loaded w/ same resistor as part B,  $H(s) = ?$




**Part E**  $\omega_c$  from part D?

$$\omega_c = \frac{1}{\frac{R}{2} \cdot C} = \frac{2}{R \cdot C} = \boxed{3,016 \text{ rad/s}}$$

**Part F** What is the gain in the passband from part D?

$$H(\infty) = \frac{\infty}{\infty + \frac{1}{\frac{R}{2} \cdot C}} \rightarrow \frac{1}{1+0} = \boxed{1}$$

Bonus

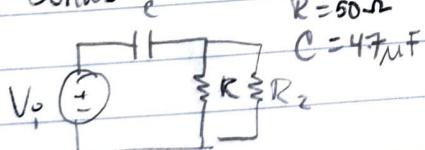

$$\omega_c = 475.33$$

$$\omega_{c+} = 468.083 = \frac{1}{R_C}$$

$$R = \frac{1}{\omega_{c+} \cdot C} = 45.45$$



$$\frac{R \cdot R_2}{R + R_2} = 45.45$$

$$50R_2 = 45.45(50 + R_2) \\ = 2272.74 + 45.45R_2$$

$$R_2 = 500$$

4

### Problem 14.28

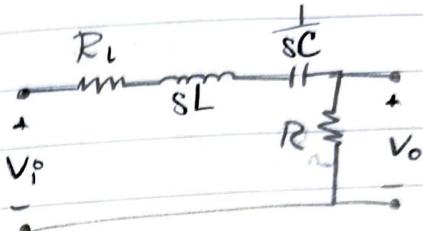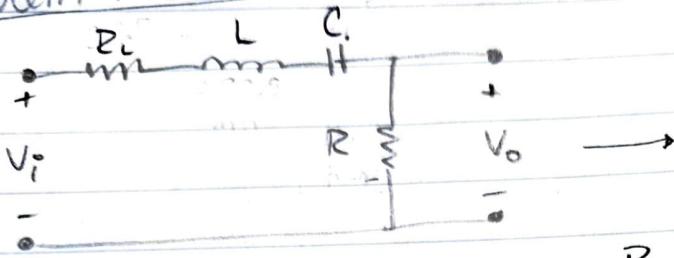

$$R_L = 22.5 \text{ k}\Omega ; L = 332.5 \text{ mH}$$

$$C = 1 \mu\text{F} ; R = 50 \text{ k}\Omega$$

### Part A | Calculate f<sub>o</sub>

$$H(s) = \frac{V_o}{V_i} = \frac{R}{R_L + sL + \frac{1}{sC} + R} = \frac{\frac{R_s}{s^2L + (R+R_L)s + \frac{1}{C}}}{s^2L + (R+R_L)s + \frac{1}{LC}} = \frac{R/L}{s^2 + \frac{(R+R_L)}{L}s + \frac{1}{LC}}$$

$$\omega_o = \sqrt{1/LC} \quad f_o = \frac{\sqrt{1/LC}}{2\pi} = 276 \text{ kHz}$$

### Part C | Calculate f<sub>c1</sub>

$$f_{c1} = \frac{\omega_c}{2\pi} = \frac{-R+R_L}{2L} + \sqrt{\left(\frac{R+R_L}{2L}\right)^2 + \frac{1}{LC}} = 259 \text{ kHz}$$

### Part D | Calculate f<sub>c2</sub>

$$f_{c2} = \frac{\omega_c}{2\pi} = \frac{R+R_L}{2L} + \sqrt{\left(\frac{R+R_L}{2L}\right)^2 + \frac{1}{LC}} = 294 \text{ kHz}$$


### Part E | Calculate B (Hz)

$$\beta = f_{c2} - f_{c1} = 35 \text{ kHz}$$

$$\text{Part B} | Q = ? \quad Q = \frac{\omega_o}{\beta} = \frac{276}{35} = 7.89$$

(5)

**Problem 14.40**

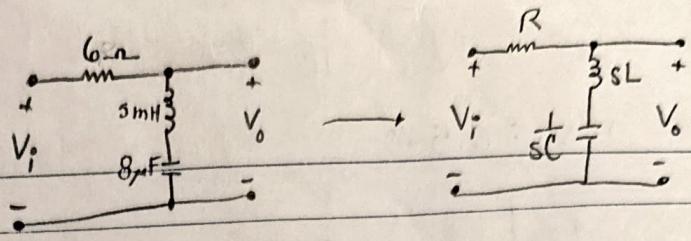

**Part A** Find the center frequency of the filter.

$$H(s) = \frac{V_o}{V_i} = \frac{sL + \frac{1}{sC}}{sL + \frac{1}{sC} + R} = \frac{s^2 L + \frac{1}{C}}{s^2 L + sR + \frac{1}{C}} = \frac{s^2 + \frac{1}{CL}}{s^2 + \frac{SR}{L} + \frac{1}{CL}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 5,000 \text{ rad/s}$$

**Part B** Calculate center frequency in hertz.  $f_0 = \frac{\omega_0}{2\pi} = 796 \text{ Hz}$

**Part D** Bandwidth  $B_0$ .  $B = R/L = 1200 \text{ rad/s} \rightarrow 191 \text{ Hz}$

**Part C** Quality factor Q?  $Q = \frac{\omega_0}{B} = 4.17$

**Part E** Find lower cutoff frequency  $\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} = 4,436 \text{ rad/s}$

**Part G** Find higher cutoff frequency  $\omega_{c2} = + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} = 5,636 \text{ rad/s}$


**Part H** Find  $f_{c2}$ .  $f_{c2} = \omega_{c2}/2\pi = 897 \text{ Hz}$

**Part F** Find  $f_{c1}$ .  $f_{c1} = \omega_{c1}/2\pi = 706 \text{ Hz}$

**Problem 14.44** Consider the RLC band reject filter. The quality factor of the filter is  $3/2$ , the center frequency is  $4 \text{ krad/s}$ , and  $C = 80 \text{nF}$ . The input to the filter is  $175 \cos \omega t \text{ V}$

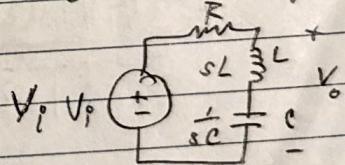**Part A** Find voltage drop across the resistor

when  $\omega = \omega_0$ . Suppose  $V_R(t) = A_R \cos(\omega t + \phi)$   
 $A_R = 175 \text{ V}$ ;  $\omega = 4 \text{ krad/s}$ ;  $\phi = 0^\circ$



**Part B** Same thing, but  $\omega = \omega_0$ .

$$\beta = \frac{\omega_0}{Q} = 6 \text{ krad/s} \quad \omega_0 = 4 \text{ krad/s}$$

$$Q = \sqrt{\frac{L}{R^2 C}} = \sqrt{\frac{R/B}{R^2 C}} \quad Q = \frac{1}{3}$$

$$Q^2 = \frac{1}{RBC} \rightarrow Q^2 BC = \frac{1}{R} \rightarrow R = Q^2 BC = \frac{1}{(3)^2 \cdot (6 \text{ krad/s}) \cdot (80 \times 10^{-9})} = 4,688 \Omega$$

$$L = \frac{R}{\beta} = \frac{4,688}{6,000} = 0.781 \text{ H}$$

$$|\omega_c| = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} = 8000$$

$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + (\beta/L)s + \frac{1}{LC}} = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2} = \frac{(j\omega_{c1})^2 + \omega_0^2}{(j\omega_{c1})^2 + \beta(j\omega_{c1}) + \omega_0^2} = 0.5 + 0.5j = 0.707 \angle 45^\circ$$

$$\frac{V_o}{V_i} = 0.707 \cos(2000t + 45^\circ)$$

$$V_o = 124 \cos(2000t + 45^\circ)$$

(6)

Part C Same thing,  $\omega = \omega_{c2}$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = 8000 \text{ rad/s}$$

$$H(s) = 0.5 + 0.5j \quad V_R(t) = 174 \cos(8000t - 45^\circ)$$

Part D Same thing,  $\omega = 0.25\omega_0 \rightarrow \omega = 1,000 \text{ rad/s}$

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + 2s\zeta\omega_0 + \omega_0^2} = \frac{(j1000)^2 + (4000)^2}{(j1000)^2 + (6000)(j1000) + (4000)^2} = 0.862 - 0.35j$$

$$= 0.928 L - 21.80 = \frac{V_o}{V_i}$$

$$V_o = 162.5 L - 21.8^\circ$$

$$V_R = V_i - V_o = 65.0 L 68.2^\circ$$

$$V_R(t) = 65.0 \cos(1000t + 68.2^\circ)$$

Part E Same thing,  $\omega = 8\omega_0 = 32,000$

$$H(s) = 0.982 L 10.784^\circ$$

$$V_o = V_i \cdot H(s) = 172 L 10.78^\circ$$

$$V_R = V_i - V_o = 32.7 L - 79.2^\circ$$

$$V_R(t) = 32.7 \cos(32,000t - 79.2^\circ)$$

FAB:

 $w \rightarrow 1$ 

$$\sqrt{1 + \left(\frac{\omega}{\omega_n}\right)^2} = \sqrt{1 + \left(\frac{1}{\omega_n}\right)^2} = 1$$

$$\sqrt{1 + \left(\frac{\omega}{\omega_d}\right)^2} = \sqrt{1 + \left(\frac{1}{\omega_d}\right)^2}$$

$$\sqrt{\frac{1 + \left(\frac{\omega}{\omega_n}\right)^2}{1 + \left(\frac{\omega}{\omega_d}\right)^2}} = \sqrt{\frac{1 + \frac{\omega^2}{\omega_n^2}}{1 + \frac{\omega^2}{\omega_d^2}}} = \begin{cases} \frac{\omega_n^2 + \omega^2}{\omega_n^2} \\ \frac{\omega_d^2 + \omega^2}{\omega_d^2} \end{cases}$$

(11)